



Concurrent VHDL

Announcements

- Homework #2 due Wednesday
- Reading Assignment
 - Ch. 3 section 6, Ch. 5 sections 1-4
- Free homework grade for critical thinking lecture
 - Don't forget to scan in

RIT

Division of Academic Affairs
Eugene H. Fram Chair in
Applied Critical Thinking

2019 Fram Signature Lecture

“POWERFUL STUFF: An Entrepreneurial Mindset Built Upon Critical Thinking” with Doug Melton of KEEN

Date: Tuesday, September 17, 2019

Time: 3:30 pm – 4:45 pm

Place: Ingle Auditorium

(Reception immediately following in Fireside Lounge)

Access Services will be providing interpreters



Proudly cosponsored by:

RIT | College of
Engineering Technology

RIT | Kate Gleason College of
Engineering



A Note about Libraries

- We will learn more about libraries later
- For now we will use the following Libraries
 - library IEEE;
 - use IEEE.STD_LOGIC_1164.ALL;
 - use IEEE.NUMERIC_STD.ALL;
 - use IEEE.STD_LOGIC_UNSIGNED.ALL
- These libraries permit use of predefined logic values, logic operations like AND, OR, and arithmetic operations like + (add) etc.

Things to know

- Comments
 - --this is a comment
 - Use lots of comments – good habit to get into
 - Use descriptive signal and port names
- Indenting
 - Use indenting to make code more ‘readable’
 - SPACES (2, 3 or 4) not TABS
- Editor
 - I recommend Notepad++
 - Free online
 - Recognizes VHDL and formats accordingly
 - Color codes comments, reserved words, etc...

Port and Signal Types

- **STD_LOGIC**
 - **Represents a single wire**
 - Can have 9 values
 - 'U' : uninitialized. This signal hasn't been set yet.
 - 'X' : unknown. Impossible to determine this value/result.
 - '0' : logic 0
 - '1' : logic 1
 - 'Z' : High Impedance
 - 'W' : Weak signal, can't tell if it should be 0 or 1.
 - 'L' : Weak signal that should probably go to 0
 - 'H' : Weak signal that should probably go to 1
 - '-' : Don't care
 - Useful in simulation
 - We will use STD_LOGIC in DSD

Port and Signal Types

- Bit
 - Also represents a single wire
 - Can only have a value of 0 or 1
 - Not as useful as `STD_LOGIC`
 - In the real world there are many more possible values on a wire than 0 and 1

Port and Signal Types (con't)

- **STD_LOGIC_VECTOR**
 - **Represents a bus or bundle of wires**
 - Must include a range
 - Ex:
 - port (a :STD_LOGIC_VECTOR(7 DOWNT0 0);
 - This is an 8 bit bus
 - It could also be specified with
STD_LOGIC_VECTOR(0 TO 7)
 - 'DOWNT0' is more common and preferred in DSD

Port and Signal Types (con't)

- **STD_LOGIC vs. STD_LOGIC_VECTOR**
 - When assigning a value to **STD_LOGIC**, use single quotes
 - Ex
 - `Var1 <= '0'; tri_state <= 'Z';`
 - When assigning a value to **STD_LOGIC_VECTOR** use double quotes
 - Ex
 - `a <= "11110000"`
 - The value on the right must contain the same number of elements as the width of the vector

Selected Signal Assignment

- Describing schematic with gates and wires is not very efficient
- Still have to design schematic first
- In a selected signal assignment you work from the truth table, not the schematic

X	Y	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Selected Signal Assignment

```
ENTITY fulladd IS
```

```
    PORT( Cin, X,Y : IN STD_LOGIC;  
          S, Cout  : OUT STD_LOGIC);
```

```
END fulladd;
```

```
ARCHITECTURE behavioral OF fulladd IS
```

```
    SIGNAL inputs : STD_LOGIC_VECTOR(2 DOWNTO 0);
```

```
    BEGIN
```

```
        inputs <= X & Y & Cin;
```

```
        WITH inputs SELECT
```

```
            S <= '1' WHEN "001" | "010" | "100" | "111",  
                '0' WHEN OTHERS;
```

```
        WITH inputs SELECT
```

```
            Cout <= '1' WHEN "011" | "101" | "110" | "111",  
                    '0' WHEN OTHERS;
```

```
    END behavioral;
```

Selected Signal Assignment

ARCHITECTURE behavioral OF fulladd IS

SIGNAL inputs : STD_LOGIC_VECTOR(2 DOWNTO 0);

BEGIN

inputs <= X & Y & Cin;

WITH inputs SELECT

S <= '1' WHEN "001" | "010" | "100" | "111",

'0' WHEN OTHERS;

WITH inputs SELECT

Cout <= '1' WHEN "011" | "101" | "110" | "111",

'0' WHEN OTHERS;

END behavioral;

Concatenation: takes three separate wires and combines them into 3-bit Bus. **Order is important.** (X, Y, Cin)

Selected Signal Assignment (con't)

WITH expression SELECT

```
signal_name <= signal_value WHEN choices,  
                signal_value WHEN choices,  
                :  
                :  
                signal_value WHEN OTHERS;
```

Conditional Signal Assignment

```
Target <= value_expression1 WHEN condition1 ELSE  
value_expression2 WHEN condition2 ELSE  
value_expression3 WHEN condition3 ELSE  
value_expression;
```

- Condition must evaluate to true or false

```
ARCHITECTURE behavioral OF fulladd IS
```

```
signal inputs : STD_LOGIC_VECTOR(2 DOWNTO 0);
```

```
BEGIN
```

```
inputs <= X & Y & Cin;
```


```
S <= '1' WHEN inputs = "001" or inputs = "010" or inputs = "100" or inputs = "111" else '0';
```

```
Cout <= '1' WHEN inputs = "011" or inputs = "101" or inputs = "110" or inputs = "111" else '0';
```

```
END behavioral;
```

Example: Mux

- Consider the following Mux

 

S1	S0	Y
0	0	A
0	1	B
1	0	C
1	1	D

- Write the architecture
 - Using selected signal assignment
 - Using conditional signal assignment

Concurrent Statements

- Concurrent Statements include
 - Simple assignment statements
 - `a <= '1';`
 - `b <= "11001100";`
 - `c <= not (a AND d);`
 - Selected assignment statements
 - Conditional assignment statements
- **Describe COMBINATORIAL logic**
- **They all evaluate at the same time**