



Introduction to Sequential VHDL

Announcements

- Homework #2 due Today
- Homework #3 posted – due next week
- Reading Assignment
 - Ch. 6 sections 3-4, 7-9
- Free homework grade for critical thinking lecture
 - Don't forget to scan in

RIT

Division of Academic Affairs
Eugene H. Fram Chair in
Applied Critical Thinking

2019 Fram Signature Lecture

“POWERFUL STUFF: An Entrepreneurial Mindset Built Upon Critical Thinking” with Doug Melton of KEEN

Date: Tuesday, September 17, 2019

Time: 3:30 pm – 4:45 pm

Place: Ingle Auditorium

(Reception immediately following in Fireside Lounge)

Access Services will be providing interpreters



Proudly cosponsored by:

RIT | College of
Engineering Technology

RIT | Kate Gleason College of
Engineering



Before we talk about sequential

- **Constants**

- function like constants in a programming language
 - Their value cannot change during execution
- Declared with signals in the architecture's 'declarative section'
 - 'declarative section is after the ARCHITECTURE line, before BEGIN
- Syntax:
 - `constant constant_name : type := value;`



Note the syntax here

VHDL Constants

- Example:

ARCHITECTURE example OF constants IS

 CONSTANT SEVEN : STD_LOGIC_VECTOR(6 downto 0) := "1111000";

BEGIN

 HEX0 <= SEVEN;


 :

 :

- Write the constant declaration for an 8-bit standard logic vector equivalent to AA_H

Constants with 7-segment display

- Seven Segment displays

 

- HEX0(0) = a

- HEX0(1) = b

- :

- :

- HEX0(6) = g

: I is OFF

constant ZERO : std_logic_vector(6 downto 0) := "1000000";

segment g is off, all other segments are on

Sequential VHDL code

- Consists of one or more process statements
 - Each process is a concurrent statement
 - All processes execute simultaneously
 - Processes communicate using signals
 - Statements within a process are executed sequentially
 - Most common structures are:
 - If-then-else
 - case

Processes

- A concurrent statement that is comprised of sequential statements
 - Sequential statements are evaluated in sequence and their order is critical
 - ***NOTE*** all signal assignments are made concurrently at the **END** of process execution. Signals assigned in the process are not available for reading in the same process

Example: Process()

BEGIN

a <= 'I';

If (a= 'I') then

Else

END process;

Which branch is taken?

Processes

- Syntax

```
[process_label:] PROCESS [(sensitivity_list)] [IS]
    {process_declarative_item}
BEGIN
    {sequential_statement}
END PROCESS [process_label];
```

- Sensitivity list

- List of signals that the process is sensitive to
- The process will execute when one of the signals in the list has an event (changes value)
- All signals that are read in the process should be included
- Do not include signals not used in the process

Sensitivity list (con't)

- Process execution in simulation is in an endless loop
 - Execution starts when a signal in the sensitivity list has an event
 - Execution suspends when the last statement is completed
- In simulation, all processes are evaluated at the same time - *concurrency*

Case Statements

- Use to select one sequence of statements for execution from a number of alternatives
 - Similar to a C 'switch' structure
 - Synthesizes to a MUX
 - Selection is based on the value of a single expression

```
CASE (expression) IS  
  WHEN choices => sequence of statements  
  {WHEN choices => sequence of statements}  
END CASE;
```

- A list of choices can be associated with one branch
 - Separate choices with |

Case example

ENTITY xor_2 IS

PORT(a, b :IN STD_LOGIC;
 c :OUT STD_LOGIC);
END xor_2;

ARCHITECTURE behavioral OF xor_2 IS

SIGNAL inputs : STD_LOGIC_VECTOR(1 DOWNTO 0);

BEGIN

inputs <= a & b;

ex_or: PROCESS(inputs)

BEGIN

CASE inputs IS

WHEN "01" => c <= '1';

WHEN "10" => c <= '1';

WHEN OTHERS => c <= '0';

END CASE;

END PROCESS;

END behavioral;

Case Example (shortened)

```
ENTITY xor_2 IS
```

```
  PORT( a, b : IN STD_LOGIC;  
        c   : OUT STD_LOGIC);
```

```
END xor_2;
```

```
ARCHITECTURE behavioral OF xor_2 IS
```

```
  SIGNAL inputs : STD_LOGIC_VECTOR(1 DOWNTO 0);
```

```
BEGIN
```

```
  inputs <= a & b;
```

```
  ex_or: PROCESS(inputs)
```

```
  BEGIN
```

```
    CASE inputs IS
```

```
      WHEN "01" | "10" => c <= '1';
```

```
      WHEN OTHERS => c <= '0';
```

```
    END CASE;
```

```
  END PROCESS;
```


```
END behavioral;
```

Case (con't)

- Others choice
 - Some compilers require WHEN OTHERS => as the last choice
 - Some only require it if the set of choices does not cover every possible value of the case expression
 - CYA and always include it
 - It has to be the last branch

Mux Example

- Consider the following Mux

 

S1	S0	Y
0	0	A
0	1	B
1	0	C
1	1	D

- Write the architecture
 - Using a case statement

IF Statements

- Selects one or none of its alternative sequence of statements depending on the value of each branch's condition
 - Priority based on order of if – elsif conditions

```
IF condition THEN
    sequence of statements
{ELSIF condition THEN
    sequence of statements}
[ELSE
    sequence of statements]
END IF;
```

If Statements (con't)

- The condition must evaluate to a boolean true or false
 - IF ((a='1') AND (b='0')) THEN
- The ELSE statement is not necessarily optional
 - If a signal is assigned a value in any branch, it must be assigned a value in all branches
 - When a signal is not assigned a value in all branches, a latch is inferred
 - Inferred latches are bad. Don't worry, the synthesis tool will give you a warning

If Statements (con't)

```
ARCHITECTURE xyz OF xor_2 IS  
BEGIN
```

```
    PROCESS (a, b)
```

```
    BEGIN
```

```
        IF a /= b then
```

```
            c <= '1';
```


```
        ELSE
```

```
            c <= '0';
```

```
        END IF;
```

```
    END PROCESS;
```

```
END xyz;
```

 

```
ARCHITECTURE xyz OF xor_2 IS  
BEGIN
```

```
    PROCESS (a, b)
```

```
    BEGIN
```

```
        IF a /= b then
```

```
            c <= '1';
```

```
        END IF;
```

```
    END PROCESS;
```

```
END xyz;
```



Signal assignments in processes


- Signals take the last value they are assigned in a process
- Assignments are made concurrently at the end of process execution
- Default assignments can be used to shorten IF statements

```
ARCHITECTURE xyz OF xor_2 IS
BEGIN
  PROCESS (a, b)
  BEGIN
    c <= '0'; -- this is the default assignment
    IF a /= b then
      c <= '1'; -- c is only re-assigned if a /= b
    END IF;
  END PROCESS;
END xyz;
```

- In this example it is okay to have an IF without and ELSE

Mux Example

- Consider the following Mux

 

S1	S0	Y
0	0	A
0	1	B
1	0	C
1	1	D

- Write the architecture
 - Using an if statement