



# Hierarchical Design and Components

# Announcements

- Homework #5 due today
- Homework #6 posted
- Please complete homework group evaluations by Sunday.

# Modular Design

- Methodology for designing complex systems
  - System partitioned into simpler modules
  - Modules are interconnected to accomplish system's overall function
  - Each module task is defined in a way that allows it to be independently designed and verified
  - Design effort is simplified by focusing on one module at a time

# Hierarchical Design

- Top-Level Design is an integration of modules
  - Each module may be the integration of smaller modules
  - The lowest level consists of behaviorally defined entities
- Also known as Top-Down Design



Entity A




Entity B



Entity C




Entity TOP

 

Entity TB





 

## Entity Test Bench

### Entity TOP

#### Entity C

Entity B

Entity A

#### Entity D

# Hierarchical Design in VHDL


- Advantages of a well partitioned hierarchical design
  - Design management is easier
  - Modules can be designed and verified by different engineers
  - Maximum re-use of modules is possible
  - Design easier to read and comprehend
  - Verification is simpler
  - Enhanced portability

# Hierarchical Design in VHDL

- Modules at each level are known as **COMPONENTS**
- Components are interconnected with signals
- A component may be used more than once in a level
- Levels
  - Lowest level modules are behavioral
  - Top level is structural
  - Other levels may be mixed



# Full Adder Example

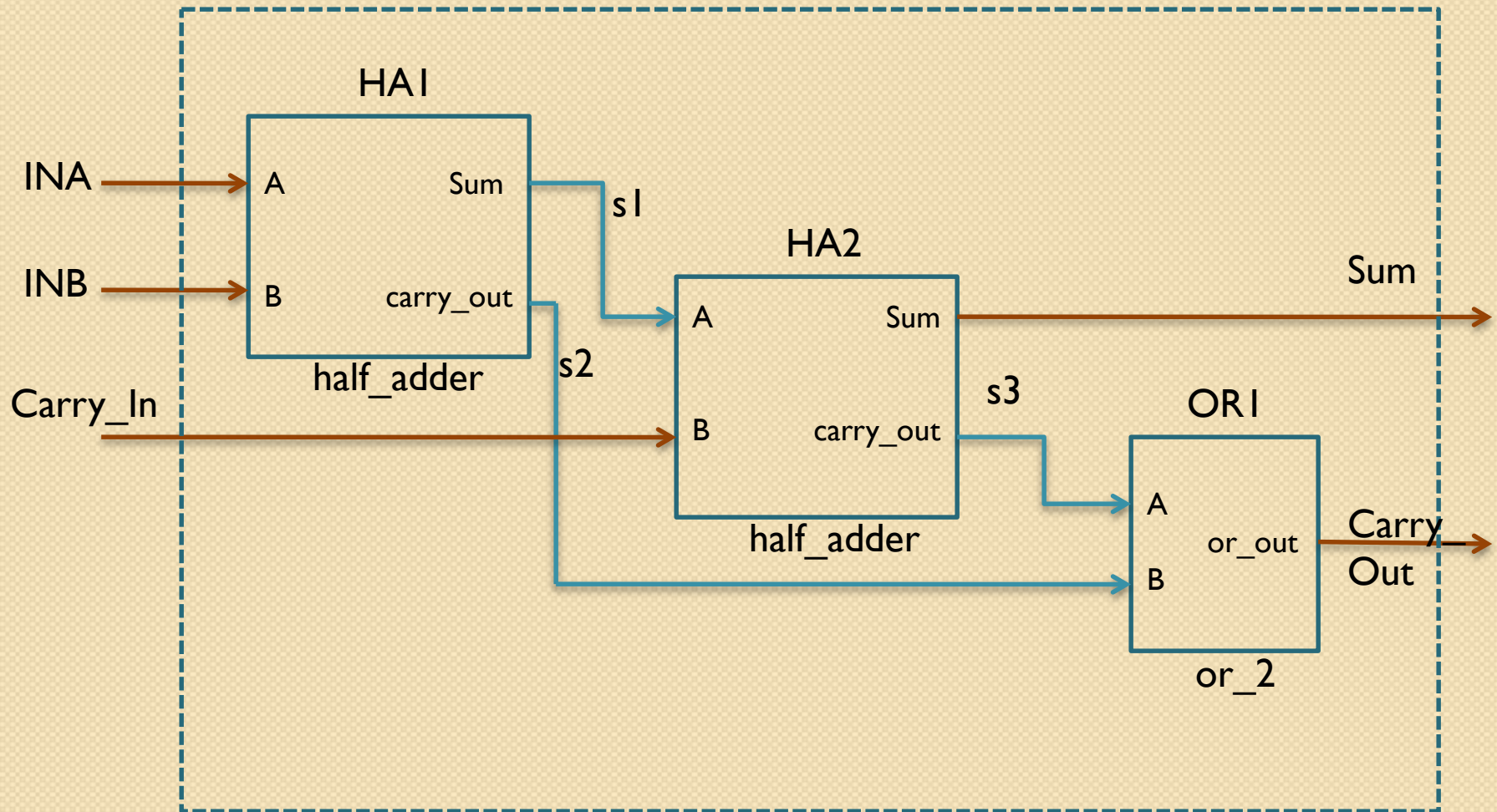

# Full Adder Example

- The Full Adder entity has
  - Three inputs; INA, INB, Carry\_in
  - Two outputs; Sum, Carry\_out
- The Full Adder architecture is comprised of
  - Two half adders
  - A 2-input OR module
  - Three interconnect signals; s1, s2, s3

# Half-Adder component

ENTITY half\_adder IS

```
    PORT( a, b          : IN STD_LOGIC;  
          sum, carry_out : OUT STD_LOGIC);  
END half_adder;
```

ARCHITECTURE dataflow OF half\_adder IS

BEGIN

```
    sum <= a XOR b;  
    carry_out <= a AND b;  
END dataflow;
```

# Two-Input OR component

ENTITY or\_2 IS

```
    PORT( a, b      : IN STD_LOGIC;  
          or_out    : OUT STD_LOGIC);  
END or_2;
```

ARCHITECTURE dataflow OF or\_2 IS

BEGIN

```
    or_out <= a OR b;  
END dataflow;
```

# Top Level – Full Adder

ENTITY full\_adder IS

PORT (INA, INB, Carry_in	: IN STD_LOGIC:
Sum, Carry_out	: OUT STD_LOGIC);

END full\_adder;

# Top Level – Full Adder

ARCHITECTURE structure OF full\_adder IS

SIGNAL s1, s2, s3 : std\_logic;

COMPONENT half\_adder IS

PORT( a, b : IN STD\_LOGIC;  
sum, carry\_out : OUT STD\_LOGIC);

END COMPONENT;

COMPONENT or\_2 IS

PORT( a, b : IN STD\_LOGIC;  
or\_out : OUT STD\_LOGIC);

END COMPONENT;

BEGIN

HA1 : half\_adder

PORT MAP(a =>INA,  
b =>INB,  
sum => s1,  
carry\_out => s2);



# Top Level – Full Adder

HA2 : half\_adder

```
    PORT MAP(a      =>s1,  
             b      =>Carry_in,  
             sum     => sum,  
             carry_out => s3);
```

OR1 : or\_2

```
    PORT MAP(a      =>s3,  
             b      =>s2,  
             or_out  => carry_out);
```

END structure;

# Terminology


- HAI, HA2 and ORI are *instantiations*
- *PORT MAP* describes how a design entity is connected in a larger structure
  - *Formal* port is on the left. This is the port of the component's entity
  - *Actual* is on the right. This is the signal or port that is connected in the architecture

# Port Map

- Components instantiations are treated as concurrent statements
  - the inputs to component represent the sensitivity list
  - whenever there is an event on one of its inputs the component is evaluated
  - component instantiations cannot be included in a process

# Another example

Example

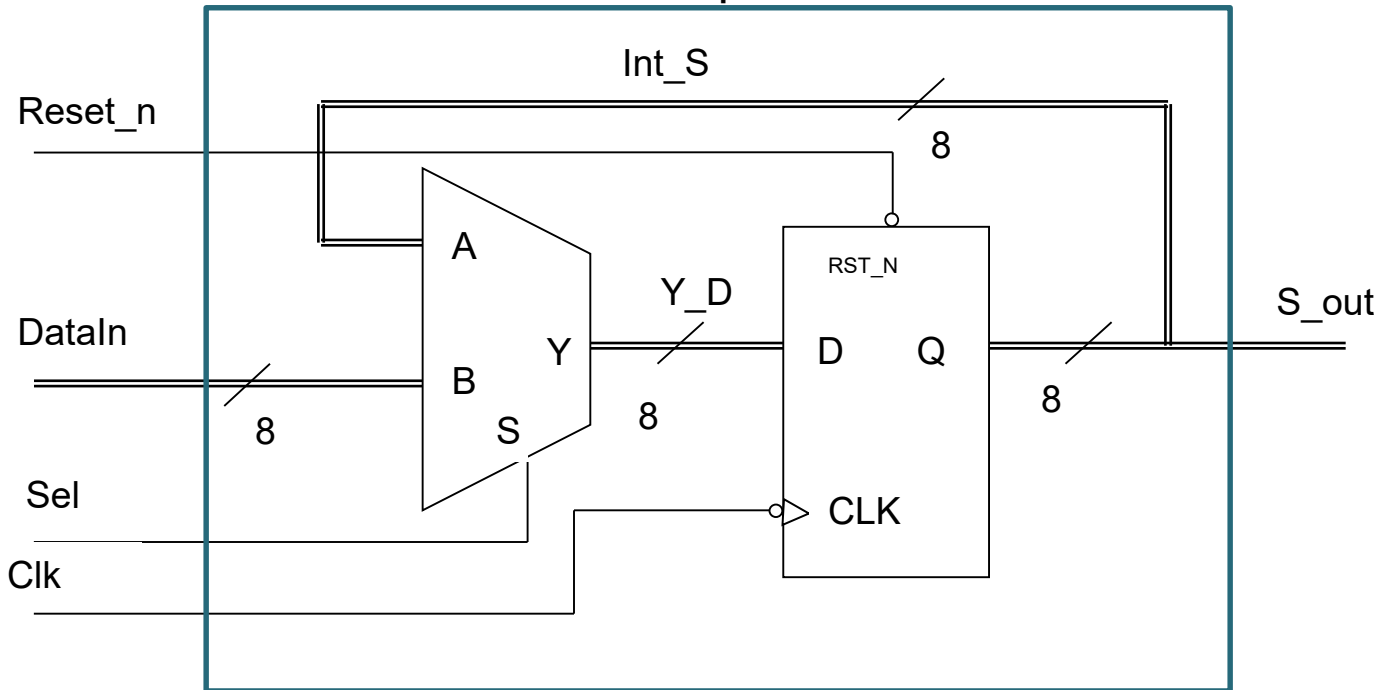

```
ENTITY mux2to1
  PORT(A,B : IN STD_LOGIC_VECTOR(7 downto 0);
        S   : IN STD_LOGIC;
        Y   : OUT STD_LOGIC_VECTOR(7 downto 0));
END mux2to1;
```

```
ENTITY Reg8 IS
  PORT(D : IN STD_LOGIC_VECTOR(7 downto 0);
        clk, rst_n : IN STD_LOGIC;
        Q : OUT STD_LOGIC_VECTOR(7 downto 0));
END Reg8
```