



Exam 2 Practice Problems

Announcements

- HW #7 due Friday
 - This is with new homework groups
- Wed and Fri labs are working on lab 7
- Exam on Monday 10/21

Exam #2 Study Jam

Saturday October 19th

12 noon - 4 pm

Golisano 1360 (ESD lab)

Bring questions

- Write the entity and architecture for a priority encoder with the following requirements:
 - Eight 1-bit inputs : I0 – I7
 - One 3-bit output: num_out
 - Use the following table

Active Input	Num_out	Priority
I7	111	1 st highest priority
I6	110	
I5	101	
I4	100	
I3	011	
I2	010	
I1	001	
I0	000	8 th lowest priority

Complete the output waves for the decode2to4 architecture below.

```
ARCHITECTURE behave OF decode2to4 IS
```


```
    signal sel_bus    : std_logic_vector(1 downto 0);  
    signal Y_bus      : std_logic_vector(3 downto 0);
```

```
BEGIN
```

```
    sel_bus <= s1 & s0;  
    y0 <= Y_bus(0);  
    y1 <= Y_bus(1);  
    y2 <= Y_bus(2);  
    y3 <= Y_bus(3);
```

```
    WITH sel_bus SELECT  
        Y_bus <= "0001" WHEN "00",  
                "0010" WHEN "01",  
                "0100" WHEN "10",  
                "1000" WHEN OTHERS;
```

```
END behave;
```

 

Rewrite the following mux architecture as a case statement

ARCHITECTURE behavioral OF mux IS

SIGNAL selects: STD_LOGIC_VECTOR(1 DOWNTO 0);


BEGIN

selects <= s1 & s0;

output <= A when (selects = "00") ELSE
B when (selects = "01") ELSE
C when (selects = "10") ELSE
D;

END behavioral;

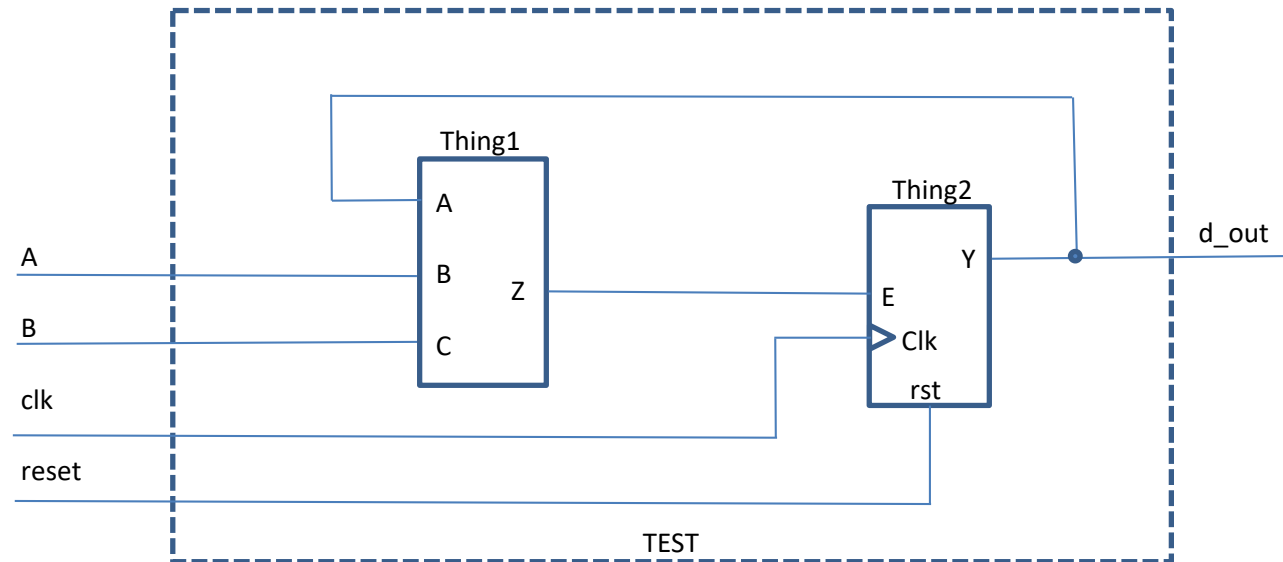Complete the *STRUCTURAL* (hierarchical) VHDL model below. The component declarations for the two components are already given



ENTITY test IS

PORT (A, B, reset, clk : IN STD_LOGIC;
d_out : OUT STD_LOGIC);

end test;

ARCHITECTURE structural OF test IS

COMPONENT Thing2 IS

PORT(E, rst, clk : IN STD_LOGIC;
Y : OUT STD_LOGIC);
END COMPONENT;

COMPONENT Thing1 IS

PORT(A, B, C : IN STD_LOGIC;
Z : OUT STD_LOGIC);
END COMPONENT;