
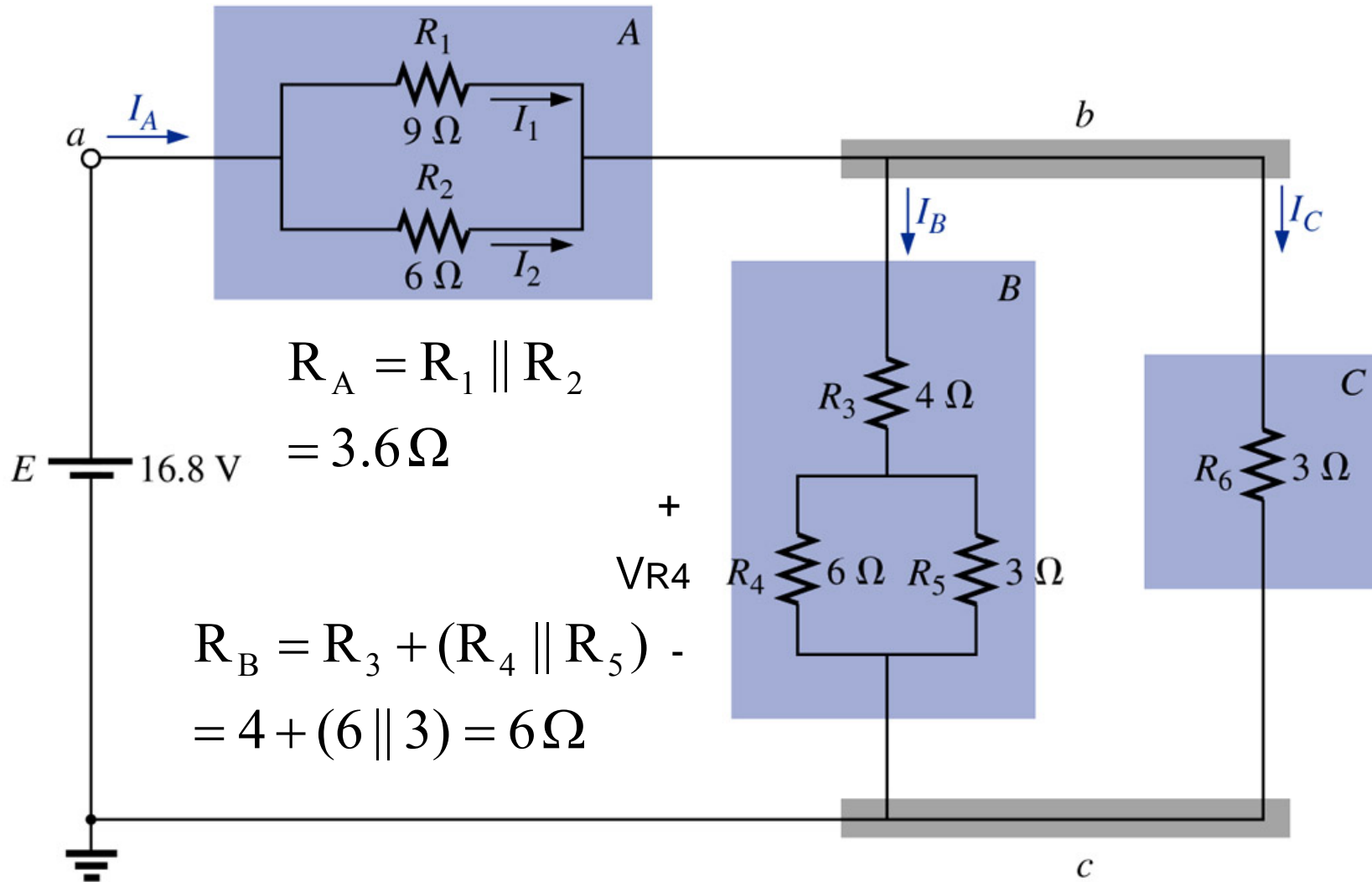

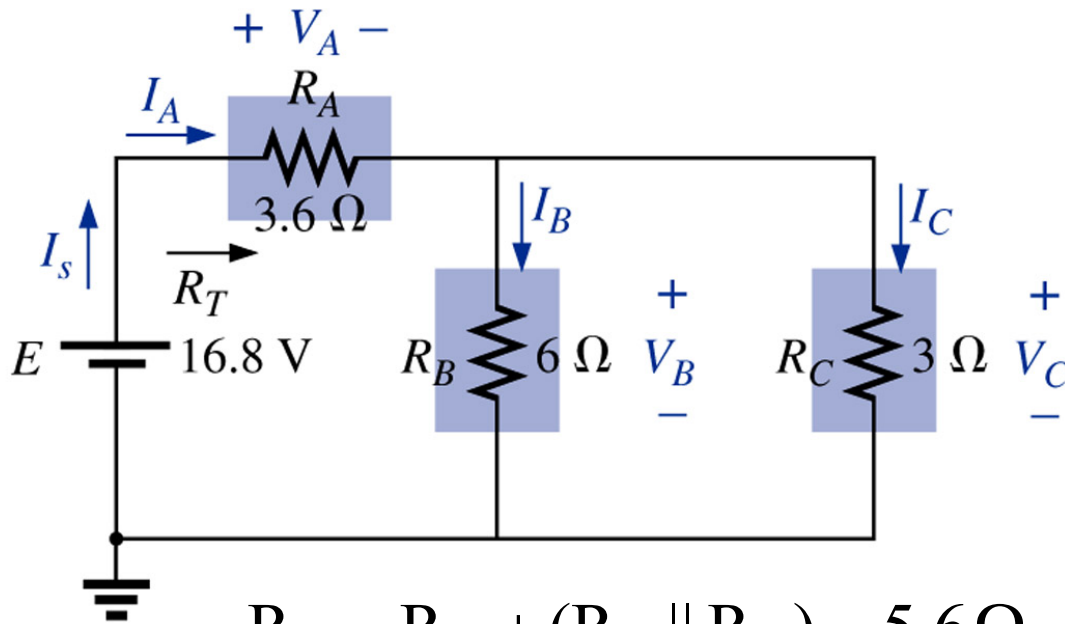
## Breakout #1 – Find $I_1$ , $I_B$ , $I_C$ , $V_{R4}$



## Breakout #1 – Find $I_1$ , $I_B$ , $I_C$ , $V_{R4}$




$$I_C = I_A - I_B \\ = 2 \text{ A}$$

$$R_T = R_A + (R_B \parallel R_C) = 5.6 \Omega$$

$$I_S = I_A = \frac{E}{R_T} = \frac{16.8 \text{ V}}{5.6 \Omega} = 3 \text{ A}$$

$$I_B = I_A \frac{R_B \parallel R_C}{R_B} = 3 \text{ A} \frac{2 \Omega}{6 \Omega} = 1 \text{ A}$$
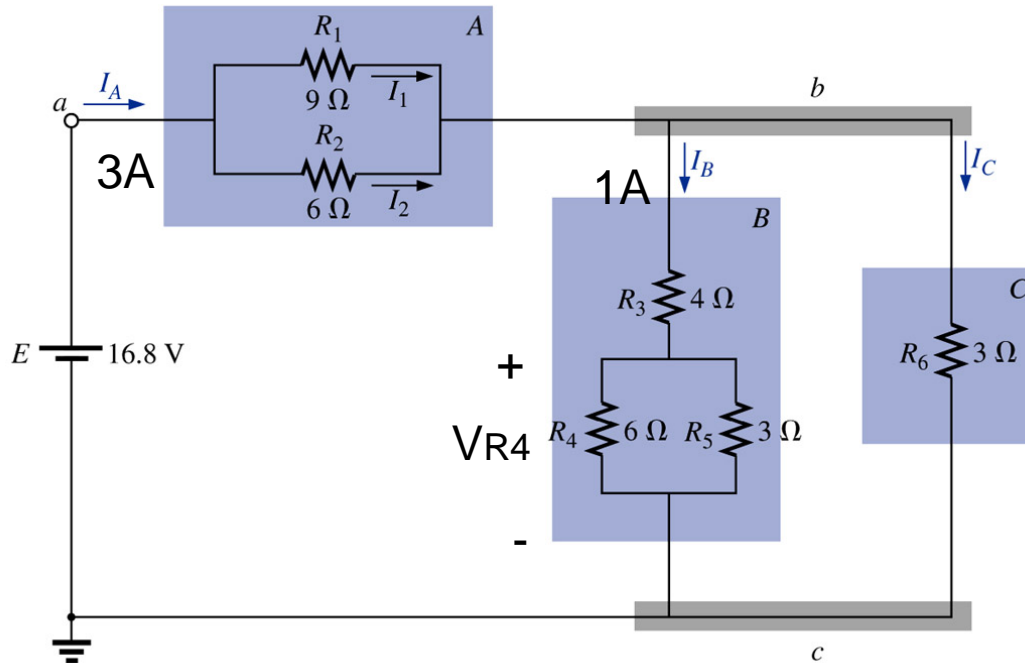
## Breakout #1 – Find $I_1$ , $I_B$ , $I_C$ , $V_{R4}$



$$V_{R4} = I_B \cdot (R_4 \parallel R_5)$$

$$V_{R4} = 1\text{ A} \cdot 2\Omega$$


$$= 2\text{ V}$$

$$I_1 = I_A \frac{R_A}{R_1} = 3\text{ A} \frac{3.6\Omega}{9\Omega} = 1.2\text{ A}$$

## Breakout #2 – Ladder Network

### ■ Find $V_1$ and $I_1$

□ Hint: Start by finding  $R_t$

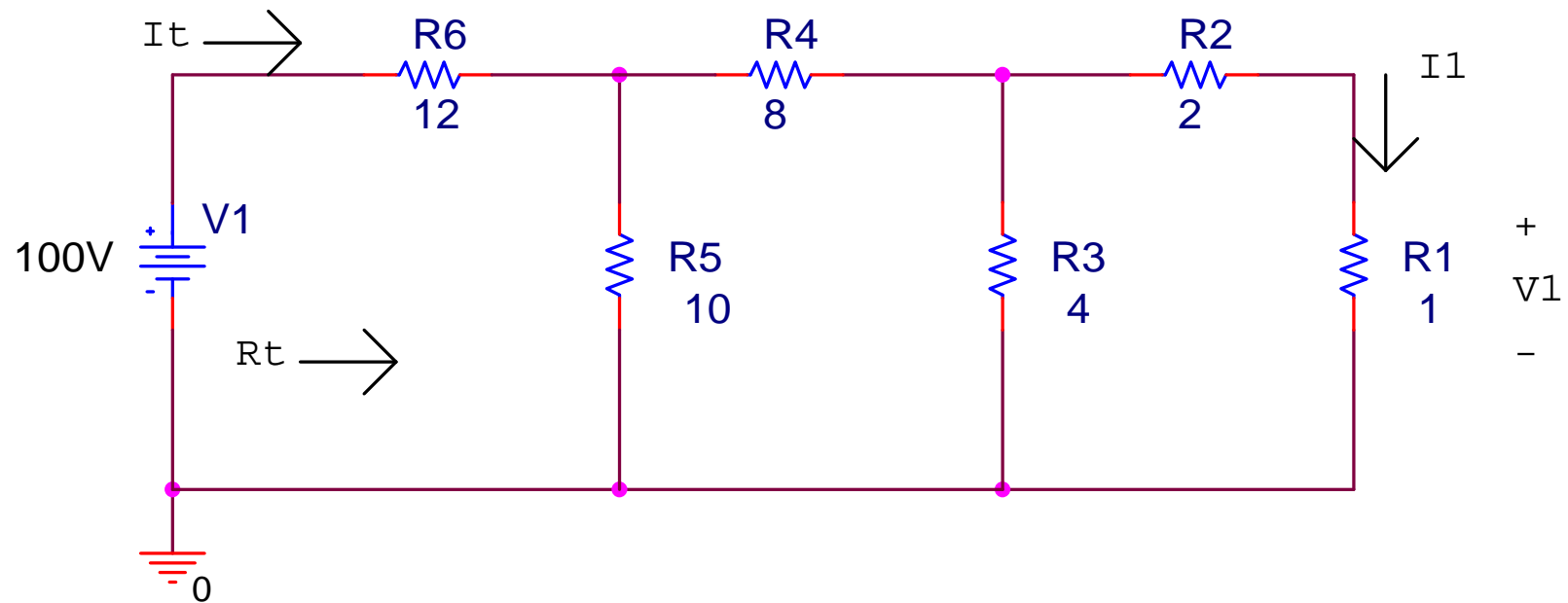


### 7.3 LADDER NETWORKS


↖ SPECIFIC CASE OF SERIES-PARALLEL NETWORKS, EASILY RECOGNIZED

METHOD 1: REDUCE THE NETWORK & FIND  $R_T$ ,  $I_T$ . THEN WORK BACK INTO THE NETWORK TO FIND THE UNKNOWN(S).

(EXAMPLE) FIND  $V_1$  &  $I_1$ :

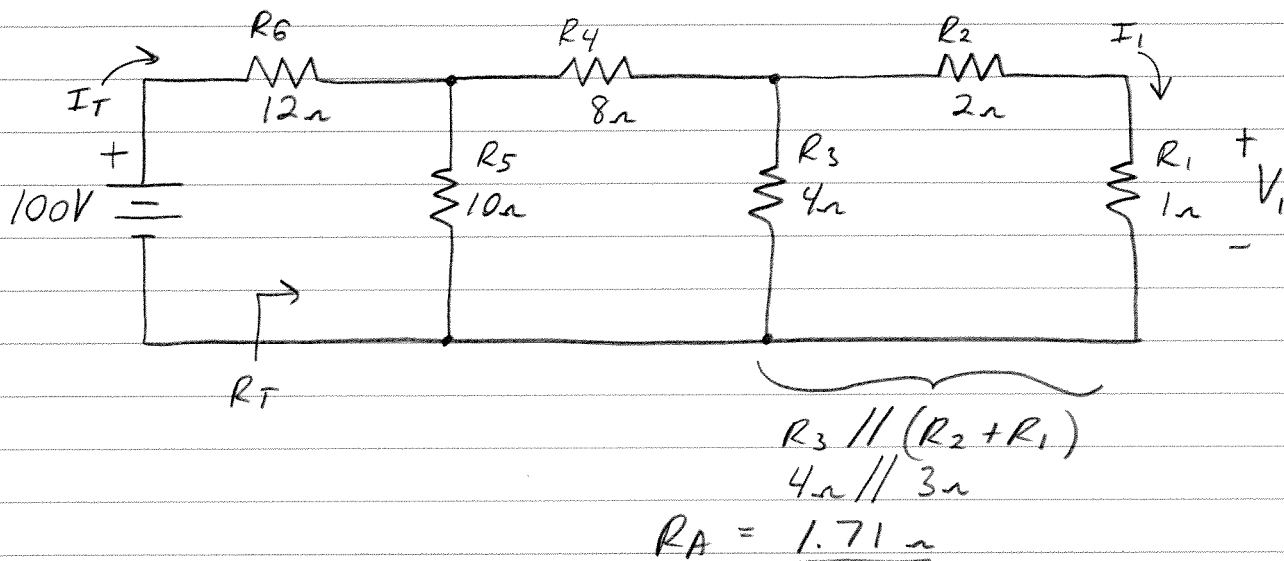


REDRAW:

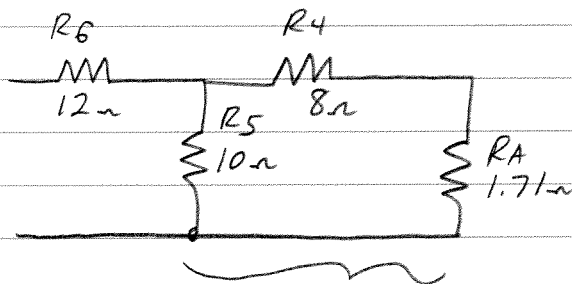

$$\begin{aligned} R_B &= R_5 \parallel (R_4 + R_A) \\ &= 10\Omega \parallel 9.71\Omega \\ \underline{R_B} &= \underline{4.93\Omega} \end{aligned}$$


REORAW :

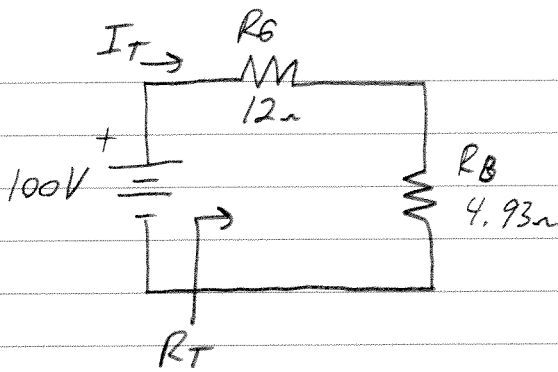

$$R_T = 16.93\Omega$$

$$I_T = \frac{100V}{R_T} = \frac{100V}{16.93\Omega} = 5.91A$$

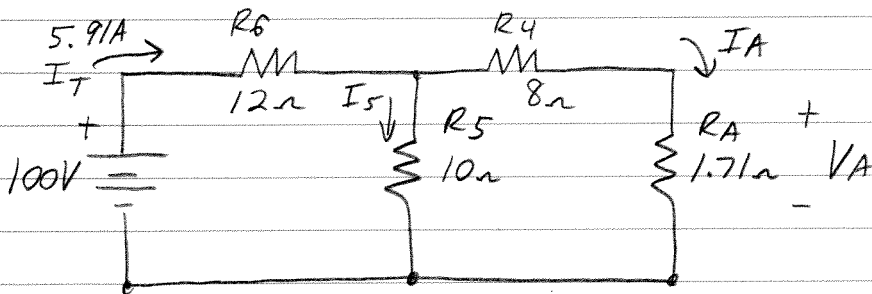
BACK TO PREVIOUS CIRCUIT (WORKING TOWARDS  $R_1$  PARAM.) :



$$I_A = I_T \left( \frac{R_5}{R_5 + (R_4 + R_A)} \right) = 5.91A \left( \frac{10}{10 + 9.71} \right) = 3A$$

$$\therefore V_A = I_A R_A = (3A)(1.71\Omega) = 5.13V$$


EXPAND  $R_A$  :

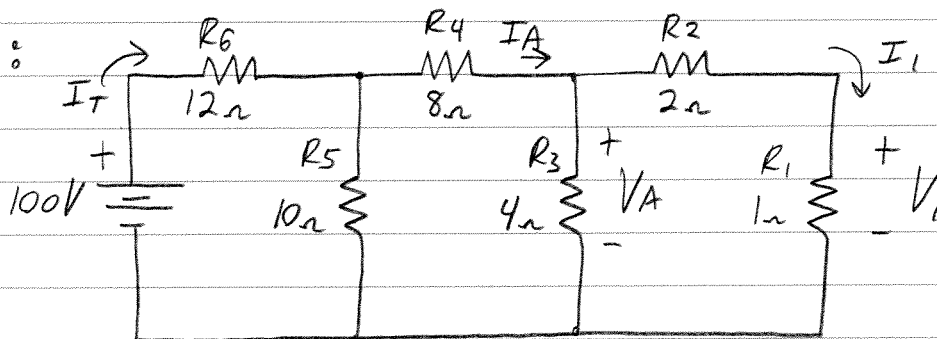

$$V_1 = V_A \frac{R_1}{R_1 + R_2} = 5.13V \left( \frac{1}{3} \right) = 1.71V$$

## Breakout #3 – Voltage Divider Supply

- Find  $V_B$  and  $V_C$

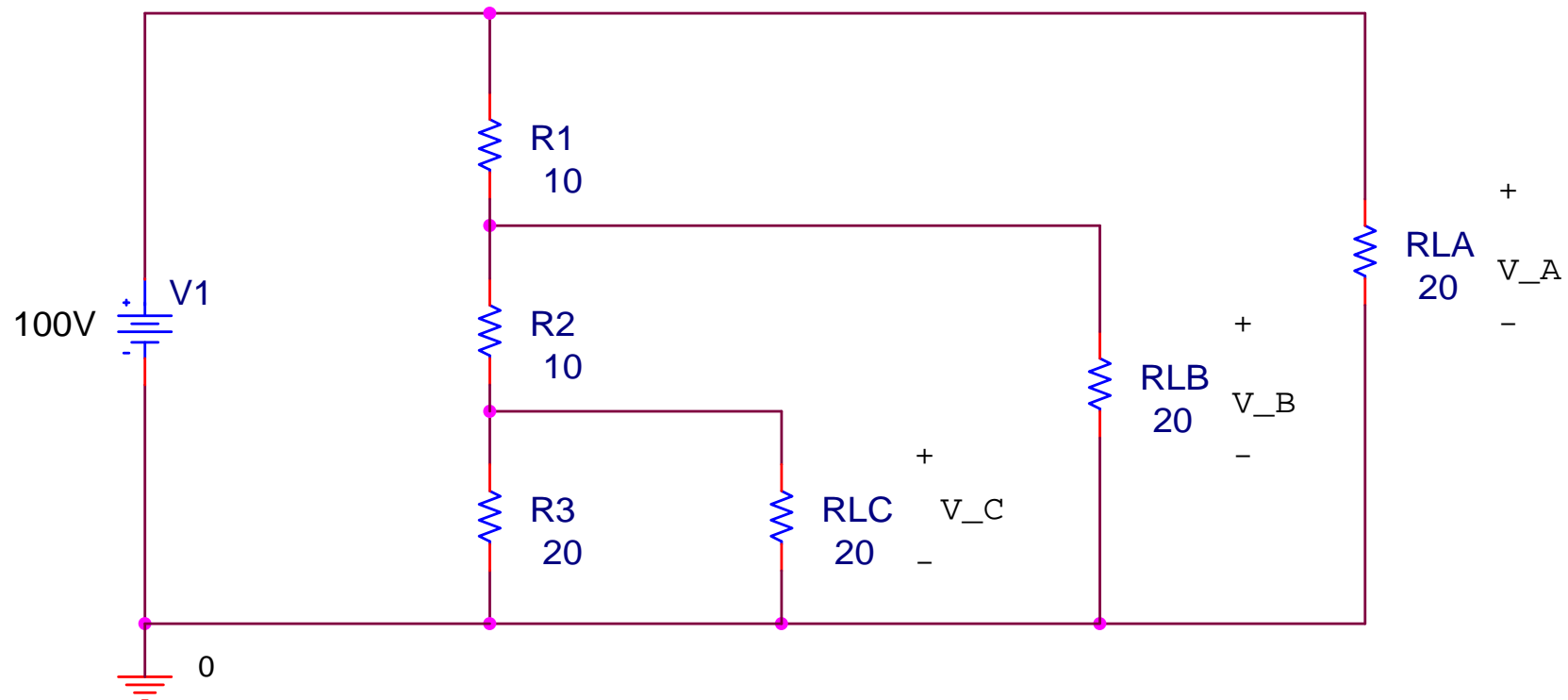


$$I_1 = I_A \left( \frac{R_3}{R_3 + R_2 + R_1} \right) = 3A \left( \frac{4}{4 + 2 + 1} \right) = \boxed{1.71A}$$

$$\text{CHECK: } I_1 = \frac{V_1}{R_1} = \frac{1.71V}{1\Omega} = \underline{1.71A} \quad \checkmark$$

7.4 VOLTAGE DIVIDER SUPPLY (LOADED & UNLOADED)  
 - UTILIZE ONE SUPPLY & RESISTORS TO PROVIDE SEVERAL OUTPUT VOLTAGES

(EXAMPLE)

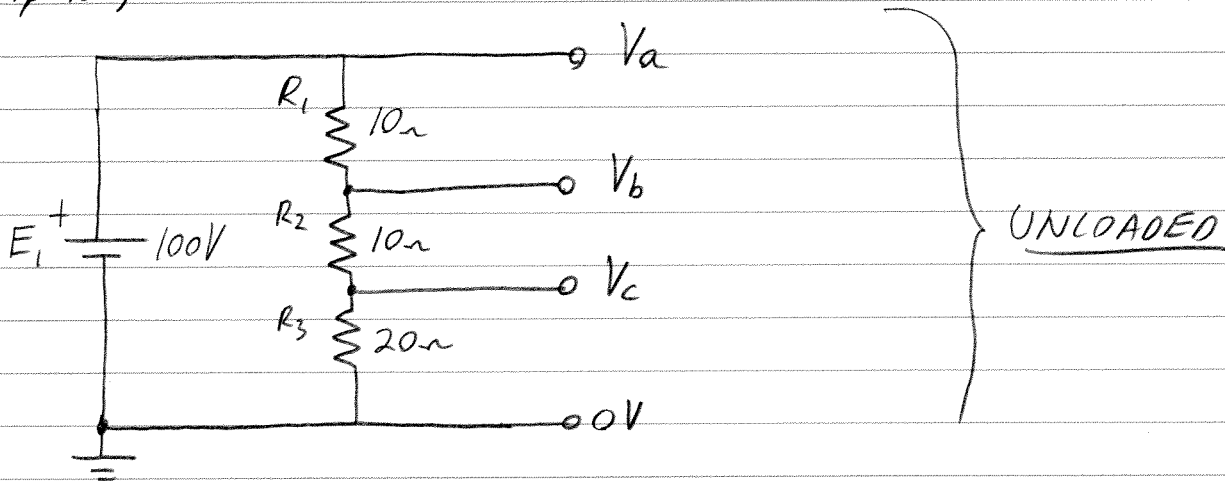

$$\underline{V_a = 100V}$$


$$V_b = 100V \frac{(R_2 + R_3)}{R_2 + R_3 + R_1} = 100V \left( \frac{30}{40} \right) = \underline{\underline{75V}}$$

$$V_c = 100V \frac{R_3}{R_1 + R_2 + R_3} = 100V \left( \frac{20}{40} \right) = \underline{\underline{50V}}$$

3 VOLTAGES FOR THE PRICE OF ONE ...  
 WHAT'S THE CATCH?



# LOADED VOLTAGE DIVIDER SUPPLY :

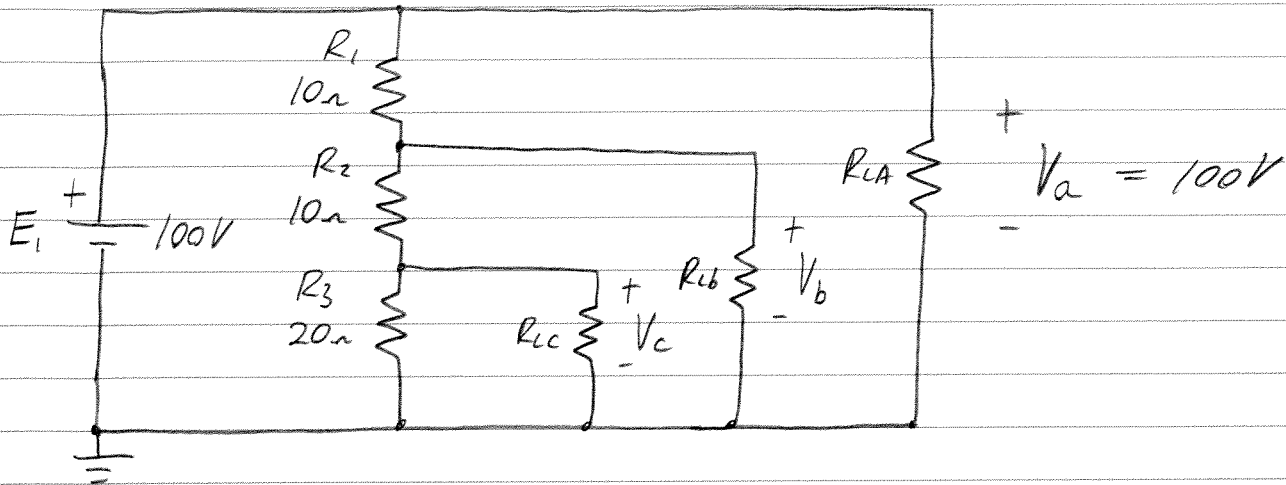

$$V_b = \left( \frac{[(R_3 // R_{Lc}) + R_2] // R_{Lb}}{[(R_3 // R_{Lc}) + R_2] // R_{Lb} + R_1} \right) E_1 \quad (1)$$

$$V_c = \left( \frac{R_3 // R_{Lc}}{R_3 // R_{Lc} + R_2} \right) V_b \quad (2)$$

FOR  $R_{Lb} = R_{Lc} = 20 \Omega$

$$1 \rightarrow V_b = \left( \frac{[20 // 20 + 10] // 20}{[20 // 20 + 10] // 20 + 10} \right) 100V = \left( \frac{20 // 20}{20 // 20 + 10} \right) 100V = \left( \frac{10}{10 + 10} \right) 100V$$

$$\therefore V_b = 50V \leftarrow \begin{matrix} 75V \\ \text{UNLOADED} \end{matrix}$$

$$2 \rightarrow V_c = \left( \frac{20 // 20}{20 // 20 + 10} \right) 50V = \left( \frac{10}{10 + 10} \right) 50V = \underline{\underline{25V}} \leftarrow \begin{matrix} 50V \\ \text{UNLOADED} \end{matrix}$$