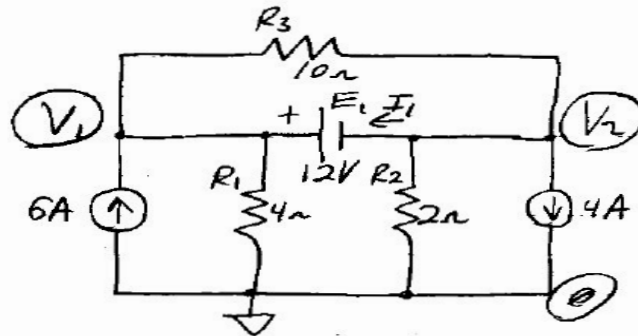


IF A VOLTAGE SOURCE IS PRESENT :

- 1 - CONVERT IT & SERIES "R" TO A PRACTICAL CURRENT SOURCE
- 2 - CHOOSE ONE END OF THE <sup>VOLTAGE</sup> SOURCE AS THE REF. NODE
- 3 - SUPERNODE APPROACH

(EXAMPLE 8.22)

Example 8.24 in 13th ed



(FIND THE NODE VOLTAGES)

"MODIFIED" SUPERNODE APPROACH

$$\textcircled{V_1} : 6 + I_1 = \frac{V_1 - V_2}{R_3} + \frac{V_1}{R_1}$$

$$6 + I_1 = \frac{V_1}{10} - \frac{V_2}{10} + \frac{V_1}{4} \Rightarrow 6 = 0.35V_1 - 0.1V_2 - I_1 \quad (1)$$

$$\textcircled{V_2} : 0 = \frac{V_2 - V_1}{R_3} + I_1 + \frac{V_2}{R_2} + 4 \Rightarrow 0 = \frac{V_2}{10} - \frac{V_1}{10} + I_1 + \frac{V_2}{2} + 4$$

$$-4 = -0.1V_1 + 0.6V_2 + I_1 \quad (2)$$

TWO EQUATIONS, THREE UNKNOWN! WE NEED ANOTHER INDEPENDENT EQUATION :


$$V_1 - V_2 = E_1 \Rightarrow 12 = V_1 - V_2 \quad (3)$$

$$\text{SOLVE : } \begin{aligned} 6 &= 0.35V_1 - 0.1V_2 - I_1 \\ -4 &= -0.1V_1 + 0.6V_2 + I_1 \\ 12 &= V_1 - V_2 + 0I_1 \end{aligned}$$

$$\boxed{\begin{aligned} V_1 &= 10.67V \\ V_2 &= -1.33V \\ I_1 &= -2.13A \end{aligned}}$$


# ANOTHER NODAL ANALYSIS PROBLEM (ICP)

(EXAMPLE)

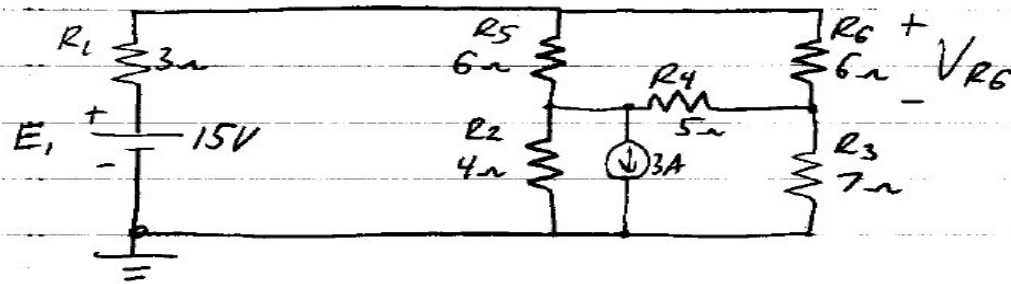

USE NODAL ANALYSIS TO FIND ALL NODE VOLTAGES &  $V_{R6}$ .

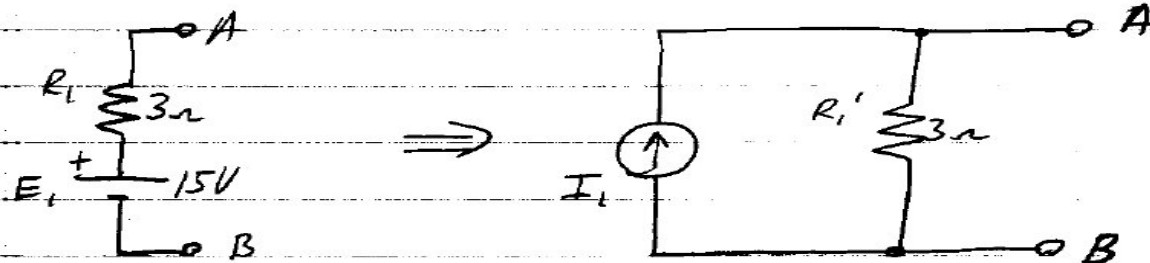
ONE APPROACH  
 (1) → CONVERT  $E_1, R_1$  TO  $I_1, R_1'$  (SOURCE TRANSFORMATION)



$$I_1 = \frac{E_1}{R_1} = \frac{15V}{3\Omega} = \underline{\underline{5A}}$$

REDRAW THE CIRCUIT :

(2) ASSIGN NODE LABELS

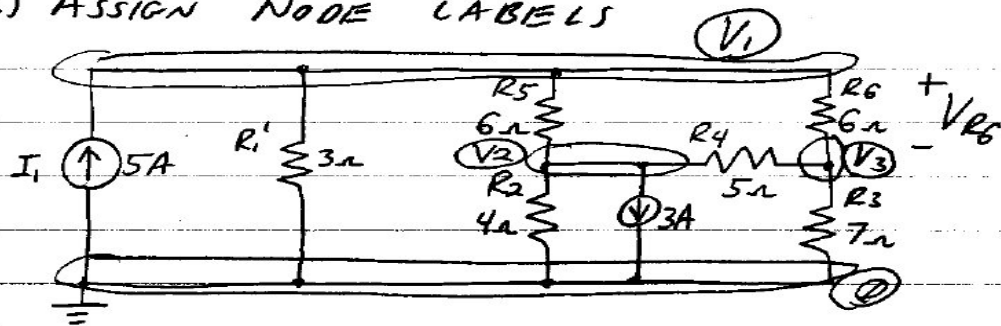

(3) KCL AT EACH NODE

$$\sum I_{\text{ENTERING}} = \sum I_{\text{LEAVING}}$$

For  $V_1$  :  $I_1 = \frac{V_1}{R_1'} + \frac{V_1 - V_2}{R_5} + \frac{V_1 - V_3}{R_6}$

$$I_1 = V_1 \left( \frac{1}{R_1'} + \frac{1}{R_5} + \frac{1}{R_6} \right) - V_2 \left( \frac{1}{R_5} \right) - V_3 \left( \frac{1}{R_6} \right)$$

$$5 = 0.6667 V_1 - 0.1667 V_2 - 0.1667 V_3 \quad (1)$$

For  $V_2$  :  $0 = 3 + \frac{V_2 - V_1}{R_5} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_4}$

$$-3 = -V_1 \left( \frac{1}{R_5} \right) + V_2 \left( \frac{1}{R_5} + \frac{1}{R_2} + \frac{1}{R_4} \right) - V_3 \left( \frac{1}{R_4} \right)$$

$$-3 = -0.1667 V_1 + 0.6167 V_2 - 0.2 V_3 \quad (2)$$

For  $V_3$ :

$$0 = (V_3 - V_1)/R_6 + (V_3 - V_2)/R_4 + V_3/R_3$$


$$0 = -V_1 \left( \frac{1}{R_6} \right) - V_2 \left( \frac{1}{R_4} \right) + V_3 \left( \frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_6} \right)$$

$$0 = -0.1667 V_1 - 0.2 V_2 + 0.5096 V_3 \quad (3)$$

Solve (1)  $\rightarrow$  (3) :

$$\boxed{\begin{aligned} V_1 &= 7.24V \\ V_2 &= -2.45V \\ V_3 &= 1.41V \end{aligned}}$$

Find  $V_{R_6}$ :

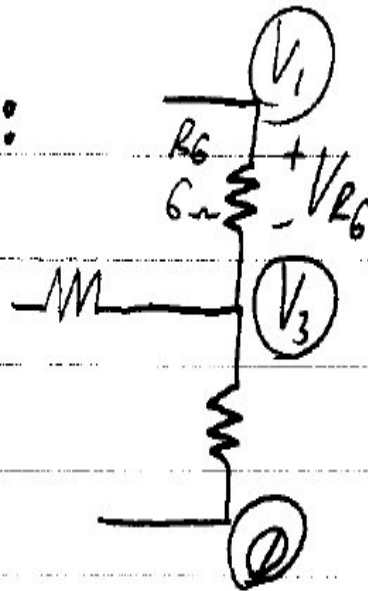

$$V_{R_6} = V_1 - V_3$$

$$= 7.24V - 1.41V = \boxed{5.83V}$$