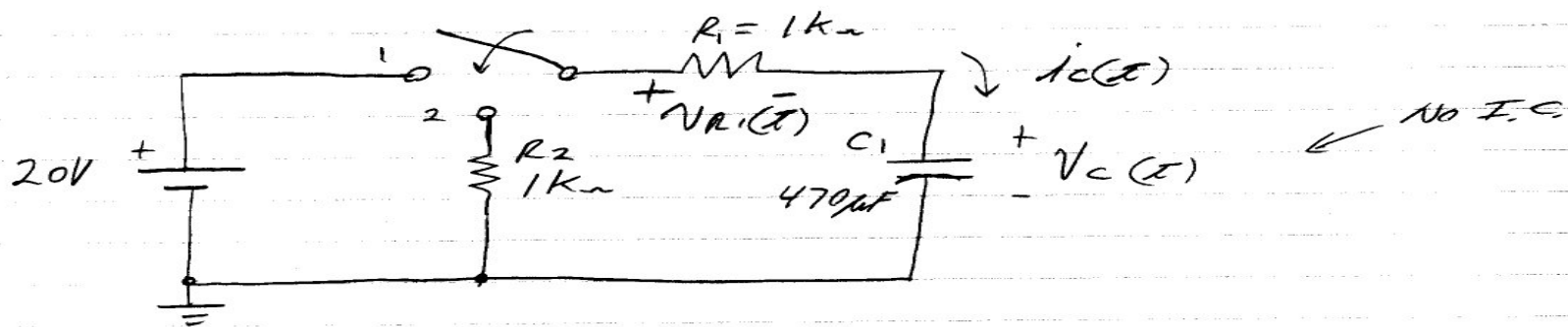


SIMPLE CAPACITOR CIRCUIT (CHARGE/DISCHARGE)




At $t = 0$, SW \rightarrow POSITION 1
 At $t = 10\text{ SEC}$, SW \rightarrow POSITION 2

FIND :

- a) τ
- b) $i_C(t)$
- c) $V_{R_1}(t)$
- d) $V_C(t)$
- e) t For $V_C(t) = 10V$

FOR BOTH CHARGE & DISCHARGE

CHARGE CIRCUIT

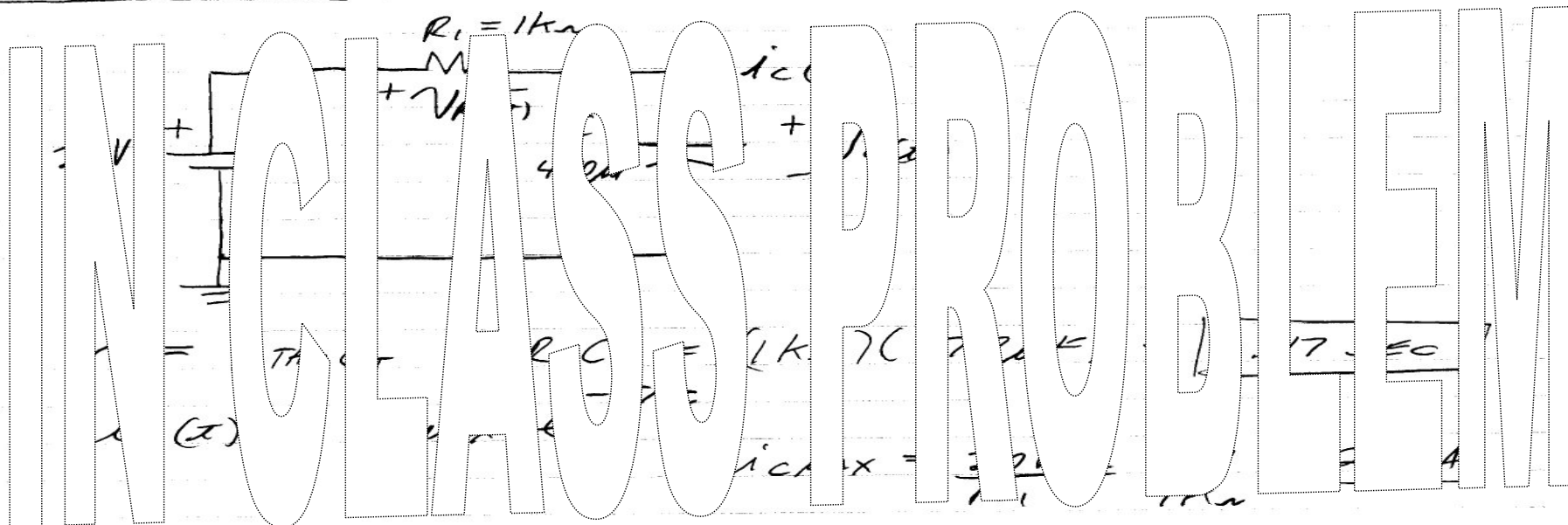

$$i_c(t) = 20 \times 10^{-3} e^{-t/0.47} \text{ A}$$


$$V_{R_1}(t) = R_1 \cdot i_c(t) = (1k\Omega) \cdot i_c(t)$$

$$V_{R_1}(t) = 20 e^{-t/0.47} \text{ V}$$

$$V_C(t) = 20V - V_{R_1}(t) = 20 - 20 e^{-t/0.47}$$

$$V_C(t) = 20(1 - e^{-t/0.47}) \text{ V}$$

SKETCH

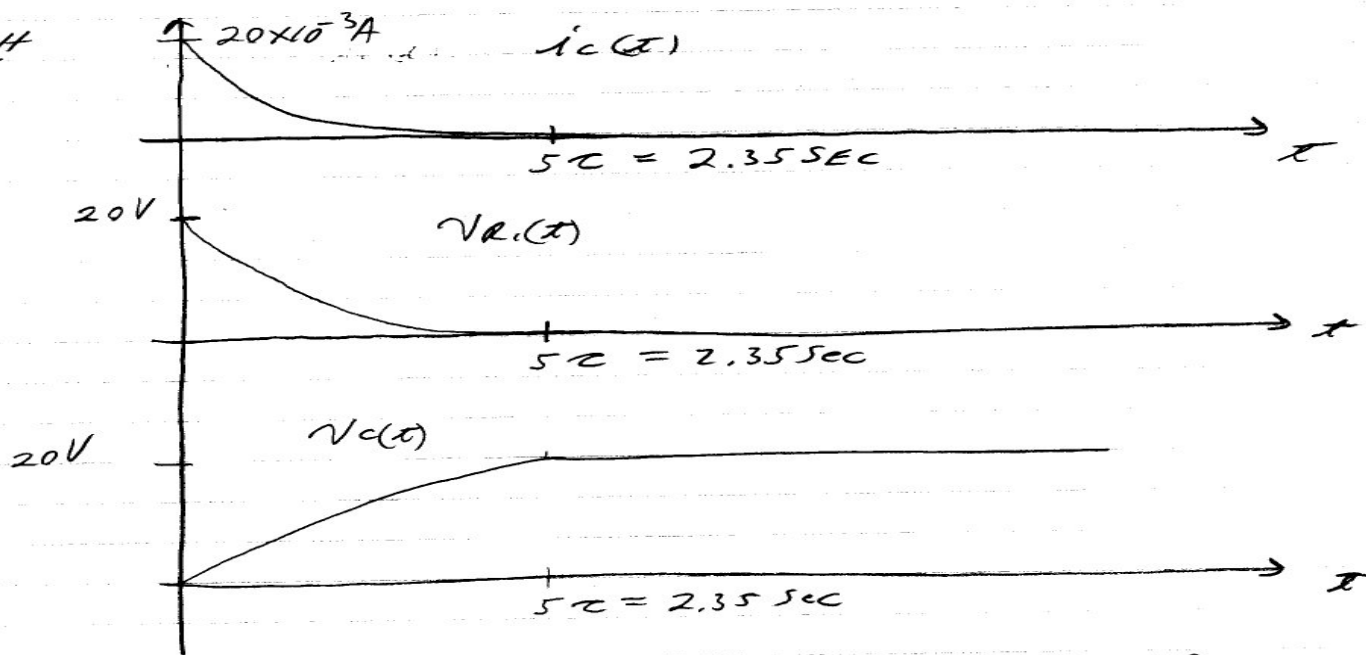

t For $V_C(t) = 10 \text{ V}$? \leftarrow AROUND 0.45 sec ($1\tau \rightarrow 63\%$)

$$10 = 20(1 - e^{-t/0.47})$$


$$+0.5 = 1 - e^{-t/0.47}$$

$$\ln(0.5) = \ln(e^{-t/0.47})$$

$$-0.693 = -t/0.47$$

$$t = 0.326 \text{ SECONDS}$$

DISCHARGE
VALID FOR
 $t > 10$

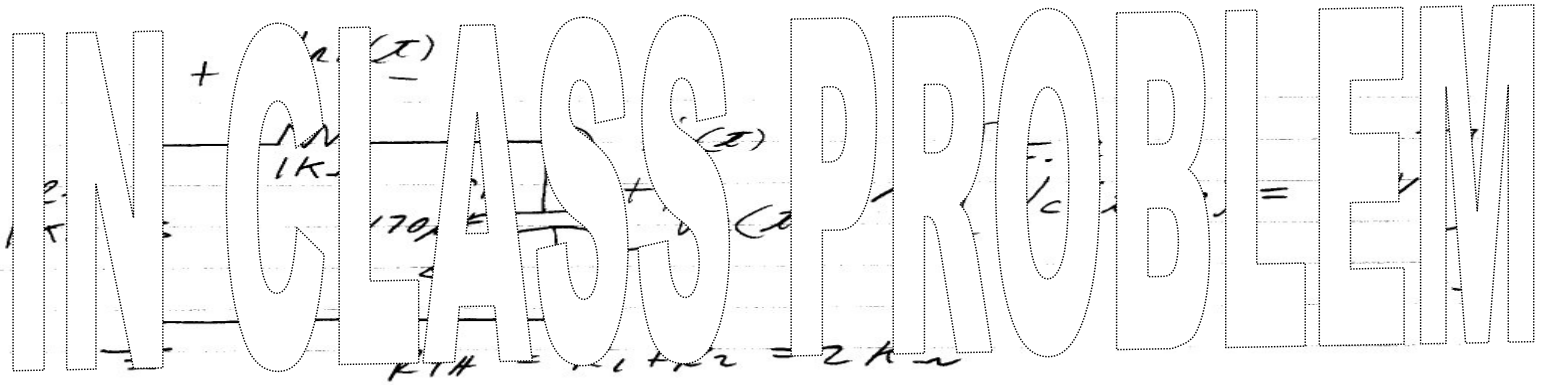

$$\tau = R_{TH} \cdot C_T = (2k\Omega)(470\mu F) = \boxed{940ms}$$

$$i_C(t) = -i_{C_{MAX}} e^{-t/\tau} \leftarrow \text{GENERAL FORM}$$

$$i_{C_{MAX}} = \frac{20V}{2k\Omega} = \underline{10mA}$$

SWITCH CLOSED AT $t = 10$

$$\therefore i_C(t) = -10 \times 10^{-3} e^{-(t-10)/0.94} \text{ A}$$

$$V_{R1}(t) = i_C(t) \cdot R_1 = \boxed{-10 e^{-(t-10)/0.94} \text{ V}}$$

$$V_C(t) = V_{C_{MAX}} e^{-(t-10)/0.94} \text{ V}$$

$$\boxed{V_C(t) = 20V e^{-(t-10)/0.94} \text{ V}}$$

t For $V_C(t) = 10V$?

$$10 = 20 e^{-(t-10)/0.94}$$

$$0.5 = e^{-(t-10)/0.94}$$

$$\ln 0.5 = \ln e^{-(t-10)/0.94}$$


$$-0.693 = -(t-10)/0.94$$

$$0.693 = (t-10)/0.94$$

$$0.652 = t - 10$$


$$t = 10.652$$

SKETCH - DISCHARGE

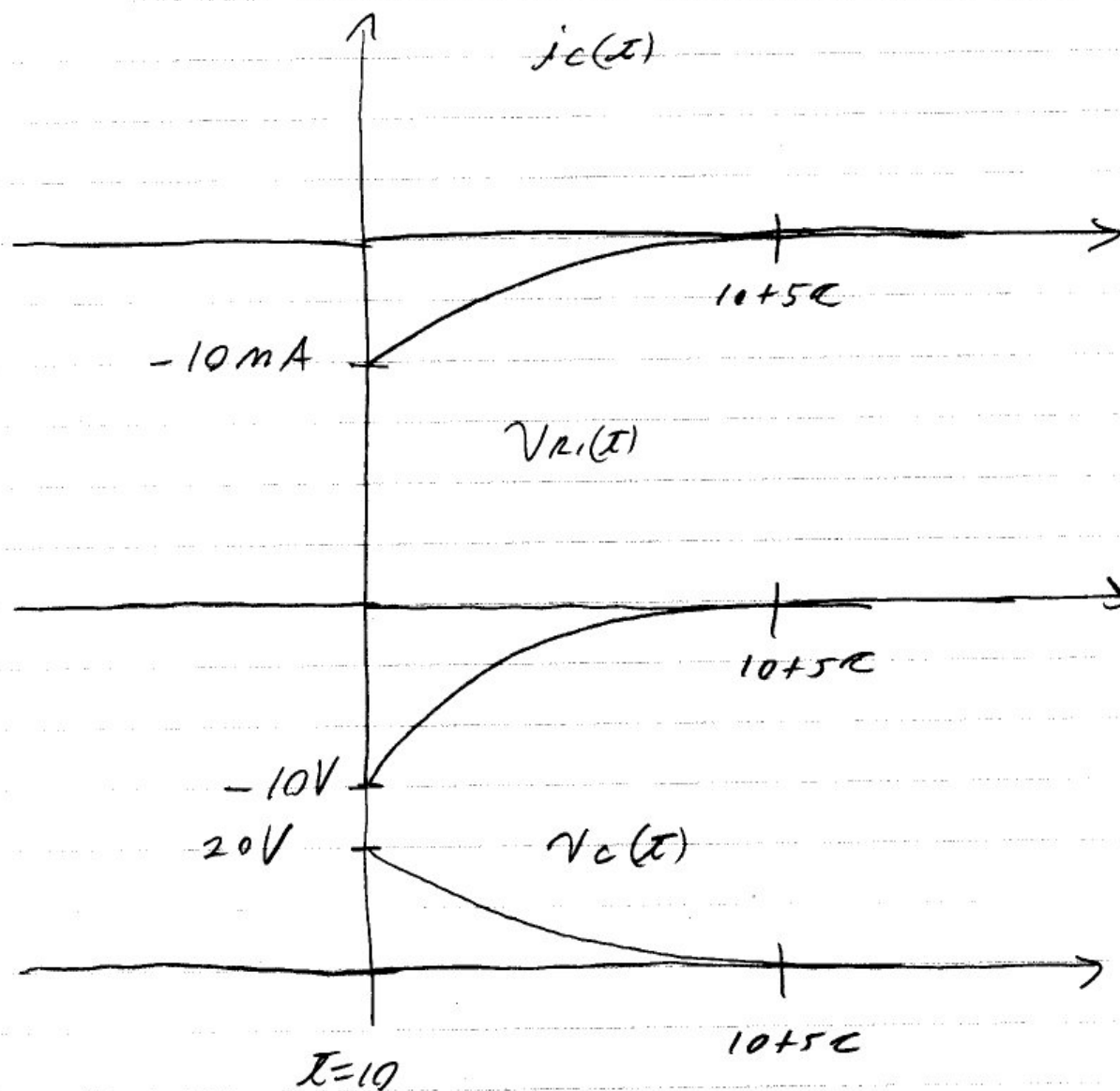

10.13 CAPACITORS IN SERIES & PARALLEL

SERIES

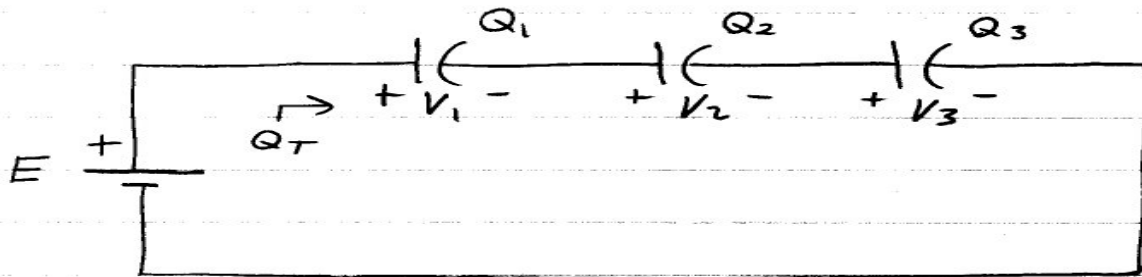

RECALL: $I = \frac{Q}{t}$.° $Q = I \cdot t$

$Q_T = Q_1 = Q_2 = Q_3$, THE SAME CHARGE EXISTS ON EACH CAPACITOR

KVL: $E = V_1 + V_2 + V_3$ (1)

RECALL: $V = \frac{Q}{C}$ (2)

(2) INTO (1):

$$\frac{Q_T}{C_T} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} + \frac{Q_3}{C_3} \quad (3)$$

SINCE $Q_T = Q_1 = Q_2 = Q_3$, (3) BECOMES :

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

°° $C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$ (4)

GENERALIZING, FOR N CAPACITORS IN SERIES:


$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$$

CAPACITORS IN
SERIES COMBINE
LIKE RESISTORS IN
PARALLEL

FOR TWO CAPACITORS IN SERIES:

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{\frac{C_1 C_2}{C_1} + \frac{C_1 C_2}{C_2}} = \boxed{\frac{C_1 C_2}{C_2 + C_1}}$$

PARALLEL

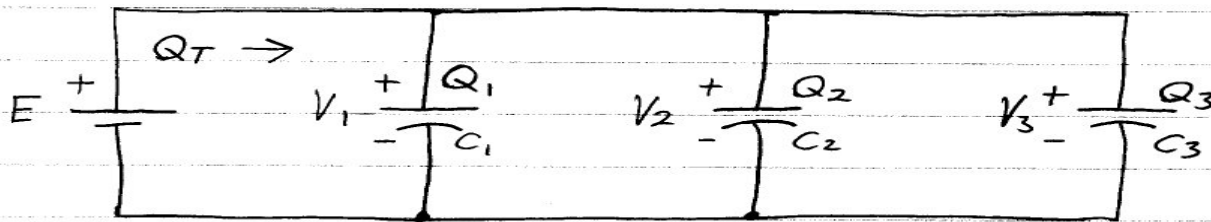

$$Q_T = Q_1 + Q_2 + Q_3 \quad (5)$$

USING $Q = CV$, (5) BECOMES:

$$C_T \cdot E = C_1 \cdot V_1 + C_2 \cdot V_2 + C_3 \cdot V_3$$

BUT $V_1 = V_2 = V_3 = E$ \therefore


$$\boxed{C_T = C_1 + C_2 + C_3}$$

FOR N CAPACITORS IN PARALLEL:

$$\boxed{C_T = C_1 + C_2 + \dots + C_N}$$

CAPACITORS IN PARALLEL
COMBINE LIKE RESISTORS
IN SERIES

(EXAMPLE 1) FIND C_T :

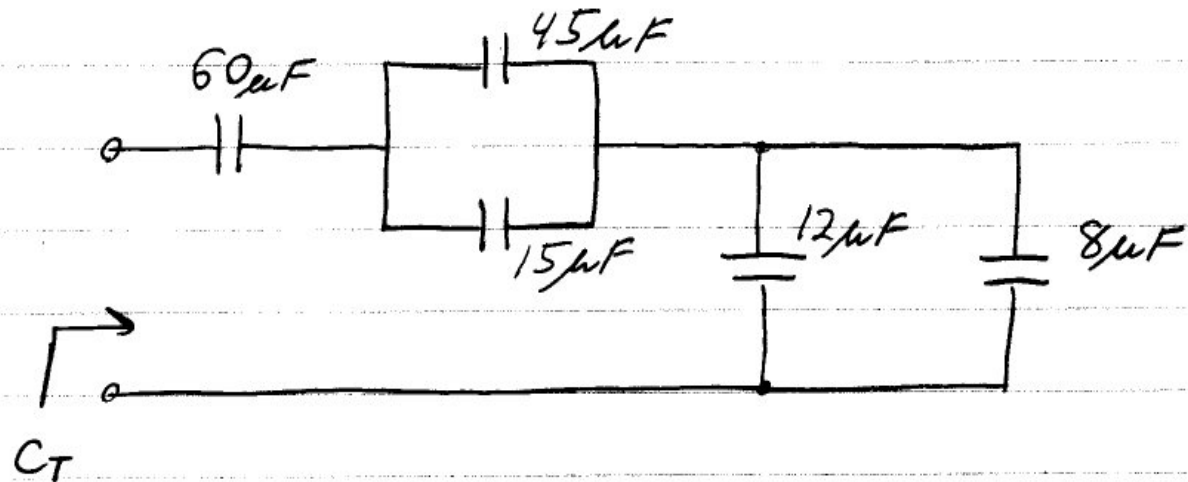

$$\begin{aligned}
 &12\mu F + 8\mu F = 20\mu F \\
 &15\mu F \parallel 45\mu F = 10\mu F \\
 &20\mu F + 10\mu F = 30\mu F \\
 &30\mu F + 60\mu F = 90\mu F
 \end{aligned}$$