


Ohm's Law

- Defines the relationship between voltage, current and resistance in a electric circuit.
- Discovered by Georg Simon Ohm in 1827
- Ohm's Law states:

That current in a resistor varies in direct proportion to the voltage applied to it and is inversely proportional to the resistor's value.



- Stated Mathematically: $I = \frac{V}{R}$

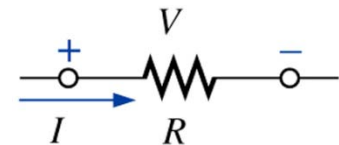Where : I is the current; in Amperes
V is the potential difference; in Volts
R is the resistance; in Ohms




Voltage Sources & Voltage Drops

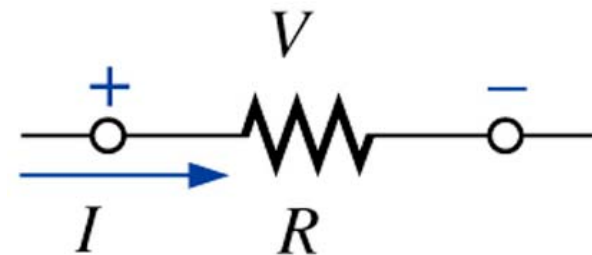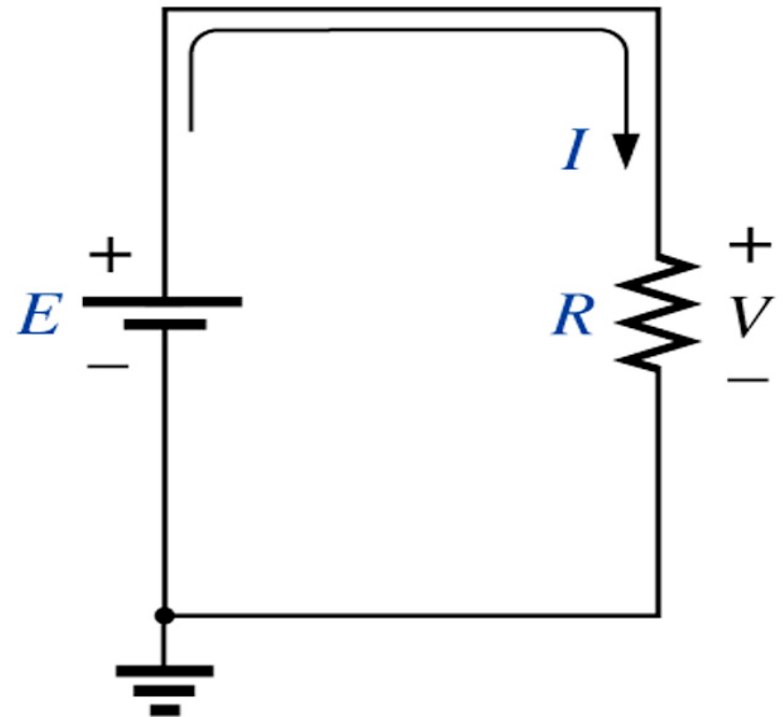- The potential difference is sometimes designated by E instead of V .
- The symbol E applies to voltage sources.
- The symbol V applies to voltage drops across resistors.
- Both (E & V) are used interchangeably in the Ohm's Law equations



Ohm's Law Triangle

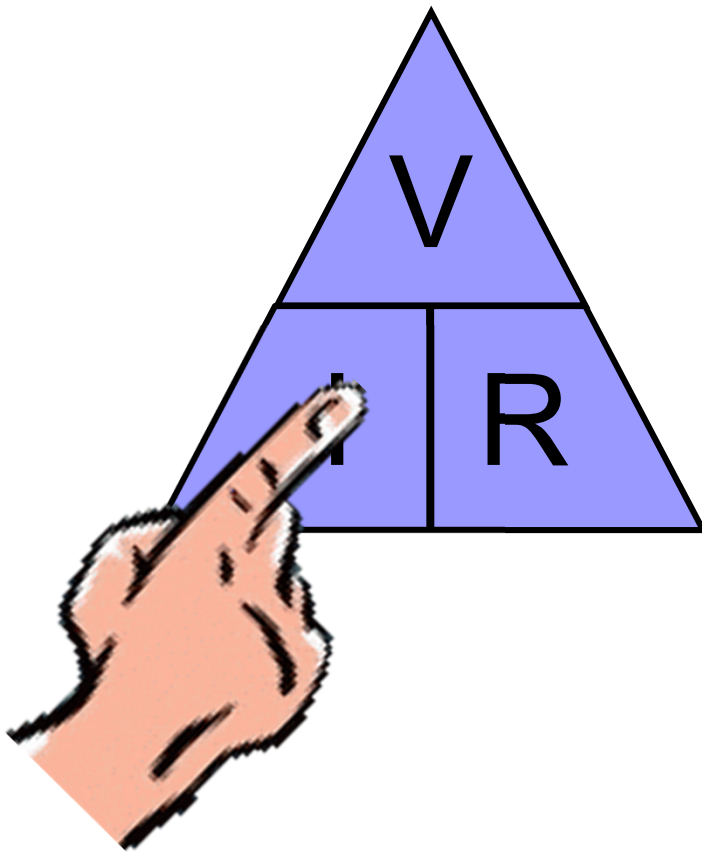


$$I = \frac{V}{R} \text{ (amperes, A)}$$

$$R = \frac{V}{I} \text{ (ohms, } \Omega \text{)}$$

$$V = IR \text{ (volts, V)}$$

Ohm's Law Triangle

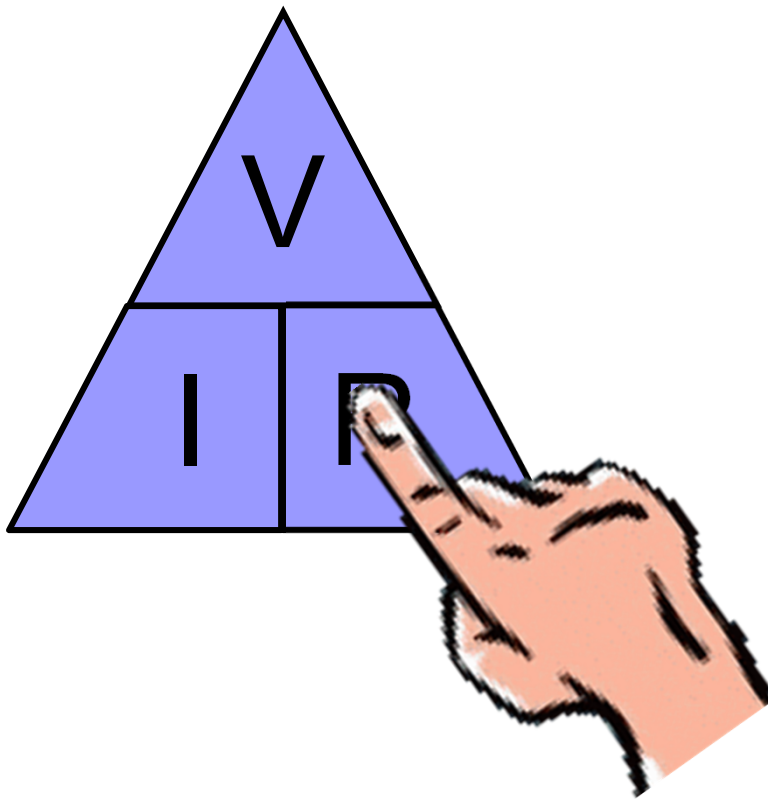


$$I = \frac{V}{R} \text{ (amperes, A)}$$

$$R = \frac{V}{I} \text{ (ohms, } \Omega \text{)}$$

$$V = IR \text{ (volts, V)}$$

Ohm's Law Triangle

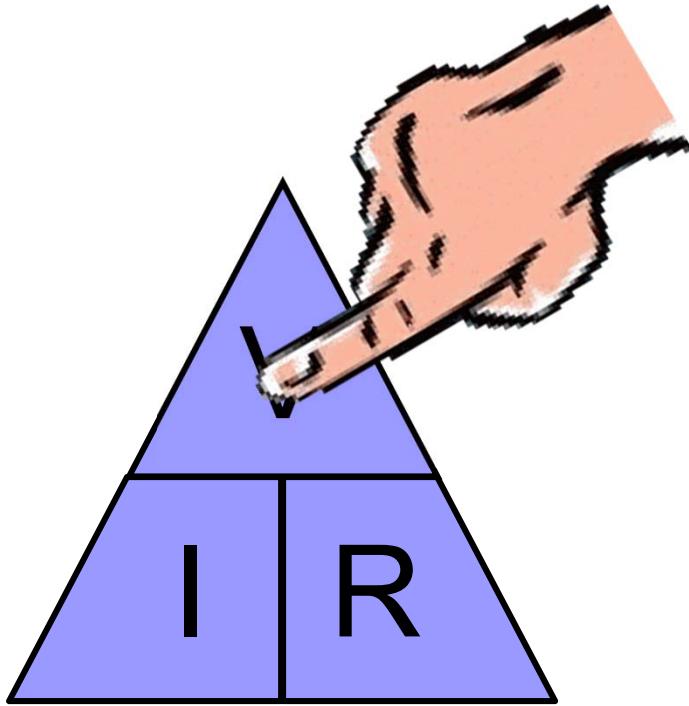



$$I = \frac{V}{R} \text{ (amperes, A)}$$

$$R = \frac{V}{I} \text{ (ohms, } \Omega \text{)}$$

$$V = IR \text{ (volts, V)}$$

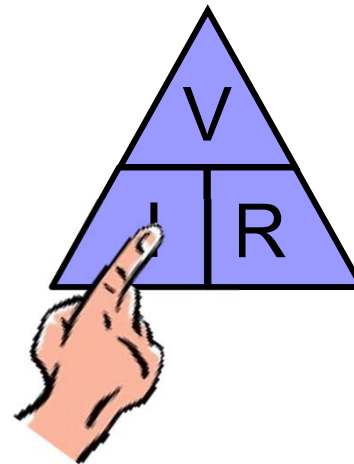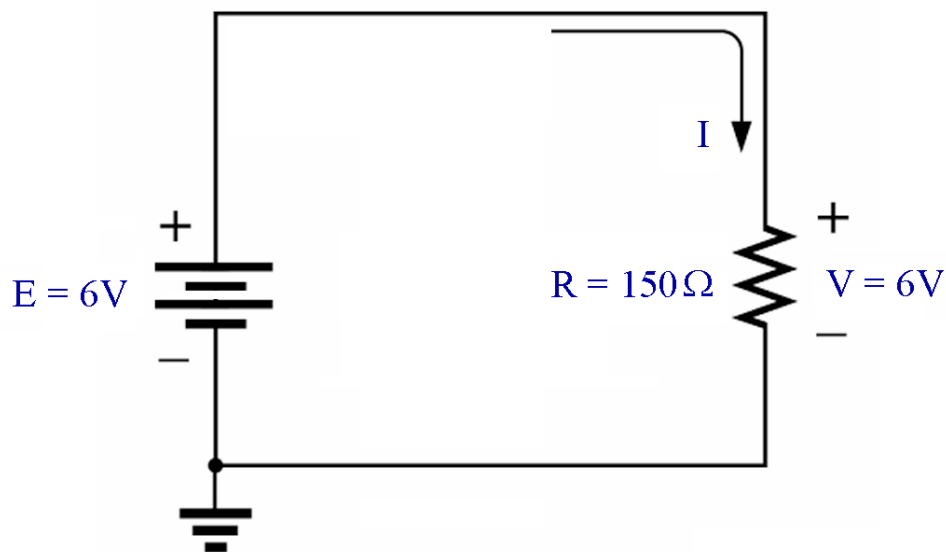Example – Ohm's Law






The flashlight shown uses a 6 volt battery and has a bulb with a resistance of $150\ \Omega$. When on, how much current will be drawn from the battery?






$$I = \frac{V}{R} = \frac{6V}{150\ \Omega} = 0.04\ A = 40\ mA$$

Breakout Exercise #1

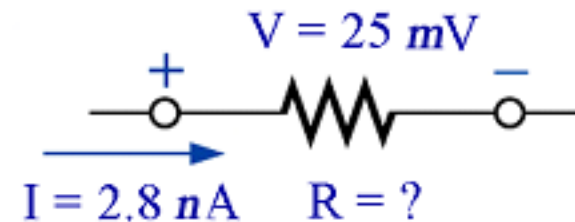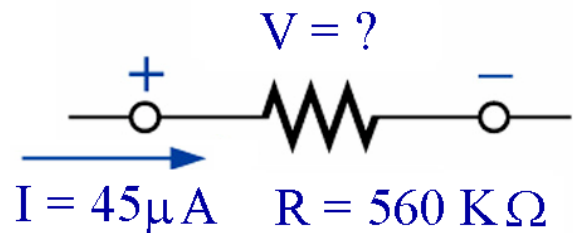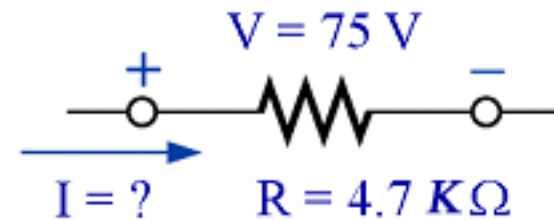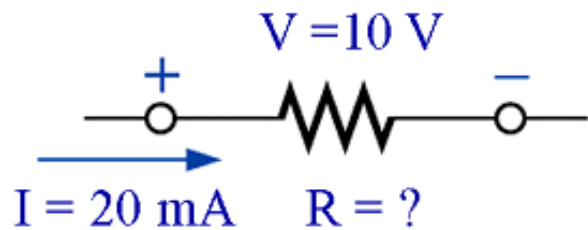
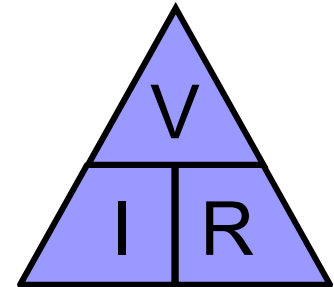
For each of the Ohm's law problems shown, find the unknown.



Plotting Ohm's Law (I-V Characteristics)

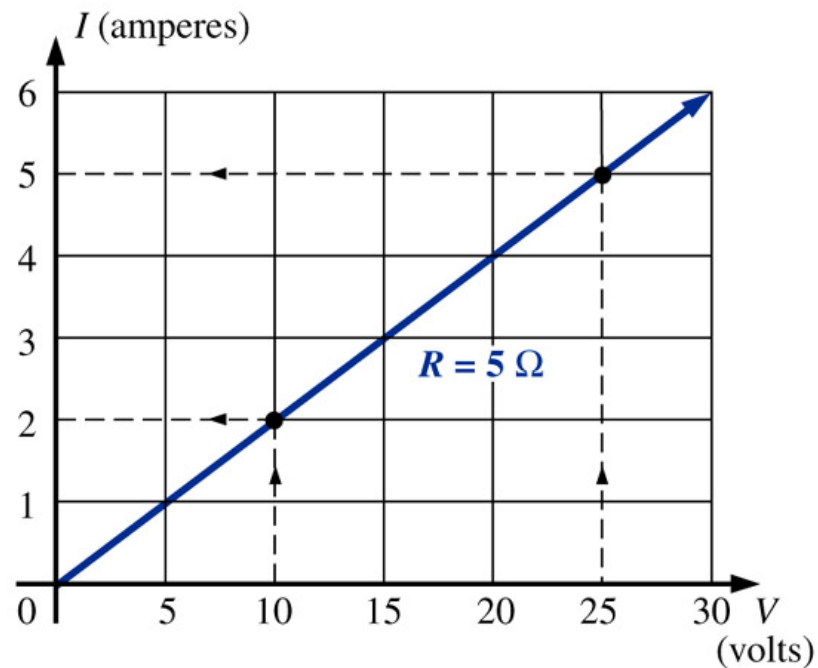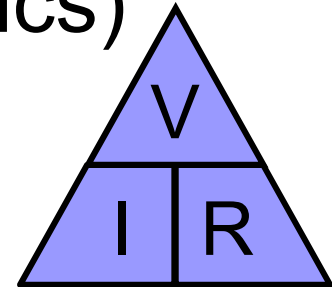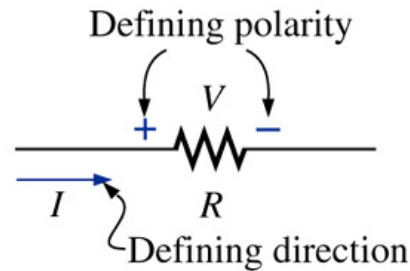

Plotting Ohm's Law (I-V Characteristics)

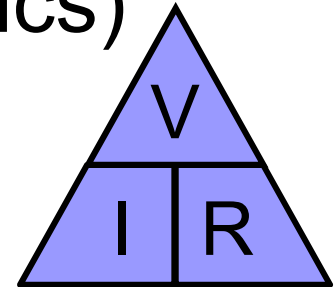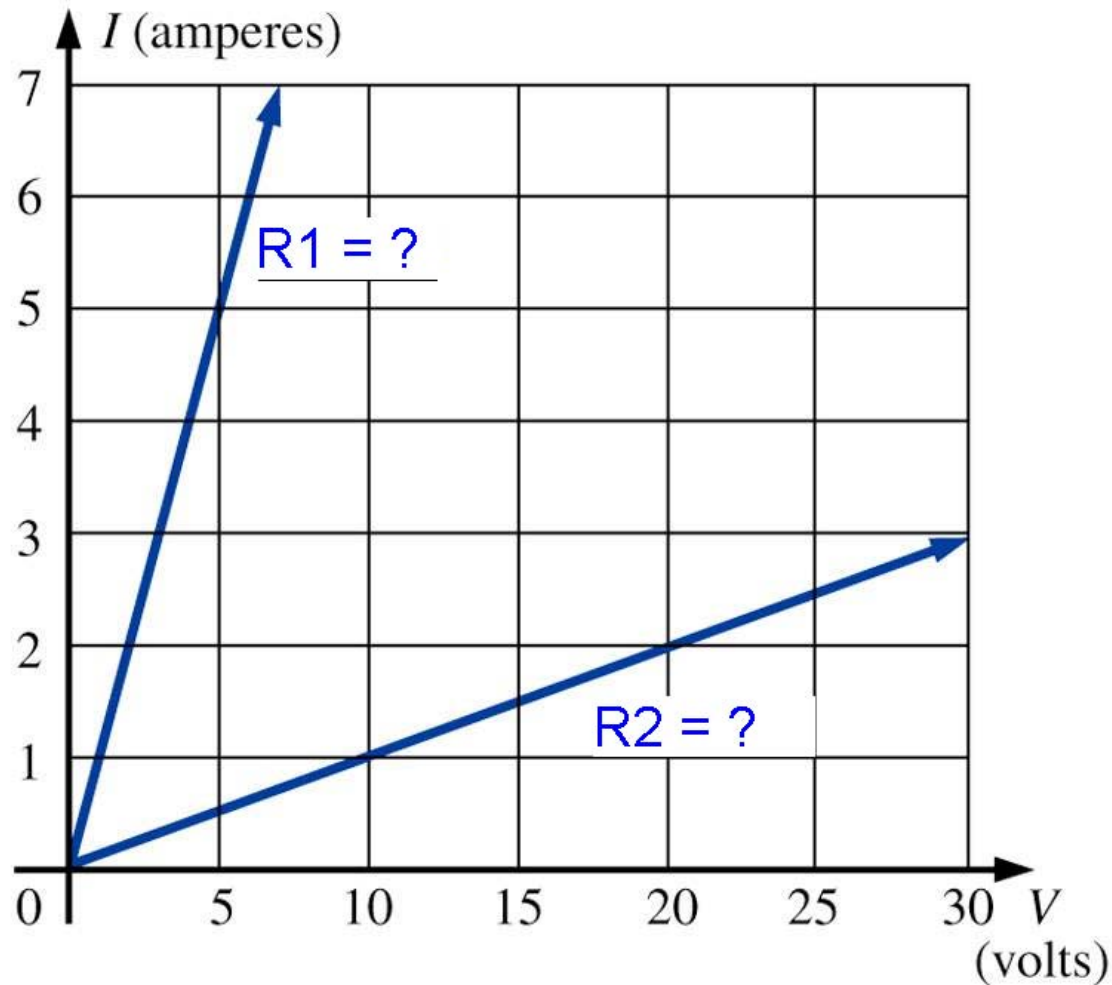

Breakout Exercise #2

- Estimate the resistance of the diode at $V_D = 1.6\text{V}$ and $V_D = 1.7\text{V}$, using the I-V characteristics shown.
- Bonus: What type of diode is this?

