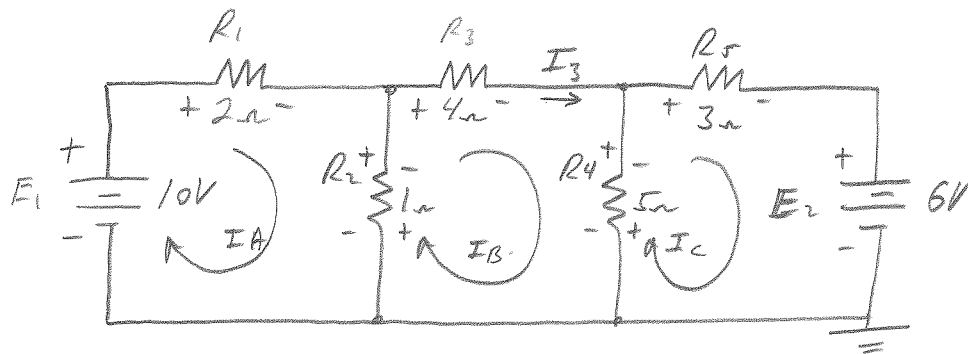


(24)



CH 8  
 (\* USE CALC  
 EQ SOLVER  
 OR MATLAB)

a) FIND THE MESH CURRENTS:

Loop IA:  $10 - R_1 I_A - R_2 I_A + R_2 I_B = 0$   
 $-2I_A - I_A + I_B = -10$   
 $-3I_A + I_B = -10 \rightarrow 3I_A - I_B + 0I_C = 10 \quad (1)$

Loop IB:  $R_2 I_A - R_2 I_B - R_3 I_B - R_4 I_B + R_4 I_C = 0$   
 $I_A - 10I_B + 5I_C = 0 \rightarrow I_A - 10I_B + 5I_C = 0 \quad (2)$


Loop IC:  $R_4 I_B - R_4 I_C - R_5 I_C - E_2 = 0$   
 $5I_B - 8I_C = 6 \rightarrow 0I_A + 5I_B - 8I_C = 6 \quad (3)$

SOLVING:

$$\begin{aligned} I_A &= 3.312 \text{ A} \\ I_B &= -63.69 \text{ mA} \\ I_C &= -789.8 \text{ mA} \end{aligned}$$

(a+b)

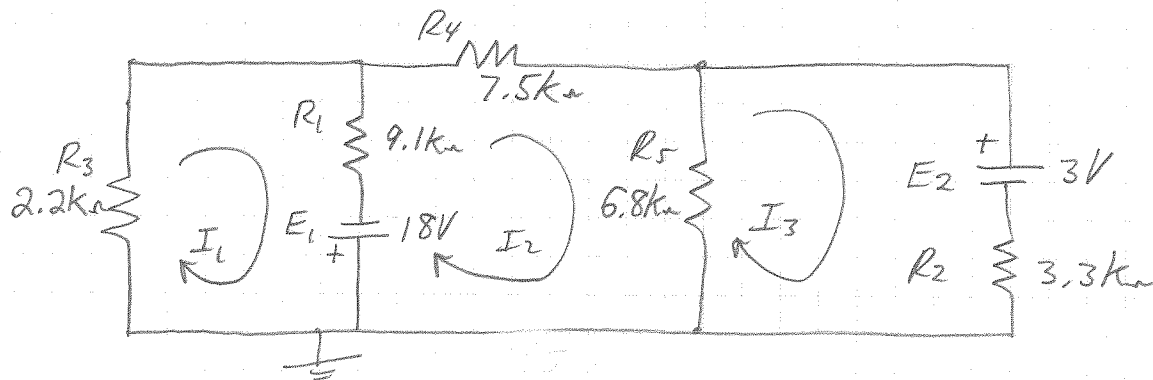(25) USE MESH ANALYSIS TO SOLVE FOR THE LOOP CURRENTS (EACH CIRCUIT):



$$\text{Loop 1: } -R_3 I_1 - R_1 I_1 + R_1 I_2 + E_1 = 0$$

$$(-11.3k) I_1 + (9.1k) I_2 + 0 I_3 = -18 \quad (1)$$

$$\text{Loop 2: } -E_1 - R_1 I_2 + R_1 I_1 - R_4 I_2 - R_5 I_2 + R_5 I_3 = 0$$

$$(9.1k) I_1 - (23.4k) I_2 + (6.8k) I_3 = 18 \quad (2)$$

$$\text{Loop 3: } -R_5 I_3 + R_5 I_2 - E_2 - R_2 I_3 = 0$$

$$(0) I_1 + (6.8k) I_2 - (10.1k) I_3 = 3 \quad (3)$$

SOLVING (1) - (3):

$$\begin{aligned} I_1 &= 1.206 \text{ mA} \\ I_2 &= -480.6 \mu\text{A} \\ I_3 &= -620.6 \mu\text{A} \end{aligned}$$

(c) THE CURRENT IN  $E_1$ 

$$I_{E1} = I_1 - I_2$$

$$I_{E1} = 1.687 \text{ mA}$$

THE CURRENT IN  $E_2$ 


$$I_{E2} = -I_3$$

$$\therefore I_{E2} = 620.6 \mu\text{A}$$

(p25) Circuit

2/1

~~(p26)~~ (a+b)

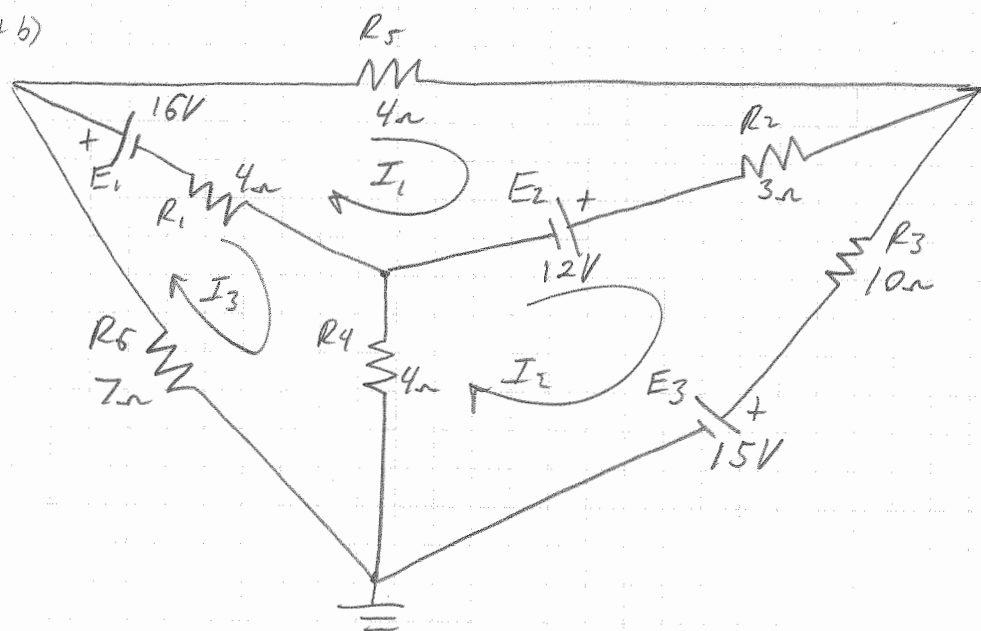

$$\text{Loop 1: } -R_1 I_1 + R_1 I_3 + E_1 - R_5 I_1 - R_2 I_1 + R_2 I_2 - E_2 = 0$$
$$-11 I_1 + 3 I_2 + 4 I_3 = -4 \quad (1)$$

$$\text{Loop 2: } -R_4 I_2 + R_4 I_3 + E_2 - R_2 I_2 + R_2 I_1 - R_3 I_2 - E_3 = 0$$
$$3 I_1 - 17 I_2 + 4 I_3 = 3 \quad (2)$$

$$\text{Loop 3: } -R_5 I_3 - E_1 - R_1 I_3 + R_1 I_1 - R_4 I_3 + R_4 I_2 = 0$$
$$4 I_1 + 4 I_2 - 15 I_3 = 16 \quad (3)$$

SOLVING YIELDS:

$$I_1 = -238.5 \text{ mA}$$

$$I_2 = -516.9 \text{ mA}$$

$$I_3 = -1.268 \text{ A}$$

(c) FIND THE CURRENT THROUGH  $R_5$

$$I_{R5} = I_1 = -238.5 \text{ mA}$$

*Problem 26.*

Loop 1:  $-R_1 I_1 + R_1 I_3 - R_5 I_1 - R_2 I_1 + R_2 I_2 = 0$

Loop 1:  $-R_1(I_1 - I_3) - R_2(I_1 - I_2) - R_5I_1 = 0$

Loop 1:  $-4I_1 - 3(I_1 + I_2) - 4(I_1 + I_3) = 0$

Loop 2:  $-R_4(I_2 - I_3) - R_2(I_2 - I_1) - R_3I_2 = E_1$

Loop 2:  $-3(I_2 - I_1) - 10I_2 - 4(I_2 - I_3) = 15$

Loop 3:  $-R_6 I_3 - R_1(I_3 - I_1) - R_4(I_3 - I_2) = 0$

Loop 3:  $-7I_3 - 4(I_3 - I_1) - 4(I_3 - I_2) = 0$


$$I_1 = -430.4mA$$

$$I_3 = -395.1mA$$

$$I_3 = -395.1mA$$

$$I_{R_5} = I_1 = -430.4mA$$

# Question 8-27

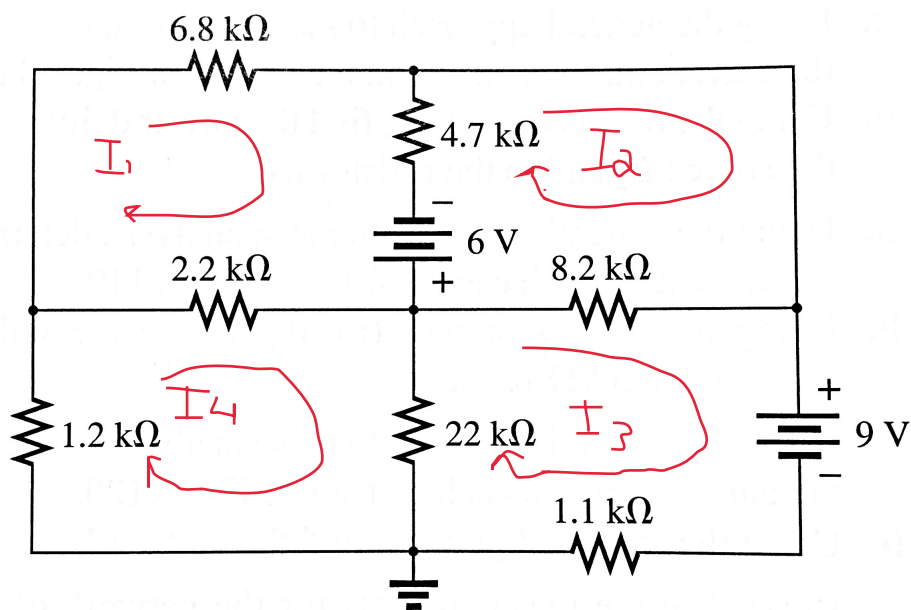

a. Write the mesh currents for the network of Fig. 8.124 using the general approach.

$$\text{Loop 1: } -6.8k\Omega \cdot I_1 - 4.7k\Omega \cdot I_1 + 4.7k\Omega \cdot I_2 + 6V - 2.2k\Omega \cdot I_1 + 2.2k\Omega \cdot I_4 = 0$$

$$\text{Loop 1: } (-6.8k\Omega) \cdot I_1 - 4.7k\Omega \cdot (I_1 - I_2) - 2.2k\Omega \cdot (I_1 - I_4) = -6V$$

$$\text{Loop 2: } 6V - 4.7k\Omega \cdot I_2 + 4.7k\Omega \cdot I_1 - 8.2k\Omega \cdot I_2 + 8.2k\Omega \cdot I_3 = 0$$

$$\text{Loop 2: } -4.7k\Omega \cdot (I_2 - I_1) - 8.2k\Omega(I_2 - I_3) = -6V$$

$$\text{Loop 3: } -22k\Omega \cdot I_3 + 22k\Omega \cdot I_4 - 8.2k\Omega \cdot I_3 + 8.2k\Omega \cdot I_2 - 9V - 1.1k\Omega \cdot I_3$$

$$\text{Loop 3: } -22k\Omega(I_3 - I_4) - 8.2k\Omega(I_3 - I_2) - 1.1k\Omega \cdot I_3 = 9V$$

$$\text{Loop 4: } -1.2k\Omega \cdot I_4 - 2.2k\Omega \cdot I_4 + 2.2k\Omega \cdot I_1 - 22k\Omega \cdot I_4 + 22k\Omega \cdot I_3$$

$$\text{Loop 4: } -1.2k\Omega \cdot I_4 - 2.2k\Omega \cdot (I_4 - I_1) - 22k\Omega \cdot (I_4 - I_3) = 0$$

b. Using determinants, calculate the mesh currents.

$$I_1 = -0.597mA$$

$$I_2 = -2.13mA$$

$$I_3 = -2.27mA$$

$$I_4 = -2.03mA$$


c. Using the results of part (b), find the power delivered by the 6 V source.

$$I_{6V} = I_1 - I_2 = -0.597mA - (-2.13mA) = 1.53mA$$

$$P_{6V} = E \cdot I_{6V} = 6V \cdot 1.53mA = 9.18mW$$

~~(2)~~ (a+b)

SOLVE FOR THE LOOP CURRENTS

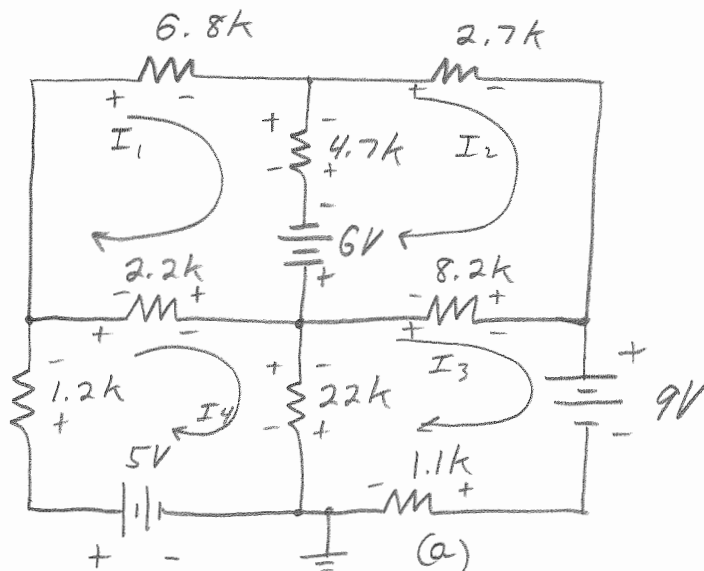

$$\begin{aligned} I_1 \text{ loop: } & -6.8kI_1 - 4.7kI_1 + 4.7kI_2 + 6 - 2.2kI_1 + 2.2kI_4 = 0 \\ & -13.7kI_1 + 4.7kI_2 + 0I_3 + 2.2kI_4 = -6 \end{aligned} \quad (1)$$

$$\begin{aligned} I_2 \text{ loop: } & -6 - 4.7kI_2 + 4.7kI_1 - 2.7kI_2 - 8.2kI_2 + 8.2kI_3 = 0 \\ & 4.7kI_1 - 15.6kI_2 + 8.2kI_3 + 0I_4 = 6 \end{aligned} \quad (2)$$


$$\begin{aligned} I_3 \text{ loop: } & -22kI_3 + 22kI_4 - 8.2kI_3 + 8.2kI_2 - 9 - 1.1kI_3 = 0 \\ & 0I_1 + 8.2kI_2 - 31.3kI_3 + 22kI_4 = 9 \end{aligned} \quad (3)$$

$$\begin{aligned} I_4 \text{ loop: } & -1.2kI_4 - 2.2kI_4 + 2.2kI_1 - 22kI_4 + 22kI_3 + 5 = 0 \\ & 2.2kI_1 + 0I_2 + 22kI_3 - 25.4kI_4 = -5 \end{aligned} \quad (4)$$

SOLVING YIELDS :

$$\begin{aligned} I_1 &= 32.11 \mu A \\ I_2 &= -883.9 \mu A \\ I_3 &= -968.2 \mu A \\ I_4 &= -639.0 \mu A \end{aligned}$$

(c) FIND  $P_{\text{DELIV}}$ , 6V SOURCE

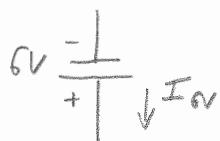


$$\begin{aligned} P_{\text{DELIV}, 6V} &= (6V)(I_{6V}) \\ I_{6V} &= I_1 - I_2 = 916 \mu A \end{aligned}$$

$$\therefore P_{\text{DELIVERED}, 6V \text{ SOURCE}} = (6V)(916 \mu A) = \boxed{5.5 \text{ mW}}$$

28) (a) REORDER THE CIRCUIT (REMOVE THE CROSSOVER)

(b) & (c) WRITE THE MESH EQS & SOLVE

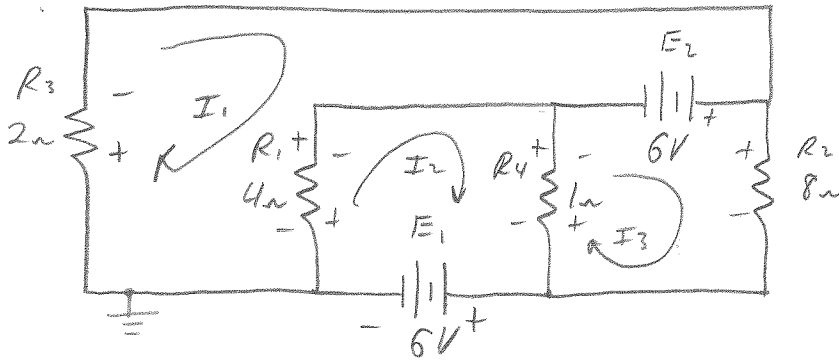

$$\begin{aligned} I_1: \quad & -R_3 I_1 - E_2 - R_1 I_1 + R_1 I_2 = 0 \\ & -6I_1 + 4I_2 + 0I_3 = 6 \end{aligned} \quad (1)$$

$$\begin{aligned} I_2: \quad & -R_1 I_2 + R_1 I_1 - R_4 I_2 + R_4 I_3 - E_1 = 0 \\ & 4I_1 - 5I_2 + I_3 = 6 \end{aligned} \quad (2)$$

$$\begin{aligned} I_3: \quad & -R_4 I_3 + R_4 I_2 + E_2 - R_2 I_3 = 0 \\ & 0I_1 + I_2 - 9I_3 = -6 \end{aligned} \quad (3)$$

SOLVING YIELDS:

$$I_1 = -3.80A$$

$$I_2 = -4.20A$$

$$I_3 = 200.0mA$$

(d) FIND THE POWER DELIVERED BY THE SOURCES:


$$P_{E1} = (E_1)(-I_2) = (6V)(4.20A) = \underline{25.2W}$$

$$P_{E2} = (E_2)(I_3 - I_1) = (6V)(4A) = \underline{24W}$$

$$\therefore \boxed{\text{TOTAL DELIVERED POWER} = 49.2W}$$

(30) FIND THE CURRENT THROUGH EACH NETWORK ELEMENT

4/10

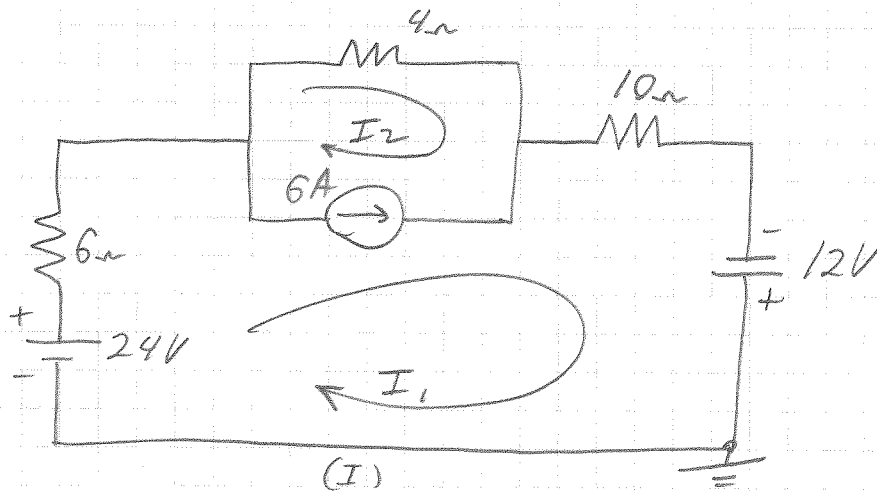

\* CAN'T WRITE A KVL EQ. W/ CURRENT SOURCE PRESENT

$$\text{KVL (OUTER)} : 24 - 6I_1 - 4I_2 - 10I_1 + 12 = 0$$

$$-16I_1 - 4I_2 = -36 \quad (1)$$

RELATING THE CURRENT SOURCE TO THE LOOP CURRENTS:

$$6 = I_1 - I_2 \quad (2)$$

$$\text{SOLVING : } I_1 = 3A$$


$$I_2 = -3A$$

$$\therefore I_{24V} = I_{6\Omega} = I_{10\Omega} = I_{12V} = 3A \rightarrow$$

$$I_{4\Omega} = -3A \rightarrow \text{OR } 3AS$$



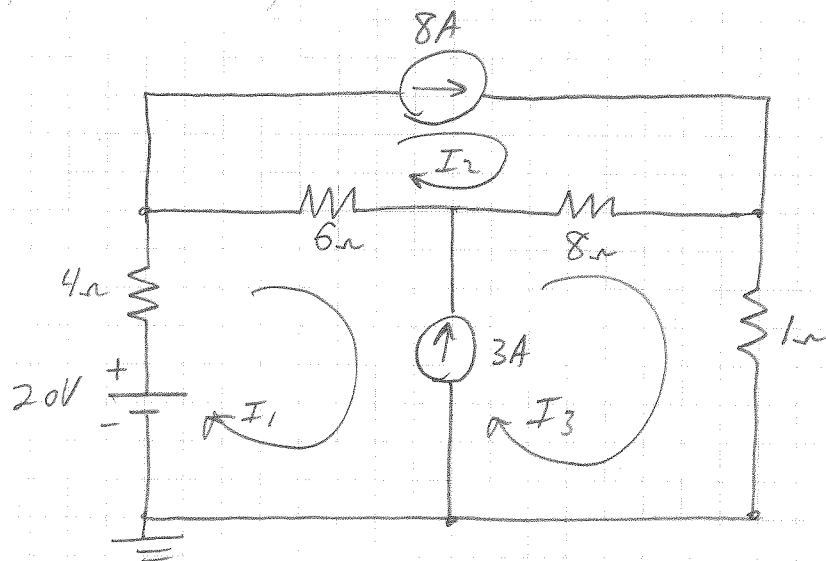(31) FIND THE CURRENT THROUGH EACH ELEMENT



$$\text{KVL (1,3)}: 20 - 4I_1 - 6I_1 + 6I_2 - 8I_3 + 8I_2 - I_3 = 0$$
$$-10I_1 + 14I_2 - 9I_3 = -20 \quad (1)$$

Also know:  $I_2 = 8A$

$$I_3 - I_1 = 3A$$

$$0I_1 + I_2 + 0I_3 = 8 \quad (2)$$

$$-I_1 + 0I_2 + I_3 = 3 \quad (3)$$

Solving:

$$\begin{bmatrix} I_1 = 5.526A \\ I_2 = 8.0A \\ I_3 = 8.526A \end{bmatrix}$$

$$I_{20V} = I_{4\Omega} = I_1 = 5.53A \rightarrow$$

$$I_{1\Omega} = I_{8\Omega} = I_3 = 8.53A \rightarrow$$

$$I_{6\Omega} = I_2 - I_1 = 2.47A \leftarrow$$

$$I_{8\Omega} = I_3 - I_2 = 526mA \rightarrow$$