
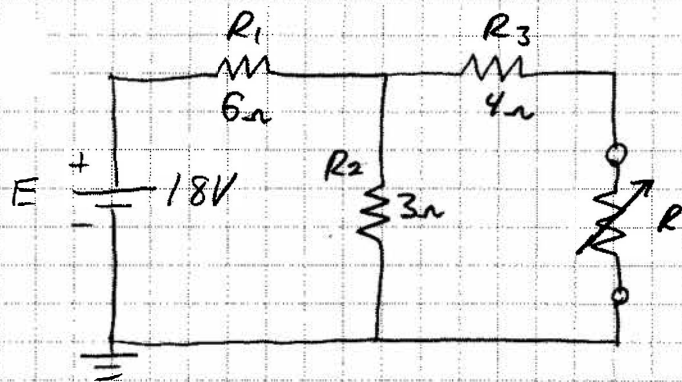


P9.9

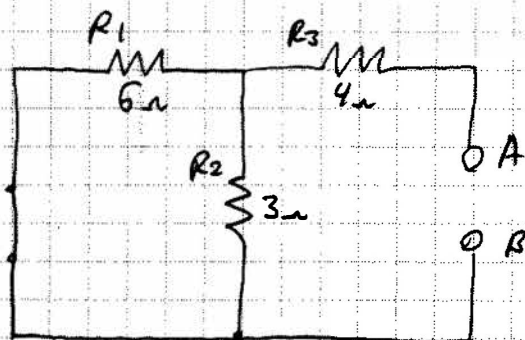

(a) FIND THE THEVENIN EQUIVALENT CIRCUIT EXTERNAL TO "R."


R_{TH} - DEACTIVATE (RELAX) SOURCES
 - O/C, & LABEL "A" & "B"
 THE COMPONENT/SYS OF INTEREST



$$R_{TH} = R_{AB} = R_1 // R_2 + R_3$$

$$= \boxed{6\Omega}$$

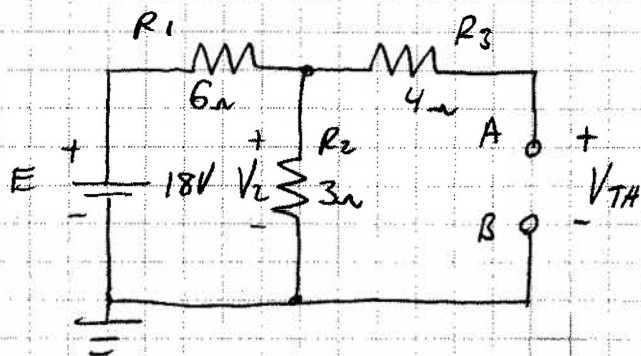V_{TH} - FIND V_{AB} (O/C) WITH THE SOURCES IN-CIRCUIT




$$V_2 = E \left(\frac{R_2}{R_1 + R_2} \right) = \underline{6V}$$


$$V_{TH} = V_2 = \boxed{6V}$$

* NO CURRENT THROUGH R₃

P9.9 Continued

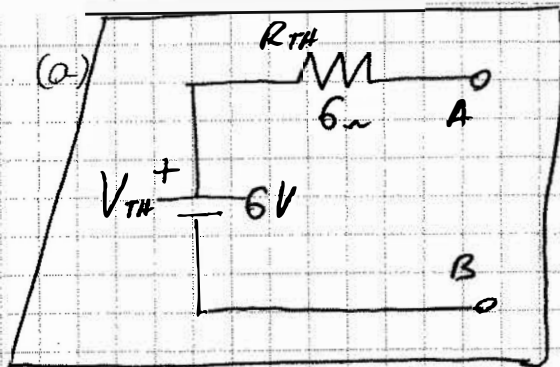

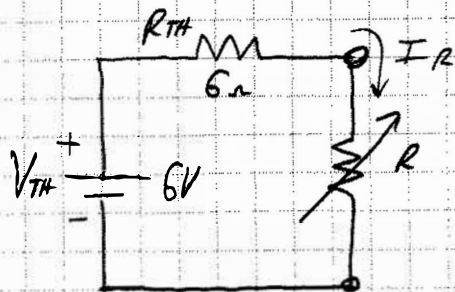(b) Find I_R For $R = 2\Omega, 30\Omega, 100\Omega$




$$I_R = \frac{V_{TH}}{R_{TH} + R} = \frac{6V}{6\Omega + R}$$

R	I_R
2Ω	750.0 mA
30Ω	166.7 mA
100Ω	56.60 mA

P9.13

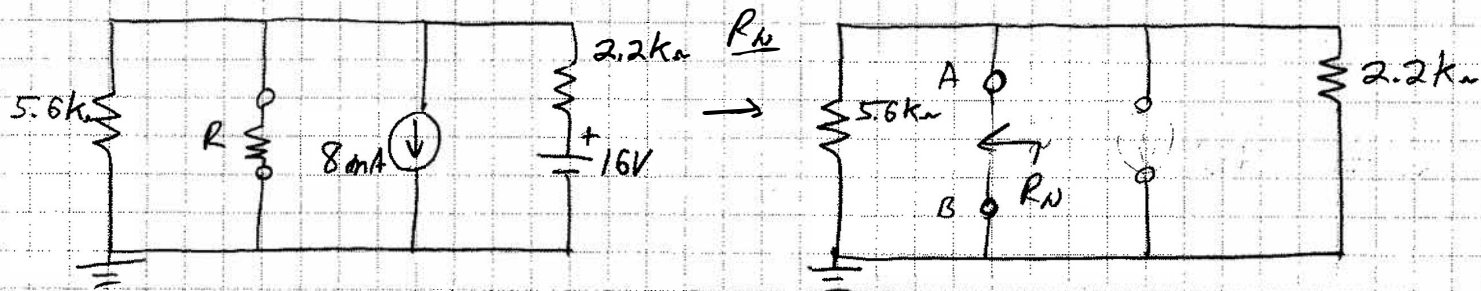
FIND THE NORTON EQUIVALENT EXTERNAL TO "R."



(redrawn)

$$R_N = 5.6k\Omega // 2.2k\Omega$$

$$\boxed{R_N = 1.580k\Omega}$$

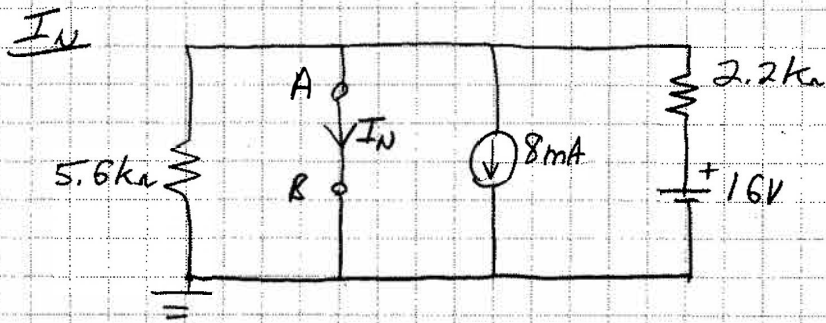

I_N (DUE TO THE 8mA SOURCE) : I_N'

$$\underline{I_N' = -8 \text{ mA}} \quad (\text{SOURCE IS } \downarrow)$$


I_N (DUE TO 16V SOURCE) : I_N''

$$I_N'' = \frac{16\text{V}}{2200\Omega} = \underline{7.273 \text{ mA}}$$

$$\therefore I_N = -8 \text{ mA} + 7.273 \text{ mA}$$


$$\boxed{I_N = -727.3 \mu\text{A}}$$

NORTON EQUIVALENT

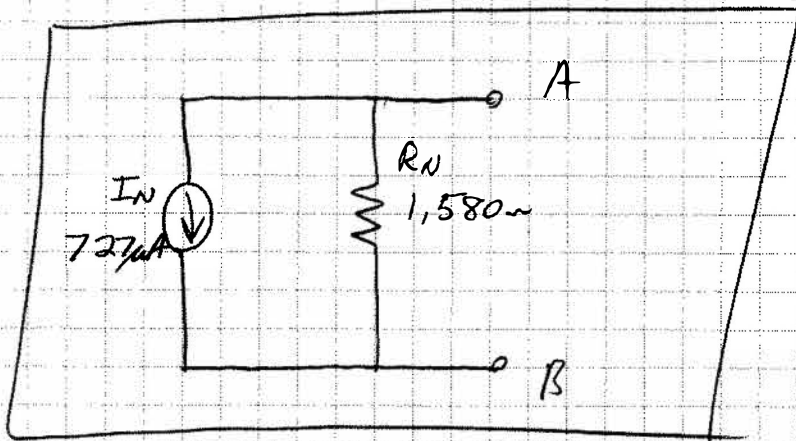


P9.14: Find the Thevenin equivalent external to "R"

REDRAWN

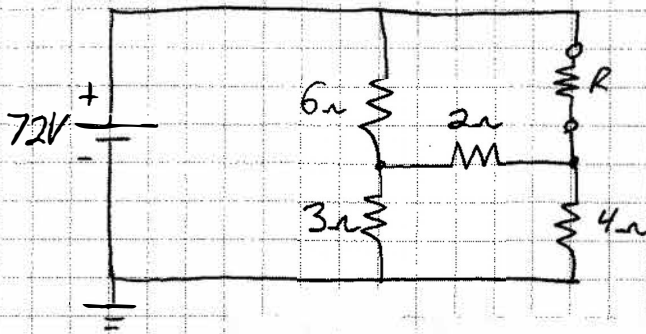


(Using a 72V source instead of a 2A source as specified)

R_{TH}

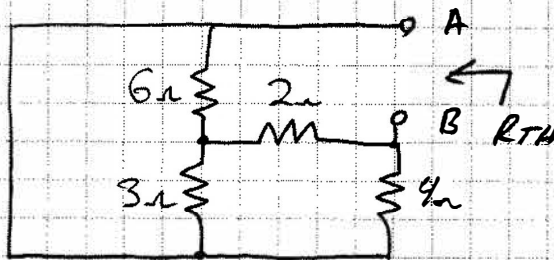

REDRAWN

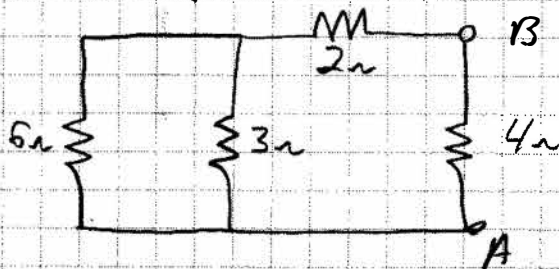


$$R_{TH} = R_{AB}$$

$$= [6\Omega // 3\Omega] + 2\Omega // 4\Omega$$

$$= (2\Omega + 2\Omega) // 4\Omega$$

$$\boxed{R_{TH} = 2\Omega}$$

V_{TH}

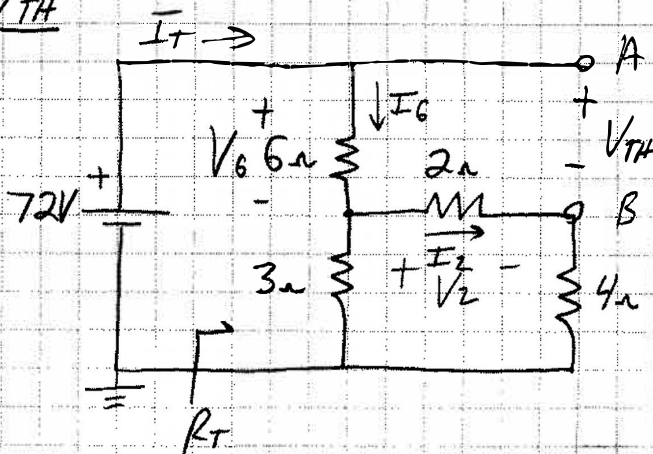

$$R_T = (4\Omega + 2\Omega) // 3\Omega + 6\Omega$$

$$R_T = 2\Omega + 6\Omega = 8\Omega$$

$$I_T = \frac{72V}{R_T} = 9A$$

$$I_6 = I_T = 9A$$

$$\therefore V_6 = (6\Omega)(9A) = 54V$$

$$I_2 = I_6 \left(\frac{2\Omega}{6\Omega} \right) = 3A$$

$$\therefore V_2 = (I_2)(2\Omega) = 6V$$


P9.14 (CONTINUED)

$$\text{KVL: } V_6 - V_{TH} + V_2 = 0$$


$$V_{TH} = V_6 + V_2 = 54V + 6V$$

$$V_{TH} = 60V$$


THEVENIN EQUIVALENT

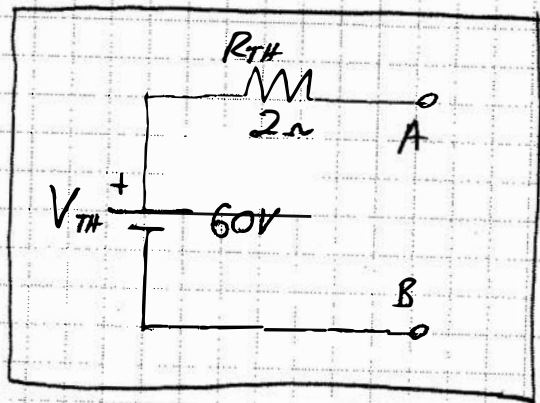

P9.19

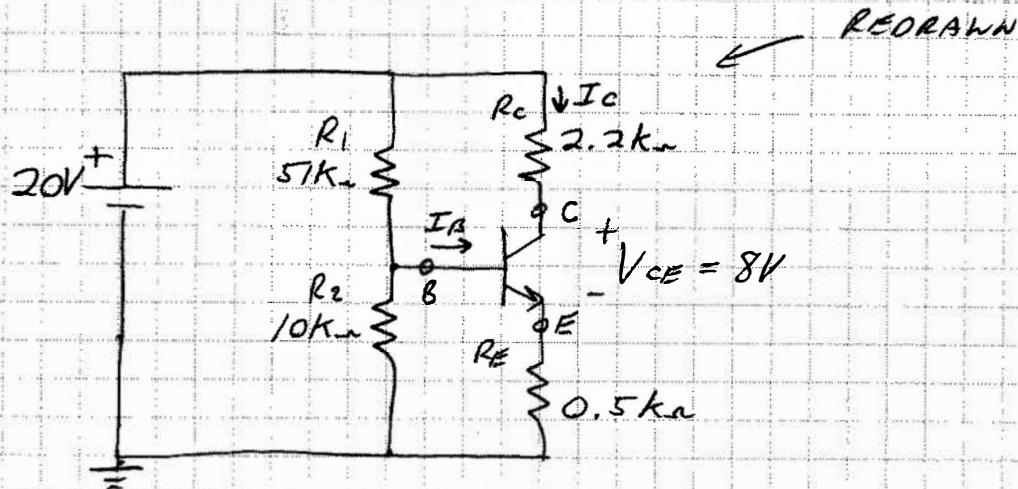


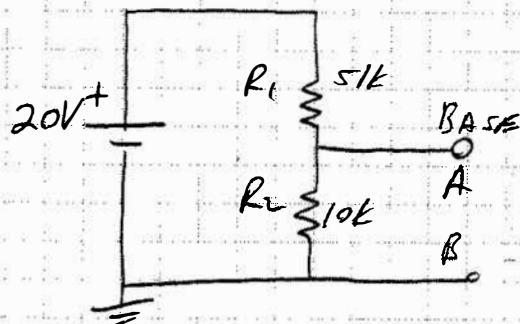(a) FIND THE THEVENIN EQUIVALENT FOR THE CIRCUIT TO THE LEFT OF THE BASE TERMINAL



P9.19 (CONTINUED)


R_{TH}

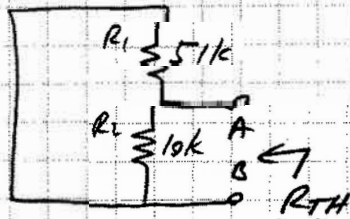

$$R_{TH} = R_1 \parallel R_2$$


$$R_{TH} = 8.361k\Omega$$

V_{TH}

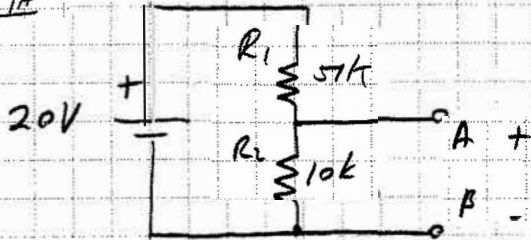


$$V_{TH} = 20V \left(\frac{R_2}{R_1 + R_2} \right) = 3.279V$$

THEVENIN EQUIVALENT

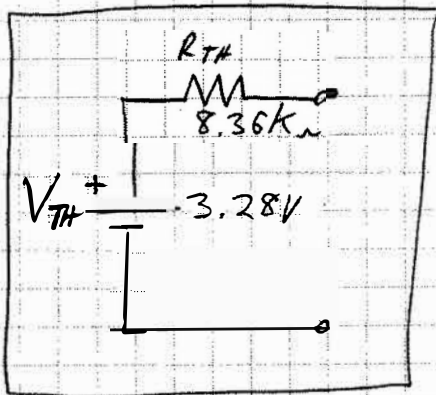

(b) USING $I_C = I_E$ & $V_{CE} = 8V$, FIND $|I_E|$

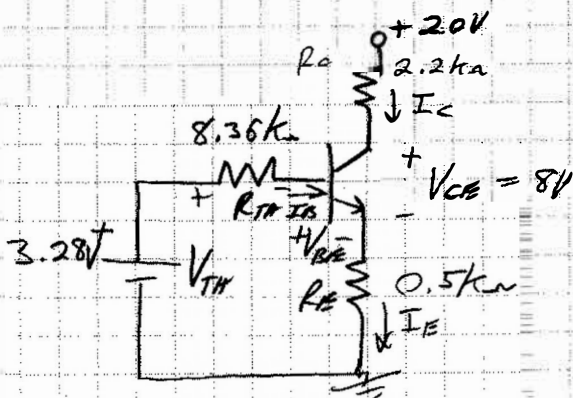

$$KVL: 20 - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\text{BUT } I_C = I_E$$

$$\therefore 20 = I_C R_C + V_{CE} + I_C R_E$$

$$20 = I_C (R_C + R_E) + V_{CE}$$

$$\text{OR } I_C = \frac{(20 - 8)V}{2.7k\Omega}$$

$$I_C = I_E = 4.44mA$$

P9.19 (CONTINUED)

(c) FIND I_B IF $V_{BE} = 0.7V$

$$KVL: 3.28V - I_B(8.36k\Omega) - V_{BE} - I_E R_E = 0$$


$$V_{BE} = 0.7V \quad (\text{GIVEN})$$

$$I_E = 4.44mA \quad (\text{PART b})$$

$$3.28V - 0.7V - (4.44mA)(500\Omega) = I_B(8.36k\Omega)$$

$$I_B = \frac{360mV}{8.36k\Omega} = \boxed{43.1\mu A}$$

(d) FIND V_C

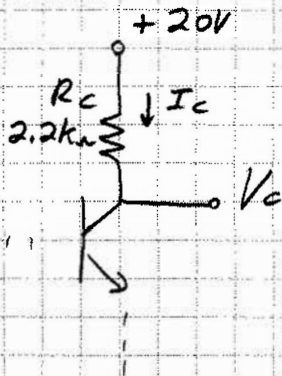

$$KVL: +20 - I_C R_C - V_C = 0$$

$$V_C = 20 - I_C R_C$$

$$I_C = I_E = 4.44mA$$

$$R_C = 2.2k\Omega$$


$$\therefore V_C = 20V - (4.44mA)(2200\Omega)$$

$$\boxed{V_C = 10.2V}$$


P9.34

FIND THE VALUE OF R_L FOR MAX POWER TRANSFER TO R_L + DETERMINE P_{MAX}

REDRAWN

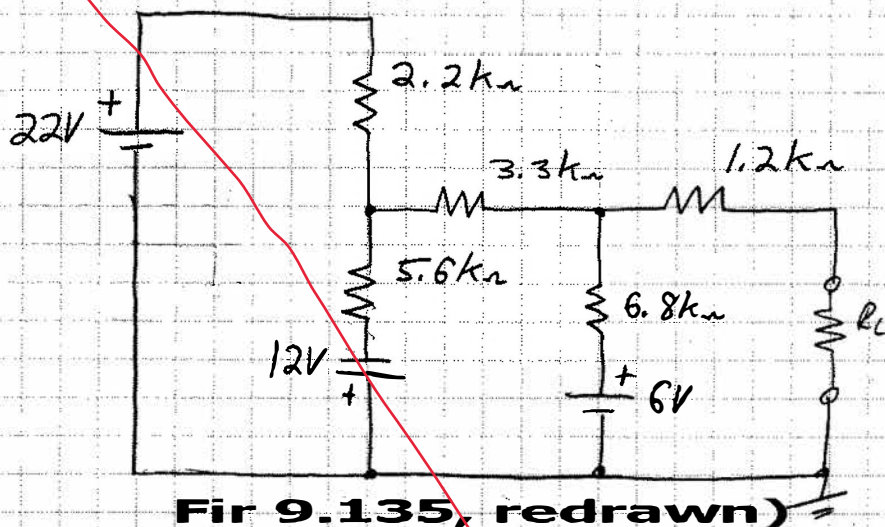

- FIND V_{TH} + R_{TH}

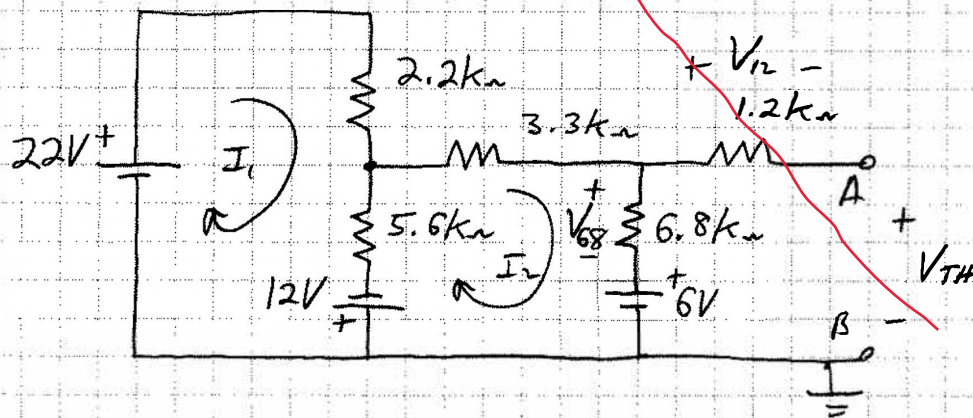

(CONTINUED)

$$1: 22 - 2.2kI_1 - 5.6kI_1 + 5.6kI_2 + 12 = 0$$

$$-7.8kI_1 + 5.6kI_2 = -34 \quad (1)$$

$$2: -12 - 5.6kI_2 + 5.6kI_1 - 3.3kI_2 - 6.8kI_2 - 6 = 0$$

$$5.6kI_1 - 15.7kI_2 = 18 \quad (2)$$

$$\text{SOLVING YIELDS: } I_1 = 4.753 \text{ mA}$$

$$I_2 = 548.9 \mu\text{A}$$

 V_{TH} :

$$\text{KVL: } 6 + V_{68} - V_{12} - V_{TH} = 0$$

$$V_{68} = (I_2)(6800\Omega)$$

$$= (548.9\mu\text{A})(6800\Omega) = \underline{3.733\text{V}}$$

$$V_{12} = 0\text{V, DUE TO O/C AT A+B}$$

$$\therefore V_{TH} = 6 + 3.733\text{V} = \underline{9.73\text{V}}$$


 R_{TH} : REPLACE VOLTAGE SOURCES w/ S/C

$$R_{TH} = (2.2k\Omega // 5.6k\Omega + 3.3k\Omega) // 6.8k\Omega + 1.2k\Omega$$

$$4.880k\Omega // 6.8k\Omega + 1.2k\Omega$$

$$\underline{R_{TH} = 4.041k\Omega}$$
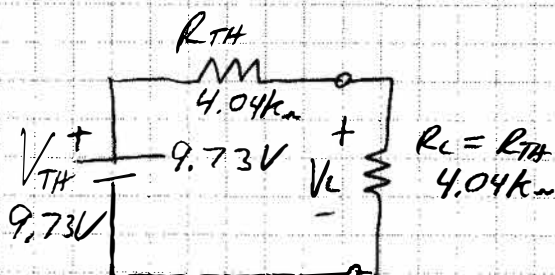
$$\therefore R_{L \text{ max PWR}} = R_{TH} = 4.04k\Omega$$




$$V_L = \frac{V_{TH}}{2} = \underline{4.87\text{V}}$$

$$\therefore P_{RL} = \frac{V_L^2}{R_L} = \underline{5.86\text{mW}}$$


IA 9.2

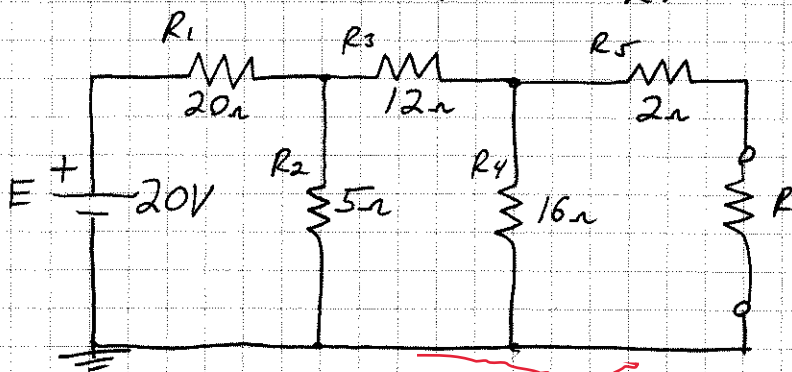FIND THE NORTON EQUIVALENT CIRCUIT
EXTERNAL TO "R."



~~Fig. 9.133~~

Fig 9.140

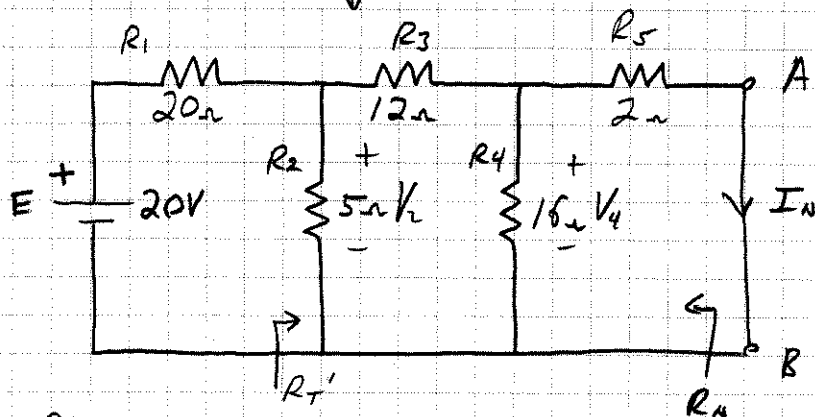


RN

$$\begin{aligned} R_N &= (R_1 // R_2 + R_3) // R_4 + R_5 \\ &= (4\Omega + 12\Omega) // 16\Omega + 2\Omega \\ &= 8\Omega + 2\Omega \end{aligned}$$

$$R_N = 10\Omega$$

IN

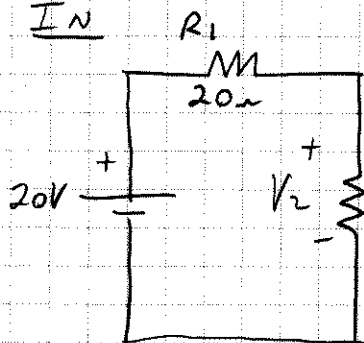

$$\begin{aligned} R_{T'} &= [(R_4 // R_5) + R_3] // R_2 \\ &= [(16\Omega // 2\Omega) + 12\Omega] // 5\Omega \\ &= 13.778\Omega // 5\Omega = 3.669\Omega \end{aligned}$$


$$V_2 = 20V \left(\frac{3.669\Omega}{20\Omega + 3.669\Omega} \right) = 3.10V$$

$$V_4 = 3.1V \left(\frac{16\Omega // 2\Omega}{16\Omega // 2\Omega + 12\Omega} \right) = 400.0mV$$

IA 9.2 (CONTINUED)



$$I_N = \frac{V_4}{R_5} = \frac{400.0mV}{2\Omega} = \boxed{200mA}$$

NORTON EQUIVALENT

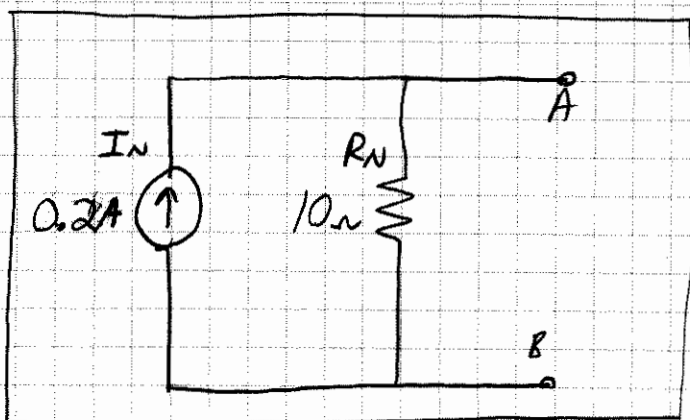

9.141 (with $R = 4.7K$ as stated)

~~FIG 9.134~~ REDRAWN

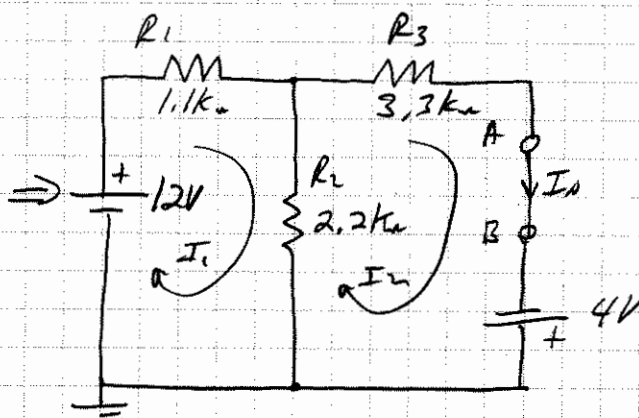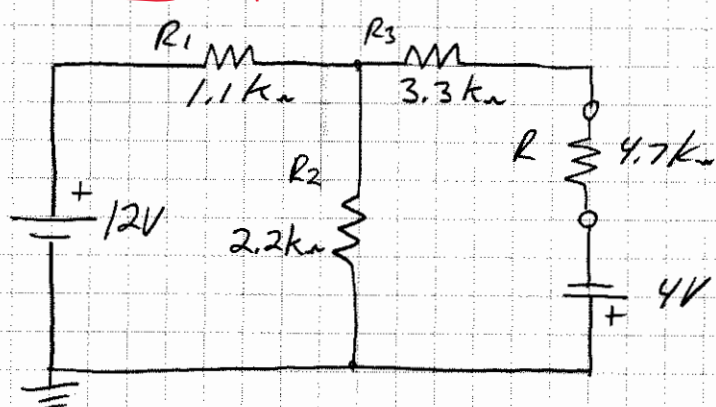

$$R_N = R_1 // R_2 + R_3 = 733.3\Omega + 3.3k\Omega$$

$$\boxed{R_N = 4.033k\Omega}$$

I_N

$$1^\circ: 12 - 1.1kI_1 - 2.2kI_1 + 2.2kI_2 = 0 \rightarrow -3.3kI_1 + 2.2kI_2 = -12 \quad (1)$$

$$2^\circ: -2.2kI_2 + 2.2kI_1 - 3.3kI_2 + 4 = 0 \rightarrow 2.2kI_1 - 5.5kI_2 = -4 \quad (2)$$

Solving yields: $I_1 = 5.62mA$

$$I_2 = 2.98mA$$

$$0^\circ: \boxed{I_N = I_2 = 2.98mA}$$

IA 9.2 (CONTINUED)

NORTON EQUIVALENT

