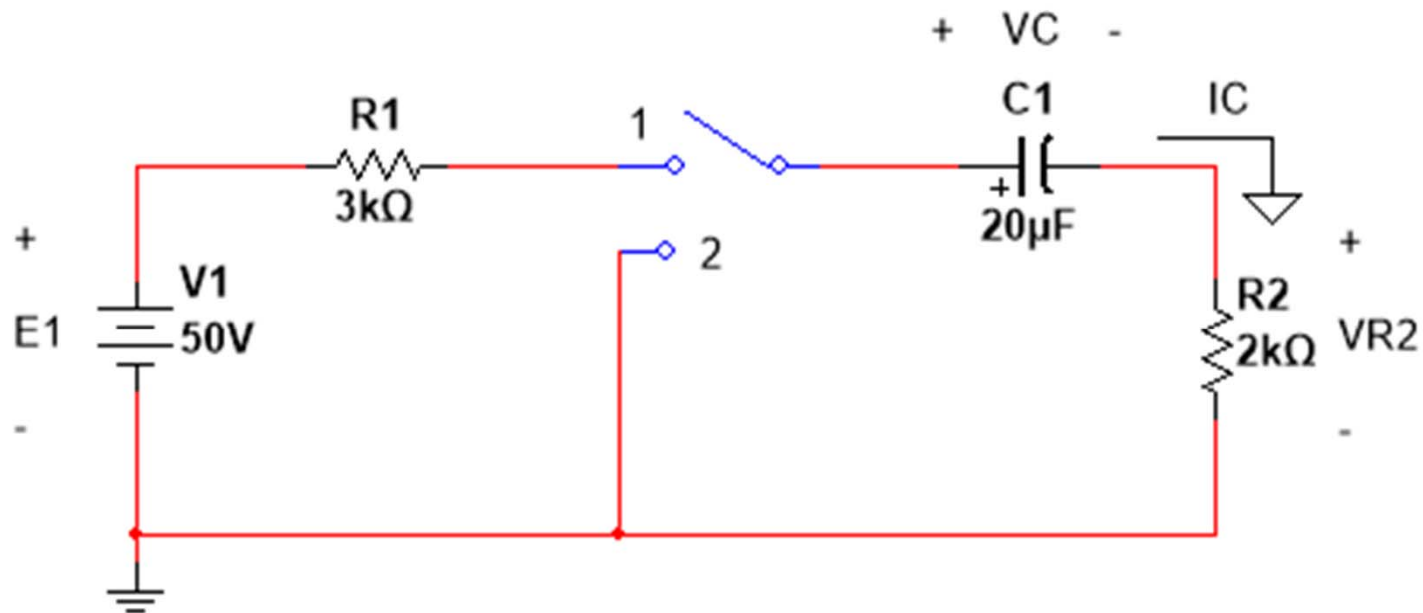


## In Class Problem

Find  $t$  for  $V_C(t) = 25 \text{ V}$  for charge and discharge

- No initial charge on  $C1$
- Switch to pos 1 at  $t = 0$
- Switch to pos 2 at  $t = 1 \text{ sec}$



Same circuit as earlier

Find  $t$  for  $V_C(t) = 25 \text{ V}$

Charge Phase:  $v_c(t) = 50(1 - e^{\frac{-t}{0.1}})V$

$$25V = 50(1 - e^{\frac{-t}{0.1}})V$$


$$0.5 = 1 - e^{\frac{-t}{0.1}}$$

$$-0.5 = -e^{\frac{-t}{0.1}}$$

$$0.5 = e^{\frac{-t}{0.1}}$$

$$\ln(0.5) = \ln(e^{\frac{-t}{0.1}})$$

$$-0.693 = \frac{-t}{0.1}$$

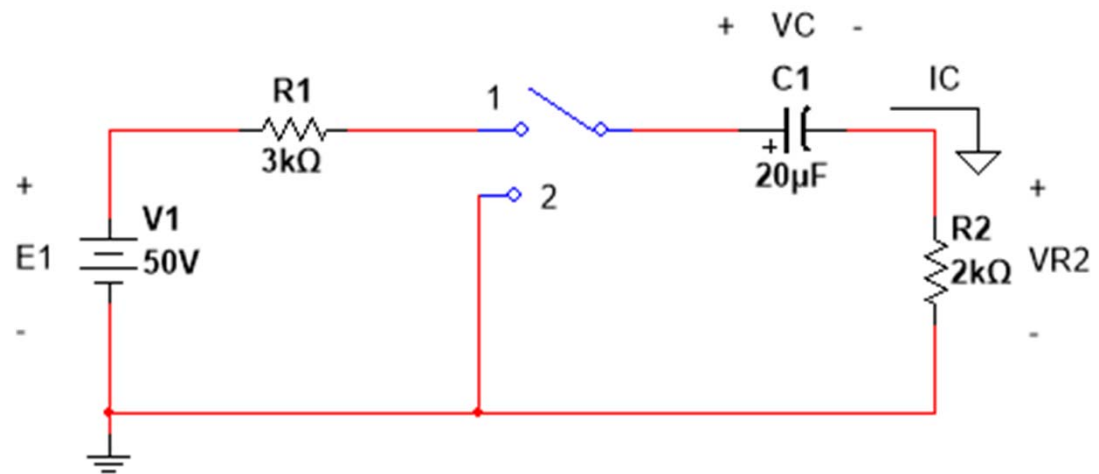

$$t = 69.32 \text{ msec}$$

Checking,  $v_C(69.32 \text{ msec}) = 25 \text{ V}$

Find  $t$  for  $V_C(t) = 25 \text{ V}$

Discharge Phase:


$$v_C(t) = 50e^{\frac{-(t-1)}{0.04}}$$

$$25 = 50e^{\frac{-(t-1)}{0.04}}$$

$$\ln(0.5) = \ln(e^{\frac{-(t-1)}{0.04}})$$

$$-0.693 = \frac{-(t-1)}{0.04}$$

$$27.726 \cdot 10^{-3} = t - 1$$

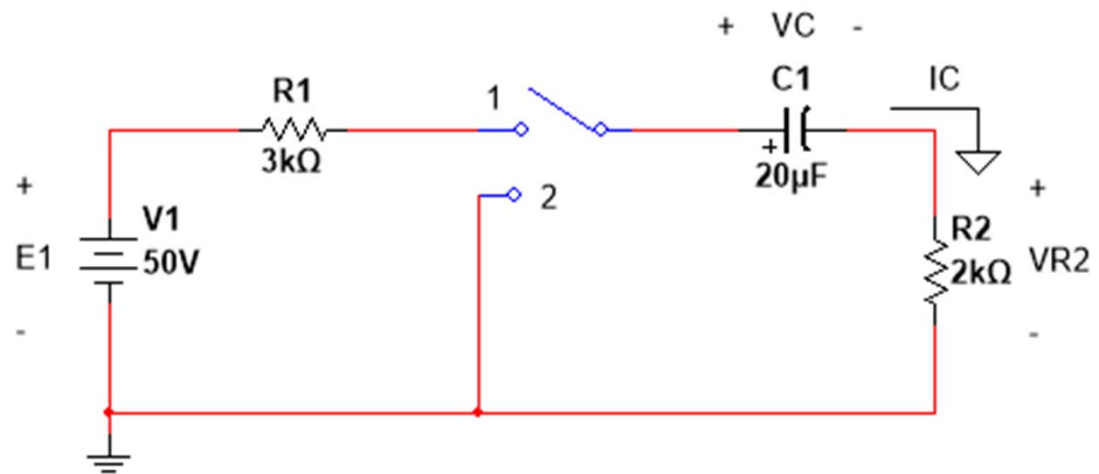

$$t = 1.0277 \text{ sec}$$

Checking,  $v_C(1.0277 \text{ sec}) = 25.02 \text{ V}$