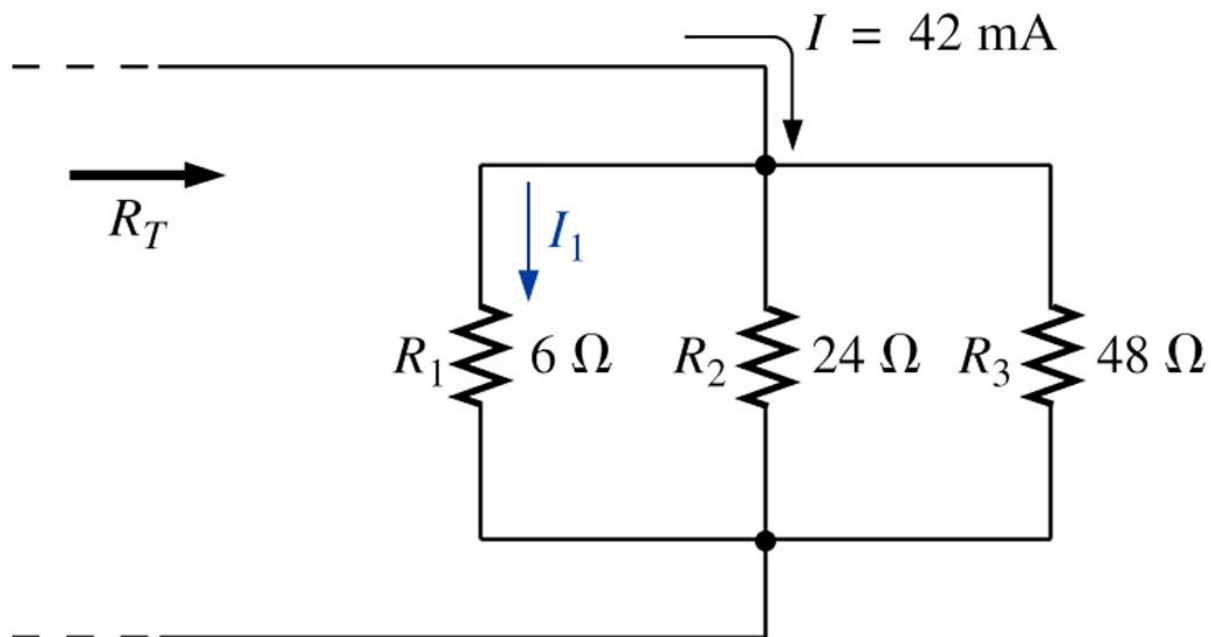


# Today's Material


- Current Divider
  - Breakout #1
- Parallel Voltage Sources
  - Ideal and realistic examples
- Open and Short-Circuits
  - Description and examples
  - Breakout #2
  - Breakout #3
- Voltmeter Loading
  - Description and example
- Application – Automotive Electrical System (partial)

## Breakout #1


- Find  $R_T$ ,  $I_1$ , and  $P_{R3}$



## Parallel Voltage Sources (ideal)

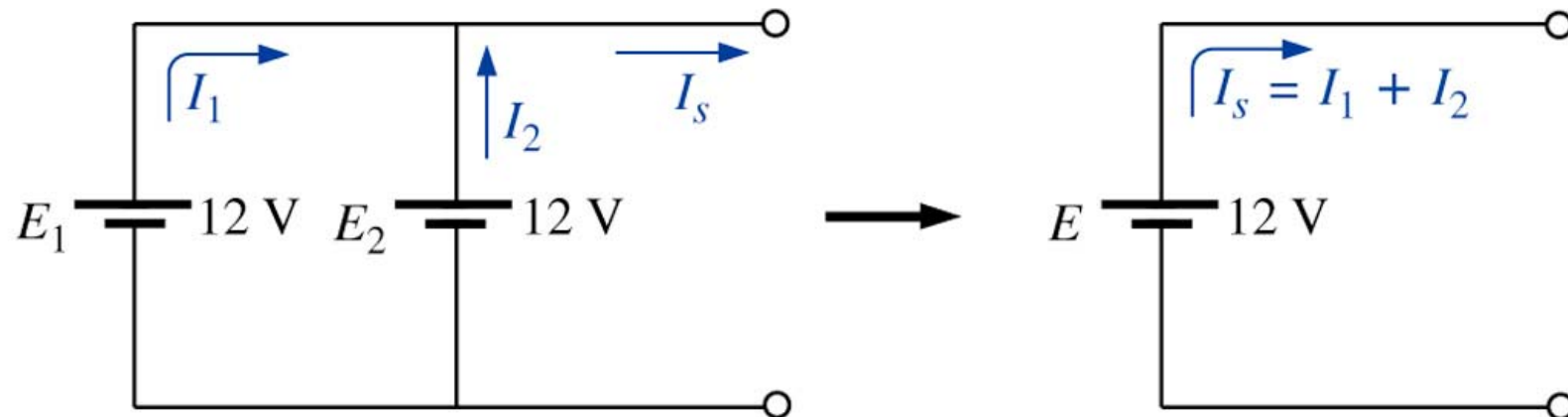

## Parallel Voltage Sources (practical)

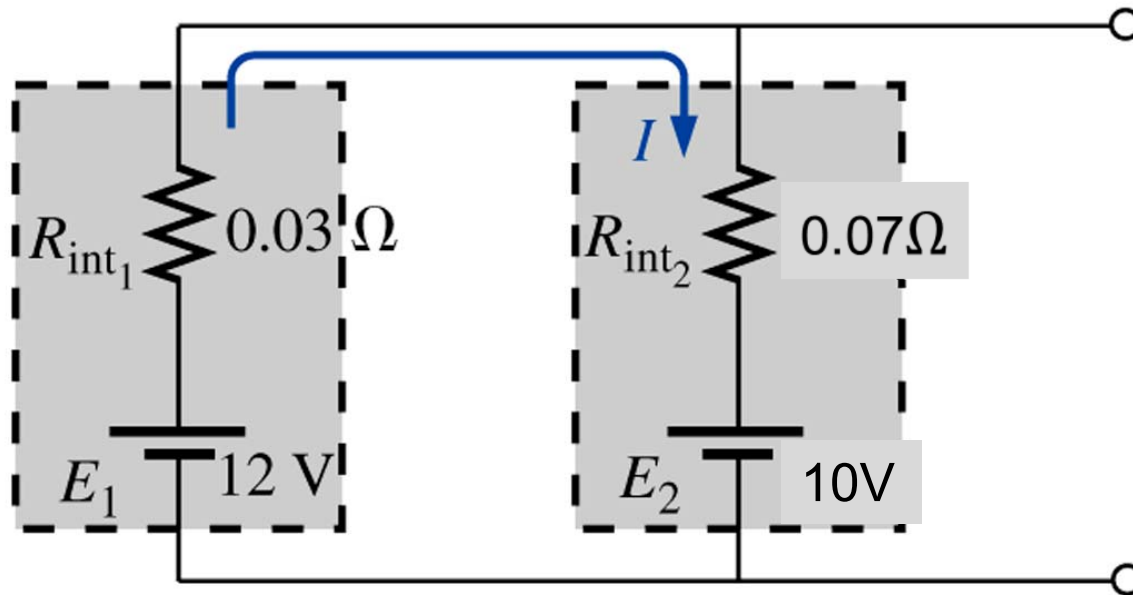


$$I = \frac{2V}{0.1\Omega} = 20 \text{ A}$$

■ Find  $I$

$$KVL: 12V - 0.03\Omega(I) - 0.07\Omega(I) - 10V = 0$$


$$2V = 0.1\Omega(I)$$

# Open and Short-Circuits

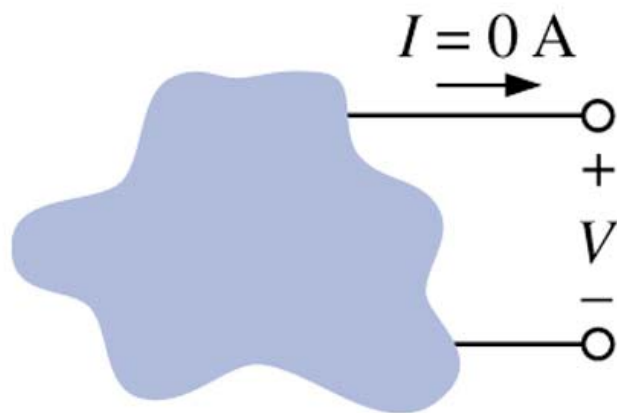

Open circuit


(a)

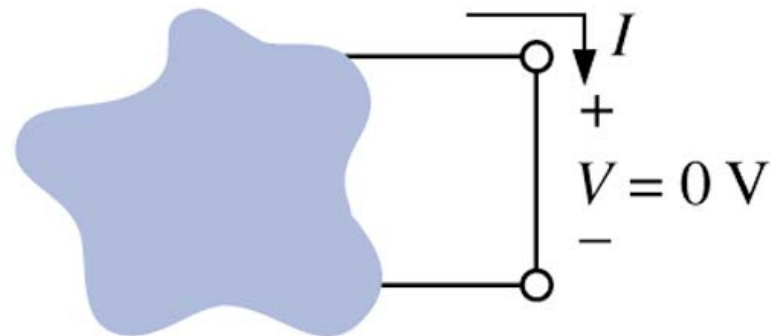


Short circuit

(b)


# Open and Short-Circuits

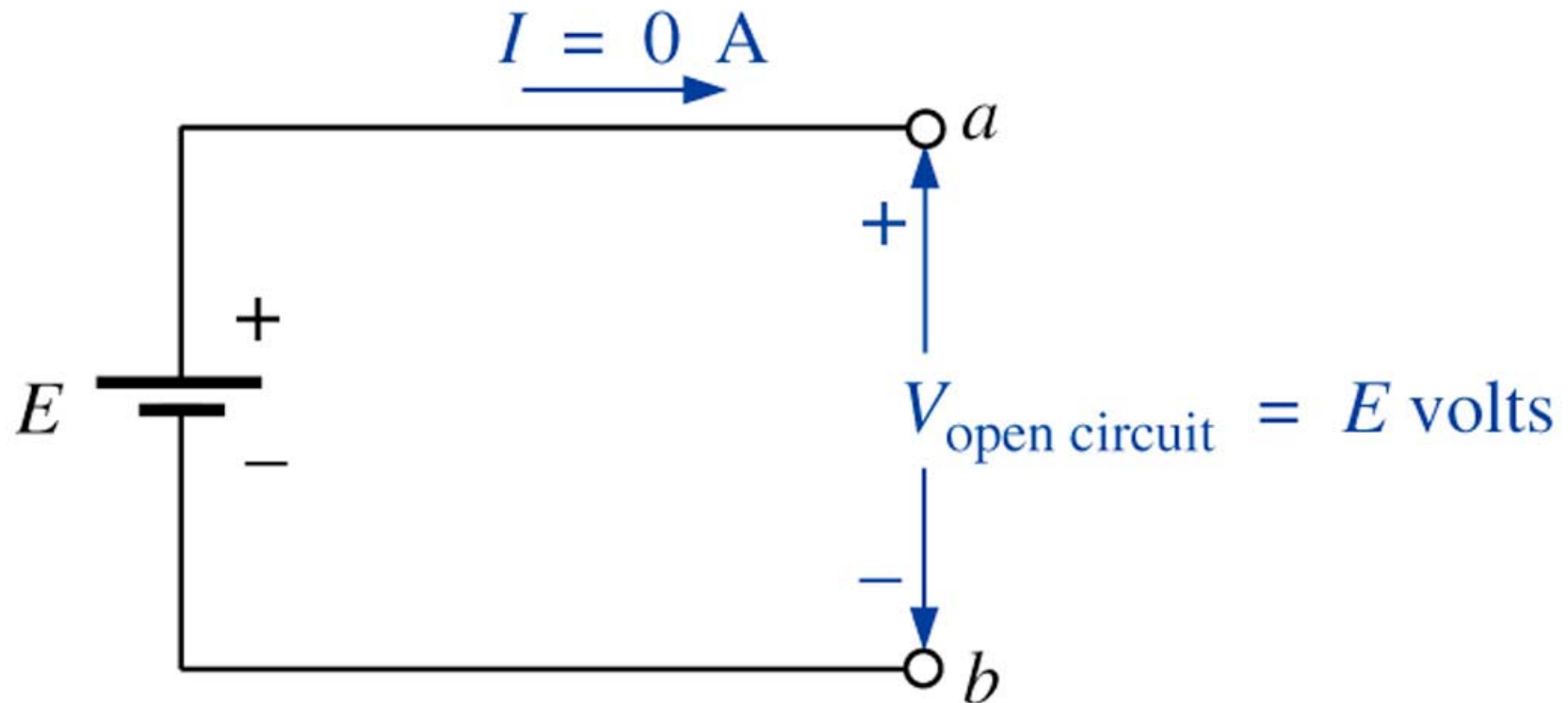

# Open and Short-Circuits

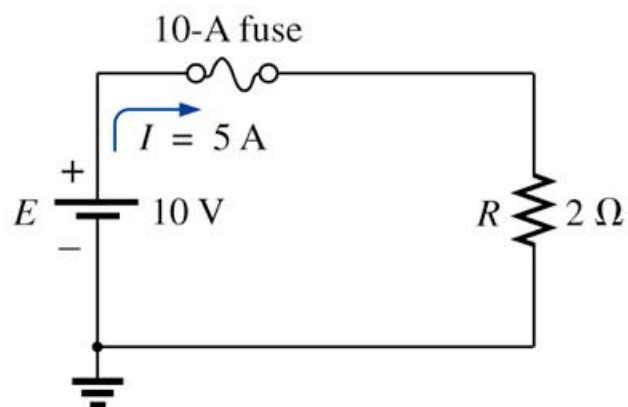


(a)

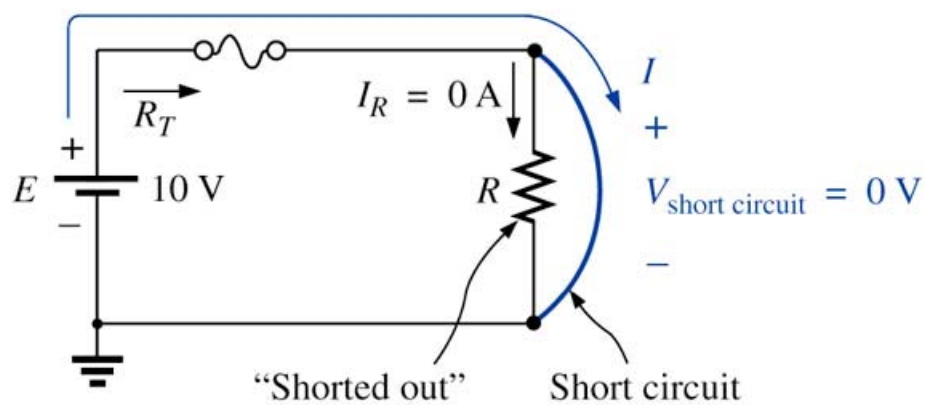


(b)

# Open and Short-Circuits

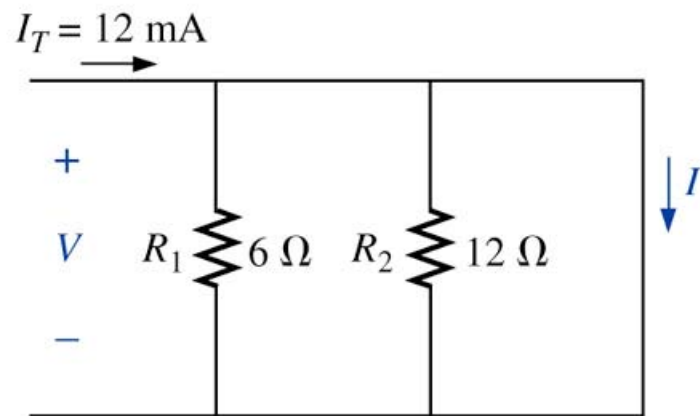


(a)

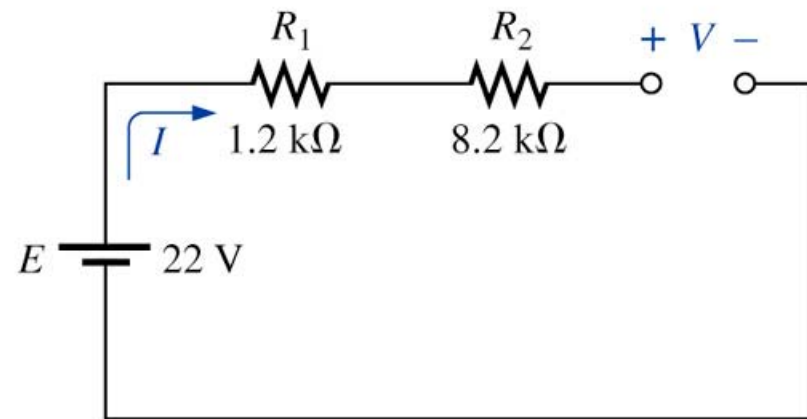


(b)



# Open and Short-Circuits

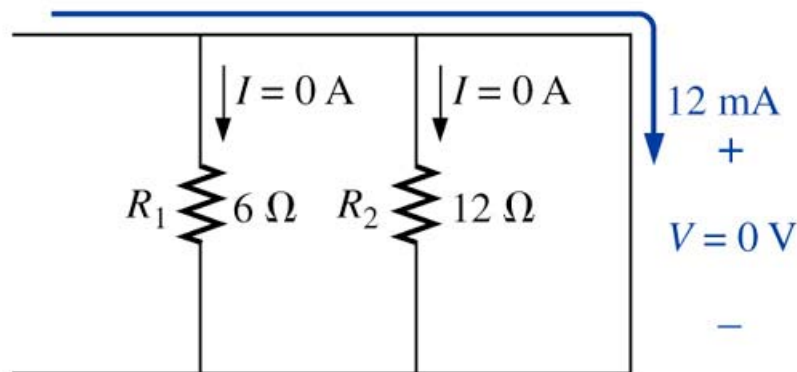


(a)

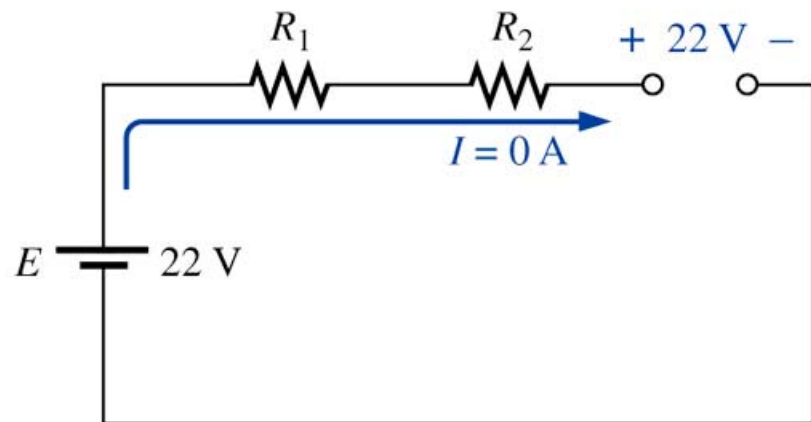

(b)


## Breakout #2

- Find  $V_{ab}$  and  $V_{cd}$

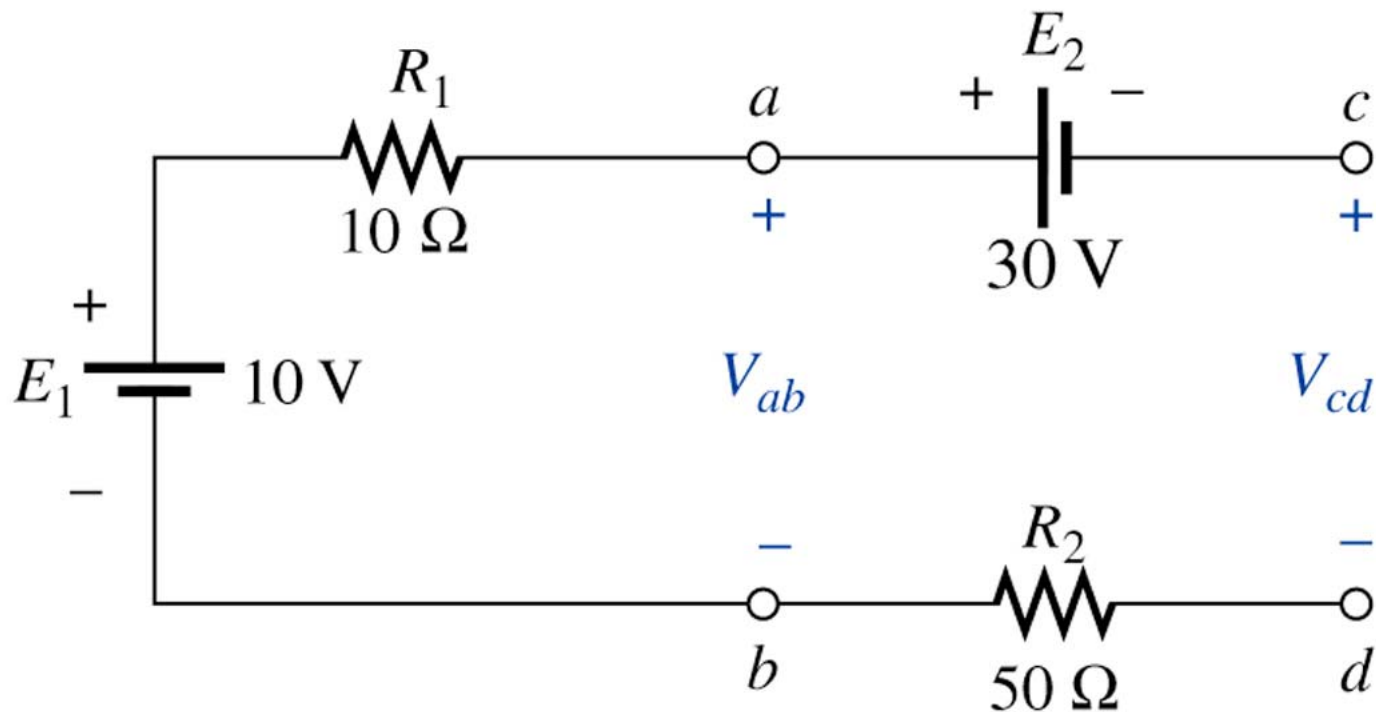


## Breakout #3

- Find  $I$  and  $V$

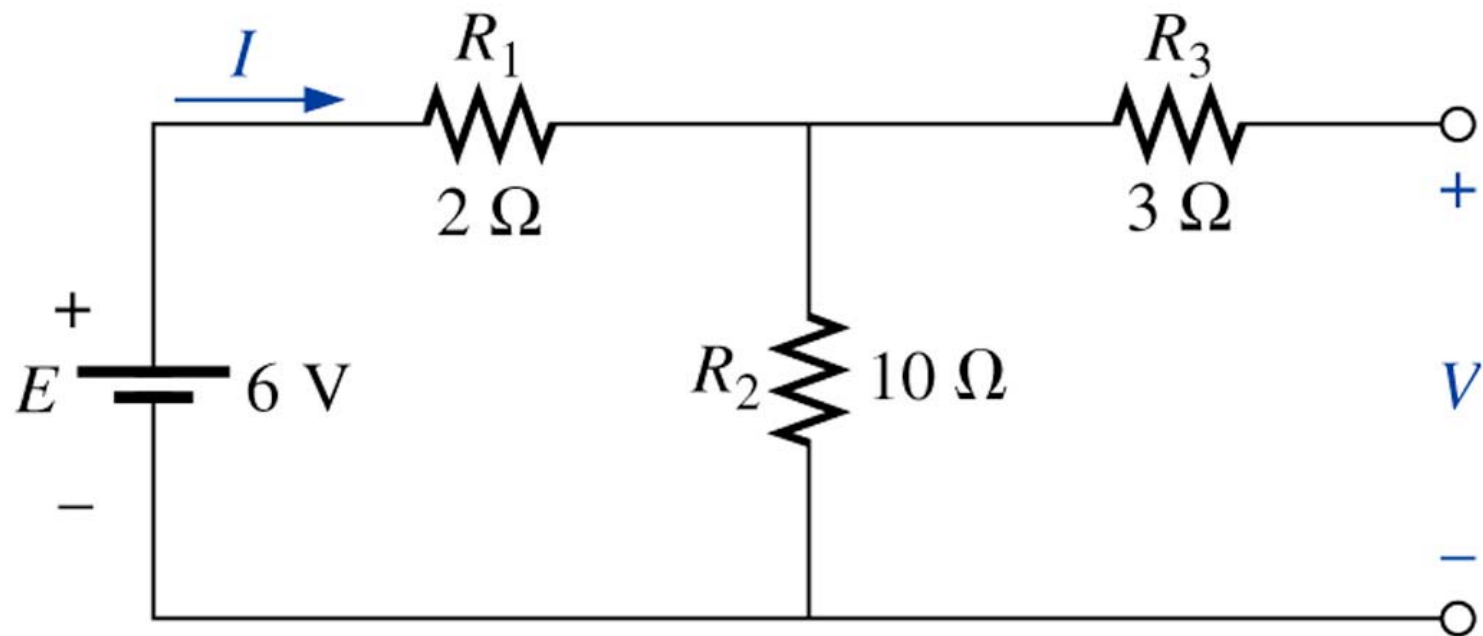


# Voltmeter Loading

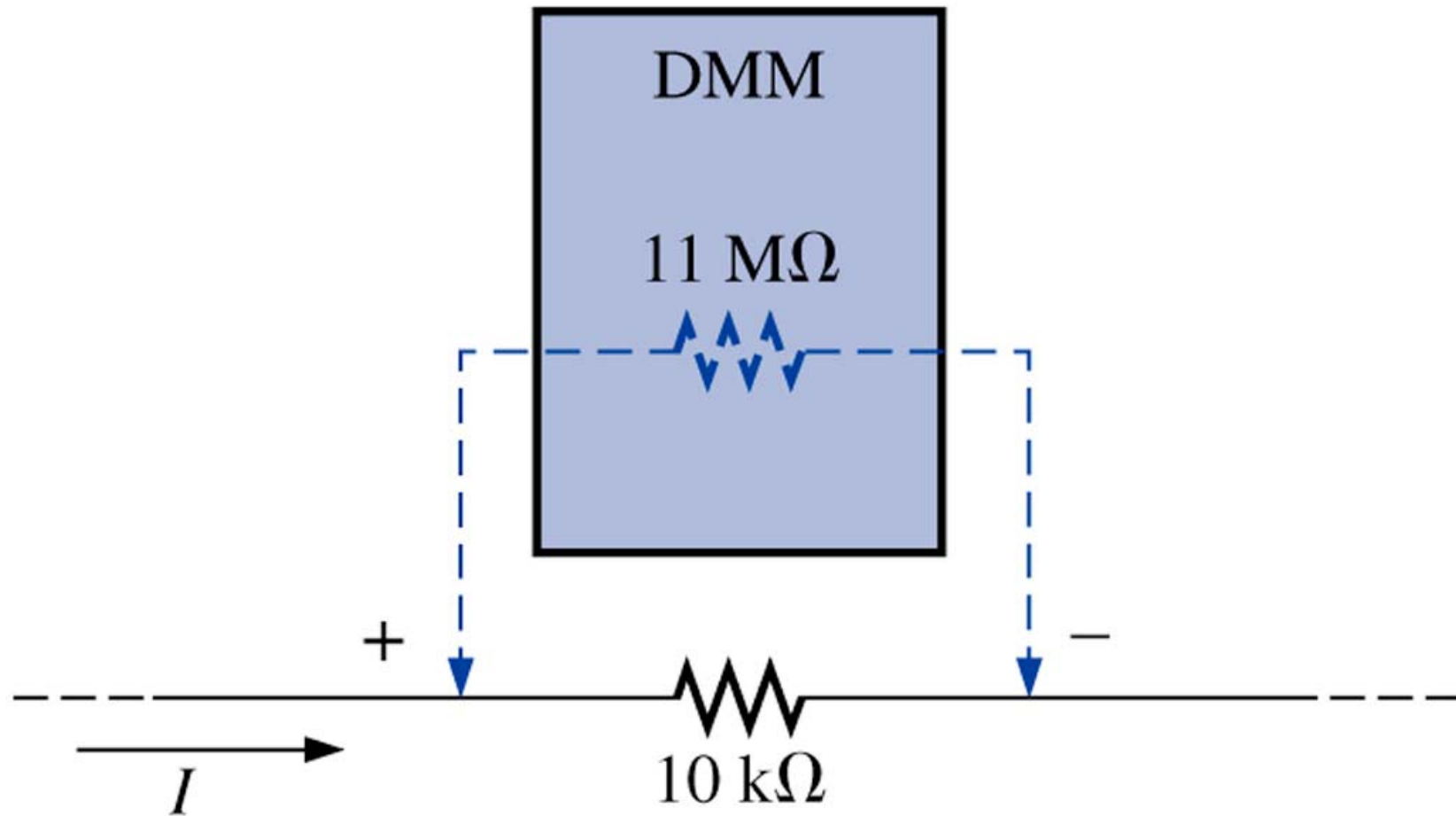

## Example – Voltmeter Loading

- Find  $V_{ab}$  w/DMM connected

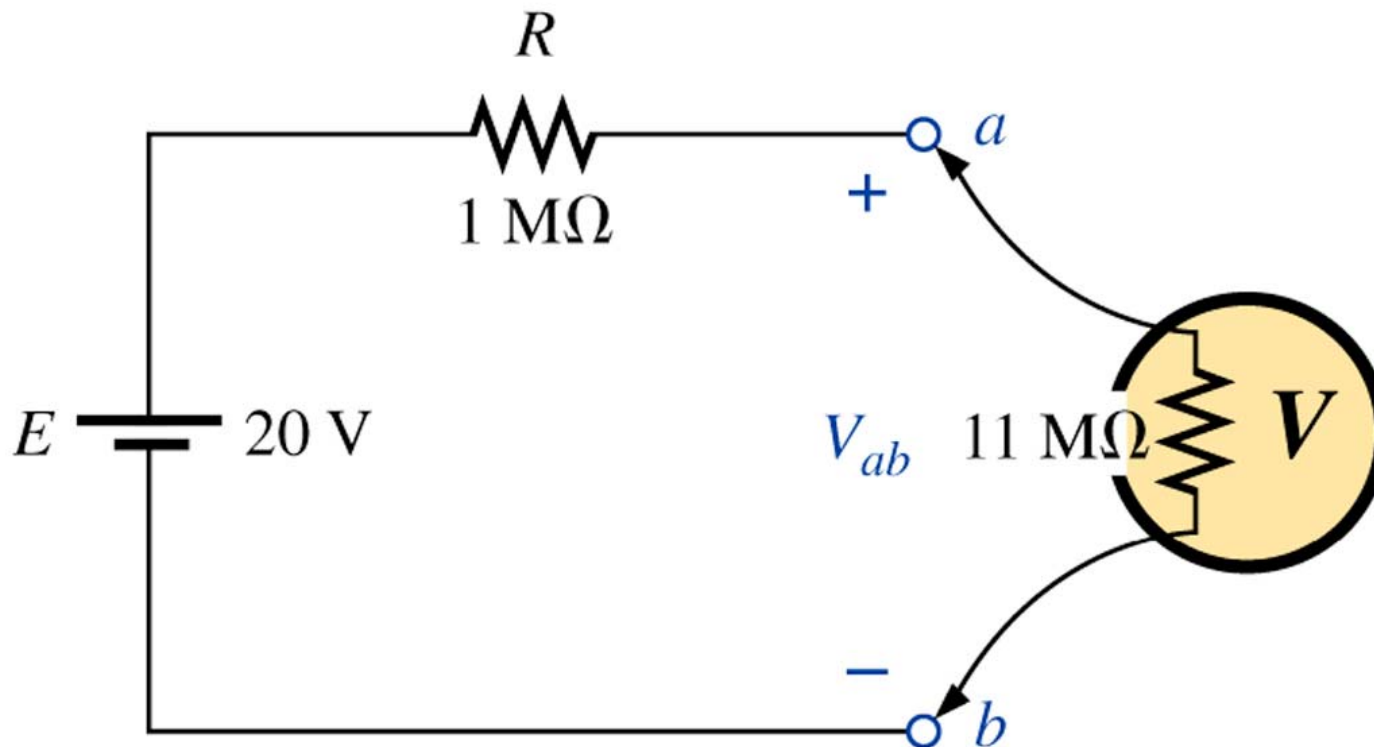

# Automotive Electrical System (partial)

