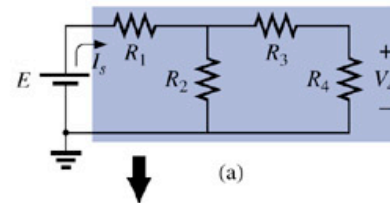


Series-Parallel Circuits


■ General Approach:

- Study the problem before “jumping in”
 - Think about the “knowns” and “unknowns”
- Examine each region of the network w.r.t. the unknowns
 - This may yield an “obvious” solution
- REDRAW the circuit as often as necessary
 - Reduces complexity
 - Leave the unknowns undisturbed (if you can)



Reduce and Return Approach




Want I_s and V_4

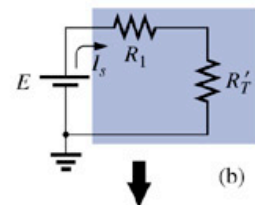

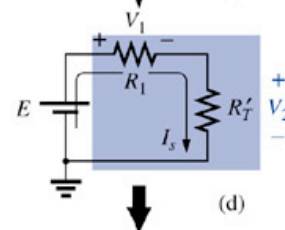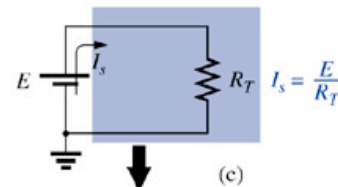Combine R_2, R_3, R_4
(allows us to solve for I_s)




Find V_2
(voltage across R_2)

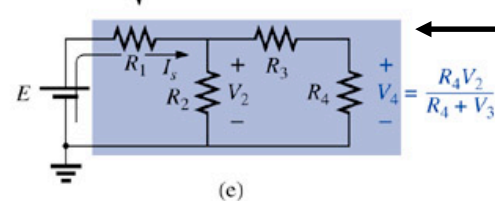


Use V_2 to solve for V_4
(voltage divider)


Example #1 – Find R_T

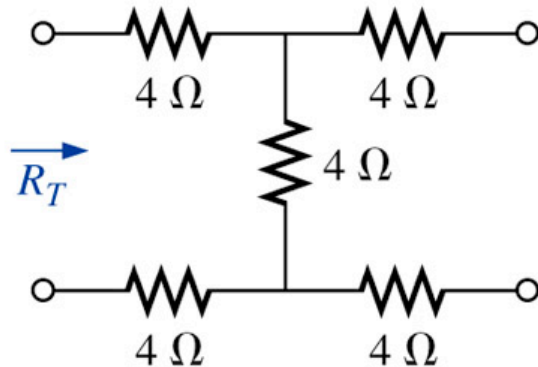


(a)

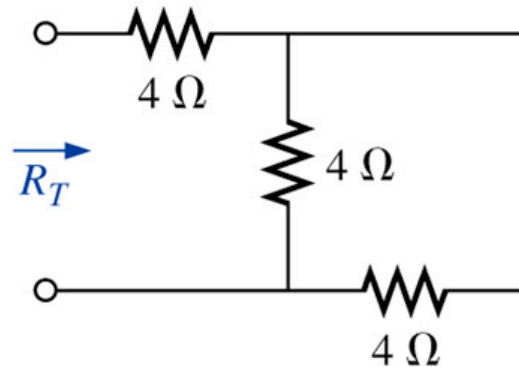

(b)

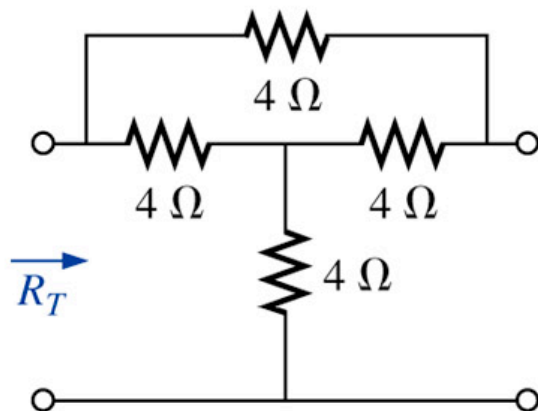


(c)

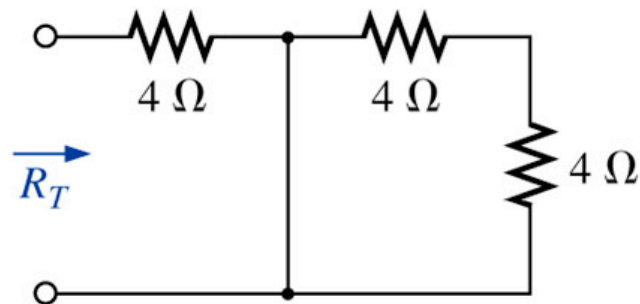

(d)


Example #1 – Find R_T

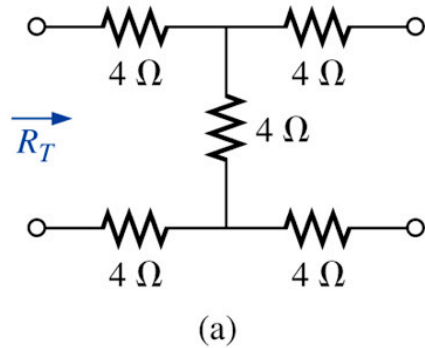

$$\begin{aligned} R_T &= 4 + 4 + 4 \\ &= 12\Omega \end{aligned}$$

$$\begin{aligned} R_T &= 4 + 4 \parallel 4 \\ &= 4 + 2 \\ &= 6\Omega \end{aligned}$$


Example #1 – Find R_T

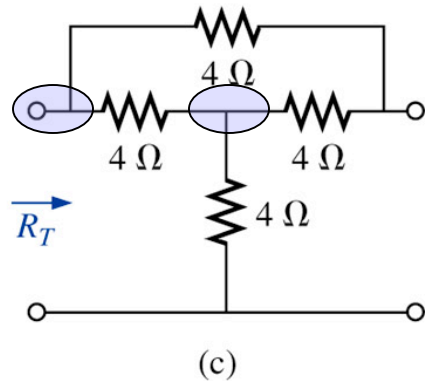


$$R_T = 4\Omega$$

$$\begin{aligned} R_T &= 4 \parallel (4 + 4) + 4 \\ &= 2.667 + 4 = 6.667 \end{aligned}$$

Example #2 – Find I , R_T , I_1 , V_3

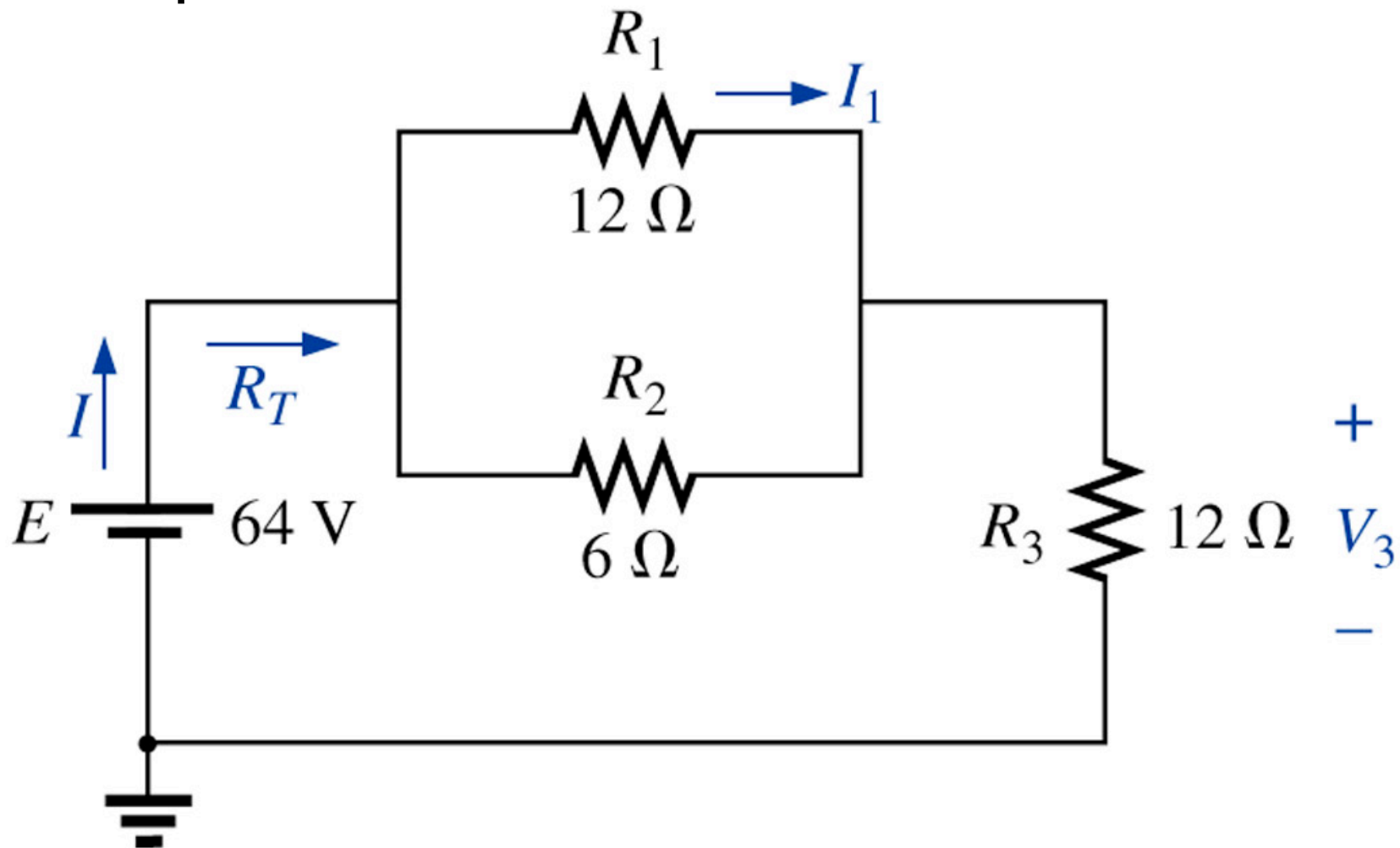

Example #2 – Find I , R_T , I_1 , V_3

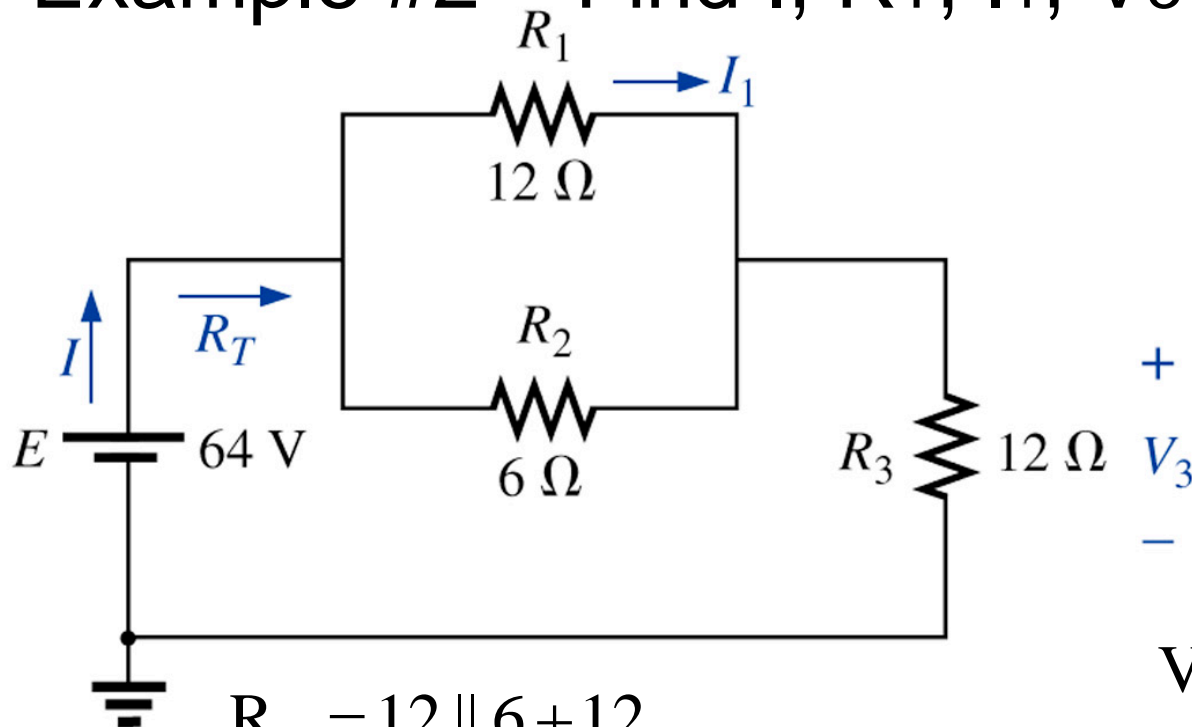

$$R_T = 12 \parallel 6 + 12$$

$$= 4 + 12 = 16\Omega$$

$$I = \frac{E}{R_T} = \frac{64\text{ V}}{16\Omega}$$

$$= 4\text{ A}$$

$$I_1 = I \frac{R_1 \parallel R_2}{R_1}$$


$$= 4\text{ A} \frac{4\Omega}{12\Omega} = 1.33\text{ A}$$

+
 V_3
–


$$V_3 = I \cdot R_3 = 4\text{ A} \cdot 12\Omega$$

$$= 48\text{ V}$$

Block Diagram Approach

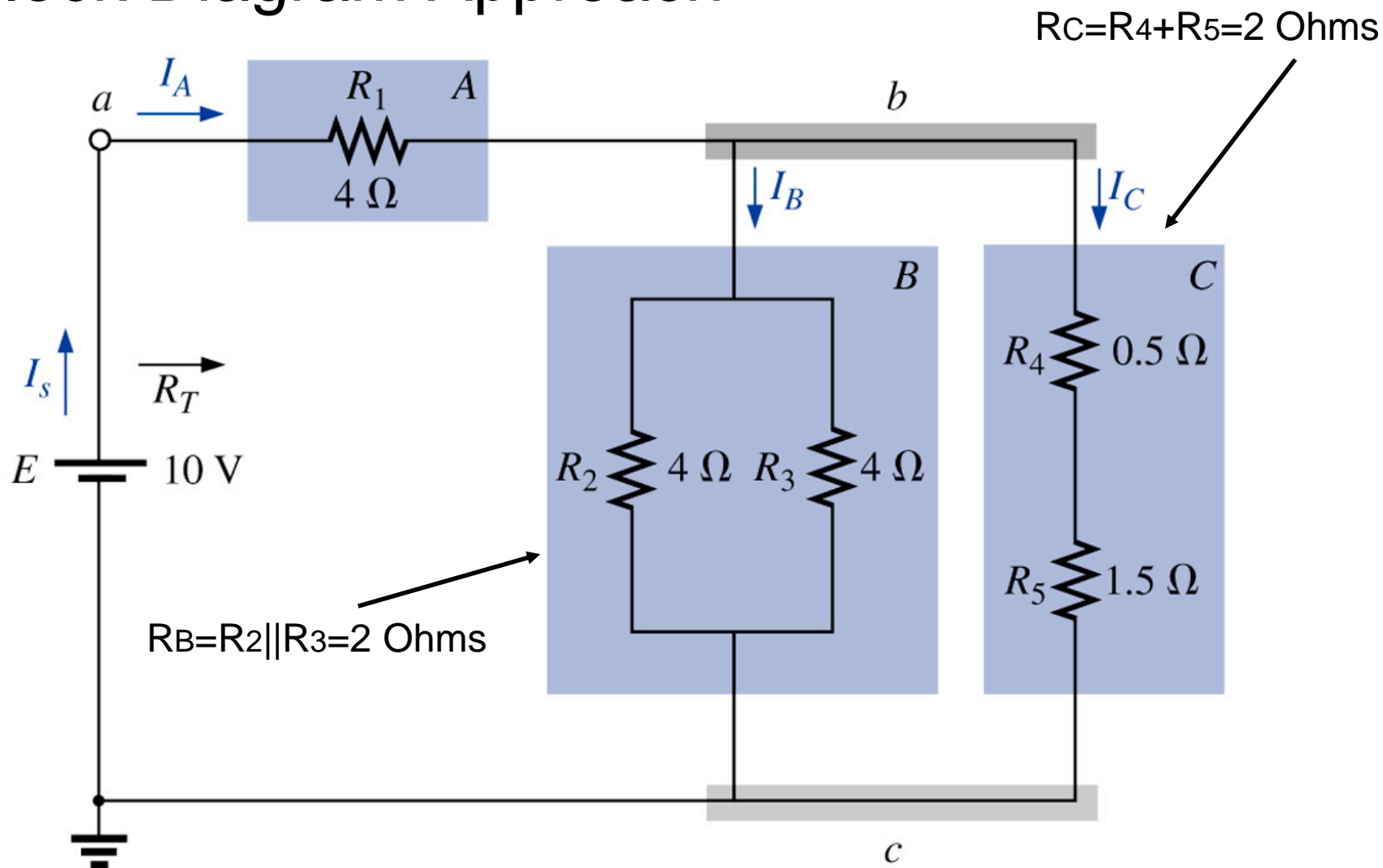

Block Diagram Approach

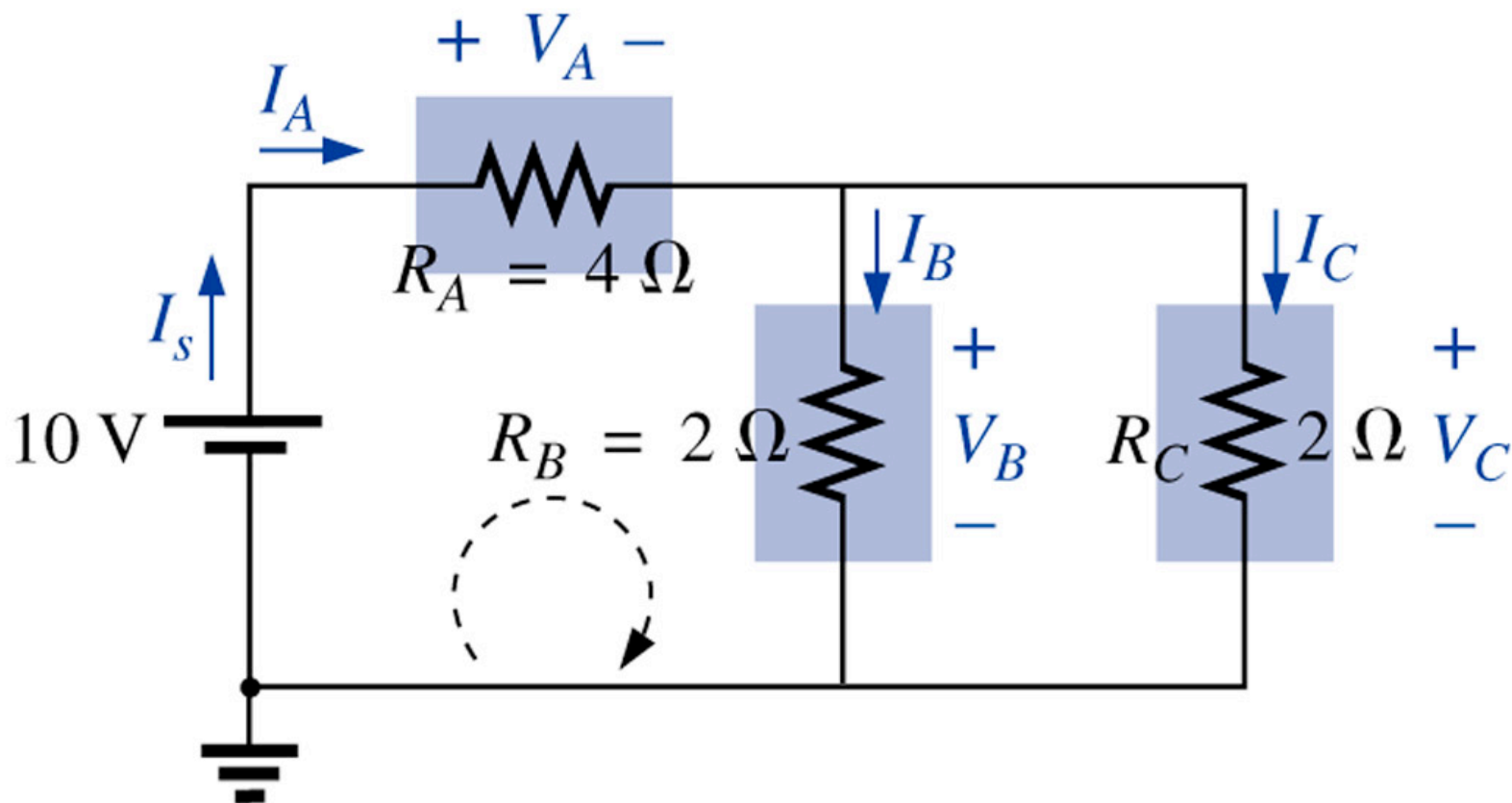


Block Diagram Approach

$$R_T = R_A + (R_B || R_C) = 5 \text{ Ohms}$$

$$I_s = \frac{10 \text{ V}}{5 \Omega} = 2 \text{ A}$$

$$I_B = I_C = 1 \text{ A}$$

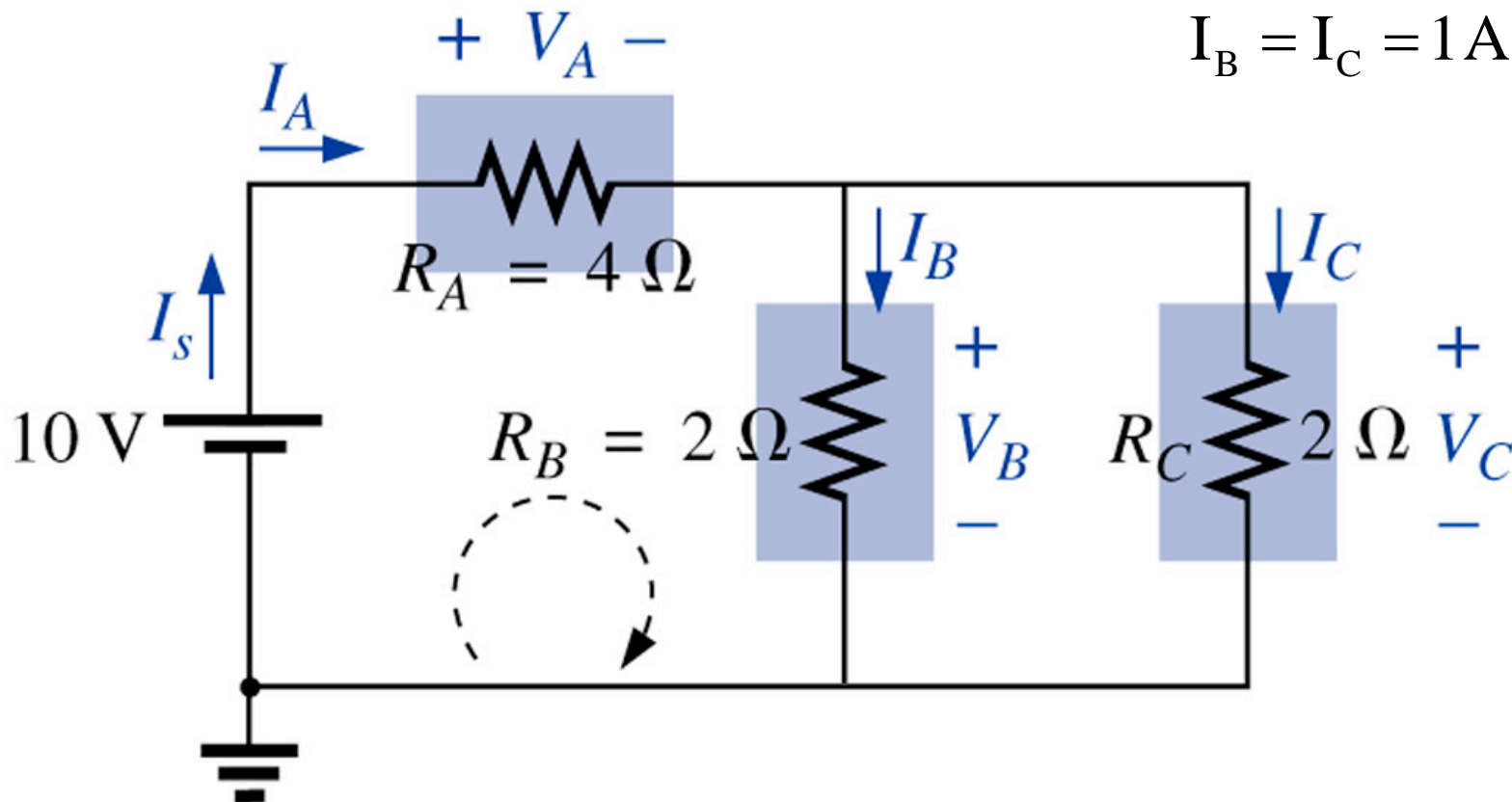

Breakout #1 – Find I_1 , I_B , I_C , V_{R4}

