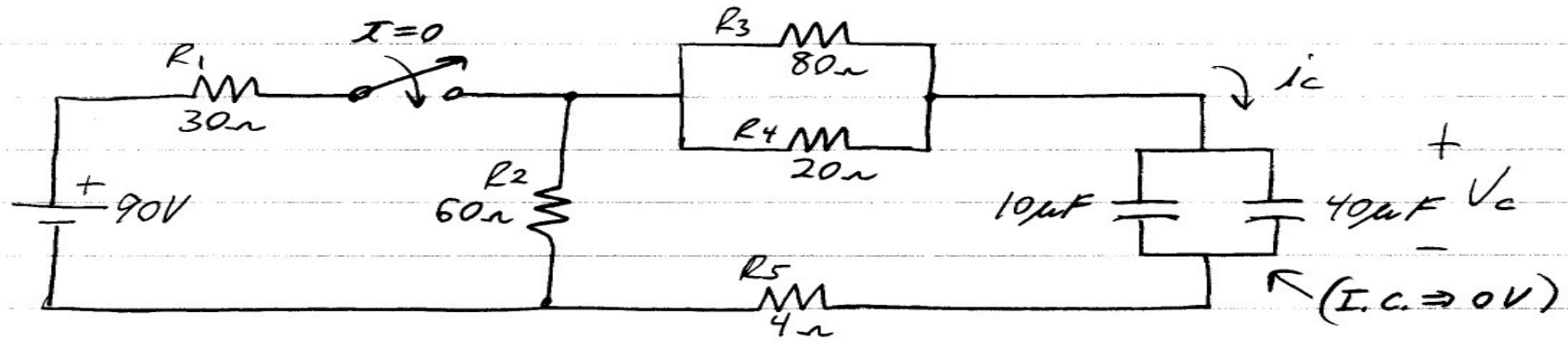



(EXAMPLE 3) Find $V_c + Q$ at $t = 1 \text{ ms}$
 & $t = 1 \text{ hour}$:



THEVENIN EQUIVALENT SEEN BY $C_{EQ} = 50\mu\text{F}$?
 (For $t \geq 0$)

$$R_{TH} = (R_1 // R_2) + (R_3 // R_4) + R_5$$

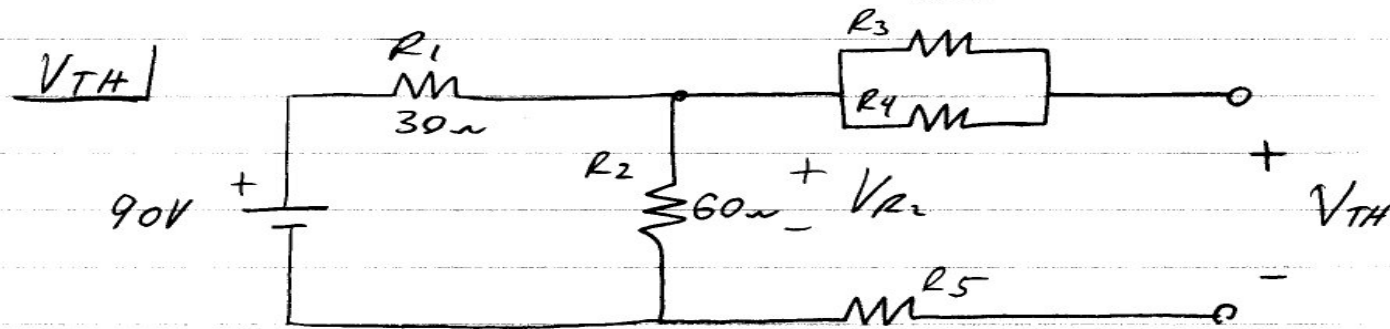
$$= 20\Omega + 16\Omega + 4\Omega = \underline{\underline{40\Omega}}$$



NO CURRENT THROUGH R_3, R_4 OR R_5

$$\therefore V_{TH} = V_{R_2} = 90V \left(\frac{60\Omega}{60\Omega + 30\Omega} \right) = \underline{\underline{60V}}$$

WE HAVE (For $t \geq 0$) ?

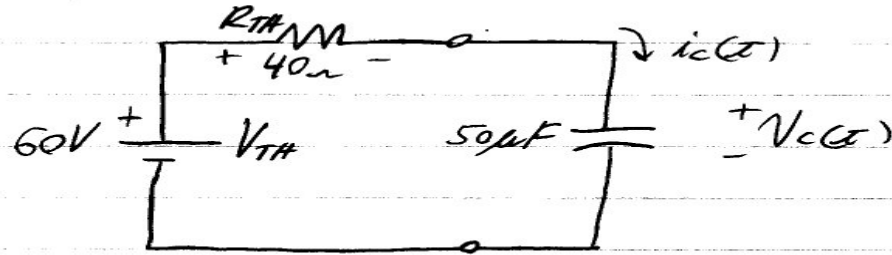

$$i_c(t) = i_{cMAX} e^{-t/\tau}$$

$$i_{cMAX} = \frac{(60 - 0)V}{40\Omega} = 1.5A$$

$$\tau = R_{TH} \cdot C_{EQ} = (40\Omega)(50\mu F) = 2ms$$

$$\therefore i_c(t) = 1.5 e^{\frac{-t}{2 \times 10^{-3}}} A, \quad t > 0$$

FIND $V_c(t)$

$$KVL: V_{TH} - i_c(t) R_{TH} - V_c(t) = 0$$


$$\therefore V_c(t) = V_{TH} - i_c(t) R_{TH}$$

$$V_c(t) = 60 - 60 e^{\frac{-t}{2 \times 10^{-3}}}$$

$$\text{OR } V_c(t) = 60 \left(1 - e^{\frac{-t}{2 \times 10^{-3}}} \right) V, \quad t \geq 0$$

$$\text{@ } t = 1ms: V_c(1 \times 10^{-3}) = 60 \left(1 - e^{\frac{-1 \times 10^{-3}}{2 \times 10^{-3}}} \right) = \boxed{23.61V}$$

WE HAVE :

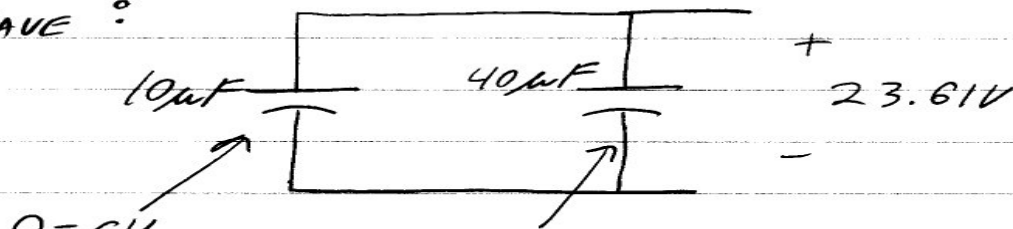

$$Q = CV$$

$$= \boxed{236.1 \mu C}$$

$$\therefore \boxed{Q = 944.4 \mu C}$$