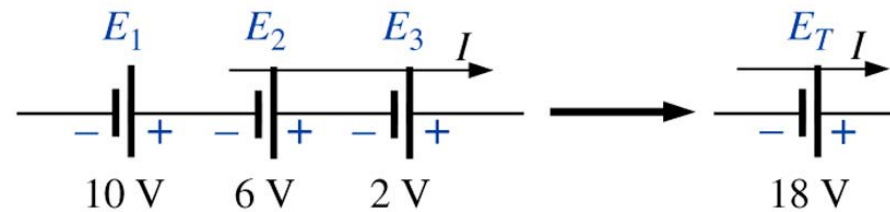


Today's Material


- Voltage Sources in Series (and series equivalent circuits)
 - Introduction
 - In the Lab (application)
 - Example
 - Breakout #1
- Kirchhoff's Voltage Law
 - Statement
 - Examples
 - Breakout #2

Voltage Sources in Series - Introduction

- To combine voltage sources in series, *algebraically* add the individual source values





(a)

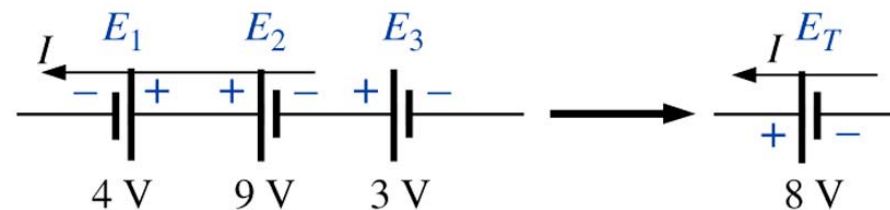

(b)


Voltage Sources in Series – In the Lab

- Series voltage sources in lab

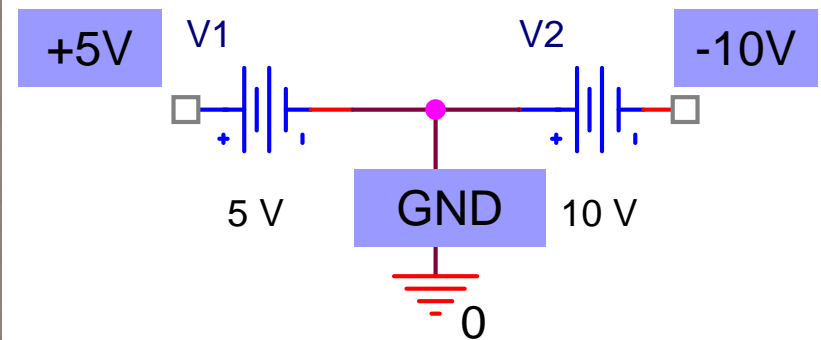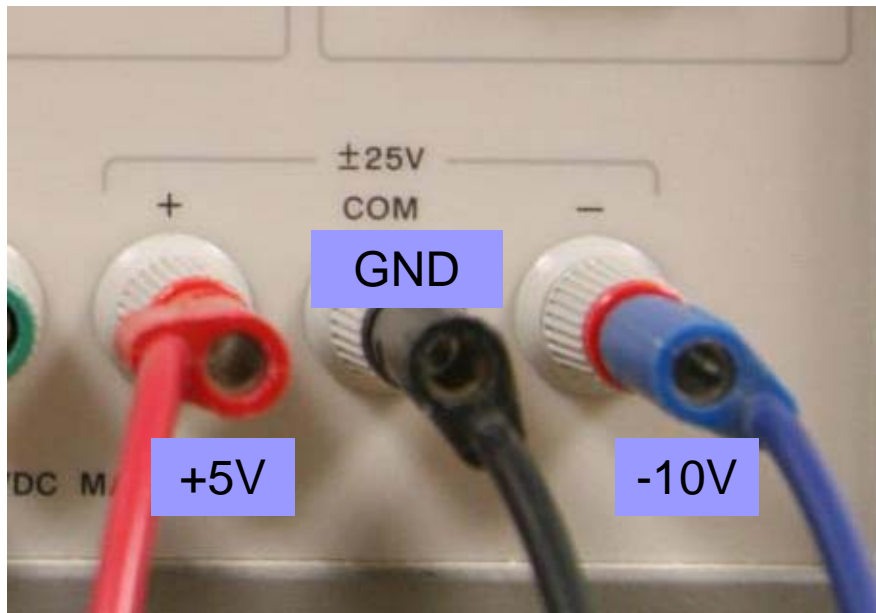

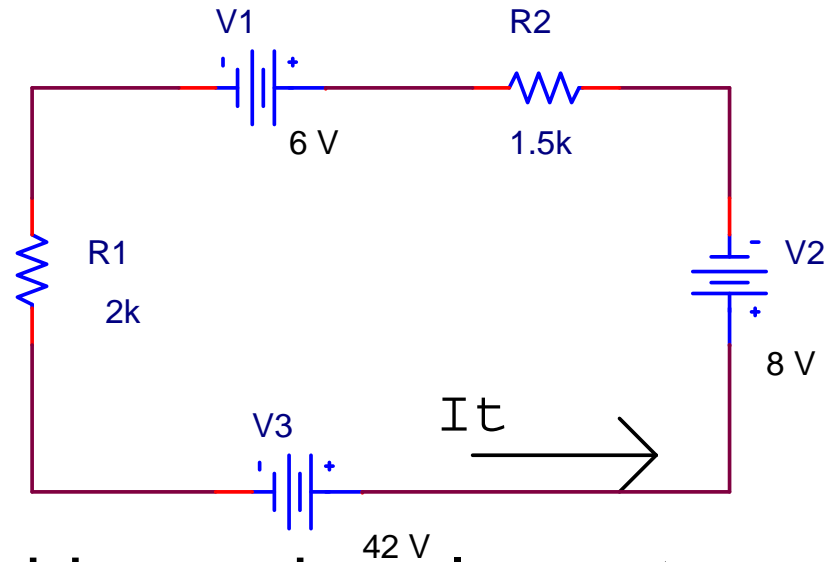Example Series Circuit

- Find I_T , The net source P_{DELIV} , P_{ABS} :



- Step 1: Combine series elements

- ☐ Find R_T


- $R_1 + R_2 = 3.5\text{k-ohms}$

- ☐ Find V_T - Polarity is *KEY*

- $V_T = V_3 - V_2 - V_1 = 28\text{ V}$

Example Series Circuit

- Step 2: Draw the equivalent circuit

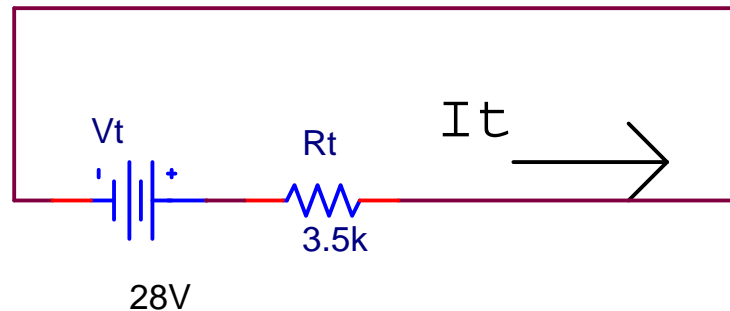

- Step 3: Analyze using standard circuit analysis techniques

$$I_T = \frac{V_T}{R_T} = \frac{28 \text{ V}}{3.5 \text{ k}\Omega} = 8 \text{ mA}$$


$$P_{\text{DELIV}} = V_T \cdot I_T = 28 \text{ V} \cdot 8 \text{ mA} = 224 \text{ mW}$$

$$P_{\text{ABS}} = I_T^2 \cdot R_T = (8 \text{ mA})^2 \cdot 3.5 \text{ k}\Omega = 224 \text{ mW}$$

Breakout #1 – Using the same circuit


■ Questions

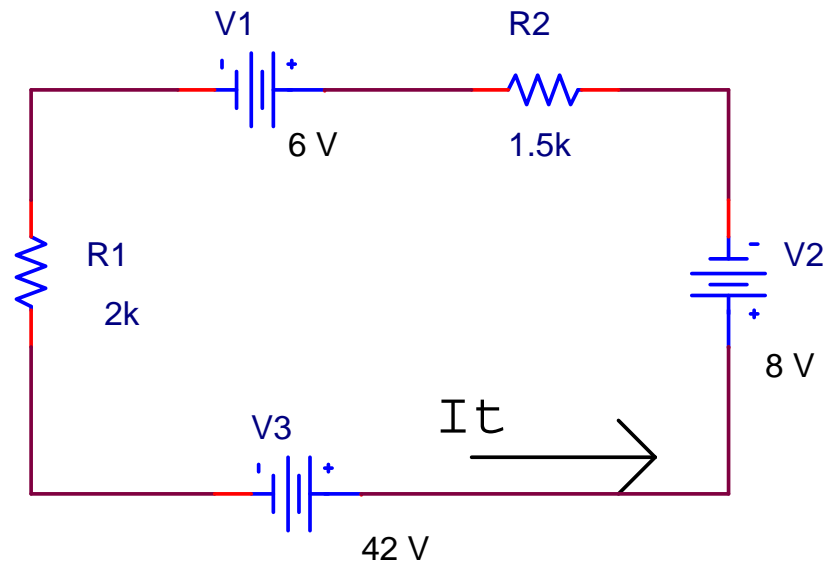- ☐ Was source V_1 delivering or absorbing power? How much?
- ☐ What about source V_2 ?
- ☐ What about source V_3 ?



Kirchhoff's Voltage Law

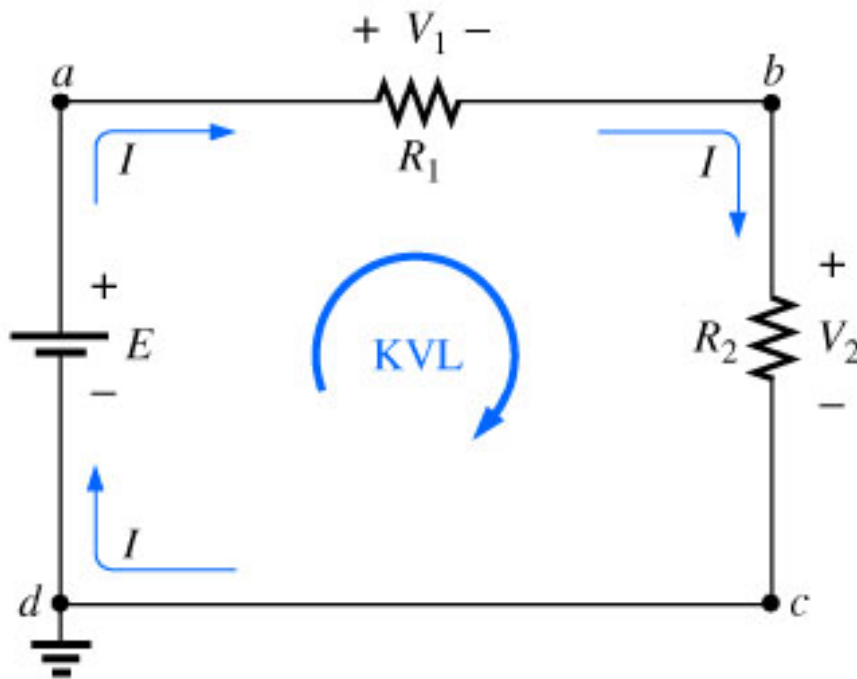- Kirchhoff's voltage law (KVL) states that the algebraic sum of the potential rises and drops around a closed loop (or path) is zero.



$$+ E - V_1 - V_2 = 0$$

$$+ V_{ad} - V_{ab} - V_{bc} = 0$$

Kirchhoff's Voltage Law


- The applied voltage of a series circuit equals the sum of the voltage drops across the series elements:

$$\sum V_{\text{rises}} = \sum V_{\text{drops}}$$

- The sum of the rises around a closed loop must equal the sum of the drops.
- The application of Kirchhoff's voltage law need not follow a path that includes current-carrying elements.
 - When applying Kirchhoff's voltage law, be sure to concentrate on the *polarities* of the voltage rise or drop rather than on the type of element.
 - Do not treat a voltage drop across a resistive element differently from a voltage drop across a source.

Kirchhoff's Voltage Law - Example

- Find V_{ab} :

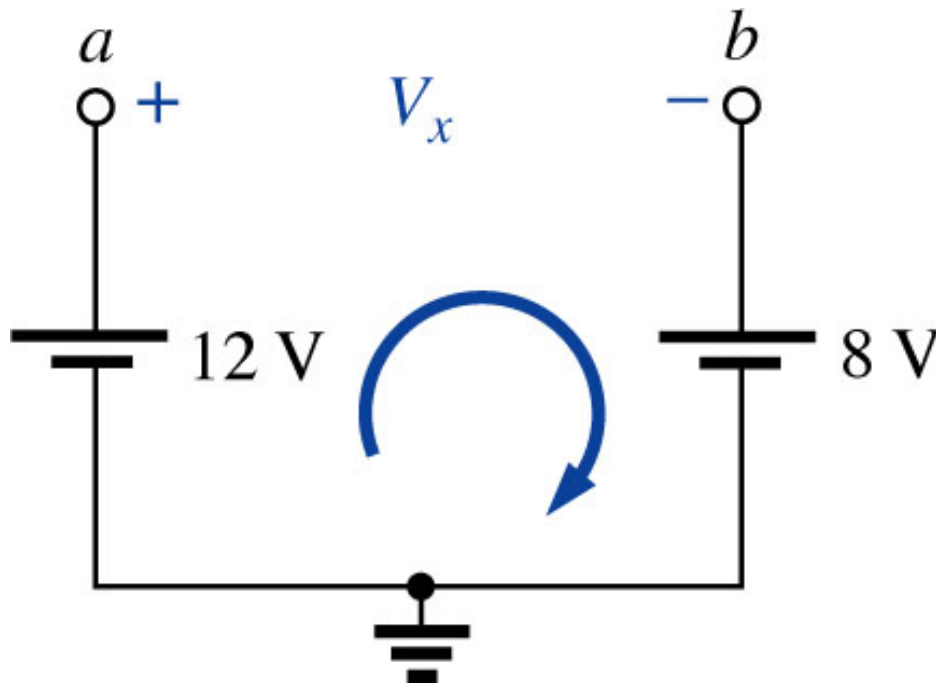


$$+12\text{ V} - V_{ab} - 8\text{ V} = 0$$

$$V_{ab} = 12\text{ V} - 8\text{ V} = 4\text{ V}$$




Kirchhoff's Voltage Law – More Examples

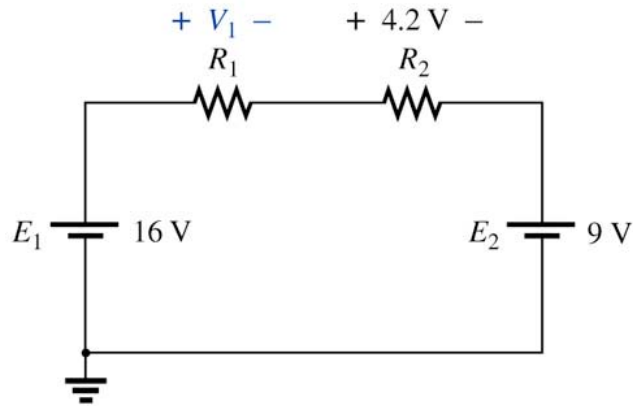

Find V_1

$$+16 - V_1 - 4.2V - 9V = 0$$

$$V_1 = 16V - 4.2V - 9V = 2.8V$$

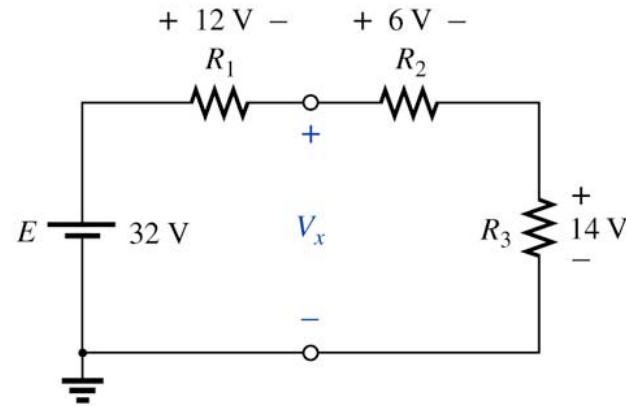

Find V_x

$$+32V - 12V - V_x = 0$$

$$V_x = 32V - 12V = 20V$$

OR

$$+V_x - 6V - 14V = 0$$

$$V_x = 14V + 6V = 20V$$

Breakout #2

- Find V_{R1} and V_2

