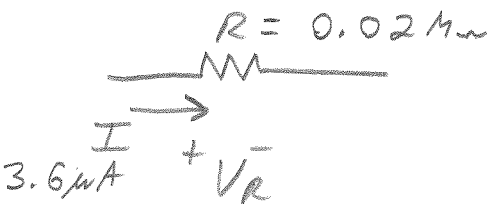


- (4-2) WHAT IS THE CURRENT THROUGH A 6.8Ω RESISTOR IF THE VOLTAGE DROP ACROSS IT IS $24V$?

$$\frac{V}{R} \rightarrow I = \frac{V}{R} = \frac{24V}{6.8\Omega} = \boxed{3.5 A}$$

- (4-5) GIVEN: 

FIND: V_R


$$\begin{aligned} V_R &= I \cdot R = (3.6\mu A)(0.02M\Omega) \\ &= (3.6 \times 10^{-6} A)(0.02 \times 10^6 \Omega) \\ &= \boxed{72.0 mV} \end{aligned}$$

- (4-10) IF A CD PLAYER DRAWS $125 mA$ WHEN $4.5V$ IS APPLIED, FIND ITS INTERNAL RESISTANCE.

$$R_{INT} = \frac{V_{APPL}}{I_{DRAWN}} = \frac{4.5V}{125 mA} = \boxed{36\Omega}$$

- (4-12) $\left. \begin{array}{l} R_{INT} = 0.5\Omega \\ I = 12A \end{array} \right\} \text{DC GENERATOR}$

FIND V_{LOSS} :

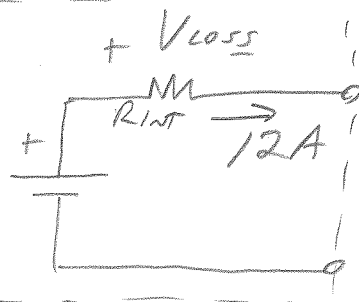

$$\begin{aligned} V_{LOSS} &= R_{INT} \cdot I \\ &= (0.5\Omega)(12A) \\ &= \boxed{6.0V} \end{aligned}$$

(4-15) a) USE EXCEL
PLOT I VS. V FOR A 120Ω
RESISTOR. USE $0 - 100V$ +
 $0 - 1A$ SCALES

* - SEE ATTACHED

b) USE THE GRAPH FROM PART a,
FIND THE CURRENT AT $V = 20V$
+
 $V = 50V$


* - SEE ATTACHED

FROM PLOT : @ $V = 20V$, $I \approx 0.165A$
 $R = \frac{20V}{0.165A} = 121.1\Omega$

R (ohms) 120

Vr (V)	Ir (A)
0	0
5	41.7E-3
10	83.3E-3
15	125.0E-3
20	166.7E-3
25	208.3E-3
30	250.0E-3
35	291.7E-3
40	333.3E-3
45	375.0E-3
50	416.7E-3
55	458.3E-3
60	500.0E-3
65	541.7E-3
70	583.3E-3
75	625.0E-3
80	666.7E-3
85	708.3E-3
90	750.0E-3
95	791.7E-3
100	833.3E-3

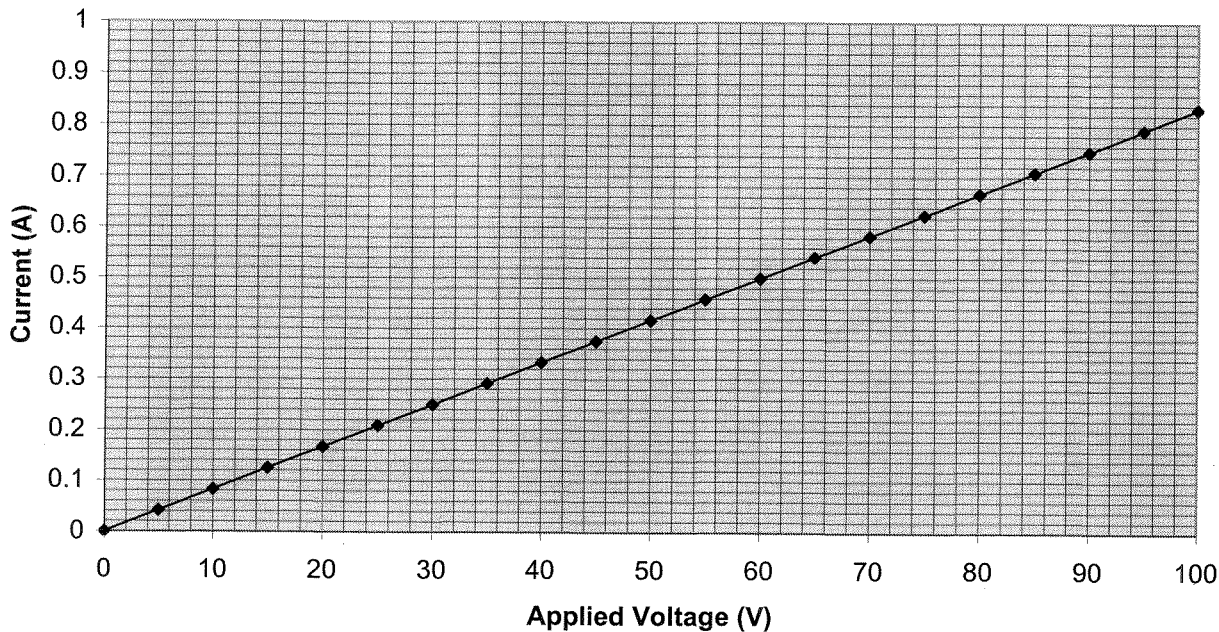Current as a Function of Applied Voltage
R = 120 ohms



(4-19) (a) PLOT THE I-V CHARACTERISTICS OF A $2\text{ k}\Omega$, $1\text{ M}\Omega$, & A 100Ω RESISTOR ON THE SAME GRAPH. USE SCALES OF 0-20V & 0-10mA.

* - SEE ATTACHED

(b) COMMENT ON THE STEEPNESS OF THE CURVES W/ DECREASING R.

$R = 1\text{ M}\Omega$, "FLAT"

\downarrow
 $R = 100\Omega$, VERY STEEP

$$\left[\begin{array}{l} \text{AS } R \downarrow \text{ SLOPE } \uparrow \\ I = mV + b \quad \Rightarrow \quad I = \left(\frac{\Delta I}{\Delta V} \right) V + 0 \\ \begin{array}{c} y' \\ \text{slope} \end{array} \quad \begin{array}{c} x \\ \text{intercept} \end{array} \quad I = \left(\frac{1}{R} \right) V \end{array} \right]$$

(c) ARE THE CURVES LINEAR OR NON-LINEAR? Why?

LINEAR, SEE (b) ABOVE

OHMS LAW \rightarrow LINEAR RELATIONSHIP BETWEEN V & I:


$$V = I \cdot R$$

\downarrow

$$I = \left(\frac{1}{R} \right) V$$

R (ohms)	2000	1.00E+06	100
Vr (V)	Ir (A)		
0	0	0	0
1	500.0E-6	1.0E-6	10.0E-3
2	1.0E-3	2.0E-6	20.0E-3
3	1.5E-3	3.0E-6	30.0E-3
4	2.0E-3	4.0E-6	40.0E-3
5	2.5E-3	5.0E-6	50.0E-3
6	3.0E-3	6.0E-6	60.0E-3
7	3.5E-3	7.0E-6	70.0E-3
8	4.0E-3	8.0E-6	80.0E-3
9	4.5E-3	9.0E-6	90.0E-3
10	5.0E-3	10.0E-6	100.0E-3
11	5.5E-3	11.0E-6	110.0E-3
12	6.0E-3	12.0E-6	120.0E-3
13	6.5E-3	13.0E-6	130.0E-3
14	7.0E-3	14.0E-6	140.0E-3
15	7.5E-3	15.0E-6	150.0E-3
16	8.0E-3	16.0E-6	160.0E-3
17	8.5E-3	17.0E-6	170.0E-3
18	9.0E-3	18.0E-6	180.0E-3
19	9.5E-3	19.0E-6	190.0E-3
20	10.0E-3	20.0E-6	200.0E-3

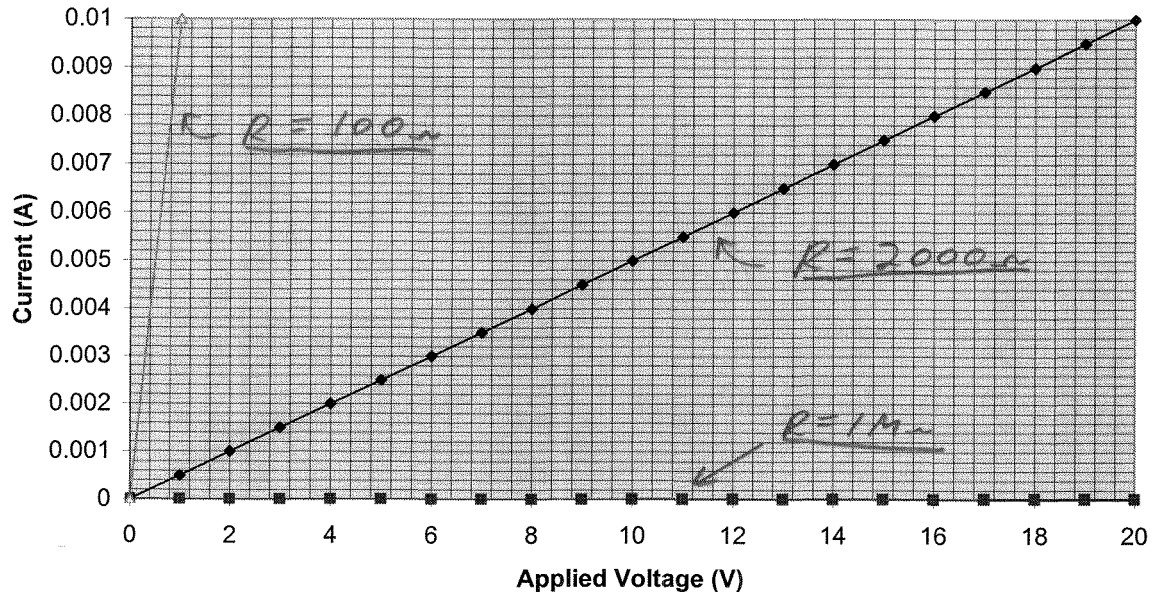Current as a Function of Applied Voltage
R = 2 k-ohms, 1 M-ohms, 100 ohms



(4-21) THE POWER TO A DEVICE IS 40 J/s.
HOW LONG WILL IT TAKE TO DELIVER 640 J?

$$\frac{640 \text{ J}}{40 \text{ J/s}} = \boxed{16 \text{ SECONDS}}$$

(4-25) FIND P_{deliv} FOR A 6V BATTERY IF
THE CHARGE RATE IS 48 C/MIN?

$$\frac{48 \text{ C}}{\text{MIN}} \cdot \left(\frac{1 \text{ MIN}}{60 \text{ SEC}} \right) = 800 \text{ MC/s}$$

$$\text{BUT } 1 \text{ A} = 1 \text{ C/s} \therefore I = \underline{800 \text{ mA}}$$

$$P = I \cdot V = (800 \text{ mA})(6 \text{ V}) = \boxed{4.8 \text{ W}}$$

(4-34) A CALCULATOR W/ A 3V BATTERY
DRAWS 0.4 mW.

(a) FIND I_{supply}

$$P = I \cdot E$$
$$\therefore I_{\text{supply}} = \frac{0.4 \text{ mW}}{3 \text{ V}}$$


$$\boxed{I_{\text{supply}} = 133.3 \mu\text{A}}$$

(b) IF THE CALCULATOR CAN RUN FOR 500h ON
THE BATT, FIND THE A.h RATING.

$$(500 \text{ h})(133.3 \mu\text{A}) = \boxed{66.7 \text{ mA} \cdot \text{h}}$$

(4-37)

GIVEN :

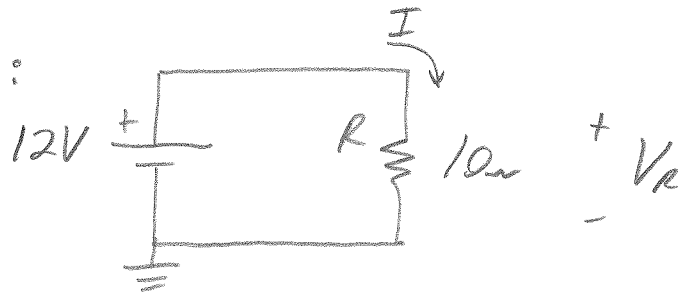

- (a) HOW MANY JOULES WILL R DISSIPATE IN 1 MINUTE ?

$$P_R = \frac{(V_R)^2}{R} = \frac{(12V)^2}{10\Omega} = 14.4W \Rightarrow \underline{14.4 \text{ J/sec}}$$

$$(14.4 \text{ J/sec}) \left(\frac{60 \text{ SEC}}{\text{MIN}} \right) = \underline{864 \text{ J/MIN}}$$

864 JOULES

- (b) IF R IS LEFT CONNECTED FOR 2 MIN, WILL THE ENERGY USE INCREASE? WILL P_R INCREASE?

YES, THE ENERGY USE WILL DOUBLE TO 1728 JOULES

NO, P_R STAYS THE SAME AT 14.4 WATTS

48.

$$\text{kWh} = \frac{(1600 \text{ W})(8 \text{ h}) + (1200 \text{ W})(1/3 \text{ h}) + (4800 \text{ W})(1 \text{ h}) + (900 \text{ W})(1/4 \text{ h}) + (200 \text{ W})(1.2 \text{ h}) + (50 \text{ W})(3.5 \text{ h})}{1000}$$

$$= \frac{12,800 \text{ Wh} + 400 \text{ Wh} + 4800 \text{ Wh} + 225 \text{ Wh} + 240 \text{ Wh} + 175 \text{ Wh}}{1000} = 18.64 \text{ kWh}$$

$$(18.64 \text{ kWh})(12\text{¢/kWh}) = \$2.24$$

(4-50) GIVEN: $P_{in} = 410 \text{ W}$
 $P_{out} = 0.5 \text{ hp}$ } motor

FIND: $\eta \%$

$$(0.5 \text{ hp}) \left(\frac{746 \text{ W}}{\text{hp}} \right) = \underline{373 \text{ W}}$$

$$\eta = \frac{P_o}{P_i} = \frac{373 \text{ W}}{410 \text{ W}} = 0.9097 \text{ or } \underline{91.0\%}$$

(4-58) GIVEN:




FIND: W_o

$$W_o = (W_i)(\eta_T) \quad , \quad \eta_T = (\eta_1)(\eta_2) = \underline{0.64}$$

$$\therefore W_o = (60 \text{ J})(0.64) = \underline{38.4 \text{ J}}$$

(4-60) GIVEN:

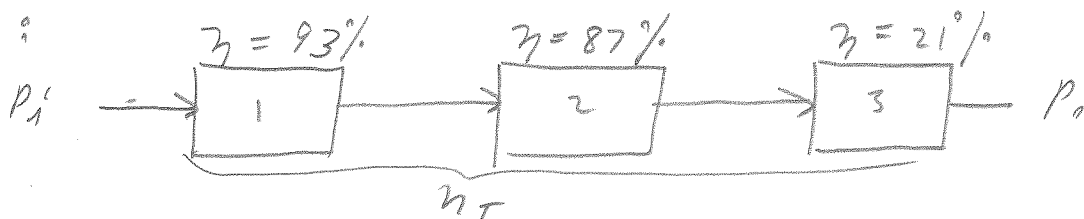

(a) FIND: η_T

$$\eta_T = (\eta_1)(\eta_2)(\eta_3) = 0.1699 \text{ or } \underline{17.0\%}$$


(b) FIND: IF SYSTEM 3 WERE REPLACED SO $\eta_3 = 90\%$,
 FIND THE $\%$ INCREASE IN η_T

$$\eta_T' = (0.93)(0.87)(0.90) = 0.647 \text{ or } \underline{64.7\%}$$


(4-60) (b) CONTINUED

$$\begin{aligned} \% \text{ INCREASE} &= \frac{\text{NEW } \# - \text{OLD } \#}{\text{OLD } \#} \times 100 \% \\ &= \frac{0.5473 - 0.1701}{0.1701} \times 100 \% \\ &= \boxed{280.6 \%} \end{aligned}$$

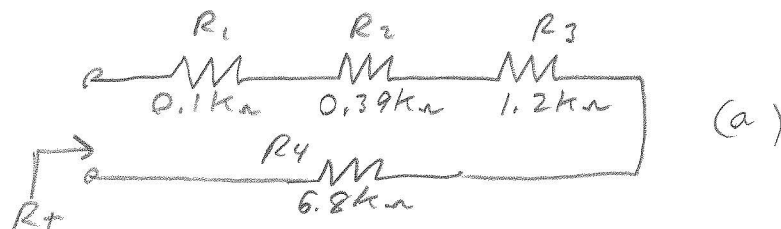
(5-2) FIND R_T FOR EACH CIRCUIT, ONLY STANDARD R VALUES WERE USED.


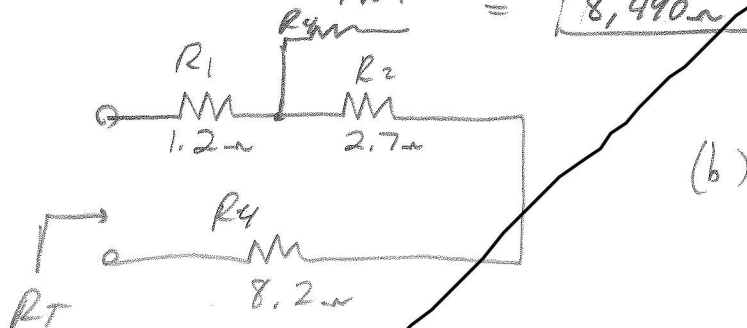
$$R_T = R_1 + R_2 + R_3 + R_4 = (100 + 390 + 1200 + 6800) = \boxed{8,490\Omega}$$



$$R_T = R_1 + R_2 + R_3 + R_4 = \boxed{12.1\Omega}$$

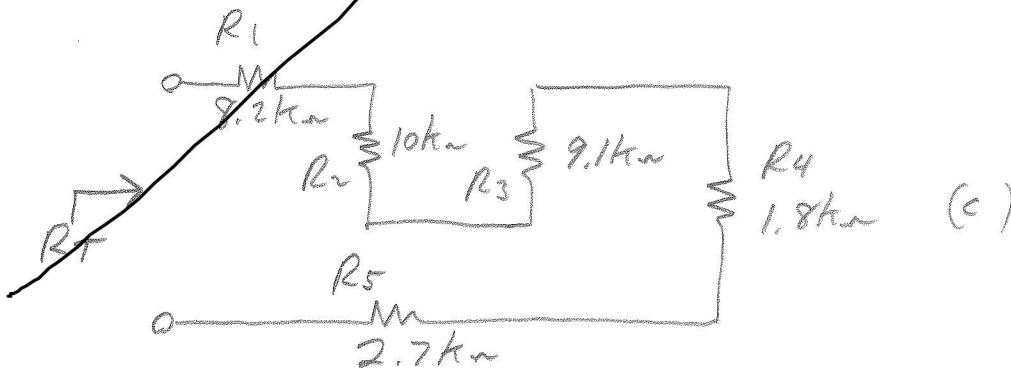


Chapter 5

3. a. $R_T = 0.1 \text{ k}\Omega + 0.39 \text{ k}\Omega + 1.2 \text{ k}\Omega + 6.8 \text{ k}\Omega = 8.49 \text{ k}\Omega$
- b. $R_T = 1.2 \text{ }\Omega + 2.7 \text{ }\Omega + 8.2 \text{ }\Omega = 12.1 \text{ }\Omega$
- c. $R_T = 1.2 \text{ }\Omega + 2.2 \text{ }\Omega + 3.3 \text{ }\Omega + 4.7 \text{ }\Omega = 11.4 \text{ }\Omega$

~~(5-3)~~


Find $R_{T1,2}$

5-5

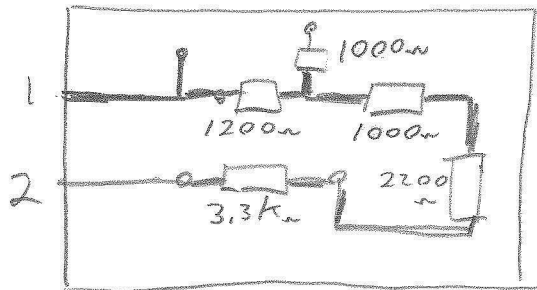

(a)
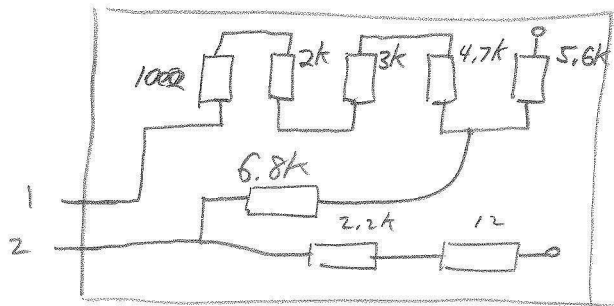
$$R_{T1,2} = 1200 + 1000 + 2200 + 3300 = \boxed{7700\Omega}$$




(b)


$$R_{T1,2} = 1000 + 2k + 3k + 4.7k + 17.5k = \boxed{17500\Omega}$$

~~5-6)~~

5-8

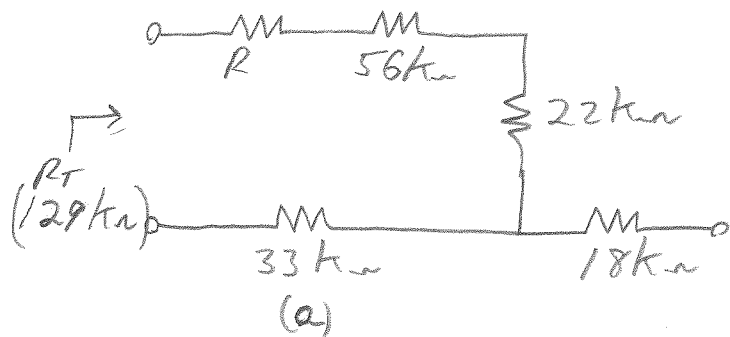

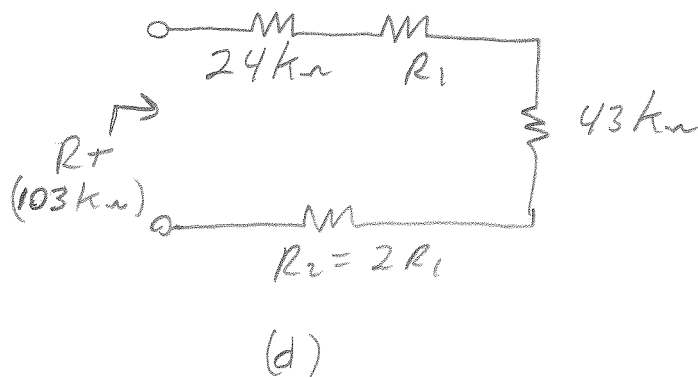
$$R_T = R + 56k + 22k + 33k$$
$$R_T = 129k$$
$$\therefore R = 18k\Omega$$



$$R_T = 24k + R_1 + 43k + 2R_1$$
$$R_T = 103k$$
$$\therefore 103k = 24k + 43k + 3R_1$$
$$R_1 = \frac{103k - 24k - 43k}{3}$$

$$R_1 = 12k\Omega$$
$$R_2 = 2R_1 = 24k\Omega$$

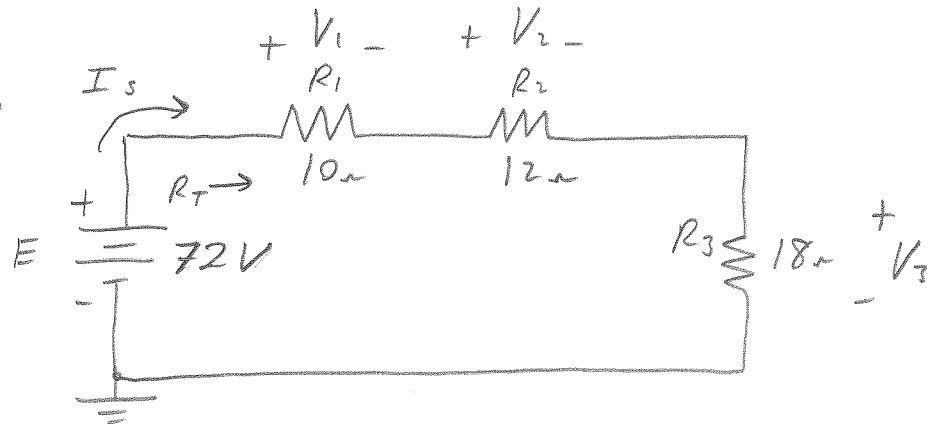~~(5-8)~~GIVEN :FIND : a) R_T

$$R_T = R_1 + R_2 + R_3 = \boxed{40\Omega}$$

b) I_s

$$I_s = \frac{E}{R_T} = \frac{72V}{40\Omega} = \boxed{1.8A}$$

c) V_1, V_2, V_3

$$V_1 = (I_s)(R_1) = (1.8A)(10\Omega) = \boxed{18V}$$

$$V_2 = (I_s)(R_2) = (1.8A)(12\Omega) = \boxed{21.6V}$$

$$V_3 = (I_s)(R_3) = (1.8A)(18\Omega) = \boxed{32.4V}$$


$$d) P_{source} = (E)(I_s) = (72V)(1.8A) = \boxed{129.6W}$$

$$e) P_{R_3} = (I_s)^2 R_3$$

$$= (1.8A)^2 (18\Omega) = \boxed{58.3W}$$

(5-13)

GIVEN :

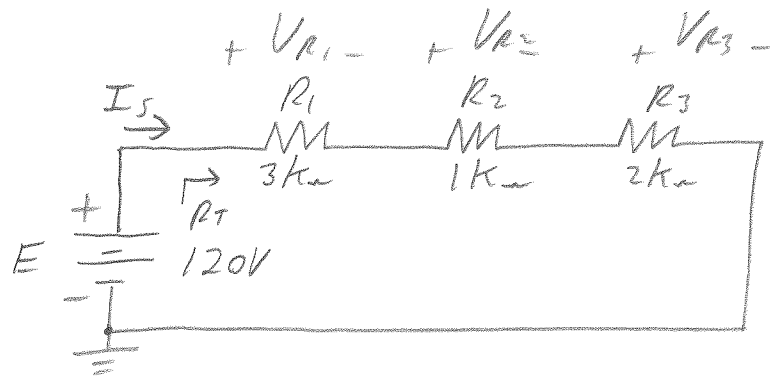FIND a) R_T , I_S , V_{R1} , V_{R2} , V_{R3}

$$R_T = R_1 + R_2 + R_3 = \boxed{6k\Omega}$$

$$I_S = \frac{E}{R_T} = \frac{120V}{6k\Omega} = \boxed{20mA}$$

$$V_{R1} = (I_S)(R_1) = \boxed{60V}$$

$$V_{R2} = (I_S)(R_2) = \boxed{20V}$$

$$V_{R3} = (I_S)(R_3) = \boxed{40V}$$

b) P_{R1} , P_{R2} , P_{R3}

$$P_{R1} = (I_S)^2 R_1 = \boxed{1.2W}$$

$$P_{R2} = (I_S)^2 R_2 = \boxed{400mW}$$

$$P_{R3} = (I_S)^2 R_3 = \boxed{800mW}$$

c) $P_{R1} + P_{R2} + P_{R3}$

$$P_T = \boxed{2.4W}$$

THE
SAMEd) P_{OELIVE}

$$P_{OELIVE} = (E)(I_S) = \boxed{2.4W}$$

e) COMPARE P_T -RESISTORS TO P_{OELIVE}

THE TOTAL POWER DELIVERED TO THE RESISTORS
IS EQUAL TO THE TOTAL POWER DELIVERED
BY THE SOURCE

~~(5-13)~~ CONTINUED

- (f) WHICH R RECEIVED THE MOST POWER?
Why?

R_1

$$P = I^2 R$$

$\downarrow R_1$ WAS LARGER THAN
 R_2 OR R_3

- (g) WHAT HAPPENED TO P_{RT} ?


DISSIPATED - FORM OF HEAT

- (h) FIND P_{MIN} -RATING FOR EACH R IF
THE CHOICES ARE $\frac{1}{2}W$, $1W$, $2W$, $5W$

$$R_1 \rightarrow 2W$$

$$R_2 \rightarrow \frac{1}{2}W$$

$$R_3 \rightarrow 1W$$

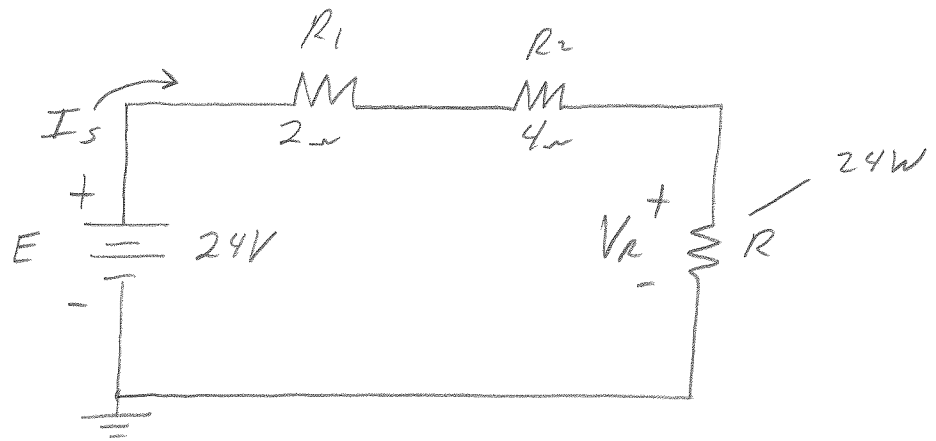~~(5-17)~~GIVEN:FIND: R

$$R_T = R_1 + R_2 + R = 6\Omega + R$$

$$I_s = \frac{E}{R_T} = \frac{24V}{R + 6\Omega} \quad (1)$$

$$P_R = (I_s)^2 R \rightarrow 24W = (I_s)^2 R \quad (2)$$

$$\text{Solve (2) for } R: R = \frac{24W}{(I_s)^2}$$

$$\text{into (1): } I_s = \frac{24V}{\frac{24W}{(I_s)^2} + 6\Omega} \quad (3)$$

$$\times \frac{I_s^2}{I_s^2}: I_s = \frac{24V (I_s^2)}{24W + 6\Omega (I_s^2)}$$

$$\text{Cross mult: } 24 I_s + 6 I_s^3 = 24 I_s^2$$

$$\text{OR } 6 I_s^3 - 24 I_s^2 + 24 I_s = 0$$

$$I_s = 0A \leftarrow \text{TRIVIAL SOLUTION}$$

$$2A \leftarrow \underline{\underline{I_s = 2A}}$$

$$2A$$

$$\text{Solve (2) for } R: R = \frac{P_R}{I_s^2} = \frac{24W}{(2A)^2} = \boxed{6\Omega}$$