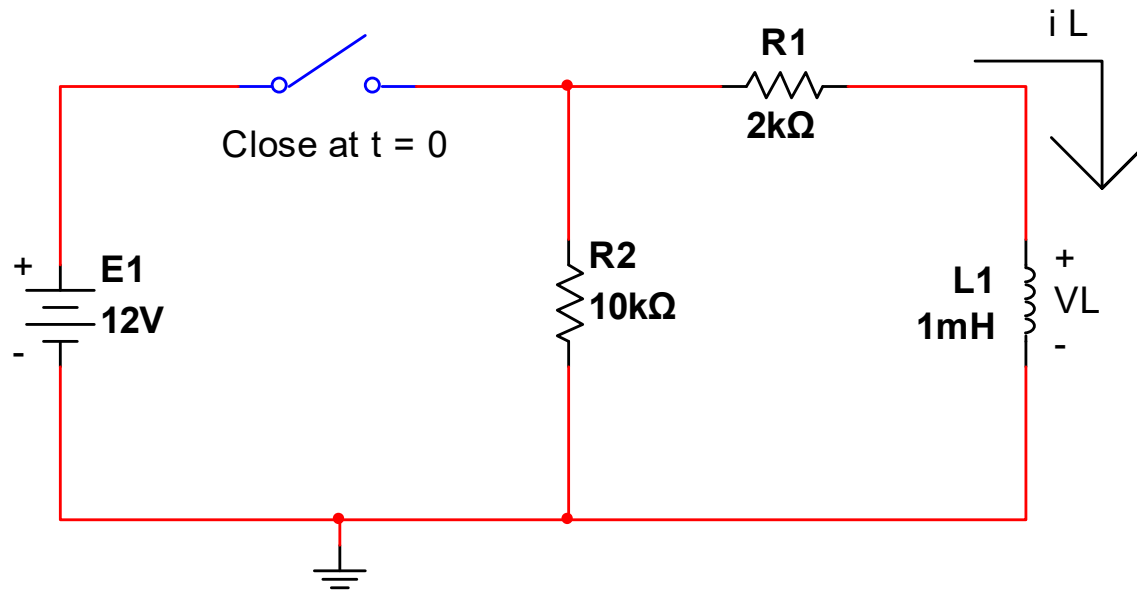


Electrical Engineering Technology

**Inductors – Decay Phase and
Series-Parallel Combinations**

Fall 2018


In Class Problem



Find

1. $v_L(t)$ & $i_L(t)$ for $t > 0$
2. $v_L(t)$ & $i_L(t)$ if the switch is opened at $t = 1\mu\text{sec}$

Inductors in Series

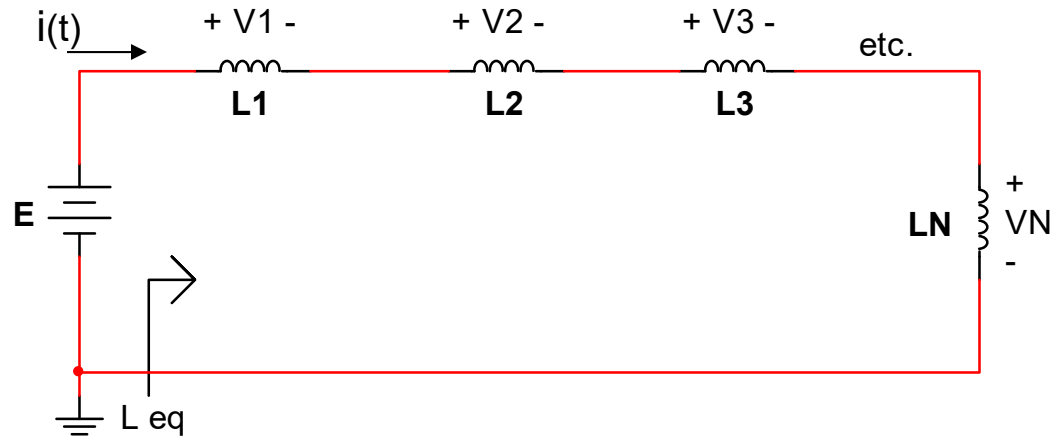


$$\text{KVL: } E = V_1 + V_2 + V_3 + \dots + V_N$$

$$\text{But, } V_1 = L_1 \frac{di}{dt}, V_2 = L_2 \frac{di}{dt}, \dots$$


$$\begin{aligned} \text{Therefore, } E &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt} \\ &= (L_1 + L_2 + L_3 + \dots + L_N) \frac{di}{dt} \end{aligned}$$

$$\text{Or } E = L_{EQ} \frac{di}{dt}$$
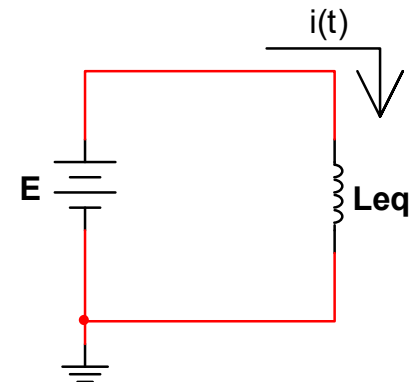
$$\text{Hence: } L_{EQ} = L_T = L_1 + L_2 + L_3 + \dots + L_N$$



Inductors in Parallel

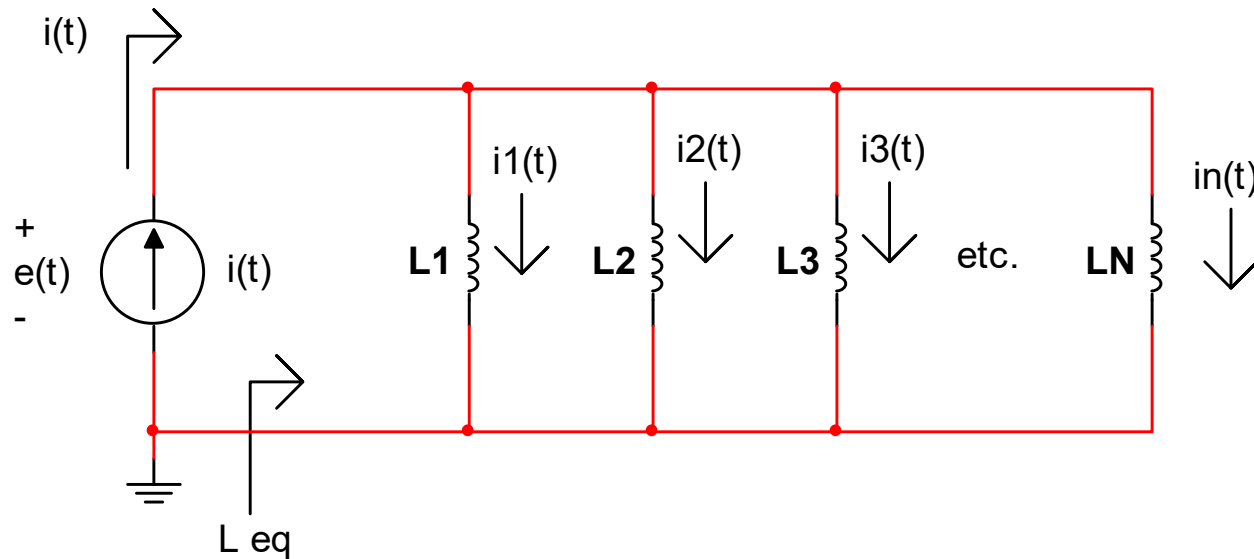

$$\text{KCL: } i(t) = i_1(t) + i_2(t) + i_3(t) + \dots + i_N(t)$$

$$\text{But, } v_N = L_N \frac{di_N}{dt}$$

$$\text{So } \frac{v_N}{L_N} = \frac{di_N}{dt}$$

$$\text{And } i_N(t) = \int \frac{v_N}{L_N} dt = \frac{1}{L_N} \int v_N dt$$

Inductors in Parallel

Into our KCL equation yields:

$$i(t) = \frac{1}{L_1} \int v_1(t) dt + \frac{1}{L_2} \int v_2(t) dt + \dots + \frac{1}{L_N} \int v_N(t) dt$$

But, $e(t) = v_1(t) = v_2(t) = \dots = v_N(t)$



$$\text{So } i(t) = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \int e(t) dt$$

$$\text{Hence: } i(t) = \frac{1}{L_{EQ}} \int e(t) dt$$

Where $L_{EQ} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$

$$i_N(t) = \int \frac{v_N}{L_N} dt = \frac{1}{L_N} \int v_N dt$$

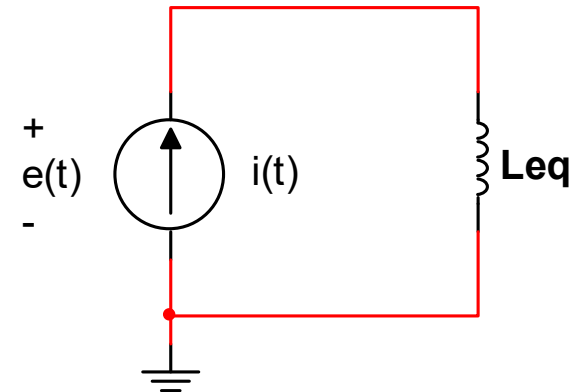
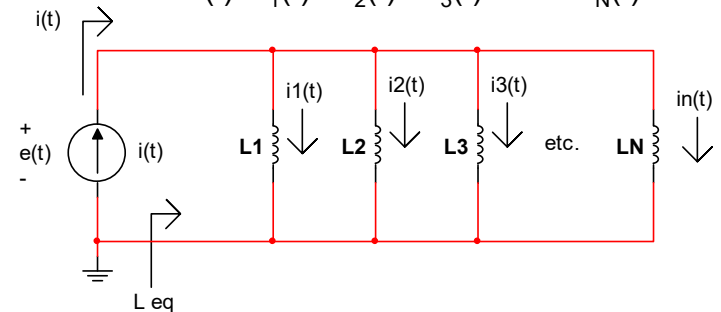
$$\text{KCL: } i(t) = i_1(t) + i_2(t) + i_3(t) + \dots + i_N(t)$$



In Class Problem

Find L_T

a.

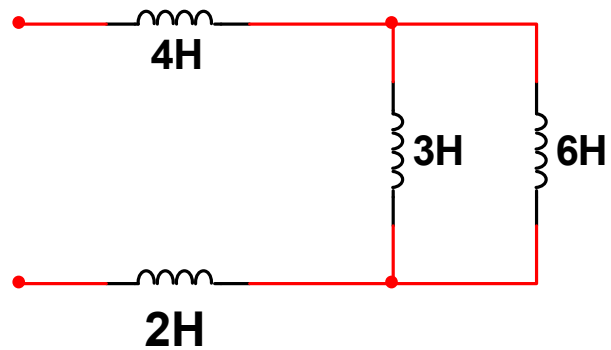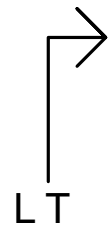

b.

