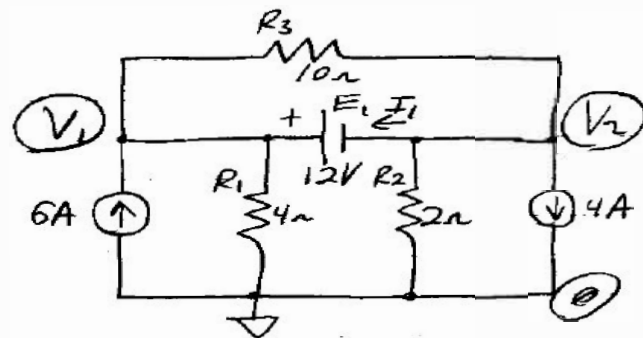


IF A VOLTAGE SOURCE IS PRESENT :

- 1 - CONVERT IT & SERIES "R" TO A PRACTICAL CURRENT SOURCE
- 2 - CHOOSE ONE END OF THE ^{VOLTAGE} SOURCE AS THE REF. NODE
- 3 - SUPERNODE APPROACH

(EXAMPLE 8.22)

Example 8.24 in 13th ed



(FIND THE NODE VOLTAGES)

"MODIFIED" SUPERNODE APPROACH


$$\begin{aligned} \textcircled{V_1} : 6 + I_1 &= \frac{V_1 - V_2}{R_3} + \frac{V_1}{R_1} \\ 6 + I_1 &= \frac{V_1}{10} - \frac{V_2}{10} + \frac{V_1}{4} \Rightarrow 6 = 0.35V_1 - 0.1V_2 - I_1 \quad (1) \end{aligned}$$

$$\begin{aligned} \textcircled{V_2} : 0 &= \frac{V_2 - V_1}{R_3} + I_1 + \frac{V_2}{R_2} + 4 \Rightarrow 0 = \frac{V_2}{10} - \frac{V_1}{10} + I_1 + \frac{V_2}{2} + 4 \\ -4 &= -0.1V_1 + 0.6V_2 + I_1 \quad (2) \end{aligned}$$

TWO EQUATIONS, THREE UNKNOWN^s! WE NEED ANOTHER INDEPENDENT EQUATION :


ANOTHER NODAL ANALYSIS PROBLEM (ICP)

(EXAMPLE)

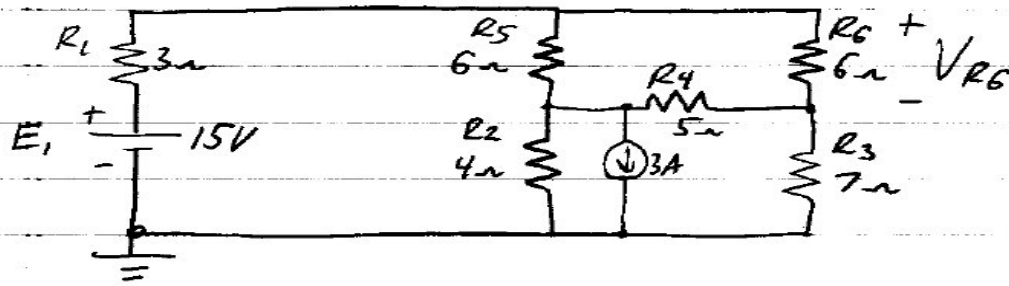

USE NODAL ANALYSIS TO FIND ALL NODE VOLTAGES & V_{R6} .

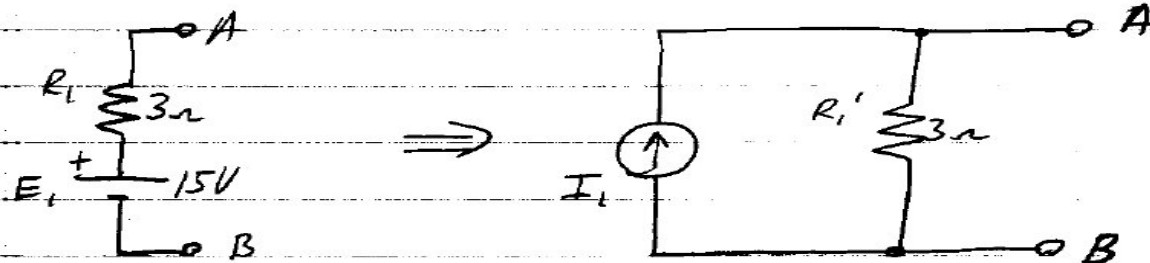
ONE APPROACH
 (1) → CONVERT E_1, R_1 TO I_1, R_1' (SOURCE TRANSFORMATION)



$$I_1 = \frac{E_1}{R_1} = \frac{15V}{3\Omega} = \underline{\underline{5A}}$$

REDRAW THE CIRCUIT :

(2) ASSIGN NODE LABELS

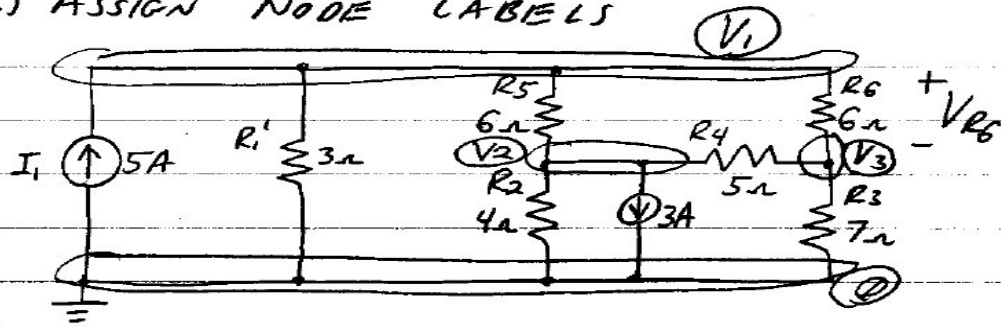

(3) KCL AT EACH NODE

$$\sum I_{\text{ENTERING}} = \sum I_{\text{LEAVING}}$$

For V_1 :

For V_2 :

For V_3 :

Solve (1) \rightarrow (3)