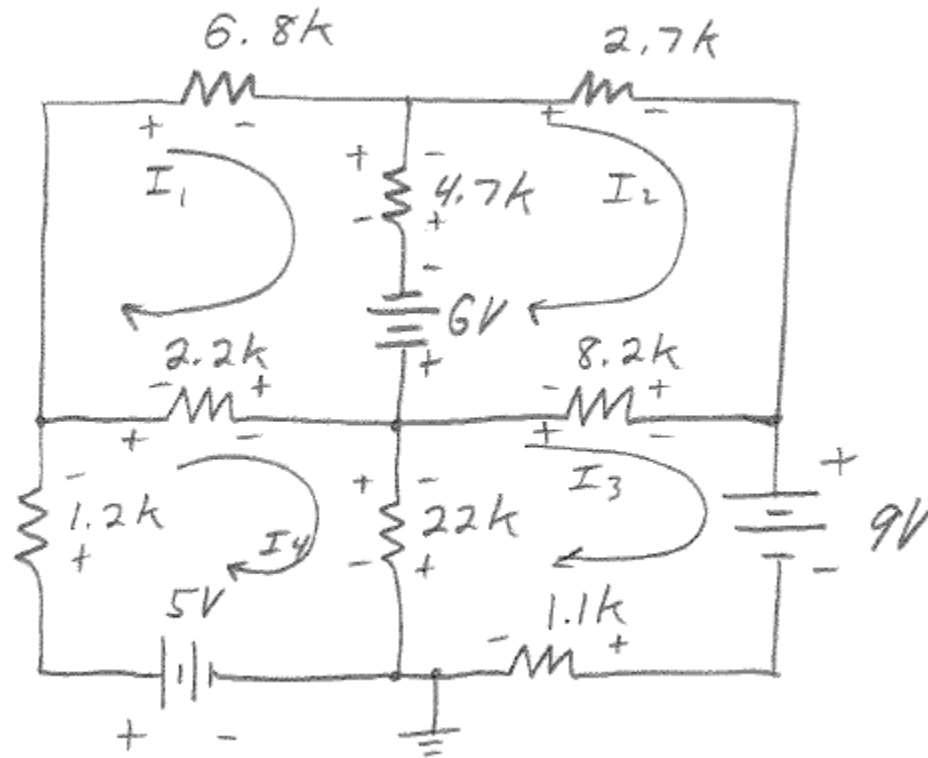


Electrical Engineering Technology

Mesh Analysis Breakout (4x4 system)

Fall 2018 (2181)


Breakout Problem #1



Find:

- The loop (MESH) currents as drawn

Breakout Problem #1

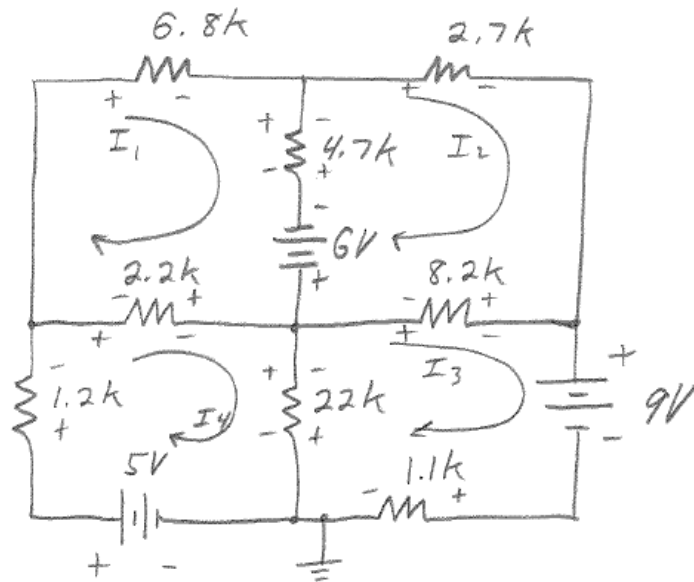

$$I_1 \text{ loop: } -6.8kI_1 - 4.7kI_1 + 4.7kI_2 + 6 - 2.2kI_1 + 2.2kI_4 = 0$$

$$-13.7kI_1 + 4.7kI_2 + 0I_3 + 2.2kI_4 = -6 \quad (1)$$

$$I_2 \text{ loop: } -6 - 4.7kI_2 + 4.7kI_1 - 2.7kI_2 - 8.2kI_2 + 8.2kI_3 = 0$$

$$4.7kI_1 - 15.6kI_2 + 8.2kI_3 + 0I_4 = 6 \quad (2)$$

$$I_3 \text{ loop: } -22kI_3 + 22kI_4 - 8.2kI_3 + 8.2kI_2 - 9 - 1.1kI_3 = 0$$

$$0I_1 + 8.2kI_2 - 31.3kI_3 + 22kI_4 = 9 \quad (3)$$

$$I_4 \text{ loop: } -1.2kI_4 - 2.2kI_4 + 2.2kI_1 - 22kI_4 + 22kI_3 + 5 = 0$$

$$2.2kI_1 + 0I_2 + 22kI_3 - 25.4kI_4 = -5 \quad (4)$$

Breakout Problem #1

$$-13.7k I_1 + 4.7k I_2 + 0 I_3 + 2.2k I_4 = -6 \quad (1)$$

$$4.7k I_1 - 15.6k I_2 + 8.2k I_3 + 0 I_4 = 6 \quad (2)$$

$$0 I_1 + 8.2k I_2 - 31.3k I_3 + 22k I_4 = 9 \quad (3)$$

$$2.2k I_1 + 0 I_2 + 22k I_3 - 25.4k I_4 = -5 \quad (4)$$

Solving Yields :

$$\begin{array}{l} I_1 = 32.11 \mu A \\ I_2 = \\ I_3 = \\ I_4 = \end{array}$$

Your AC Circuits
calculator will handle
this with ease

But how using the Sharp EL-516?

Method of Determinants (Appendix B and your calculator manual)

Breakout Problem #1

EXPANDING FROM APPENDIX B TO SOLVE A 4x4

$$\begin{aligned} a_1 w + b_1 x + c_1 y + d_1 z &= e_1 \\ a_2 w + b_2 x + c_2 y + d_2 z &= e_2 \\ a_3 w + b_3 x + c_3 y + d_3 z &= e_3 \\ a_4 w + b_4 x + c_4 y + d_4 z &= e_4 \end{aligned}$$

VARIABLES
 w, x, y, z

WHERE

$$D = \begin{vmatrix} a_1 & b_1 & c_1 & d_1 \\ a_2 & b_2 & c_2 & d_2 \\ a_3 & b_3 & c_3 & d_3 \\ a_4 & b_4 & c_4 & d_4 \end{vmatrix}$$

$$w = \begin{vmatrix} e_1 & b_1 & c_1 & d_1 \\ e_2 & b_2 & c_2 & d_2 \\ e_3 & b_3 & c_3 & d_3 \\ e_4 & b_4 & c_4 & d_4 \end{vmatrix}$$

D

$$x = \begin{vmatrix} a_1 & e_1 & c_1 & d_1 \\ a_2 & e_2 & c_2 & d_2 \\ a_3 & e_3 & c_3 & d_3 \\ a_4 & e_4 & c_4 & d_4 \end{vmatrix}$$

D

- Column 1 is the vector e_1, e_2, e_3, e_4
- The remaining columns are the variable coefficients from the system of equations

- Column 2 is the vector e_1, e_2, e_3, e_4
- The remaining columns are the variable coefficients from the system of equations

And so on for variables y and z ...

Breakout Problem #1

$$-13.7k I_1 + 4.7k I_2 + 0 I_3 + 2.2k I_4 = -6 \quad (1)$$

$$4.7k I_1 - 15.6k I_2 + 8.2k I_3 + 0 I_4 = 6 \quad (2)$$

$$0 I_1 + 8.2k I_2 - 31.3k I_3 + 22k I_4 = 9 \quad (3)$$

$$2.2k I_1 + 0 I_2 + 22k I_3 - 25.4k I_4 = -5 \quad (4)$$

WHERE

$$D = \begin{vmatrix} a_1 & b_1 & c_1 & d_1 \\ a_2 & b_2 & c_2 & d_2 \\ a_3 & b_3 & c_3 & d_3 \\ a_4 & b_4 & c_4 & d_4 \end{vmatrix}$$

Becomes ->

$$D = \begin{vmatrix} -13,700 & 4700 & 0 & 2,200 \\ 4700 & -15,600 & 8200 & 0 \\ 0 & 8,200 & -31,300 & 22,000 \\ 2200 & 0 & 22,000 & -25,400 \end{vmatrix}$$

$$W = \begin{vmatrix} e_1 & b_1 & c_1 & d_1 \\ e_2 & b_2 & c_2 & d_2 \\ e_3 & b_3 & c_3 & d_3 \\ e_4 & b_4 & c_4 & d_4 \end{vmatrix}$$

D

Becomes ->

$$I_1 = \begin{vmatrix} -6 & 4700 & 0 & 2,200 \\ 6 & -15,600 & 8200 & 0 \\ 9 & 8,200 & -31,300 & 22,000 \\ -5 & 0 & 22,000 & -25,400 \end{vmatrix}$$

D

Breakout Problem #1

Solving D on the EL-516T:

$$D = \begin{vmatrix} -13,700 & 4700 & 0 & 2,200 \\ 4700 & -15,600 & 8200 & 0 \\ 0 & 8,200 & -31,300 & 22,000 \\ 2200 & 0 & 22,000 & -25,400 \end{vmatrix}$$

MODE 5 (MATRIX)
 MATH 1 (EDIT)
 4 4 (4x4)
 ENTER
 ENTER COEFFICIENTS
 ON/C
 MATH 3 0 (STORES IN A)
 ON/C
 MATH 4 (DET)
 MATH 0 0 (RECALLS A) ENTER

Yields: D = 30.4341E15

- See the posted Sharp EL-516 manual and accompanying examples for previous versions of the EL-516

Following the same procedure for the numerator of:

$$I_1 = \begin{vmatrix} -6 & 4700 & 0 & 2,200 \\ 6 & -15,600 & 8200 & 0 \\ 9 & 8,200 & -31,300 & 22,000 \\ -5 & 0 & 22,000 & -25,400 \end{vmatrix}$$

D

Yields:

$$I_1 = \frac{977.2880E9}{30.4341E15}$$

Or $I_1 = 32.11 \mu A$

- Find I_2 , I_3 and I_4 using the same method... i.e. I_2 is variable x and so on
- Find I_2 , I_3 and I_4 by substituting I_1 into the original equations and solving the remaining 3x3 system