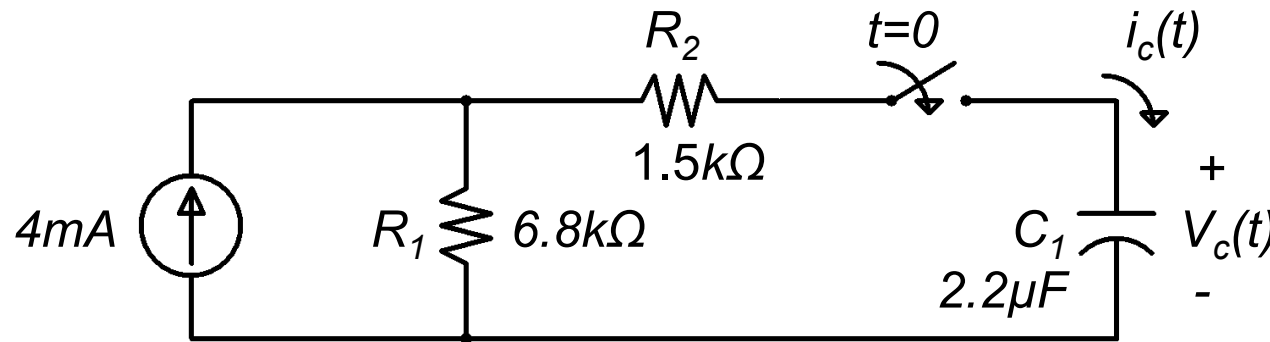


Initial Values


- (Example) a) Find $V_c(t)$ & $i_c(t)$ for $t > 0$
b) Sketch $V_c(t)$ & $i_c(t)$



$V_c(t) = 2V$
@ $t = 0^-$ (Initial Charge)


What's our first step??

Find V_{TH} & R_{TH} for $t > 0$:

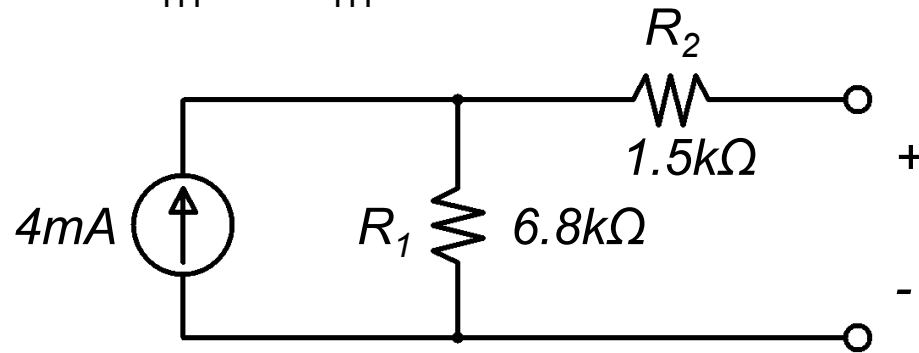

$$V_{TH} = (4mA)(6.8k\Omega) = \underline{27.2V}$$
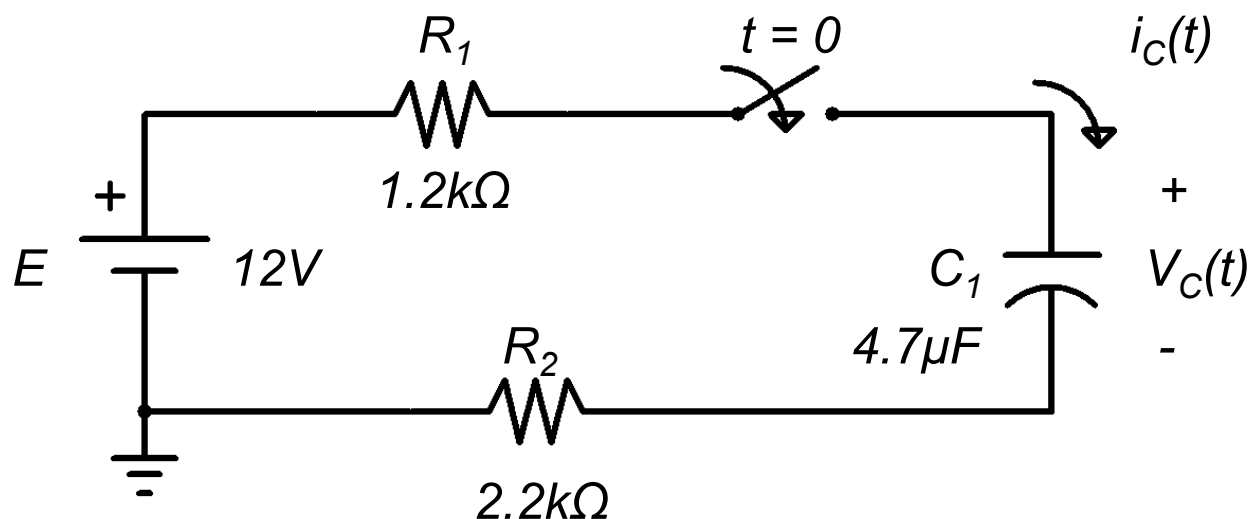
$$R_{TH} = R_1 + R_2 = \underline{8.3k\Omega}$$



Given: $V_C(0) = 4V$, initial charge

(a) Find $V_C(t)$, $t \geq 0$

(b) $i_C(t)$, $t > 0$

(c) Sketch $V_C(t)$ & $i_C(t)$


$$(b) \quad i_C(t) = i_{Cmax} \cdot e^{-t/\tau} \quad R_{TH}$$

$$\tau = (R_1 + R_2)C_1$$

$$\tau = (3.4k\Omega)(4.7\mu F) = 15.98ms$$

$$i_{Cmax} = \frac{V_{TH} - V_C(0)}{3.4k\Omega} = \frac{12V - 4V}{3.4k\Omega} = 2.353mA$$
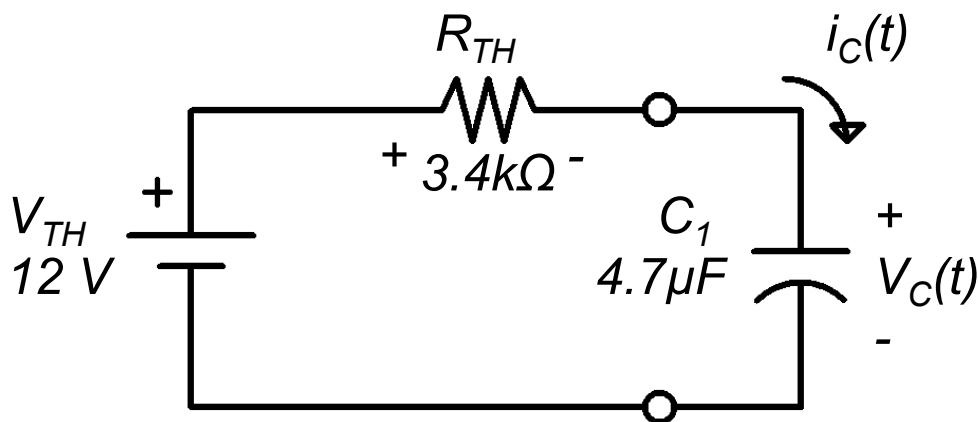
$$\therefore i_C(t) = 2.353 \cdot 10^{-3} \cdot e^{-t/15.98 \cdot 10^{-3}} A, t > 0$$



$$(a) \quad KVL : V_{TH} - i_C(t)R_{TH} - V_C(t) = 0$$

$$KVL: V_{TH} - i_C(t)R_{TH} - V_C(t) = 0$$

$$\text{or } V_c(t) = 12 - \left(2.353 * 10^{-3} * e^{-t/15.98*10^{-3}} \right) (3.4 * 10^3)$$

$$V_c(t) = 12 - 8 * e^{-t/15.98*10^{-3}}$$

$$V, t \geq 0$$

