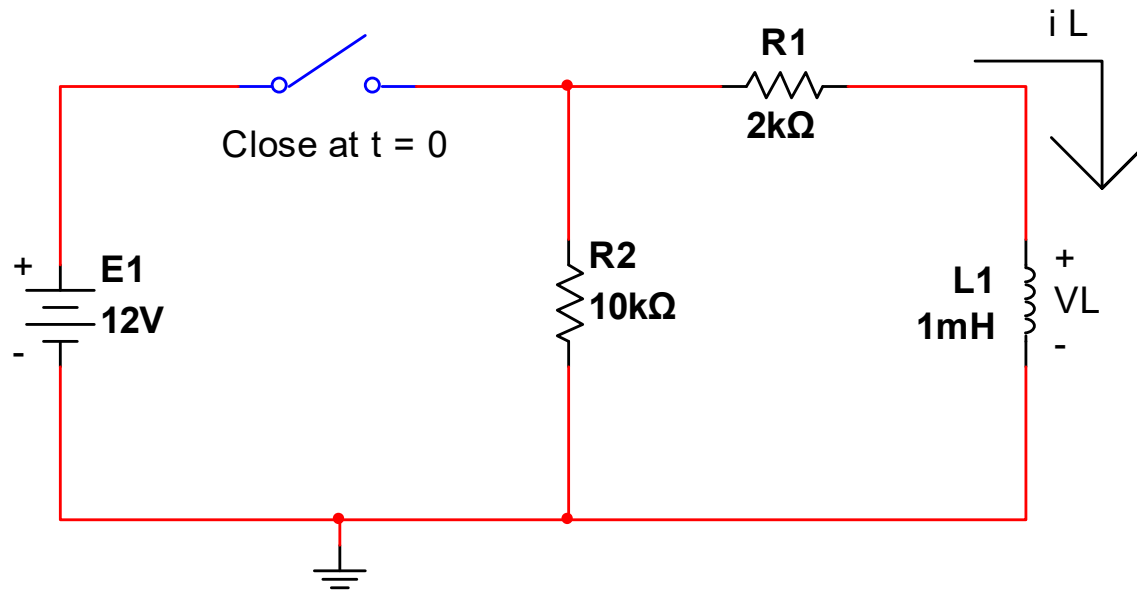


In Class Problem



Find

1. $v_L(t)$ & $i_L(t)$ for $t > 0$
2. $v_L(t)$ & $i_L(t)$ if the switch is opened at $t = 1\mu\text{sec}$

In Class Problem

1. $v_L(t)$ & $i_L(t)$ for $t > 0$

- **Storage Phase**

$$\tau = \frac{L}{R} = \frac{1mH}{2k\Omega} = 500 \text{ ns}$$

$$i_L \text{ Max} = 12V/2k\Omega$$


$$i_{L_1}(t) = \frac{E_1}{R_1}(1 - e^{-t/\tau})A, t \geq 0$$

$$i_{L_1}(t) = 6 \cdot 10^{-3}(1 - e^{-t/500 \text{ ns}})A$$

$$v_{L_1}(t) = E_1 - i_{L_1}(t) \cdot R_1$$


$$v_{L_1}(t) = 12V - 12(1 - e^{-t/500 \text{ ns}})V$$
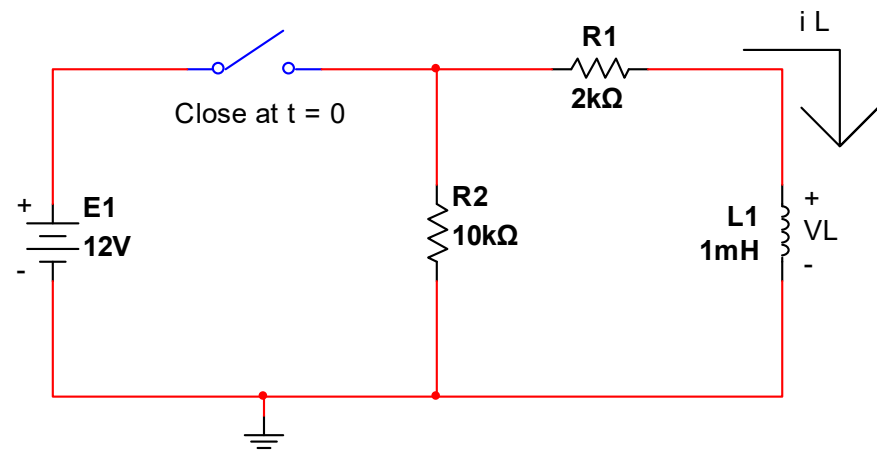
$$v_{L_1}(t) = 12e^{-t/500 \text{ ns}}V$$



In Class Problem

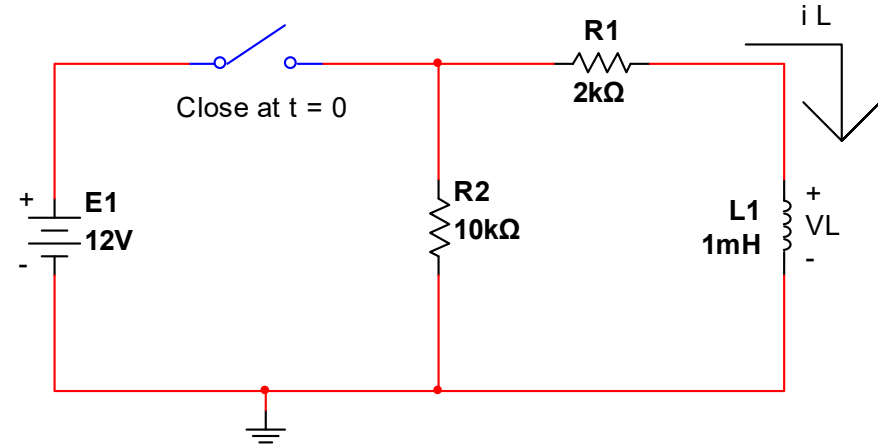2. $v_L(t)$ & $i_L(t)$ if the switch is opened at $t = 1\mu\text{sec}$ (this is less than 5τ)
 - **Decay Phase**



$$i_{L_1}(1\mu s) = 6 \cdot 10^{-3} (1 - e^{-1\mu s / 500 \text{ ns}}) \text{ A} = 5.188 \text{ mA}$$

$$\tau_{\text{decay}} = \frac{L}{R_{TH}} = \frac{1 \text{ mH}}{10 \text{ k}\Omega + 2 \text{ k}\Omega} = 83.33 \text{ ns}$$

Starting current for decay phase



$$i_{L_1}(t) = 5.188 \cdot 10^{-3} e^{-t/83.33 \text{ ns}} \text{ A}$$

$$v_{L_1}(t) = -i_{L_1}(t)(R_1 + R_2) = -62.26 e^{-t/83.33 \text{ ns}} \text{ V}$$



In Class Problem

Find L_T

a.

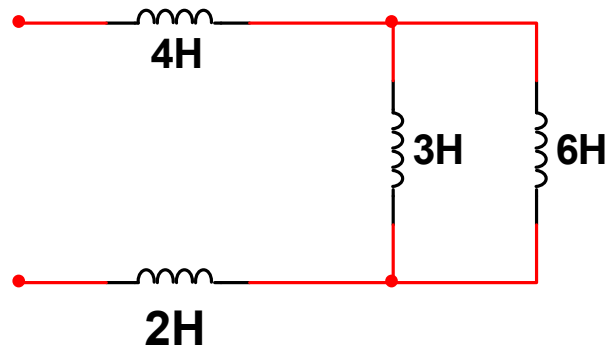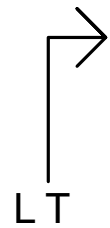


b.

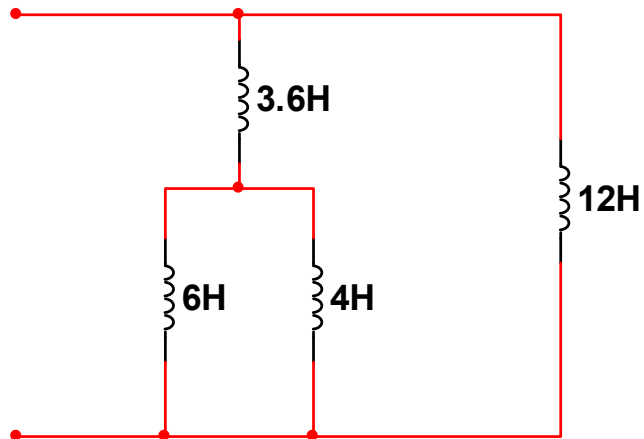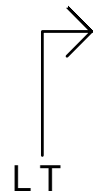

In Class Problem


Find L_T

a.

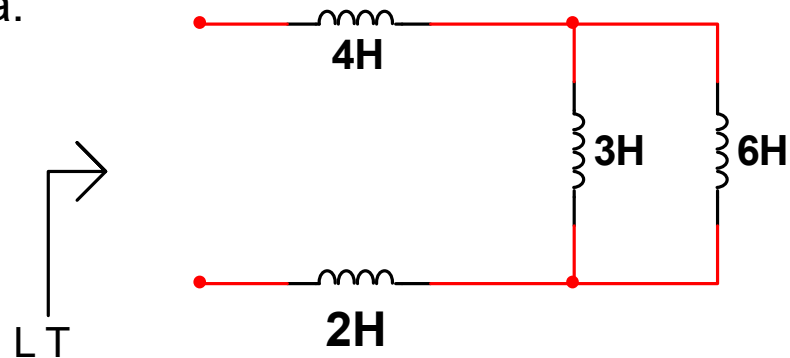

$$L_T = \frac{1}{\frac{1}{3H} + \frac{1}{6H}} + 4H + 2H = 8H$$

b.

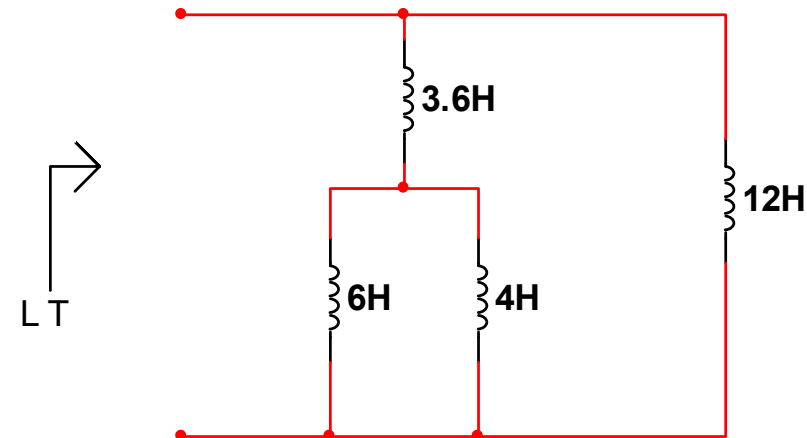

$$\begin{aligned} 6H // 4H &= 2.4H \\ 2.4H + 3.6H &= 6H \\ L_T &= 6H // 12H = 4H \end{aligned}$$