


# Today's Material

- Breakout #1 and #2
  - Review (Chapter 5)
- Parallel Resistors
  - Introduction and examples
  - Breakout #3
- Kirchhoff's Current Law (KCL)
  - Introduction
  - Examples

## Breakout #1
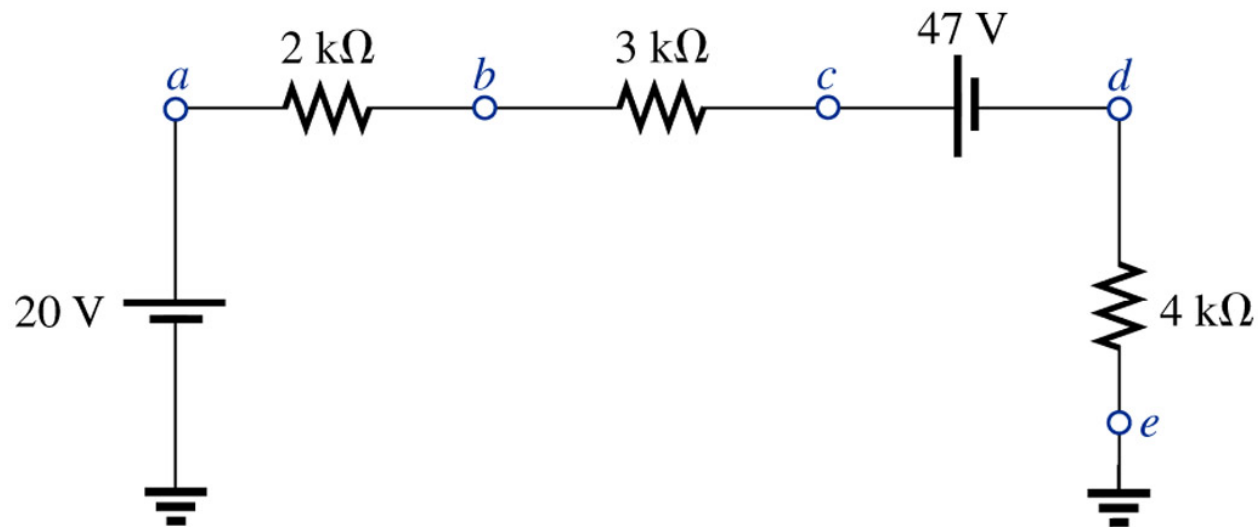
### ■ Find


- ☐ The magnitude and direction of current flow
- ☐  $V_b$ ,  $V_c$ ,  $V_d$
- ☐  $V_{ab}$ ,  $V_{cd}$ ,  $V_{de}$



## Breakout #2


### ■ Find

□  $V_0$ ,  $V_2$ ,  $V_{12}$ ,  $I_i$

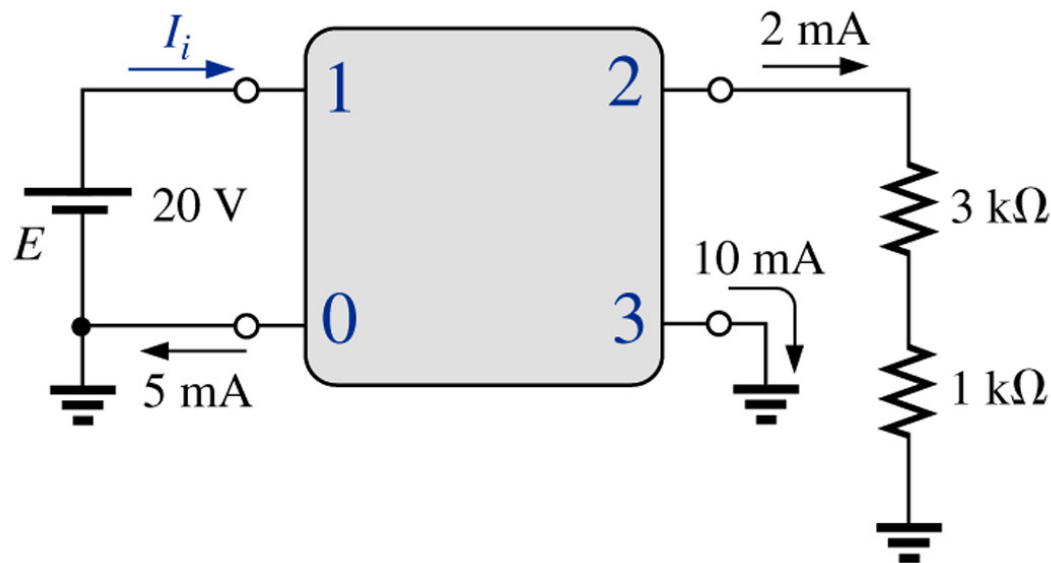
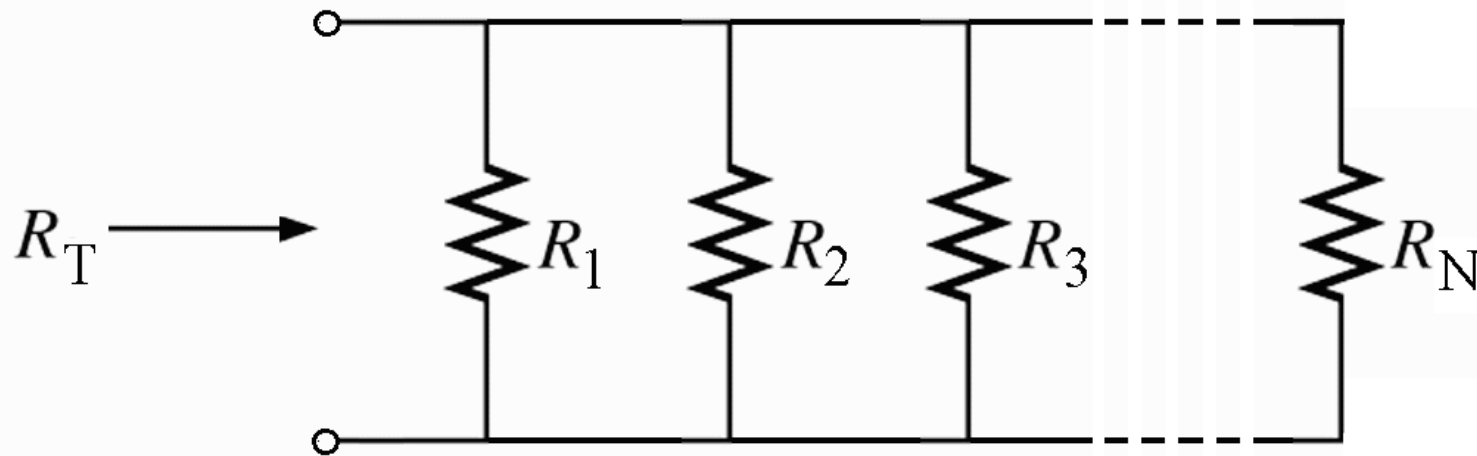
## Parallel Resistors


The total resistance of a parallel configuration is the reciprocal of the sum of the reciprocals of all the individual resistor values.



$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}}$$
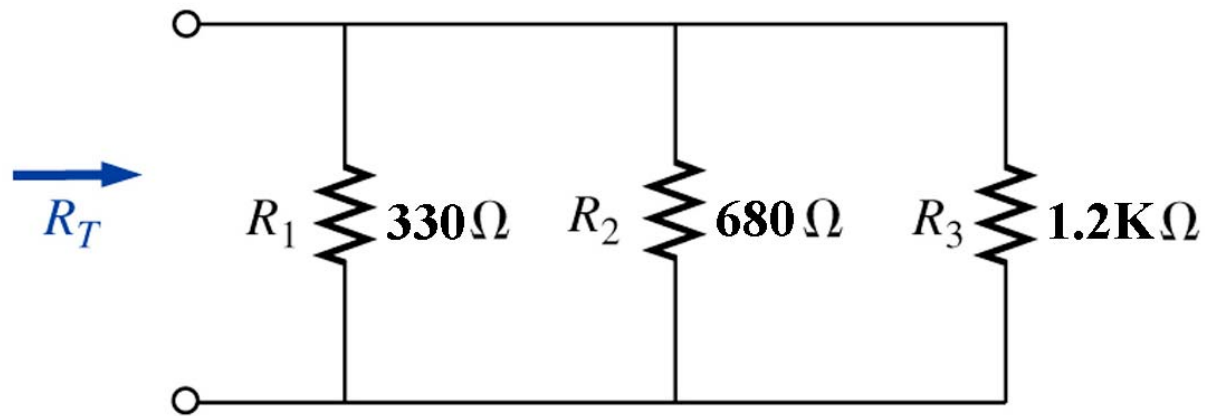
## Example – Parallel Resistors




Find  $R_T$  for the parallel circuit shown below...



$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{330\Omega} + \frac{1}{680\Omega} + \frac{1}{1.2\text{K}\Omega}}$$


$$R_T = 187.47\Omega$$

## Example – Parallel Components

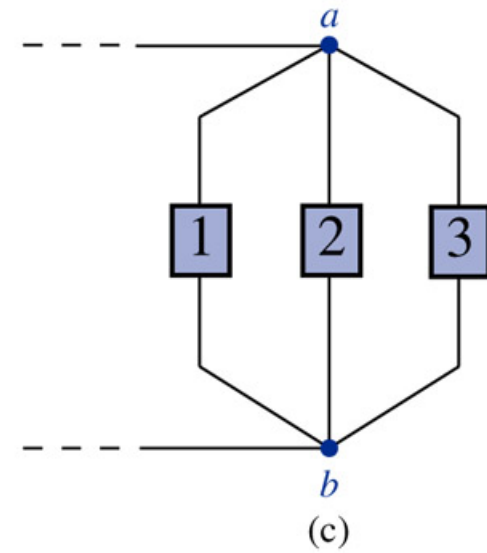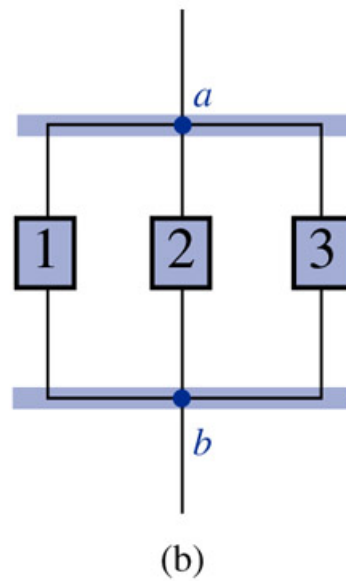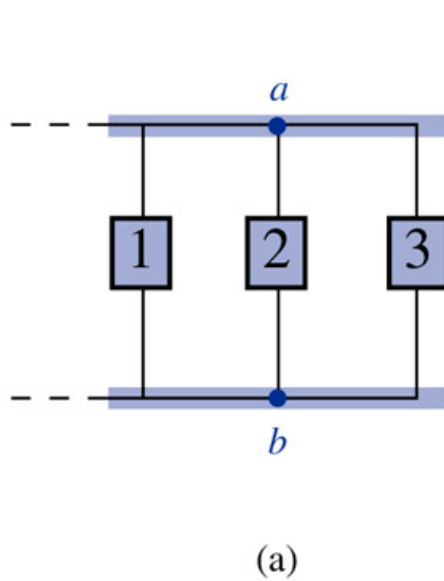


# Which Elements are in Parallel? Series?

(1 and 2 in parallel) in series with 3

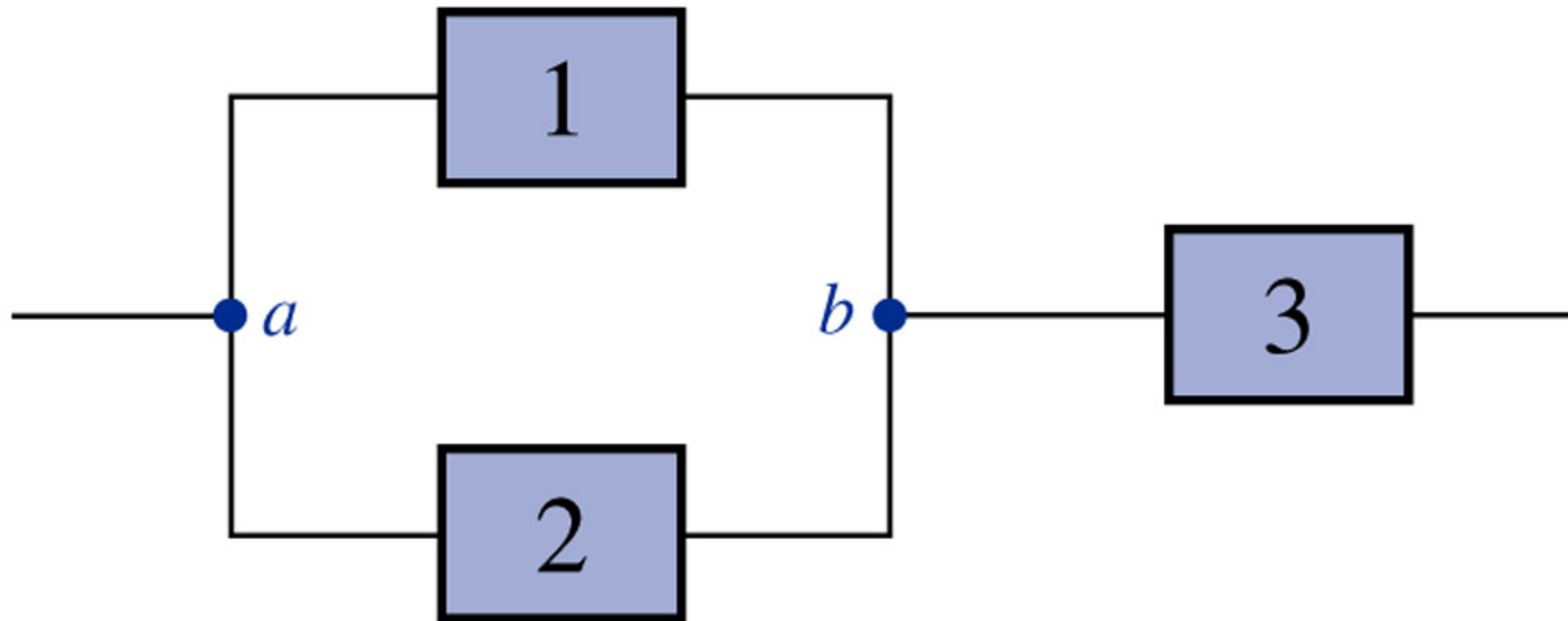


1 and 2 in parallel
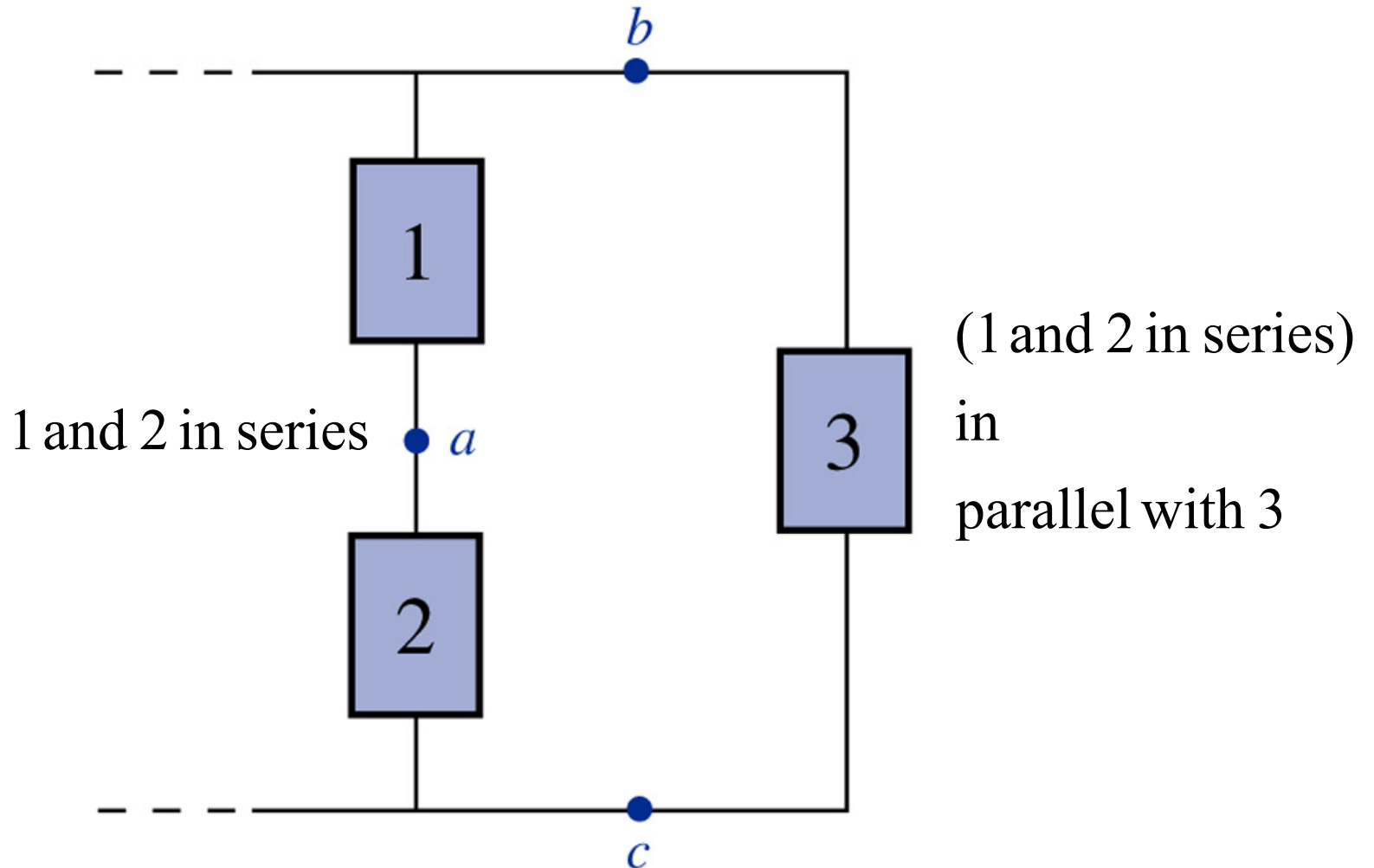
## Which Elements are in Parallel? Series?






# Conductance in Parallel

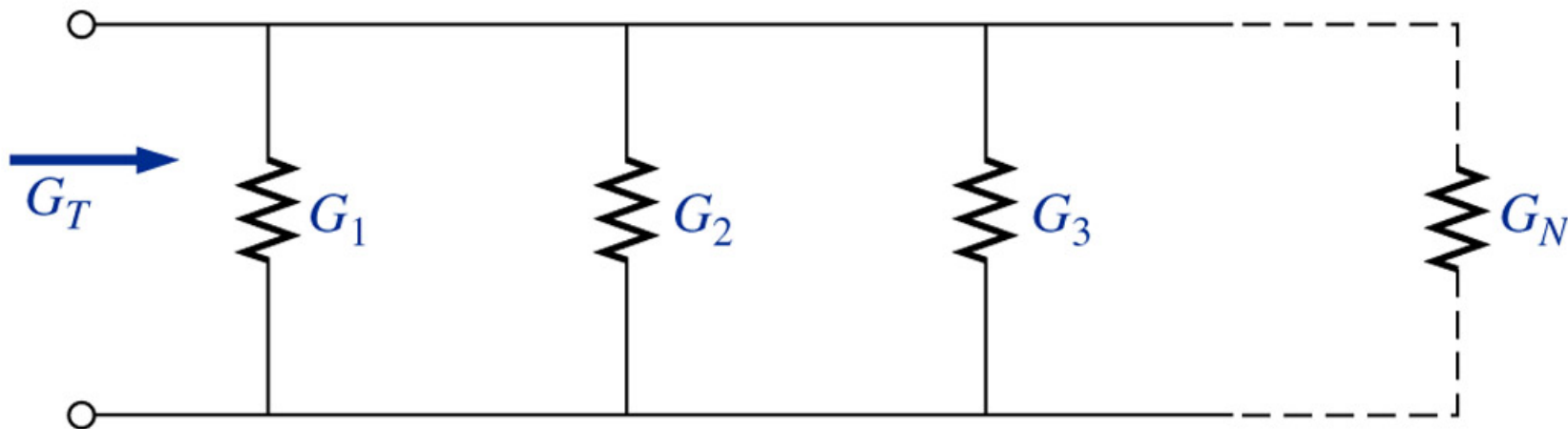

$$G_T = G_1 + G_2 + G_3 + \dots + G_N$$

## Conductance in Parallel - Example

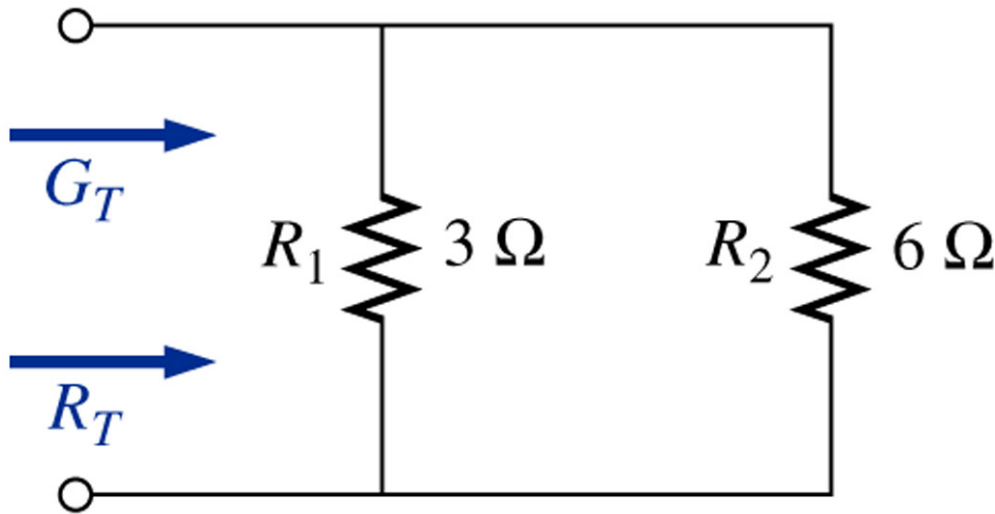

$$G_1 = \frac{1}{3\ \Omega} = 333.33\ \text{mS}$$

$$G_2 = \frac{1}{6\ \Omega} = 166.67\ \text{mS}$$

$$G_T = G_1 + G_2 = 0.5\ \text{S}$$



$$R_T = \frac{1}{G_T} = 2\ \Omega$$

$$\text{or, use : } R_T = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{18\ \Omega^2}{9\ \Omega} = 2\ \Omega$$

## Breakout #3


### ■ Find

□  $R_T$  and  $G_T$  for each circuit

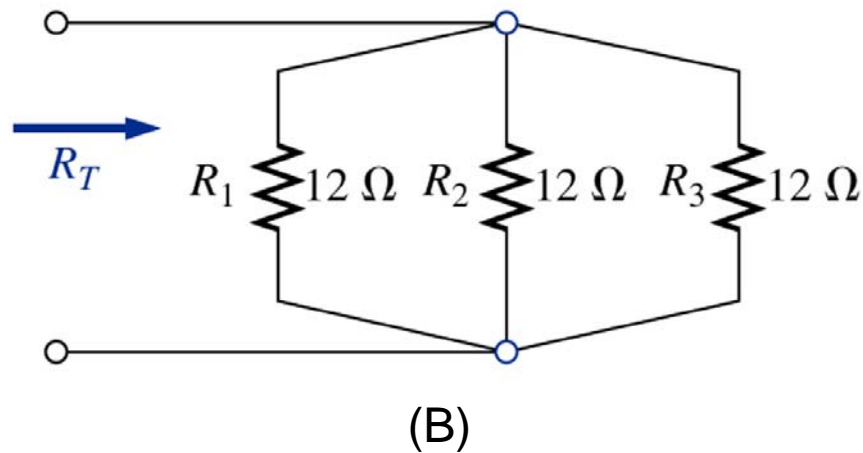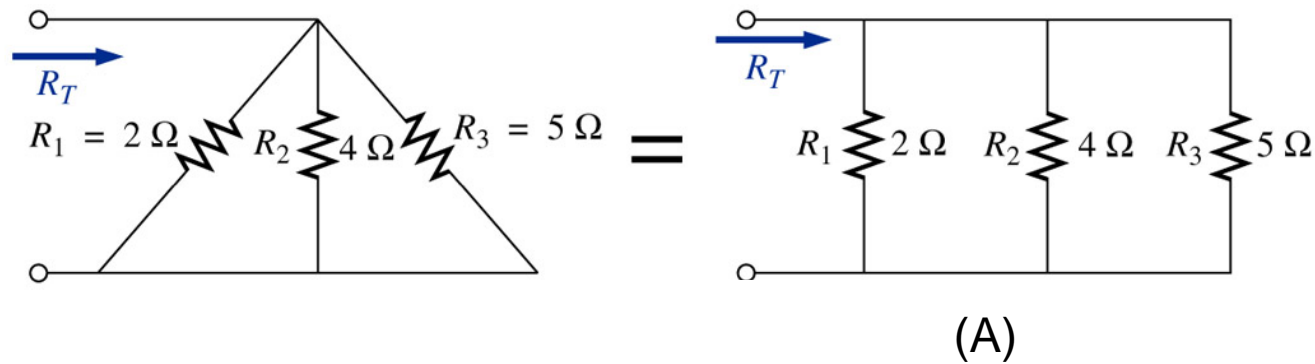
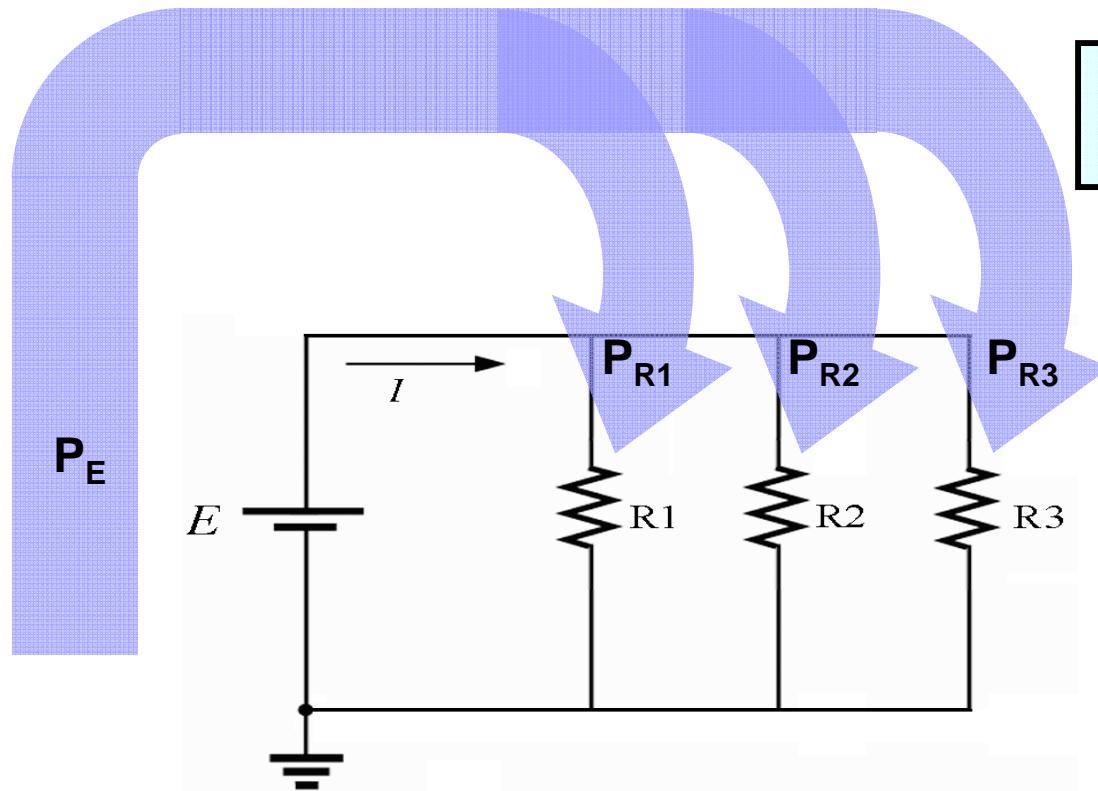
## Power in a Parallel Circuit (Review)


The total power delivered by the voltage source must equal the total power absorbed by the resistive elements.



$$P_E = P_{R1} + P_{R2} + P_{R3}$$
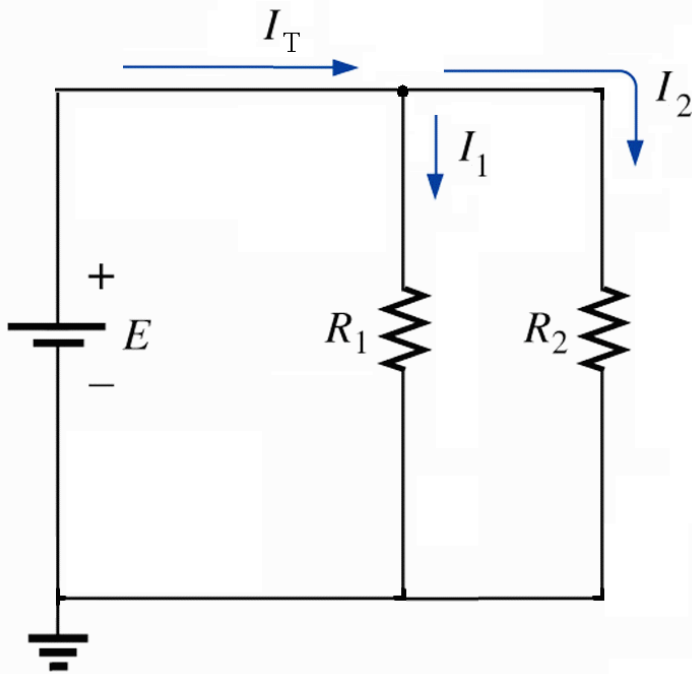
## Kirchhoff's Current Law

The algebraic sum of the current entering and leaving a node is zero.




$$I_T - I_1 - I_2 = 0$$

$$I_T = I_1 + I_2$$

$$\sum_{\text{C}} I_{\text{IN}} = \sum_{\text{C}} I_{\text{OUT}}$$

# Kirchhoff's Current Law

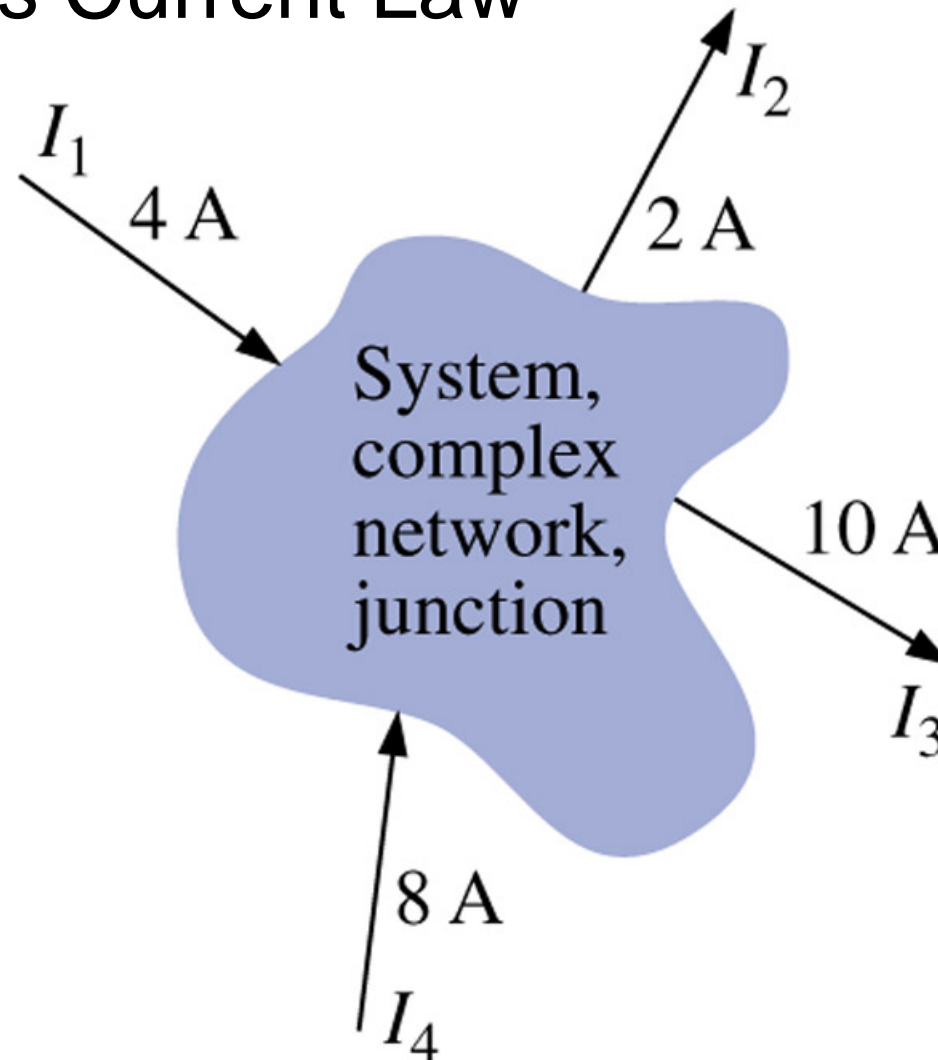

# Kirchhoff's Current Law

