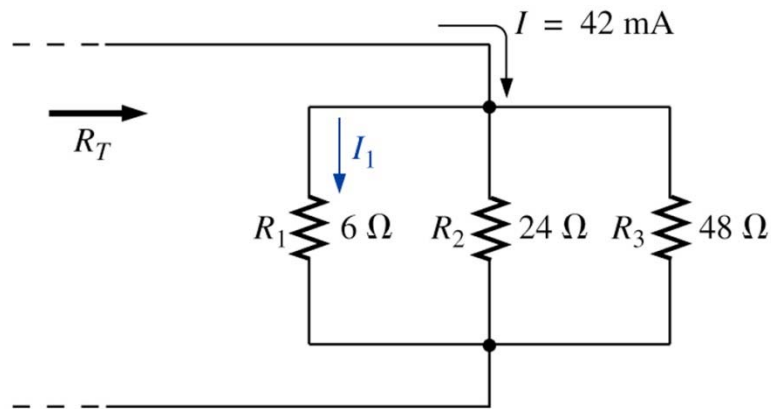


Breakout #1

- Find R_T , I_1 , and P_{R3}



$$I_1 = I_T \frac{R_T}{R_1}$$

$$I_1 = 42 \text{ mA} \frac{4.36 \Omega}{6 \Omega} = 30.55 \text{ mA}$$

$$P_{R3} = \frac{V_{R3}^2}{R_3}$$

$$V_{R3} = 42 \text{ mA} \cdot 4.36 \Omega = 183.3 \text{ mV}$$


$$\therefore P_{R3} = \frac{(183.3 \text{ mV})^2}{48 \Omega} = 699.8 \mu\text{W}$$

$$R_T = \frac{1}{\frac{1}{6 \Omega} + \frac{1}{24 \Omega} + \frac{1}{48 \Omega}}$$

$$= 4.36 \Omega$$

Breakout #2

- Find V_{ab} and V_{cd}

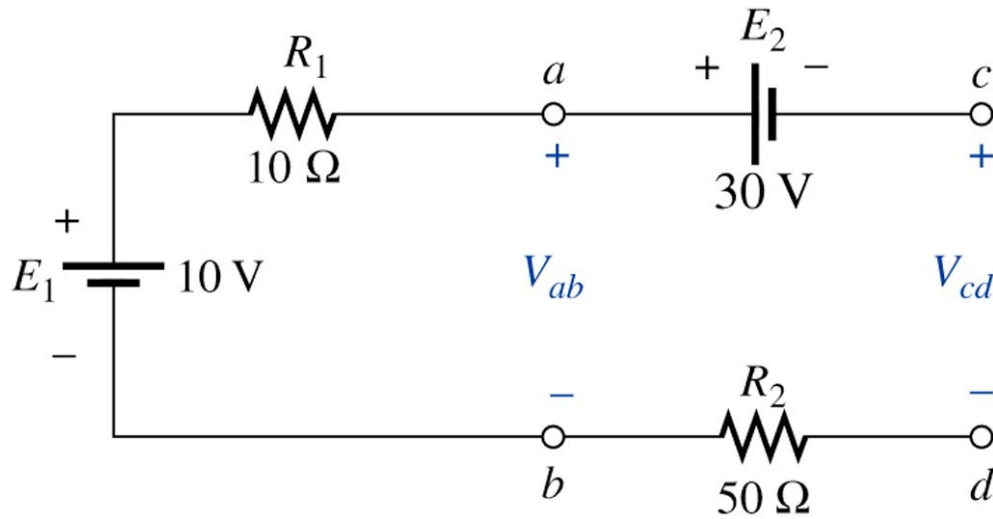


$$\begin{aligned} V_{cd} &= 10\text{ V} - 30\text{ V} \\ &= -20\text{ V} \end{aligned}$$

$$V_{ab} = 10\text{ V}$$

$$\text{KVL: } V_{ab} - 30\text{ V} - V_{cd} + 0 = 0$$

Breakout #3

- Find I and V

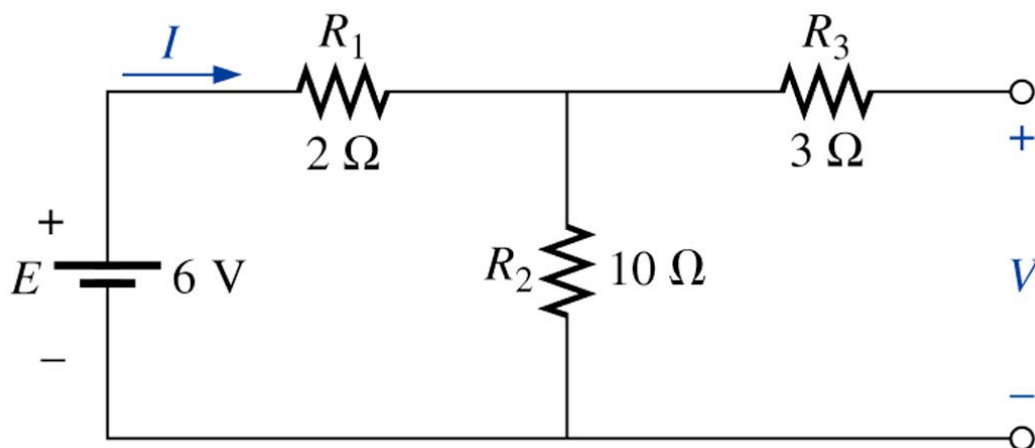


$$I = \frac{6\text{ V}}{12\ \Omega} = 0.5\text{ A}$$

$$\begin{aligned} V &= V_{R_2} = 0.5\text{ A} \cdot 10\ \Omega \\ &= 5\text{ V} \end{aligned}$$

Example

- Find V_{ab} w/DMM connected

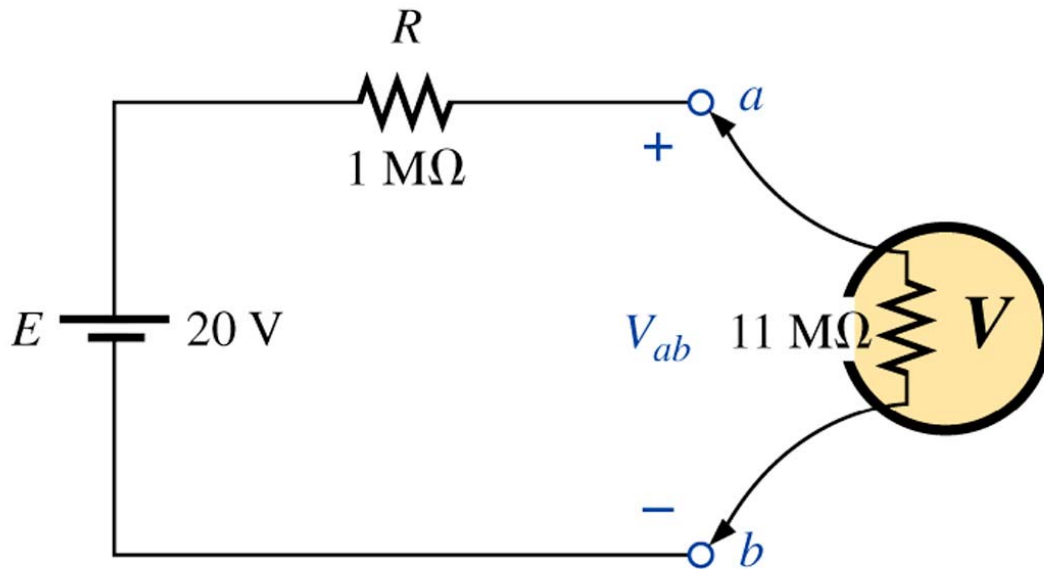

$$V = 20\text{ V} \cdot \frac{11\text{ M}\Omega}{12\text{ M}\Omega} = 18.33\text{ V}$$