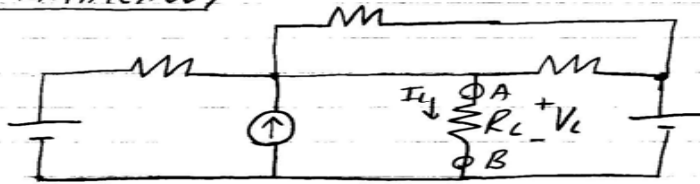



9.3 THÉVENIN'S THEOREM

ANY TWO-TERMINAL, LINEAR BILATERAL DC NETWORK CAN BE REPLACED BY AN EQUIVALENT CIRCUIT CONSISTING OF A VOLTAGE SOURCE + A SERIES RESISTOR.

GRAPHICALLY :



REPLACE EVERYTHING EXCEPT R_L WITH :

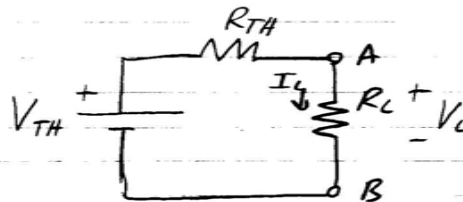


V_L & I_L THE SAME AS ABOVE

* EQUIVALENT AT TERMINALS A-B ONLY

PROCEDURE :


- (1) REMOVE THE LOAD (OR PORTION OF THE NETWORK ACROSS WHICH THE THÉVENIN EQUIVALENT CIRCUIT IS TO BE FOUND) & MARK THE TERMINALS (A-B).
- (2) FIND R_{TH} - REPLACE VOLTAGE SOURCES w/ SHORT-CIRCUITS
- REPLACE CURRENT SOURCES w/ OPEN-CIRCUITS
- FIND $R_{TH} = R_{AB}$
- (3) FIND V_{TH} - ALL SOURCES IN CIRCUIT
- FIND o/c VOLTAGE $V_{A-B} = V_{TH}$
- (4) DRAW THE THÉVENIN EQUIVALENT CIRCUIT

(EXAMPLE)

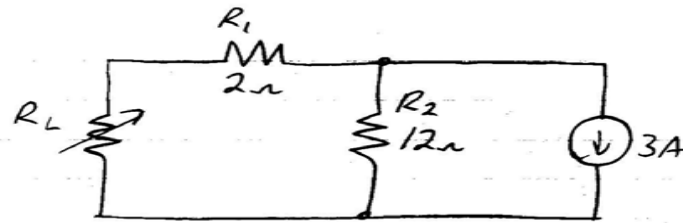


→ FIND THE
THEVENIN EQUIV.
CIRCUIT AS
SEEN BY R_L
→ FIND P_{RL}
FOR $R_L = 10\Omega$

(1) REMOVE R_L & MARK TERMINALS A & B :

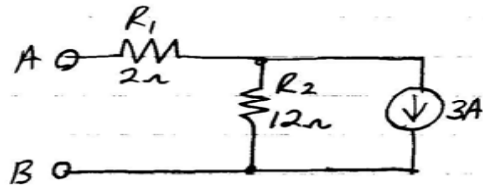


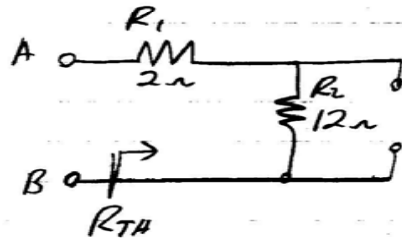(2) FIND R_{TH} (VOLT SOURCES \rightarrow S/C
CURRENT SOURCES \rightarrow O/C)




$$R_{TH} = R_{AB} = R_1 + R_2$$
$$R_{TH} = 14\Omega$$

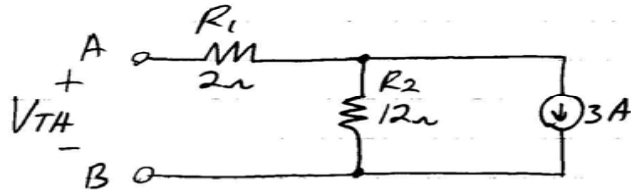(3) FIND V_{TH} (SOURCES IN - CIRCUIT)
 $V_{TH} = V_{AB} = V_{O/C}$




$$V_{TH} = (-3A)(12\Omega)$$
$$V_{TH} = -36V$$

(4) THEVENIN EQUIVALENT CIRCUIT :

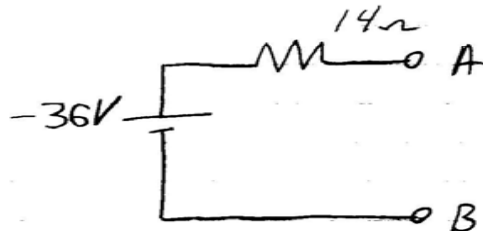


OR

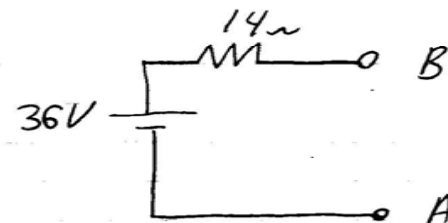


FIND P_{R_L} FOR $R_L = 10\ \Omega$

ORIGINAL CIRCUIT

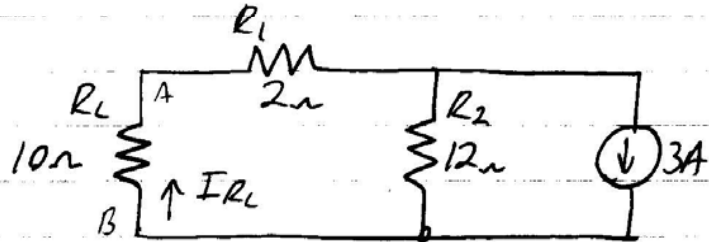

In Class Problem

THEVENIN EQUIVALENT

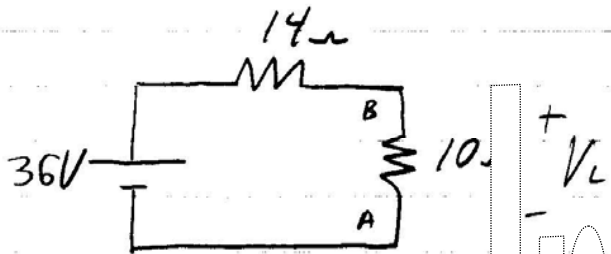


$$V_L = 36V \left(\frac{10}{10 + 14} \right) = 15V$$


FOR MORE COMPLICATED CIRCUITS
TO ANALYZE THE THEVENIN EQUIVALENT CIRCUIT
(REPEATEDLY) INSTEAD OF THE ORIGINAL CIRCUIT

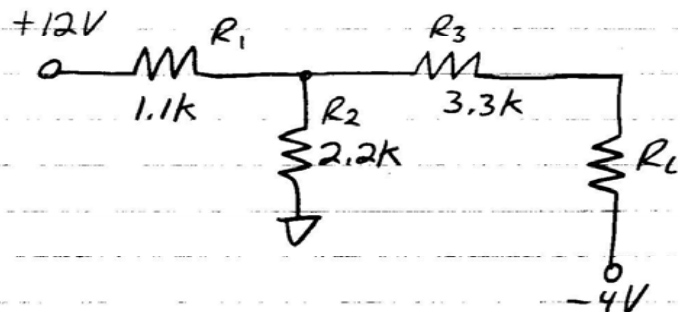(EXAMPLE)


DETERMINE THE THEVENIN EQUIVALENT
CIRCUIT AS SEEN BY R_L .



REDRAW, REMOVE R_L , LABEL A-B:

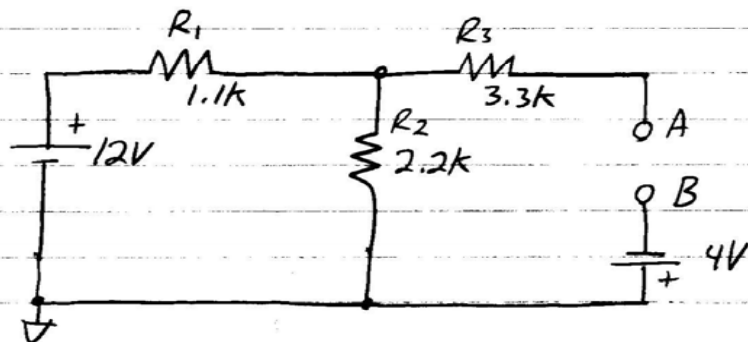


R_{TH} :

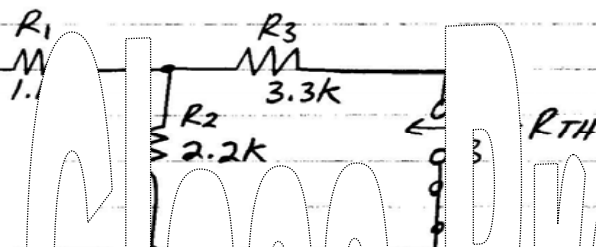

$$R_{TH} = [R_1 \parallel R_2] + R_3$$

$$R_{TH} = [1.1k \parallel 2.2k] + 3.3k$$

$$R_{TH} = 3.3k$$

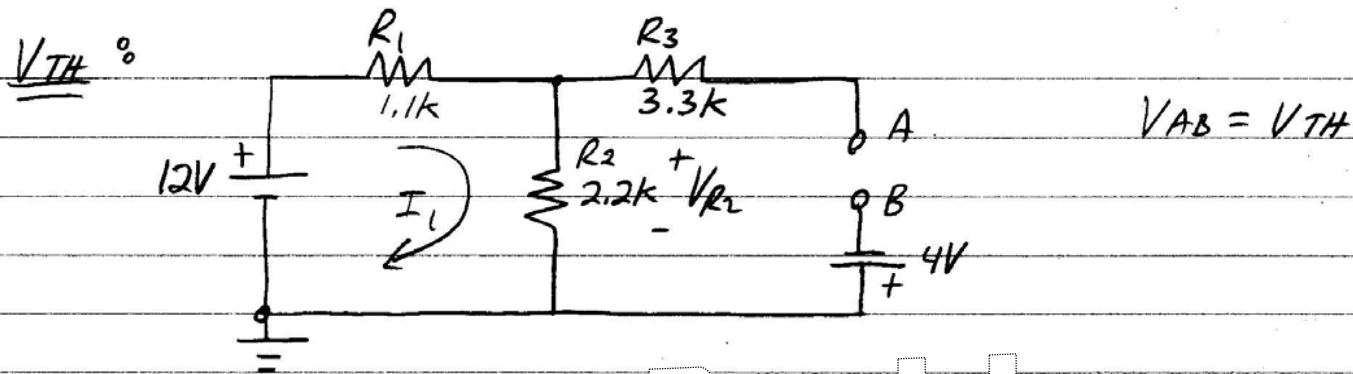

$$I_1 = \frac{12V}{R_1 + R_2} = \frac{12V}{1.1k + 2.2k} = 636mA$$


$$V_{R2} = I_1 R_2 = 636mA \cdot 2.2k = 1.4V$$

$$V_{AB} + 4V = 0 \Rightarrow V_{AB} = -4V$$

$$V_{TH} = -4V$$

THÉVENIN EQUIV. CKT


$$R_{TH} = 1.1k + 3.3k = 4.4k$$

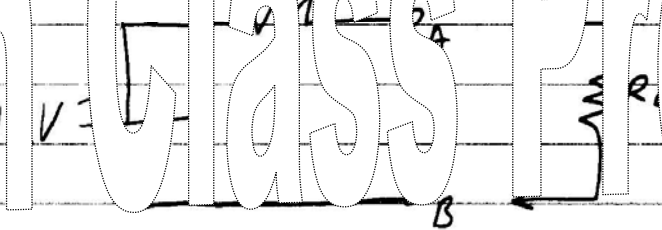

9.3 THEVENIN'S THEOREM (CONTINUED)

EXPERIMENTALLY: FIND R_{TH} & V_{TH}

CONSIDER

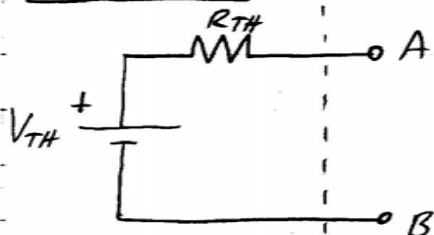

Any two -

TERMINAL, LINEAR


BILATERAL DC

NETWORK

- FIND V_{TH} EXPERIMENTALLY:

$$\underline{V_{AB} \text{ o/c} = V_{TH}}$$

- HOW ABOUT R_{TH} EXPERIMENTALLY?

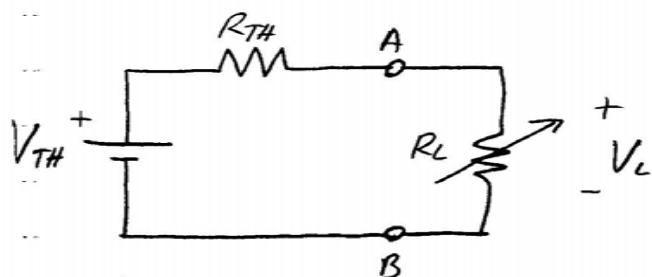

$$V_L = V_{TH} \left(\frac{R_L}{R_L + R_{TH}} \right)$$

FOR $R_L = R_{TH}$: $V_L = V_{TH} \left(\frac{R_{TH}}{R_{TH} + R_{TH}} \right)$


$$\underline{\underline{V_L = \frac{V_{TH}}{2}}}$$

o o ADJUST R_L UNTIL $V_L = \frac{1}{2} V_{TH}$

$$\underline{\underline{R_L = R_{TH}}}$$

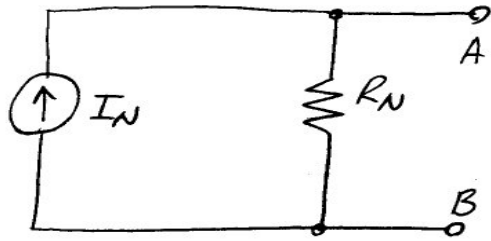9.4 NORTON'S THEOREM

ANY TWO-TERMINAL LINEAR BILATERAL DC NETWORK CAN BE REPLACED WITH :




PROCEDURE

R_N : - REMOVE R_L (OR THAT PORTION OF THE NETWORK ACROSS WHICH THE NORTON EQUIVALENT CIRCUIT IS TO BE FOUND).

- MARK THE TWO TERMINALS (A-B)
- CALCULATE $R_N = R_{AB o/c}$ BY RELAXING ALL SOURCES & LOOKING INTO A-B
- * $R_N = R_{TH}$, SOURCE CONVERSION


I_N : - PUT THE SOURCES BACK INTO THE CIRCUIT

- FIND $I_N = I_{AB}$:

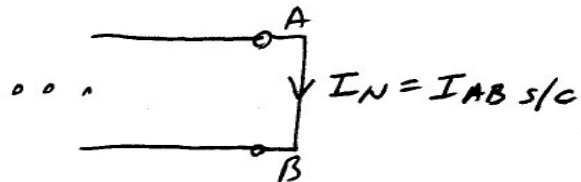


* $I_N = \frac{V_{TH}}{R_{TH}}$, SOURCE CONVERSION

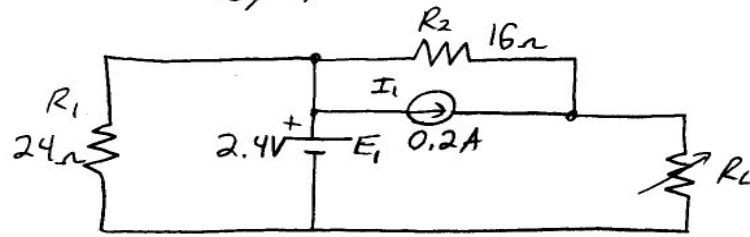(EXAMPLE) FIND THE NORTON EQUIVALENT AS SEEN
By R_L :




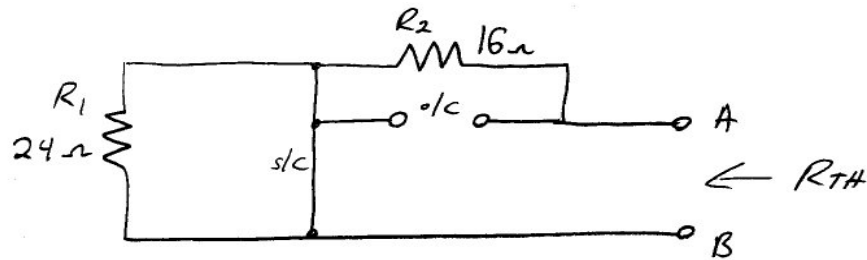$R_N = R_{TH}$ - RELAX SOURCES
- CALCULATE R_{AB}



$$R_N = R_{TH} = R_2 = 16\Omega$$

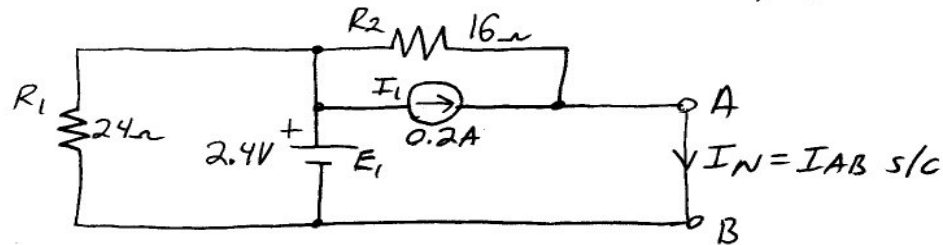
I_N - SOURCES IN CIRCUIT I
- R_L OUT OF CIRCUIT (A-B s/c)



SUGGESTIONS ON FINDING I_N ?


FIND I_N BY SUPERPOSITION:

DUE TO E_1

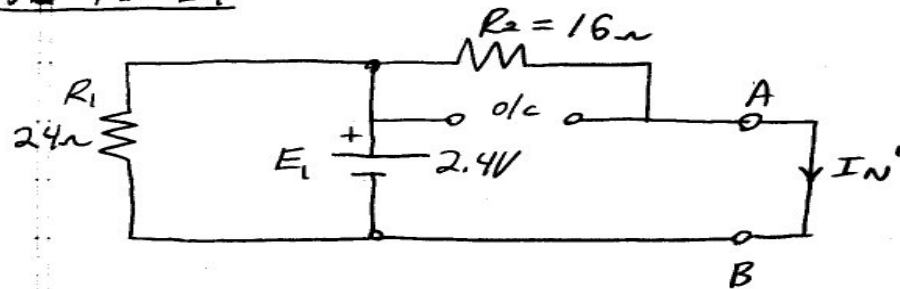

$$I_N' = \frac{E_1}{R_2} = \frac{2.4V}{16\Omega} = \underline{150mA}$$

DUE TO I_1

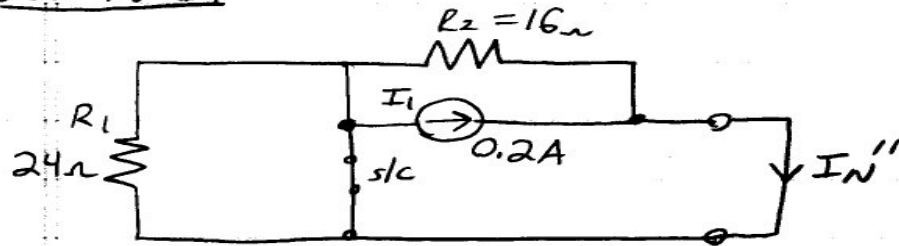

$$I_N'' = \underline{0.2A}$$

$$\therefore I_N = 150mA + 200mA = \boxed{350mA}$$

EQUIVALENT CIRCUIT

