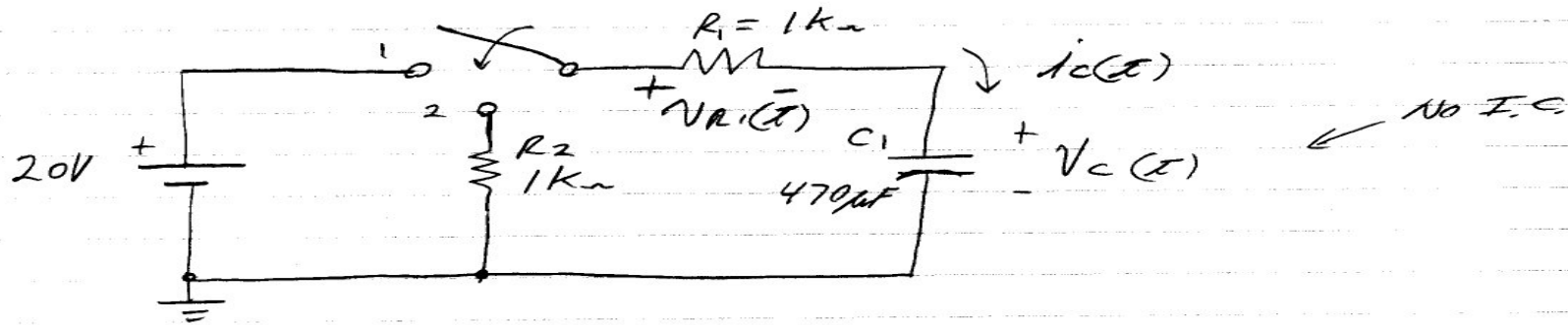


SIMPLE CAPACITOR CIRCUIT (CHARGE/DISCHARGE)



At $t = 0$, SW \rightarrow POSITION 1

At $t = 10\text{ SEC}$, SW \rightarrow POSITION 2

FIND :

a) τ

b) $i_C(t)$


c) $V_{R_1}(t)$

d) $V_C(t)$

e) t For $V_C(t) = 10V$

FOR BOTH CHARGE & DISCHARGE

CHARGE CIRCUIT

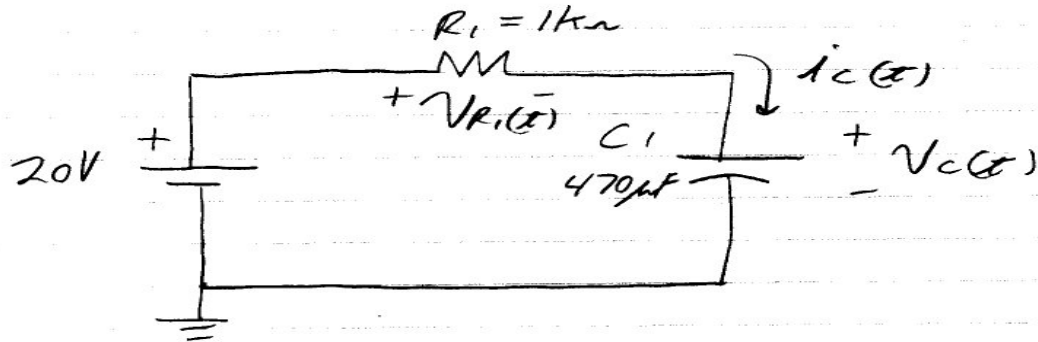


$$\tau = R_{TH} \cdot C_T = R_1 C_1 = (1k\Omega)(470\mu F) = \boxed{0.47 \text{ SEC}}$$

$$i_C(t) = i_{C\text{MAX}} e^{-t/\tau}$$

$$i_{C\text{MAX}} = \frac{20V}{R_1} = \frac{20V}{1k\Omega} = 20\text{MA}$$

DISCHARGE
VALID FOR
 $t > 10$

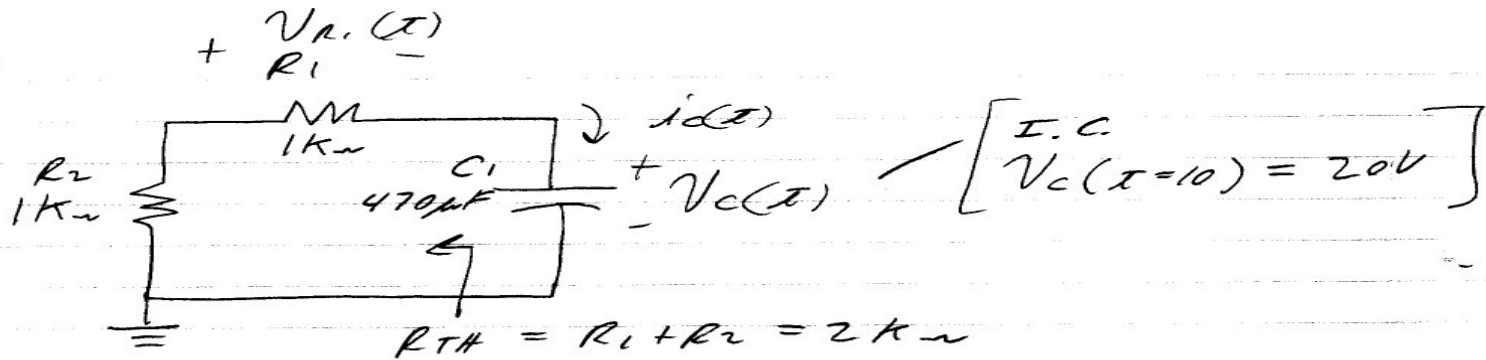

$$\tau = R_{TH} \cdot C_T = (2k\Omega)(470\mu F) = \boxed{940ms}$$

$$i_C(t) = -i_{C_{MAX}} e^{-t/\tau} \leftarrow \text{GENERAL FORM}$$

$$i_{C_{MAX}} = \frac{20V}{2k\Omega} = \underline{10mA}$$

SWITCH CLOSED AT $t = 10$

$$\therefore \boxed{i_C(t) = -10 \times 10^{-3} e^{-(t-10)/0.94} \text{ A}}$$

$$V_{R1}(t) = i_C(t) \cdot R_1 = \boxed{-10 e^{-(t-10)/0.94} \text{ V}}$$

$$V_C(t) = V_{C_{MAX}} e^{-(t-10)/0.94} \text{ V}$$

$$\boxed{V_C(t) = 20V e^{-(t-10)/0.94} \text{ V}}$$

t For $V_C(t) = 10V$?


$$10 = 20 e^{-(t-10)/0.94}$$

$$-0.693 = -(t-10)/0.94$$

$$0.652 = (t-10)$$

$$\therefore \boxed{t = 10.65 \text{ SECONDS}}$$


(EXAMPLE 1) FIND C_T :

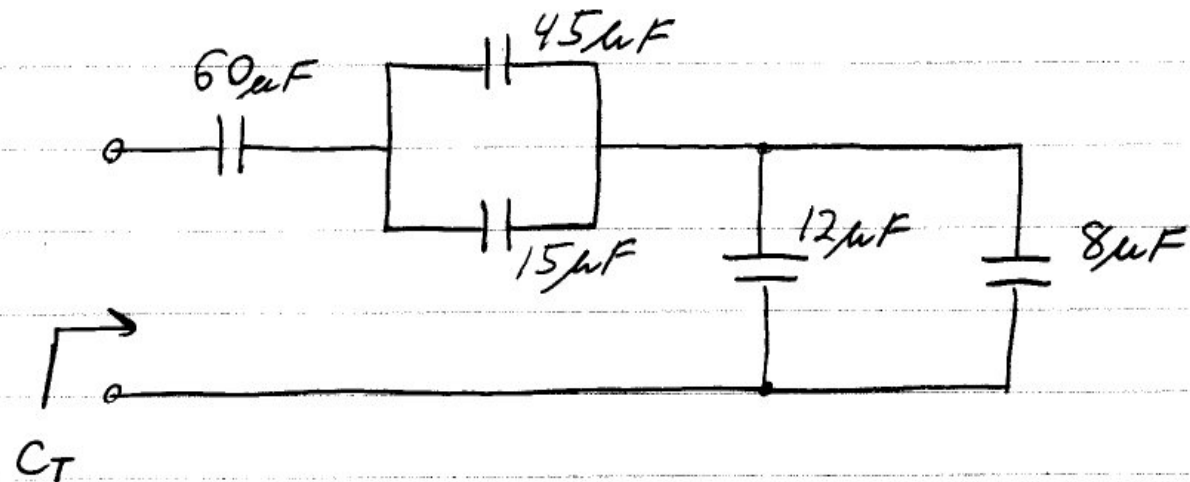

$$12\mu F // 8\mu F = 20\mu F$$

$$45\mu F // 15\mu F = 60\mu F$$

REDRAWN:

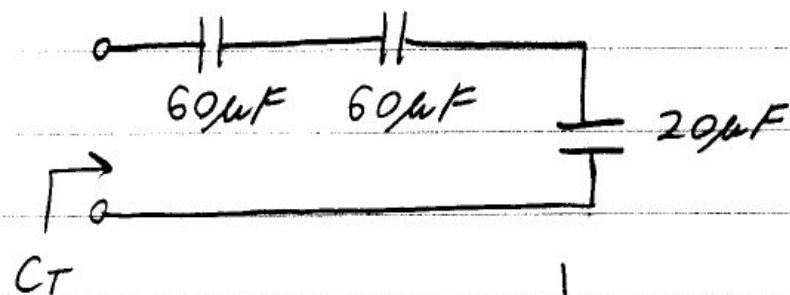

$$C_T = \frac{1}{\frac{1}{60\mu F} + \frac{1}{60\mu F} + \frac{1}{20\mu F}} = \boxed{12\mu F}$$