

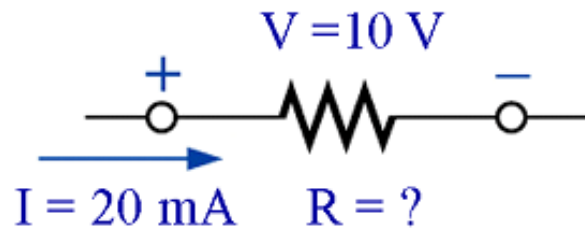

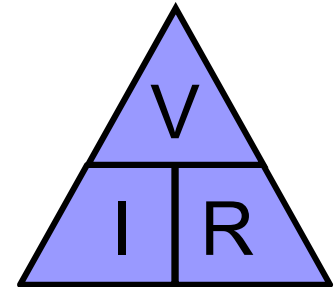
## Breakout Exercise #1


For each of the Ohm's law problems shown, find the unknown.



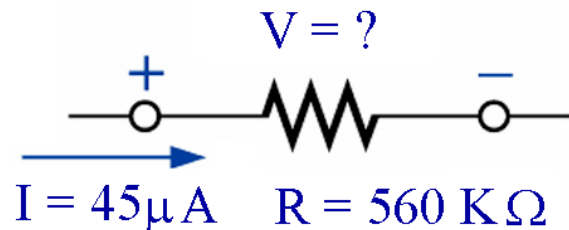
$$R = \frac{V}{I} = \frac{10\text{ V}}{20\text{ mA}} = 500\ \Omega$$


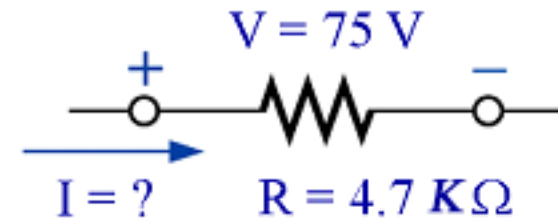
$$V = 45\ \mu\text{A} \cdot 560\text{ K}\Omega = 25.2\text{ V}$$



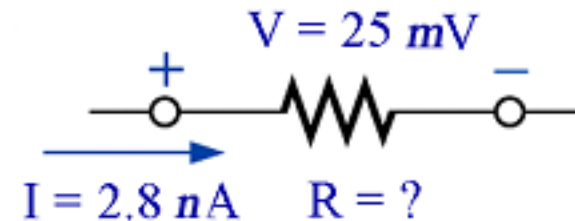
$$I = \frac{V}{R} = \frac{75\text{ V}}{4.7\text{ K}\Omega} = 15.96\text{ mA}$$



$$R = \frac{V}{I} = \frac{25\text{ mV}}{2.8\text{ nA}} = 8.93\text{ M}\Omega$$
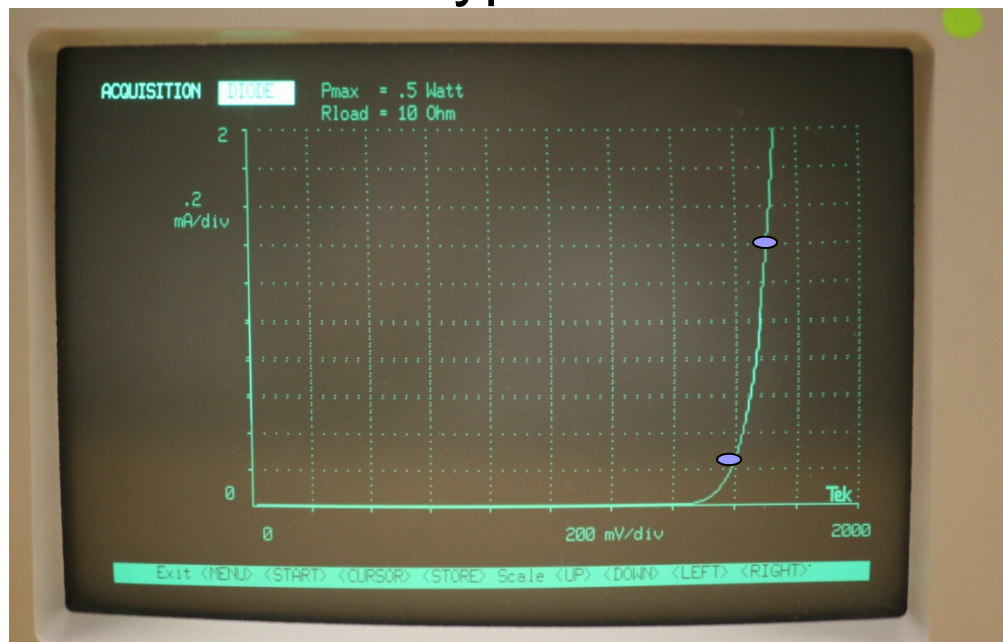
## Breakout Exercise #2

- Estimate the resistance of the diode at  $V_D = 1.6\text{V}$  and  $V_D = 1.7\text{V}$ , using the I-V characteristics shown.
- Bonus: What type of diode is this?



$V_D = 1.7\text{V}$ ,  $I_D \sim 1.4\text{mA}$   
 $R = 1.21\text{ K}\Omega$

$V_D = 1.6\text{V}$ ,  $I_D \sim 250\mu\text{A}$   
 $R = 6.4\text{ K}\Omega$