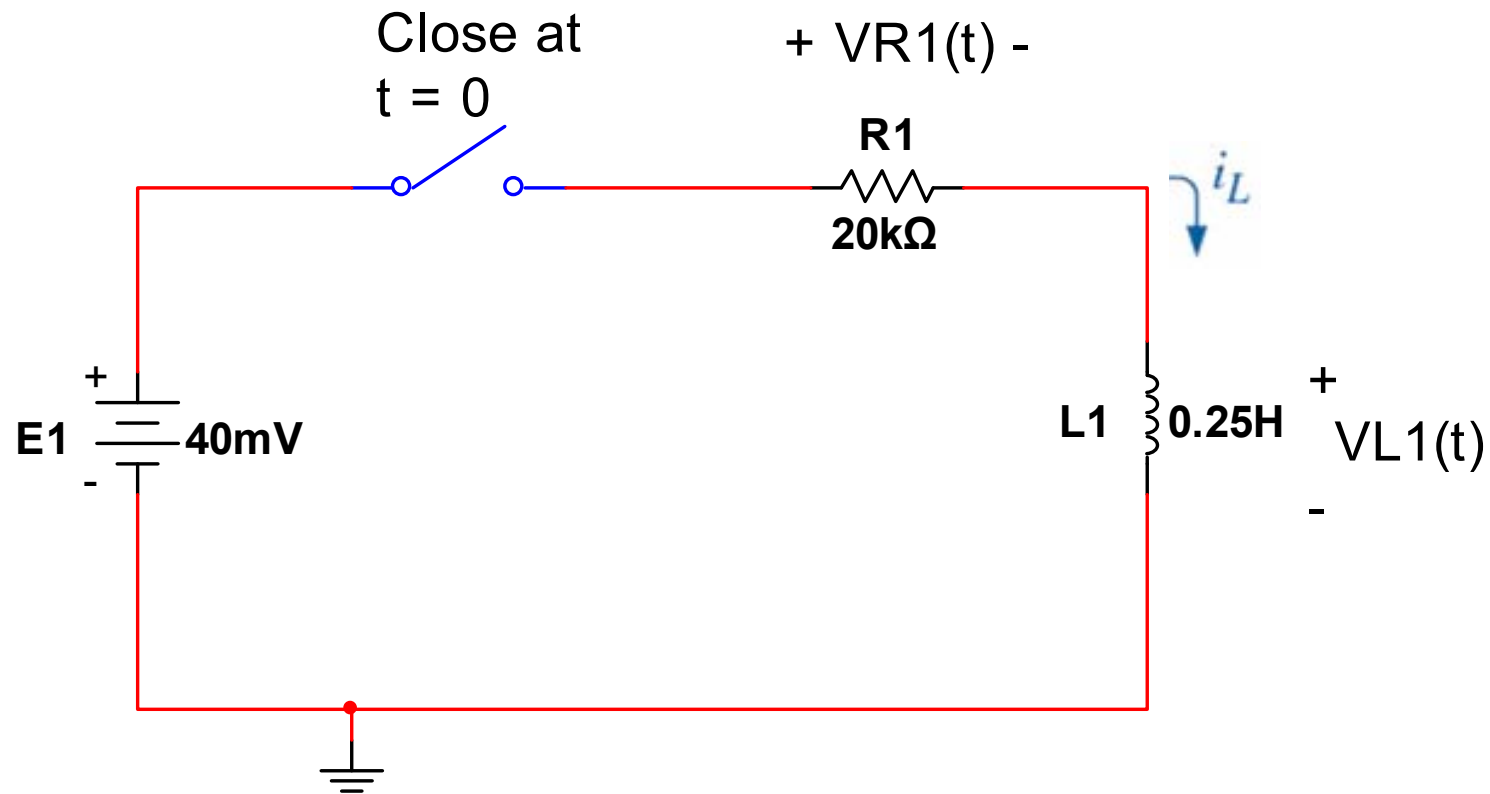


Electrical Engineering Technology

**Inductors – Transient/Storage Phase and
Decay Phase Intro**

Fall 2018

R-L Storage Phase – In Class Problem



1. Find τ
2. Find $i_{L1}(t)$, $t \geq 0$ (eq)
3. Find $v_{L1}(t)$ and $v_{R1}(t)$, $t \geq 0$ (eq)
4. Find i_L and v_L for 1τ , 3τ , & 5τ
5. Sketch $i_{L1}(t)$, $v_{L1}(t)$, & $v_{R1}(t)$, $t \geq 0$

R-L Decay Phase – Issue with our standard Thevenin equivalent circuit approach

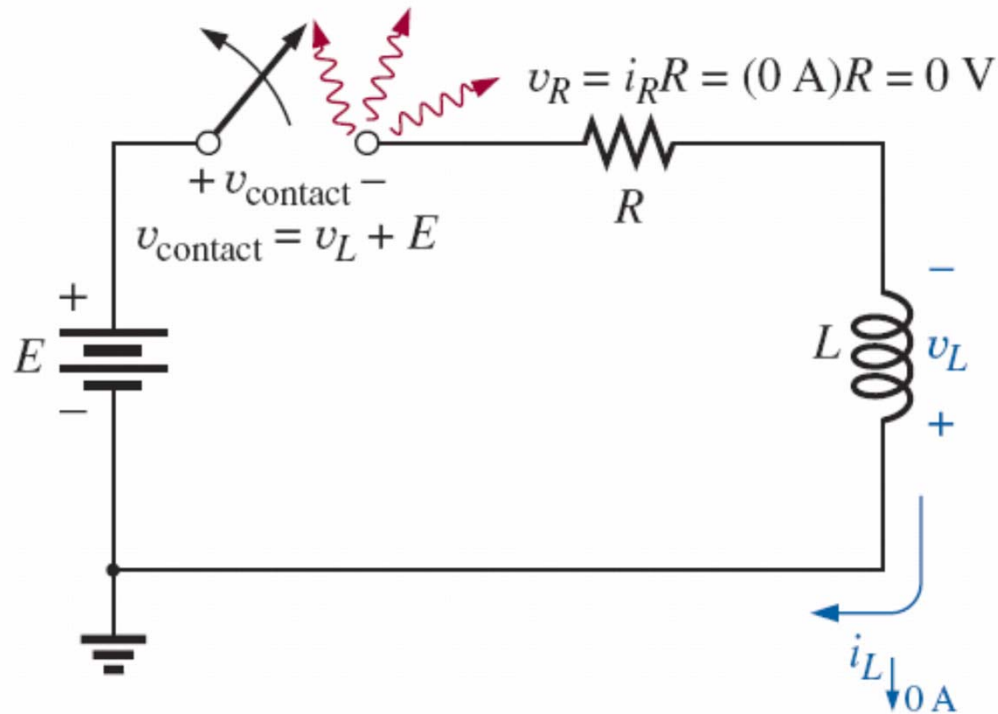


FIG. 11.41 *Demonstrating the effect of opening a switch in series with an inductor with a steady-state current.*

R-L Decay Phase – Fix to overcome the high voltage problem

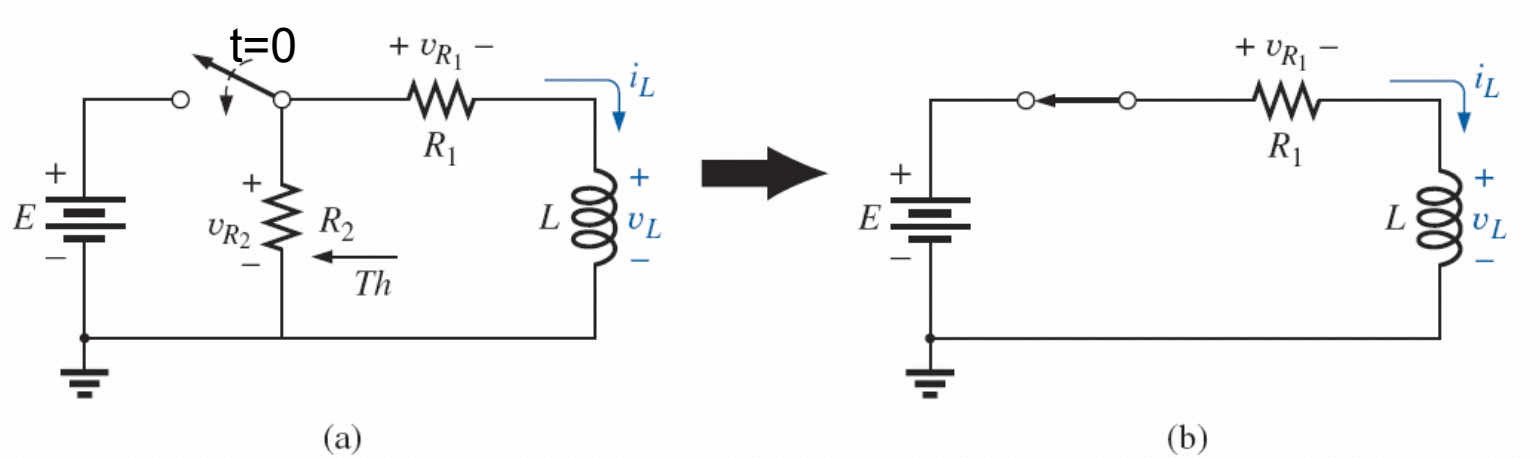


FIG. 11.42 Initiating the storage phase for an inductor by closing the switch.

*Note that R_2 has no effect on the storage phase: $i_{L \text{ Final}} = E/R_1$


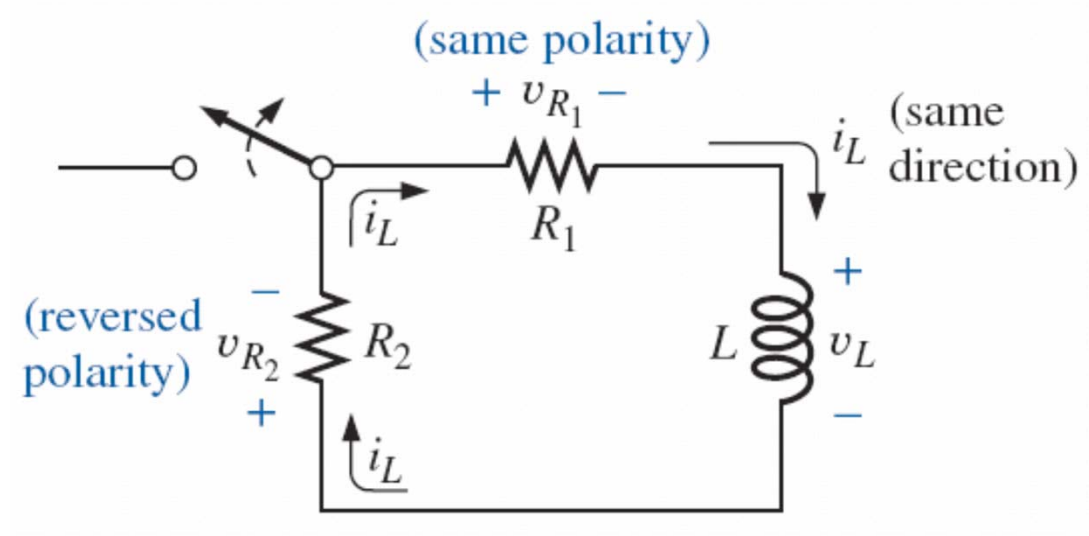


FIG. 11.43 Network in Fig. 11.42 the instant the switch is opened.

$t = 0^+$ so $i_L = i_{L \text{ Final}}$ from the storage phase

R-L Decay Phase - Analysis

For $t = 0^+$

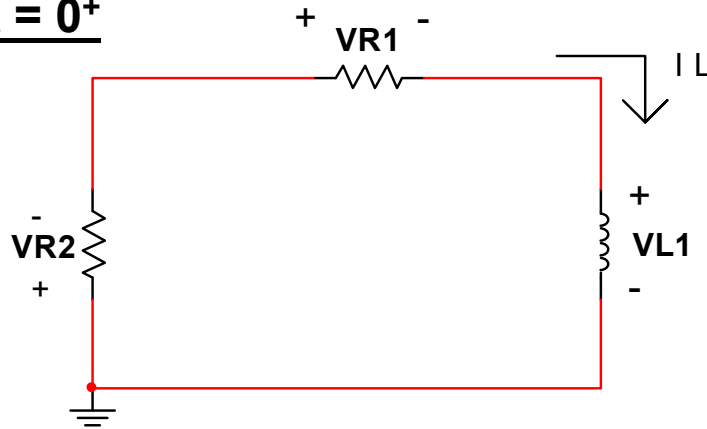

$i_L(0^+) = E / R_1$ <- Final value from storage phase

Finding $v_L(0^+)$:

$$-V_{R2} - V_{R1} - V_L = 0 \text{ (KVL)}$$

$$V_L = -V_{R2} - V_{R1}$$

$$\text{But: } v_{R2} = i_L * R_2, v_{R1} = i_L * R_1$$

$$\begin{aligned} \text{So, } v_L(0^+) &= -i_L * R_2 - i_L * R_1 \\ &= -i_L * (R_2 + R_1) \\ &= -(E / R_1) * (R_2 + R_1) \end{aligned}$$

$$\mathbf{v_L(0^+) = -E(R_2 / R_1 + 1)}$$

We can also use $i_L(0^+)$ to find $v_{R2}(0^+)$ and $v_{R1}(0^+)$


For $t \gg \tau$

i_L will exponentially decrease from its max value of (E/R_1) to zero

v_L will exponentially decrease to 0

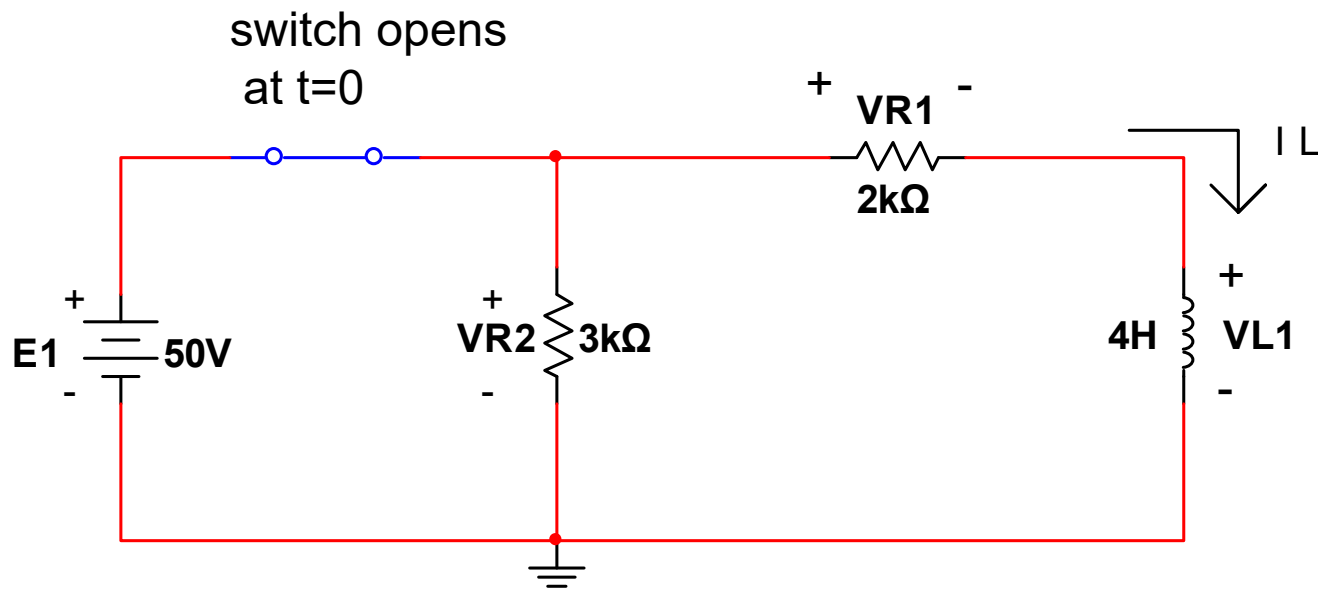Example – Decay Phase

Assume the circuit was in the storage phase for $> 5\tau$ and find $i_L(t)$, $v_L(t)$, $v_{R1}(t)$, & $v_{R2}(t)$ for the decay phase (switch opens at $t=0$)



$$V_{th} = 50V, R_{th} = 2k\text{-Ohms (for } t < 0)$$

Example – Decay Phase

$$i_{LMax} = \frac{50V}{2k\Omega} = 25mA, t = 0$$

L1 acts as a s/c once steady state conditions are met

$$i_L(t) = i_{LMax}e^{-t/\tau} A \quad \tau = L/R = L/R_{Th}, R_{Th} = R_1 + R_2 = 5k\Omega$$


$$i_L(t) = (25 \cdot 10^{-3})e^{-t/0.8 \cdot 10^{-3}} A$$

Exponential decay to 0

$$v_{R_1}(t) = i_L(t) \cdot R_1 = 50e^{-t/0.8 \cdot 10^{-3}} V$$

$$v_{R_2}(t) = -i_L(t) \cdot R_2 = -75e^{-t/0.8 \cdot 10^{-3}} V$$

Rth = 5k-Ohms (for t>0)

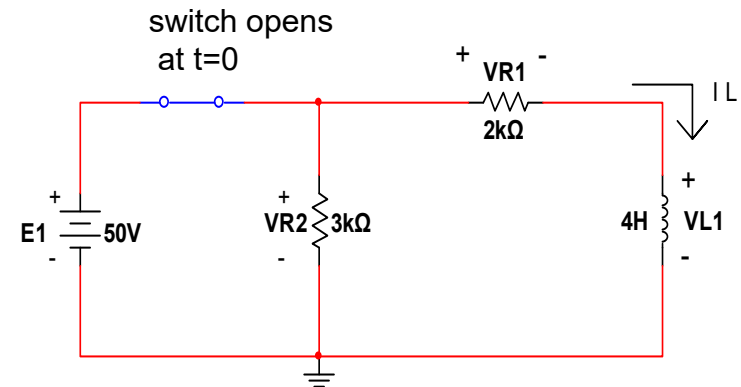


$$KVL : v_L(t) = v_{R_2}(t) - v_{R_1}(t)$$


$$v_L(t) = -75e^{-t/0.8 \cdot 10^{-3}} - 50e^{-t/0.8 \cdot 10^{-3}}$$

$$v_L(t) = -125e^{-t/0.8 \cdot 10^{-3}} V$$


Example – Decay Phase (sketches)

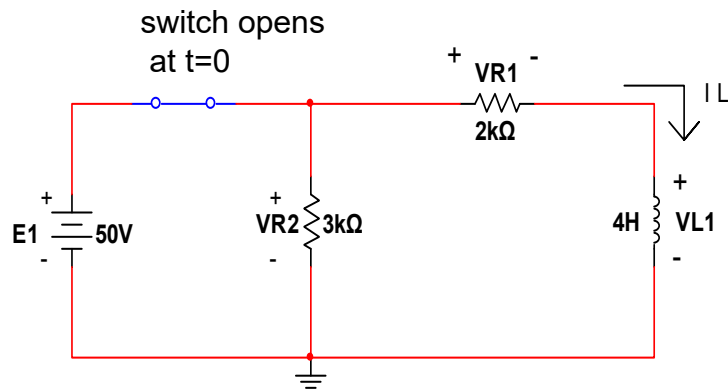
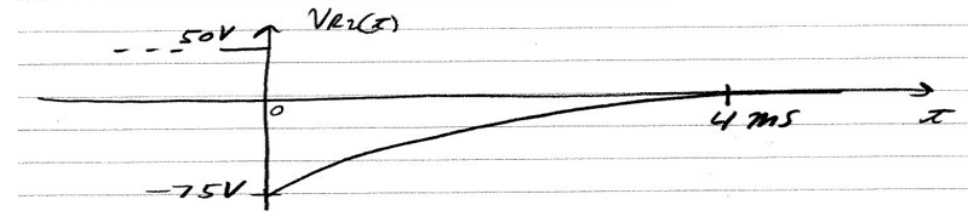
$$v_{R_2}(t) = i_L(t) \cdot R_2 = -75e^{-t/0.8 \cdot 10^{-3}} \text{ V}$$



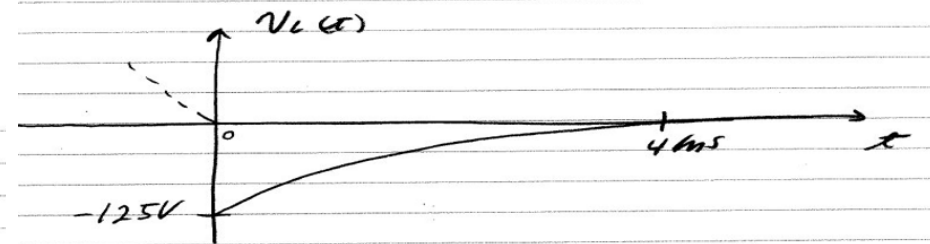
$$v_L(t) = -125e^{-t/0.8 \cdot 10^{-3}} \text{ V}$$



$$i_L(t) = (25 \cdot 10^{-3})e^{-t/0.8 \cdot 10^{-3}} \text{ A}$$

($t=0$, SWITCH OPENED)

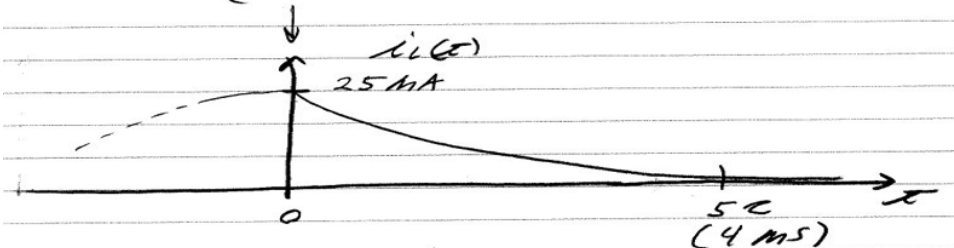

$$v_{R_1}(t) = i_L(t) \cdot R_1 = 50e^{-t/0.8 \cdot 10^{-3}} \text{ V}$$

