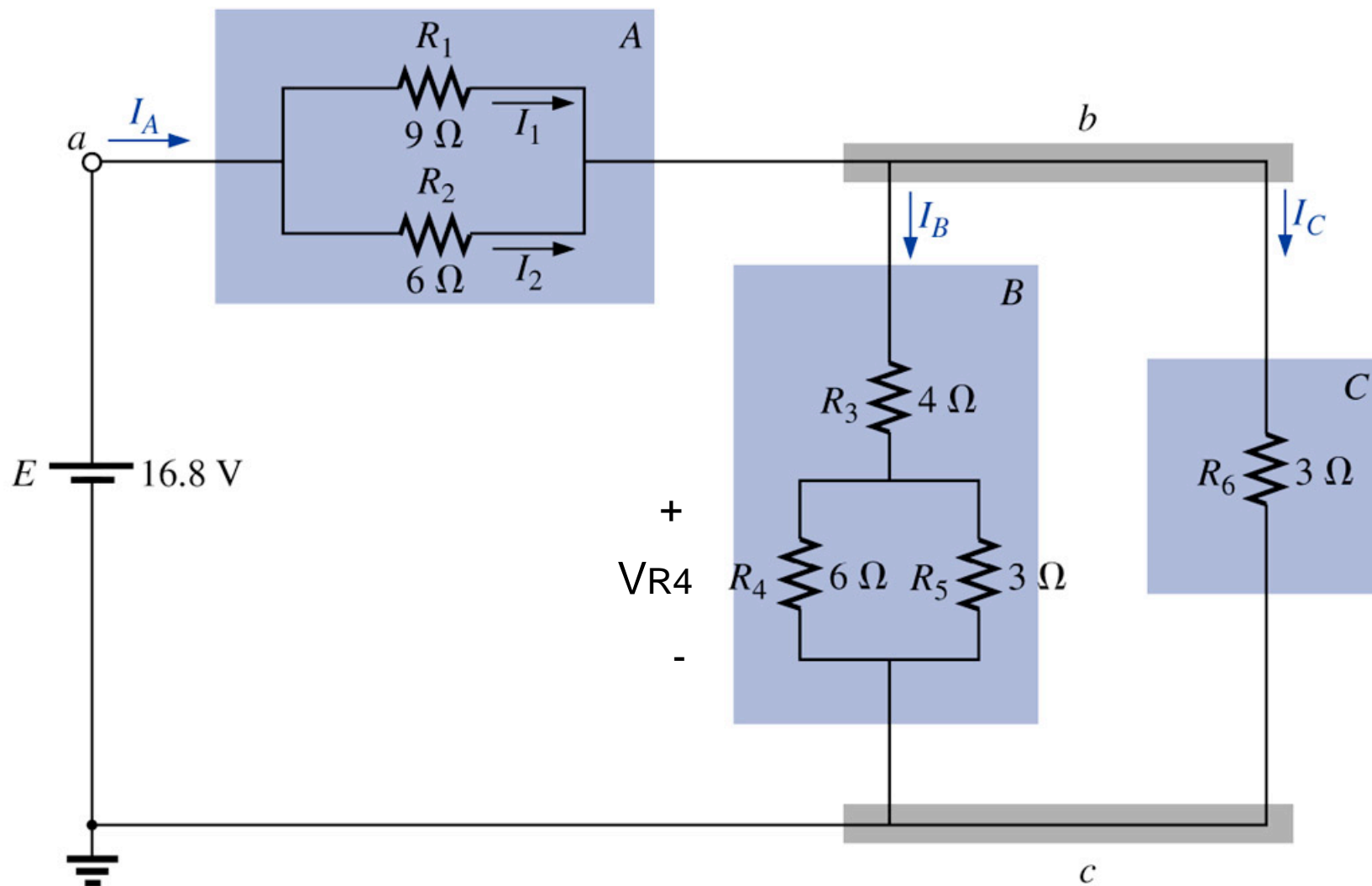



Breakout #1 – Find I_1 , I_B , I_C , V_{R4}



Breakout #2 – Ladder Network

■ Find V_1 and I_1

□ Hint: Start by finding R_t

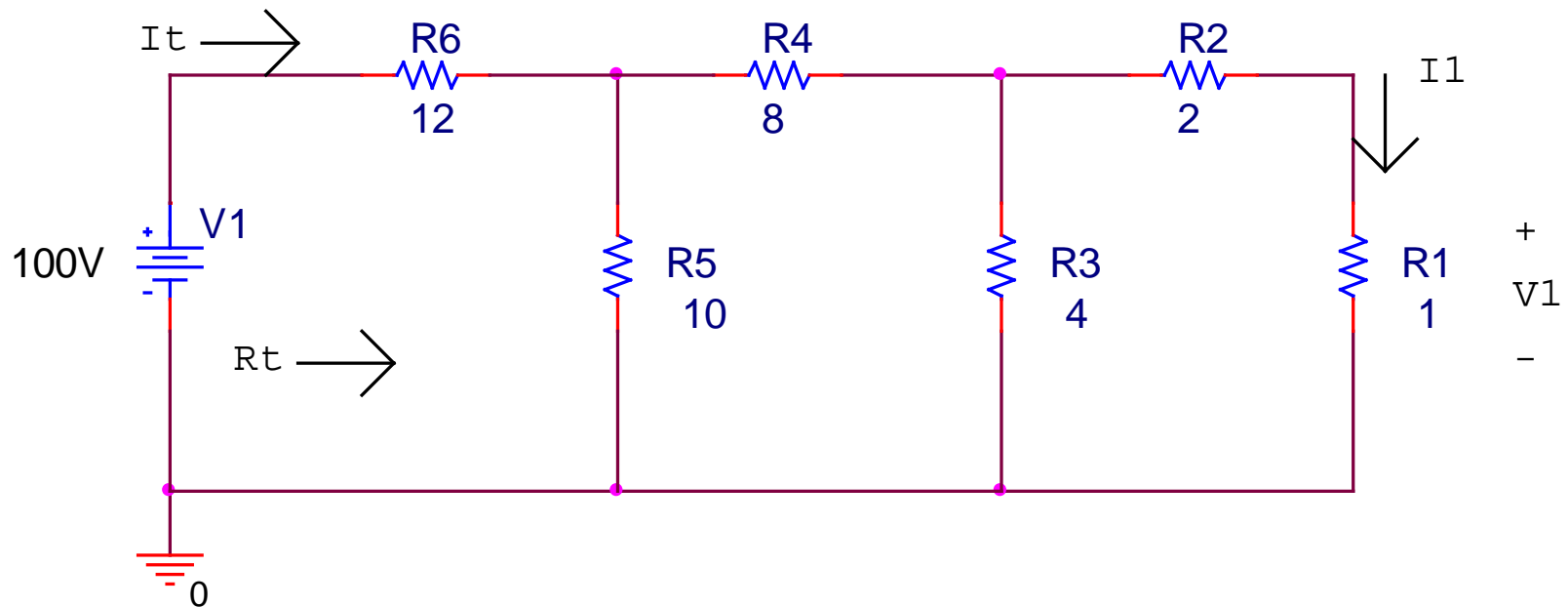

Breakout #3 – Voltage Divider Supply

- Find V_B and V_C

