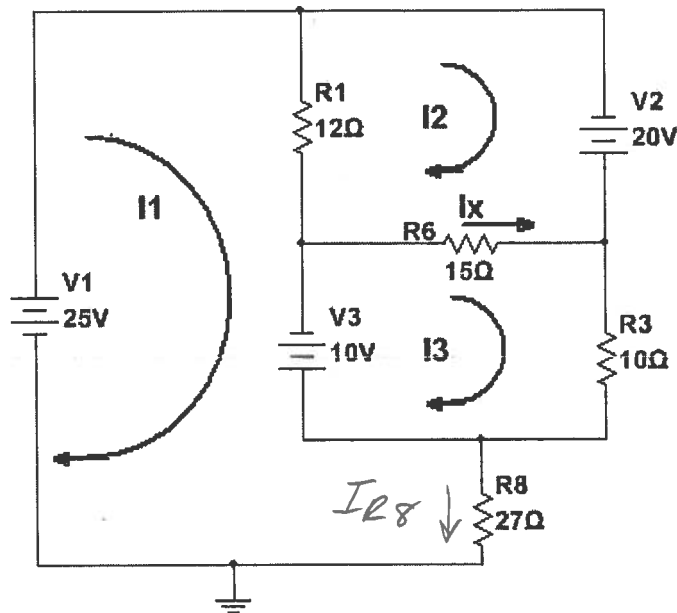


**Find:**

- 1) The total resistance seen by the source
- 2) The current through R3

$$\begin{aligned}
 (1) \quad R_T &= [R_7 // (R_4 + R_5) + R_6] // (R_1 + R_2 // R_3) \\
 &= [(10k\Omega // 2200\Omega) + 330\Omega] // (560\Omega + 470\Omega // 680\Omega) \\
 &= [1,803.3\Omega + 330\Omega] // (560\Omega + 277.9\Omega) \\
 &= 2,133.3\Omega // 837.9\Omega \\
 \boxed{R_T = 601.6\Omega}
 \end{aligned}$$

$$\begin{aligned}
 (2) \quad & \text{Circuit diagram for finding } I_{R_3}: \text{A } 10V \text{ source is in series with } R_1 (560\Omega). \text{ This is followed by a parallel combination of } R_2 (470\Omega) \text{ and } R_3 (680\Omega). \text{ The current through } R_1 \text{ is } I_{R_1}. \text{ The current through } R_3 \text{ is } I_{R_3}. \text{ The ground is connected to the bottom of } R_2 \text{ and } R_3. \\
 I_{R_1} &= \frac{10V}{R_1 + (R_2 // R_3)} = \frac{10V}{837.9\Omega} = \underline{11.934 \text{ mA}} \\
 \therefore I_{R_3} &= I_{R_1} \cdot \frac{R_2 // R_3}{R_3} \\
 &= 11.934 \text{ mA} \left( \frac{277.9\Omega}{680\Omega} \right) \\
 \boxed{I_{R_3} = 4.88 \text{ mA, DOWNWARD}}
 \end{aligned}$$



Given that:

$$I_1 = 1.43 \text{ A}$$

$$I_2 = 1.73 \text{ A}$$

$$I_3 = 0.639 \text{ A}$$

$$\begin{aligned} \text{Loop 1: } V_1 - R_1 I_1 + R_1 I_2 + V_3 - R_8 I_1 &= 0 \\ -39 I_1 + 12 I_2 + 0 I_3 &= -35 \quad (\text{EQ 1}) \\ \text{Loop 2: } -I_2 R_1 + I_1 R_1 + V_2 - I_2 R_6 + R_6 I_3 &= 0 \\ 12 I_1 - 27 I_2 + 15 I_3 &= -20 \quad (\text{EQ 2}) \\ \text{Loop 3: } -V_3 - I_3 R_6 + I_2 R_6 - I_3 R_3 &= 0 \\ 0 I_1 + 15 I_2 - 25 I_3 &= 10 \quad (\text{EQ 3}) \end{aligned}$$

- You should calculate/verify these currents later, before Exam #3 to check your MESH analysis technique and equation solver prowess!

Find:


- $I_x$ , the current through  $R_6$  (direction as shown)
- The power dissipated by  $R_8$
- The power delivered by source  $V_1$
- The voltage across  $R_1$  (value and polarity)

$$(1) I_x = I_3 - I_2 = \boxed{-1.09 \text{ A}}$$

$$(2) P_{R8} = I_{R8}^2 R_8 = (I_1)^2 R_8 = \boxed{55.2 \text{ W}}$$

$$(3) P_{V1} = V_1 \cdot I_1 = \boxed{35.75 \text{ W}}$$
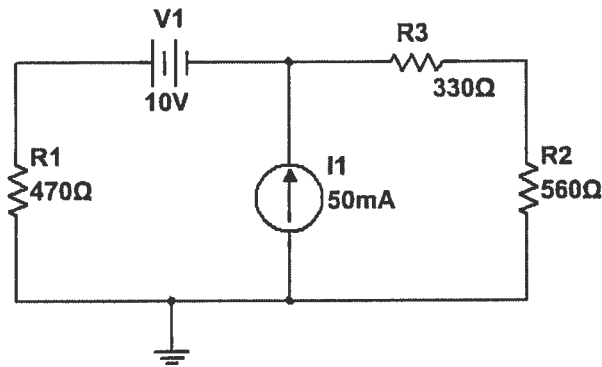
$$\begin{aligned} (4) R_1 \text{ with } V_{R1} \text{ across it} \quad V_{R1} &= (I_1 - I_2) R_1 \\ &= \boxed{-3.6 \text{ V}} \end{aligned} \quad \begin{aligned} \text{OR } R_1 \text{ with } V_{R1} \text{ across it} \quad V_{R1} &= (I_2 - I_1) R_1 \\ &= \boxed{3.6 \text{ V}} \end{aligned}$$




**Find:**

- 1) The current that flows through R3 due only to the 10V source and the direction of this current
- 2) The total current that flows through R3 and the direction of this current

(1)

$V_1$  ONLY

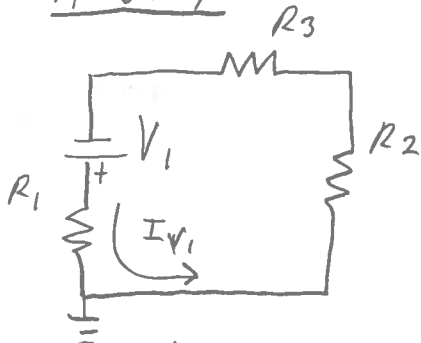

$$I_{V_1} = V_1 / R_T$$

$$R_T = R_1 + R_2 + R_3$$


$$\therefore I_{V_1} = \frac{10V}{1360\Omega}$$

$$I_{V_1} = 7.353 \text{ mA}$$

$$\therefore I_{R_3}' = 7.353 \text{ mA}$$

RIGHT T. LEFT

$I_1$  ONLY

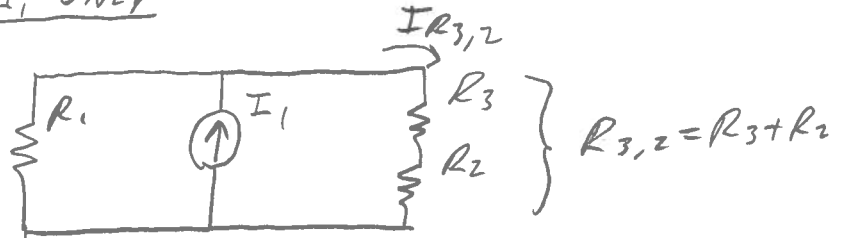

$$I_{R_{3,2}} = I_1 \left( \frac{R_1 // R_{3,2}}{R_{3,2}} \right)$$

$$= 50 \text{ mA} \left( \frac{307.6\Omega}{890\Omega} \right) = 17.279 \text{ mA}$$


LEFT TO RIGHT


$$I_{R_3}^{\text{TOTAL}} = (17.279 \text{ mA} - 7.353 \text{ mA})$$

LEFT T. RIGHT

OR
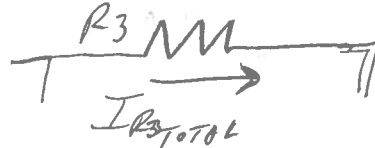
$$I_{R_3}^{\text{TOTAL}} = 9.93 \text{ mA}$$




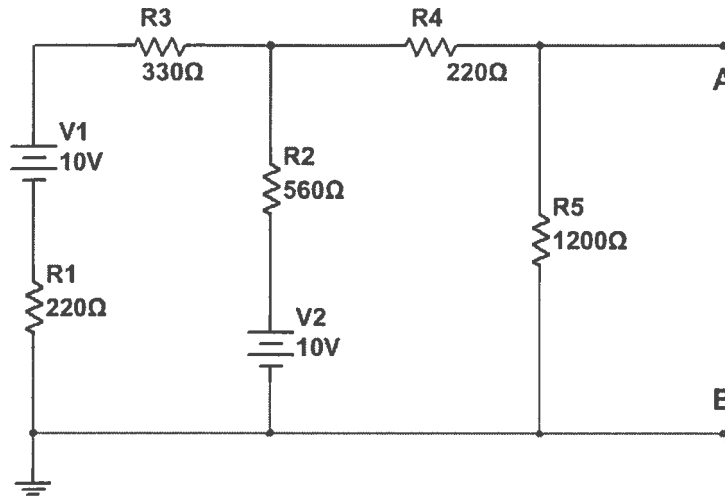

**Find:**

- 1) The Thevenin equivalent resistance ( $R_{TH}$ ) looking back into the circuit from terminals A-B (the load has already been removed)
- 2) The Thevenin equivalent voltage ( $V_{TH}$ ) looking back into the circuit from terminals A-B (the load has already been removed)
- 3) The power dissipated by a 100 Ohm resistor placed between terminals A-B

(1)

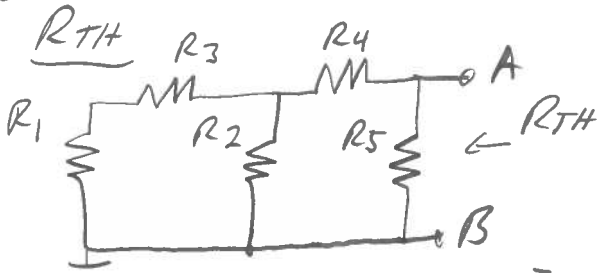


$$R_{TH} = [(R_1 + R_3) \parallel R_2] + R_4 \parallel R_5$$

$$= [(550\Omega \parallel 560\Omega) + 220\Omega] \parallel 1200\Omega$$

$$= 497.5\Omega \parallel 1200\Omega$$

$$R_{TH} = 351.7\Omega$$

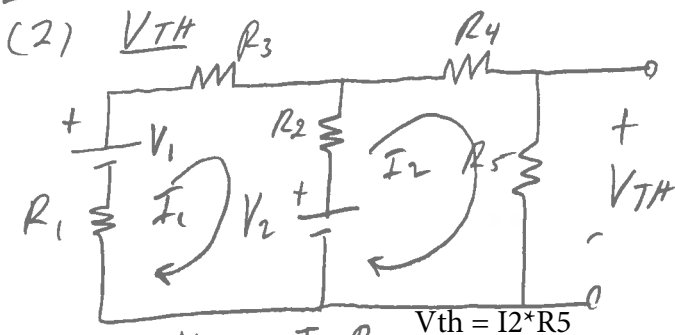

Loop 1

$$-I_1 R_1 + V_1 - I_1 R_3 - I_1 R_2 + I_2 R_2 - V_2 = 0$$

$$-1110 I_1 + 560 I_2 = 0 \quad (1)$$

Loop 2


$$V_2 - I_2 R_2 + I_1 R_2 - I_2 R_4 - I_2 R_5 = 0$$

$$560 I_1 - 1980 I_2 = -10 \quad (2)$$

YIELDS:  $I_1 = 2.97 \text{ mA}$

$$I_2 = 5.89 \text{ mA}$$

$$\therefore V_{TH} = 7.07 \text{ V}$$

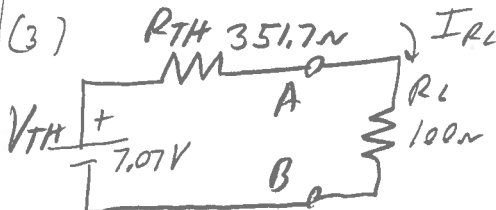

$$I_{R_L} = \frac{V_{TH}}{R_{TH} + R_L} = 15.65 \text{ mA}$$

$$\therefore P_{R_L} = (I_{R_L})^2 \cdot R_L = 24.5 \text{ mW}$$