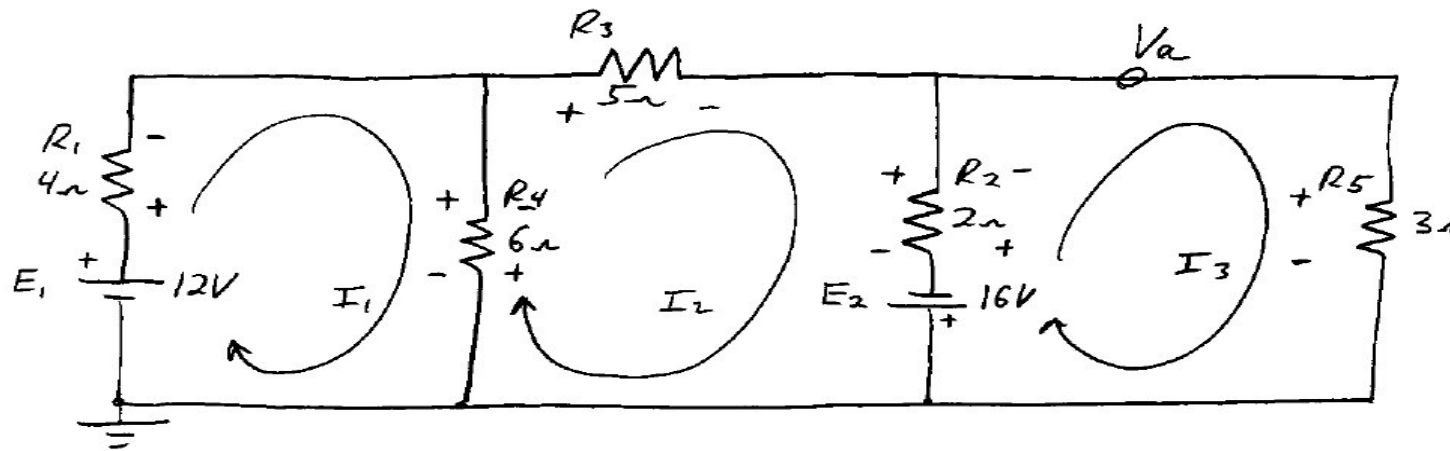


REDRAWN (PLANAR NETWORK)



$$\begin{aligned} \text{Loop 1 : } E_1 - I_1 R_1 - I_1 R_4 + I_2 R_4 &= 0 \\ -I_1 (R_1 + R_4) + I_2 R_4 &= -E_1 \\ I_1 (R_1 + R_4) - I_2 R_4 + 0 I_3 &= E_1 \rightarrow 10 I_1 - 6 I_2 + 0 I_3 = 12 \quad (1) \end{aligned}$$

$$\begin{aligned} \text{Loop 2 : } I_1 R_4 - I_2 R_4 - I_2 R_3 - I_2 R_2 + I_3 R_2 + E_2 &= 0 \\ I_1 R_4 - I_2 (R_2 + R_3 + R_4) + I_3 R_2 &= -E_2 \\ -I_1 R_4 + I_2 (R_2 + R_3 + R_4) - I_3 R_2 &= 16 \rightarrow -6 I_1 + 13 I_2 - 2 I_3 = 16 \quad (2) \end{aligned}$$

$$\begin{aligned} \text{Loop 3 : } -E_2 + I_2 R_2 - I_3 R_2 - I_3 R_5 &= 0 \\ I_2 R_2 - I_3 (R_2 + R_5) &= E_2 \\ 0 I_1 - R_2 I_2 + (R_2 + R_5) I_3 &= -E_2 \rightarrow 0 I_1 - 2 I_2 + 5 I_3 = -16 \quad (3) \end{aligned}$$

$$\begin{aligned} \text{Solve : } 10 I_1 - 6 I_2 + 0 I_3 &= 12 \\ -6 I_1 + 13 I_2 - 2 I_3 &= 16 \\ 0 I_1 - 2 I_2 + 5 I_3 &= -16 \end{aligned}$$

$$\begin{aligned} I_1 &= 2.372 \text{ A} \\ I_2 &= 1.954 \text{ A} \\ I_3 &= -2.419 \text{ A} \end{aligned}$$

$$V_a = (I_3)(R_5) = \boxed{-7.26 \text{ V}}$$