

8.9 NODAL ANALYSIS (GENERAL APPROACH)

- USES KCL IN AN ORGANIZED MANNER TO SOLVE CIRCUITS PROBLEMS.

PROCEDURE: (1) DETERMINE THE # OF NODES

- (2) CHOOSE A REFERENCE NODE, LABEL IT NODE 0. OFTEN WE CHOOSE GROUND AS NODE 0.

LABEL ALL OTHER NODES V_1, V_2, \dots, V_N


- (3) APPLY KCL AT EACH NODE (EXCEPT NODE 0). ASSUME UNKNOWN CURRENTS LEAVE THE NODE IN EACH CASE.

- (4) SOLVE THE EQUATIONS FOR THE NODE VOLTAGES.

RECALL

$$\text{KCL: } \sum (\text{CURRENTS ENTERING}) = \sum (\text{CURRENTS LEAVING})$$

(EXAMPLE)

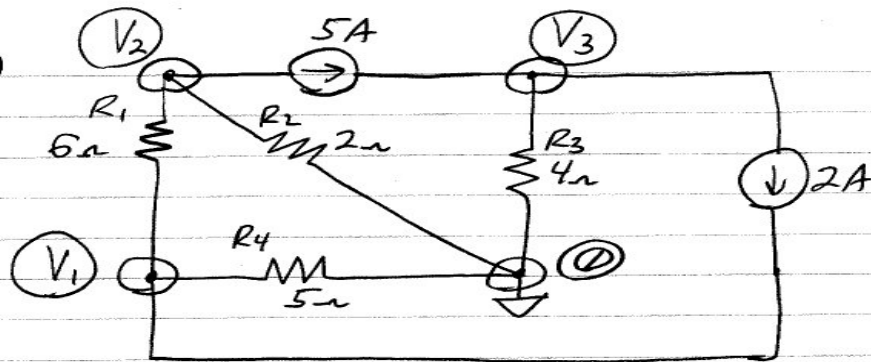


- 4 NODES
- LABELED 0, V_1, V_2, V_3

Apply KCL AT EACH NODE ?

NODE

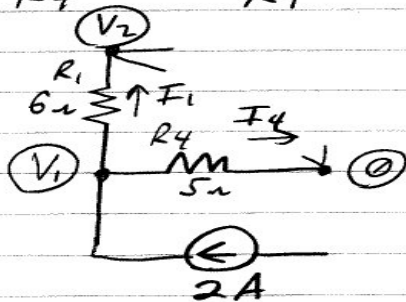(1)

$$2 = \frac{V_1}{R_4} + \frac{V_1 - V_2}{R_1}$$



2A INTO NODE $V_1 =$

$$(I_1 + I_4)$$

SUM OF CURRENTS LEAVING

$$I_1 = \frac{V_1 - V_2}{R_1}$$

$$+ I_4 = \frac{V_1 - 0}{R_4} = \frac{V_1}{R_4}$$

$$\therefore 2 = \frac{V_1 - V_2}{R_1} + \frac{V_1}{R_4}$$

$$2 = \frac{V_1}{5} + \frac{V_1}{6} - \frac{V_2}{6} \Rightarrow 2 = 0.367V_1 - 0.167V_2 \quad (1)$$

NODE

(2)

$$-0 = 5 + \frac{V_2}{R_2} + \frac{V_2 - V_1}{R_1} \Rightarrow -5 = -\frac{V_1}{6} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$-5 = -0.167V_1 + 0.667V_2 \quad (2)$$

NODE

(3)

$$5 = 2 + \frac{V_3}{R_3} \Rightarrow$$

$$3 = \frac{V_3}{4}$$

$$3 = 0.25V_3 \quad (3)$$

SOLVE EQ (1) \rightarrow (3) :

$$2 = 0.367 V_1 - 0.167 V_2 + 0 V_3 \quad (1)$$

$$-5 = -0.167 V_1 + 0.667 V_2 + 0 V_3 \quad (2)$$

$$3 = 0 V_1 + 0 V_2 + 0.25 V_3 \quad (3)$$

$$V_1 = \frac{\begin{vmatrix} 2 & -0.167 & 0 \\ -5 & 0.667 & 0 \\ 3 & 0 & 0.25 \end{vmatrix}}{\begin{vmatrix} 0.367 & -0.167 & 0 \\ -0.167 & 0.667 & 0 \\ 0 & 0 & 0.25 \end{vmatrix}} \quad \begin{matrix} \sim \text{NUM} \\ \sim \text{DEN} \end{matrix}$$

$$\begin{matrix} \text{NUM} \\ \rightarrow \end{matrix} \begin{vmatrix} 2 & -0.167 & 0 \\ -5 & 0.667 & 0 \\ 3 & 0 & 0.25 \end{vmatrix} = 2 \begin{vmatrix} 0.667 & 0 \\ 0 & 0.25 \end{vmatrix} - (-0.167) \begin{vmatrix} -5 & 0 \\ 3 & 0.25 \end{vmatrix} + (0) \begin{vmatrix} -5 & 0.667 \\ 3 & 0 \end{vmatrix}$$

$$= 2 [(0.667)(0.25) - (0)(0)] + 0.167 [(-5)(0.25) - (0)(3)] + 0 [(-5)(0) - (0.667)(3)]$$


$$= 0.3335 - 0.2088 + 0 = \underline{0.1248}$$

$$\text{DEN} \rightarrow 54.23 \times 10^{-3}$$

$$V_1 = \frac{\text{NUM}}{\text{DEN}} = \boxed{2.30 \text{ V}}$$

$$\text{SIMILARLY : } \boxed{\begin{matrix} V_2 = -6.92 \text{ V} \\ V_3 = 12 \text{ V} \end{matrix}}$$

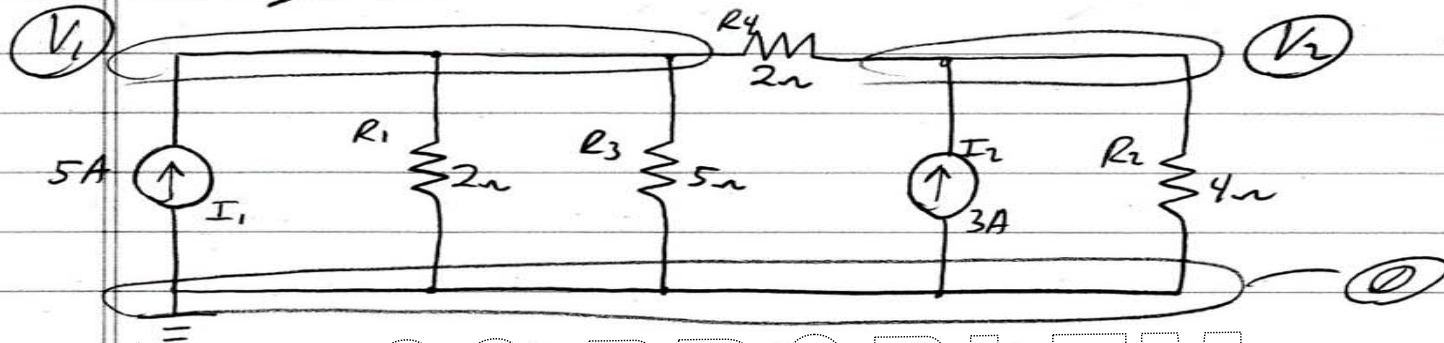Write the nodal equations & using determinants, solve for the node voltages.



IN CLASS PROBLEM

IN CLASS PROBLEM

IN CLASS PROBLEM

IN CLASS PROBLEM