
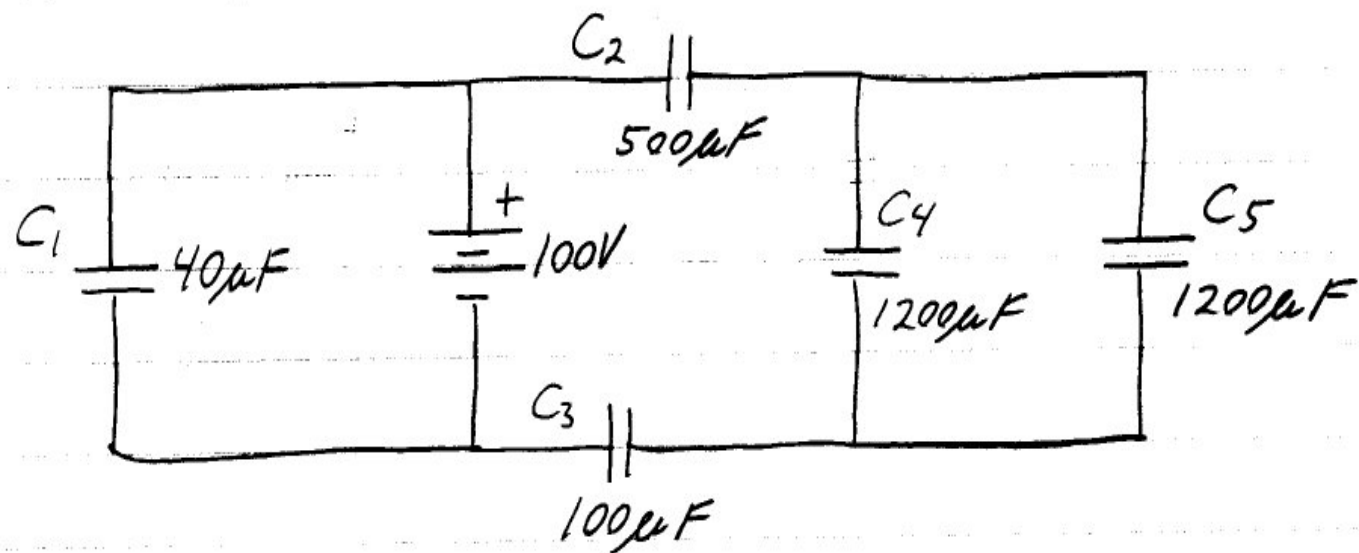


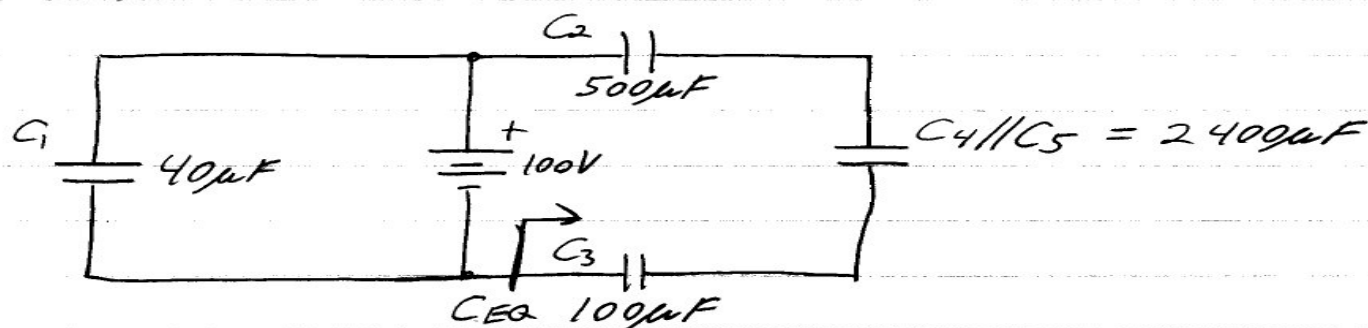CHARGE & VOLTAGE (EXAMPLE 2) FIND THE VOLTAGE
ACROSS & CHARGE ON EACH CAPACITOR:



REDRAW :



USE $Q = CV$:

For $C_1 \rightarrow Q_1 = (40\mu F)(100V) = \boxed{4mC}$

$Q_2 = Q_3 = (Q_4 + Q_5)$

$$C_{eq} = \frac{1}{\frac{1}{500\mu F} + \frac{1}{100\mu F} + \frac{1}{2400\mu F}} = \underline{80.54\mu F}$$

For $C_{eq} \rightarrow Q_{Ceq} = (80.54\mu F)(100V) = \underline{8.054mC}$

$\therefore Q_2 = \boxed{8.054mC}$
 $V_2 = Q_2 / C_2 = \frac{8.054mC}{500\mu F} = \boxed{16.11V}$


$Q_3 = \boxed{8.054mC}$
 $V_3 = Q_3 / C_3 = \frac{8.054mC}{100\mu F} = \boxed{80.54V}$

$(Q_4 + Q_5) = 8.054mC$
 $\therefore V_4 = V_5 = \frac{8.054mC}{2400\mu F} = \boxed{3.36V}$

$Q_4 = Q_5 = (1200\mu F)(3.36V) = \boxed{4.027mC}$

KVL ✓

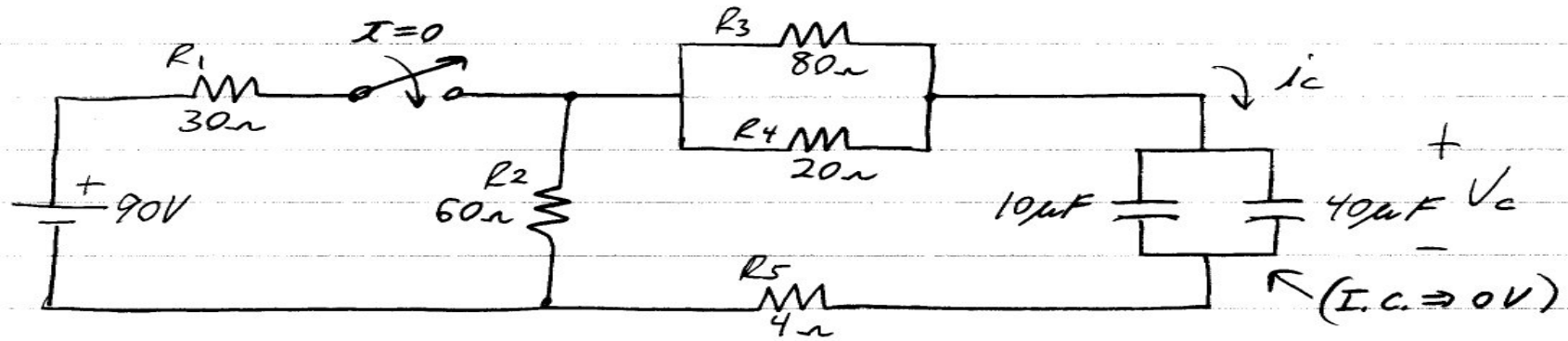
(EXAMPLE 3) Find $V_c + Q$ at $t = 1\text{ms}$
 + $t = 1\text{ hour}$:



THEVENIN EQUIVALENT SEEN BY $C_{EQ} = 50\mu\text{F}$?
 (For $t \geq 0$)

$$R_{TH} = (R_1 || R_2) + (R_3 || R_4) + R_5$$
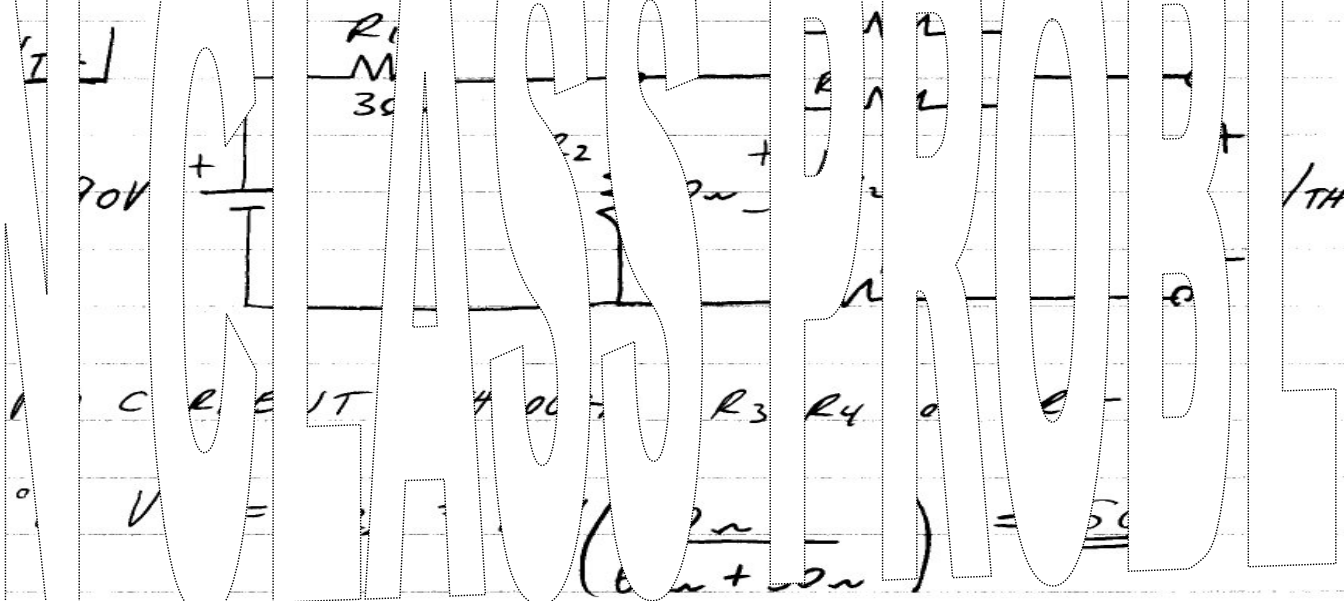
$$= 20\Omega + 16\Omega + 4\Omega = 40\Omega$$



IN CLASS PROBLEM

IN CLASS PROBLEM

FIND $V_C(x)$


KVL: $V_{TH} - i_C(x) R_{TH} - V_C(x) = 0$

IN CLASS PROBLEM

IN CLASS PROBLEM

@ $t = 1 \text{ hour}$ $V_C(t) \Big|_{t \gg \tau} = \underline{60V}$

WE HAVE :

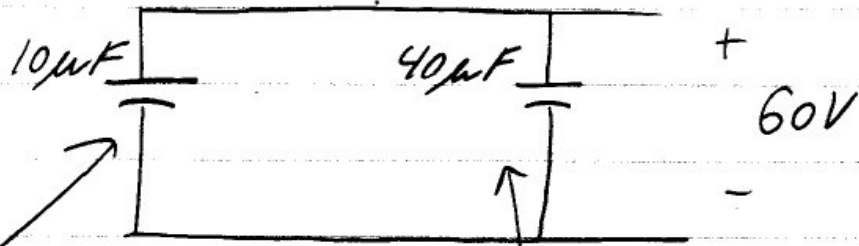

$$Q = CV$$

$$= (10\mu F)(60V)$$

$$\boxed{Q = 600\mu C}$$

$$Q = CV$$

$$= (40\mu F)(60V)$$

$$\boxed{Q = 2.4mC}$$