

Team Name: _____ Section: _____

Members Present (full names printed):

- 1) _____
- 2) _____
- 3) _____
- 4) _____

* SOLUTIONS *



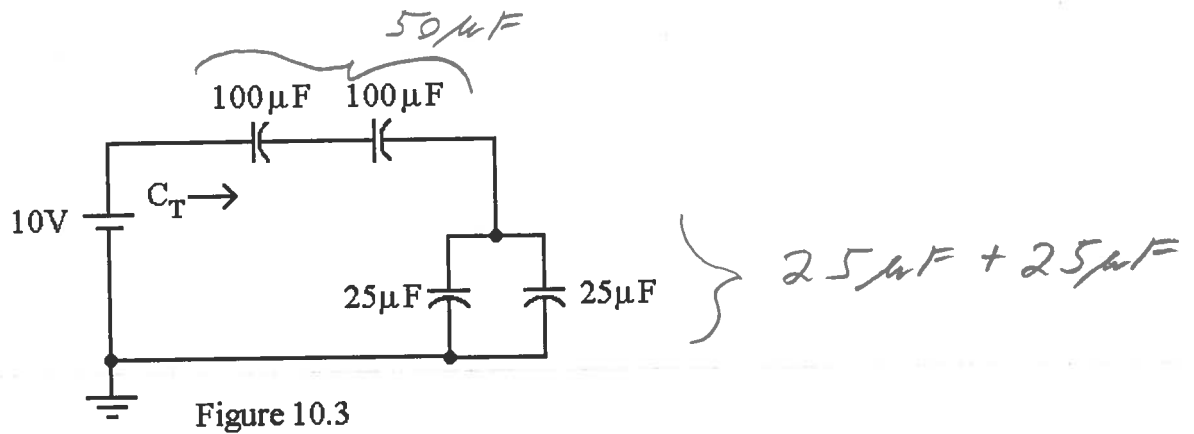


Figure 10.3

Find:

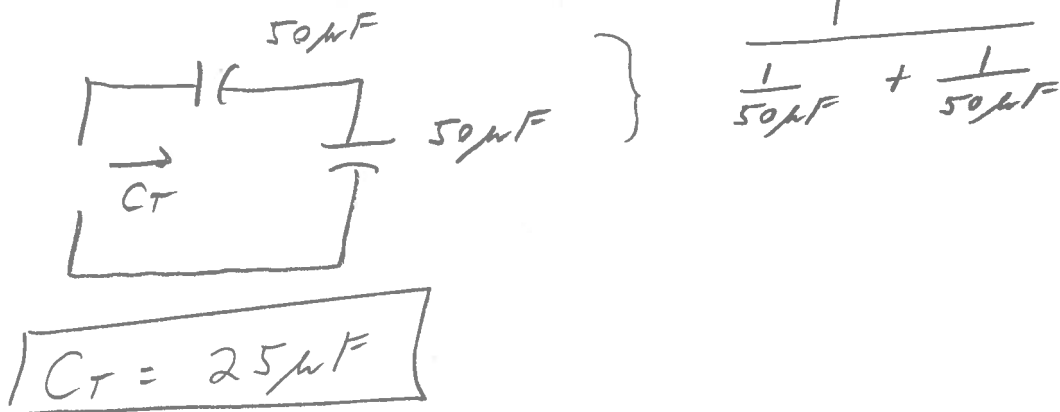- 1) C_T , the total capacitance seen by the source




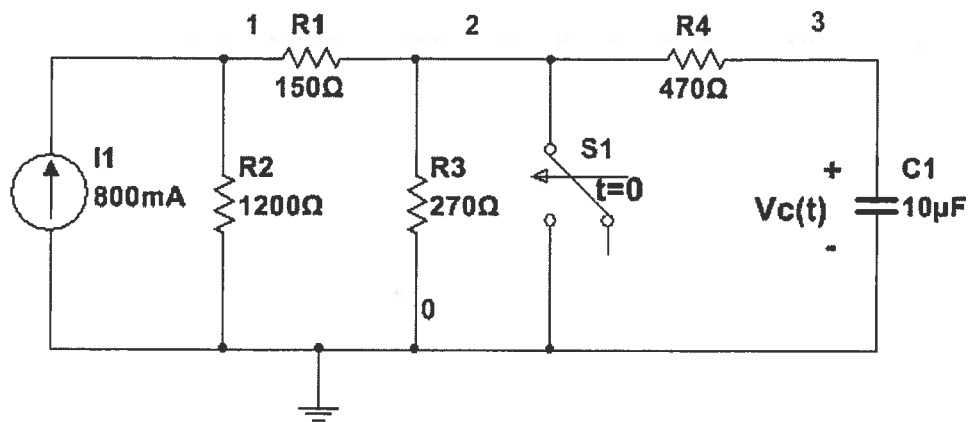

Given that switch S1 has been open for a long time BEFORE $t=0$

Find:

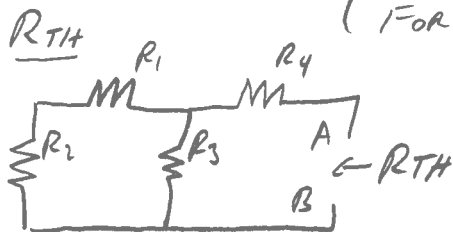- 1) $V_c(t)$ at $t=0$
- 2) The maximum current through R4 AFTER $t=0$
- 3) The time constant of the charging circuit ($t < 0$)
- 4) The time constant of the discharge circuit ($t > 0$)
- 5) $V_c(t)$ for $t > 0$
- 6) The charge on the capacitor (C1) at $t = 10\text{msec}$




(FIND THEVENIN EQUIV
FOR CHARGE PHASE)

$$R_{TH} = [(R_1 + R_2) // R_3] + R_4$$

$$= (1350\Omega // 1200\Omega) + 470\Omega$$

$$= 225\Omega + 470\Omega$$

$$R_{TH} = 695\Omega$$

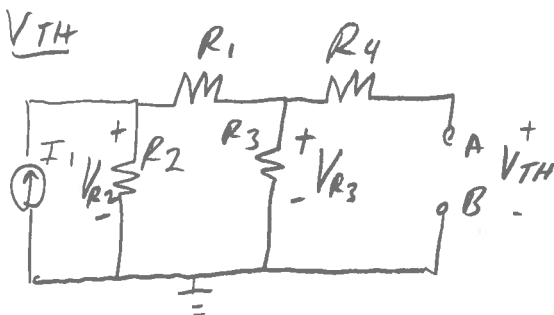

$$V_{R2} = (I_1) [(R_1 + R_3) // R_2]$$

$$= (0.8A) (420\Omega // 1200\Omega)$$

$$= (0.8A) (311.1\Omega)$$

$$V_{R2} = 248.9V$$


$$\therefore V_{R3} = V_{R2} \left(\frac{R_3}{R_3 + R_1} \right)$$

$$V_{R3} = 160.01V$$

HENCE

$$V_{TH} = 160.01V$$

HENCE, FOR $t < 0$

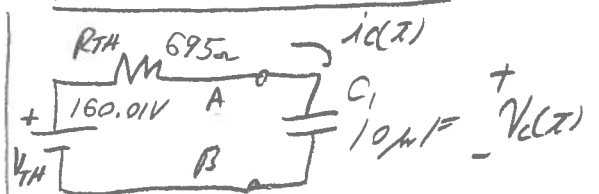

$$V_c(t) \text{ For } t \geq 5\tau = V_{TH}$$


$$\text{OR } 160.01V \quad (1)$$

$$\tau_{CH} = (R_{TH})(C_1)$$

$$= 6.95\text{ms} \quad (3)$$

@ $t = 0$

$$V_c = V_{TH} = 160.01V$$

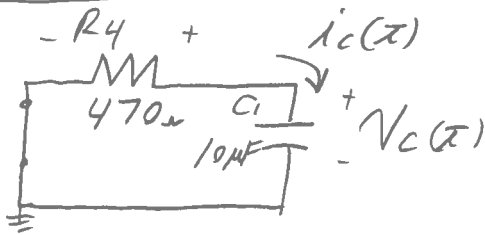DISCHARGE CIRCUIT ($t > 0$)

$$V_c(0) = 160.01V, \text{ INITIAL VALUE}$$

$$V_c(t) = 160.01 e^{-t/\tau_{015}}$$

$$\tau_{015} = (R_4)(C_1) = \boxed{4.7 \text{ ms}} \quad (4)$$

$$\therefore \text{For } t > 0, \quad -\frac{t}{4.7 \text{ ms}} \quad (5)$$

$$V_c(t) = 160.01 e^{-\frac{t}{4.7 \text{ ms}}}$$

$$i_c(t) = -\frac{V_c(t)}{R_4} = -340.4 \text{ mA } e^{-\frac{t}{4.7 \text{ ms}}}$$


$$\therefore i_{c \text{ MAX}}|_{t > 0} = \boxed{-340.4 \text{ mA}} \quad (2)$$

$$V_c(t=10 \text{ ms}) = 160.01V e^{-\frac{10 \text{ E-3 Sec}}{4.7 \text{ E-3 Sec}}} = \underline{\underline{19.06V}}$$

$$\text{BUT } Q = CV$$

$$\therefore Q = (10 \mu\text{F})(19.09V)$$
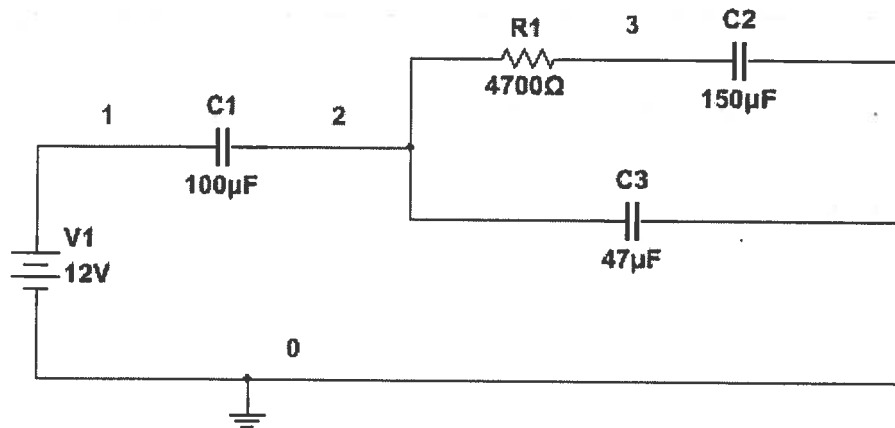
$$\boxed{Q = 190.9 \mu\text{C}} \quad (6)$$




$$Q = C \cdot V$$

Find:

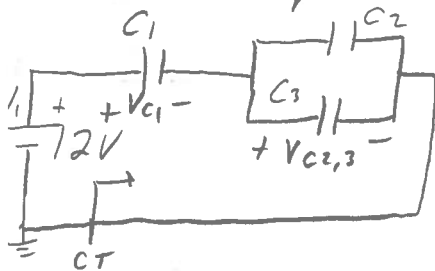- 1) The voltage across and the charge on each capacitor (steady-state)

REDRAWN IN S.S.

- NO CURRENT THROUGH R_1 ,
 \therefore NO V_{DROP} ACROSS IT



$C_T = C_2 // C_3$ COMBINED IN SERIES
 W/C

$$C_2 // C_3 = C_2 + C_3 = 197 \mu\text{F}$$

$$\therefore C_T = \frac{1}{\frac{1}{197 \mu\text{F}} + \frac{1}{100 \mu\text{F}}} = 66.33 \mu\text{F}$$

$$\text{HENCE } Q_T = C_T \cdot V = (66.33 \mu\text{F})(12\text{V}) = 795.96 \mu\text{C}$$

$$Q_{C1} = Q_T = 795.96 \mu\text{C} \quad (\text{SERIES CIRCUIT})$$

$$\therefore Q_{C1} = 796 \mu\text{C}$$

$$\therefore V_{C1} = \frac{Q_{C1}}{C_1} = 7.96\text{V}$$

$$\therefore V_{C2,3} = V_1 - V_{C1} = 4.04\text{V}, \text{ KVL}$$

$$V_{C2} = 4.04\text{V}$$

$$V_{C3} = 4.04\text{V}$$

$$Q_{C2} = C_2 \cdot V_{C2} = 606 \mu\text{C}$$

$$Q_{C3} = C_3 \cdot V_{C3} = 189.9 \mu\text{F}$$

↑
CHECK:

$$Q_T = Q_{C1} = Q_{C2} + Q_{C3}$$

$$796 \mu\text{C} = 795.9 \mu\text{C}$$

✓ (SMALL ROUNDING ERROR)