
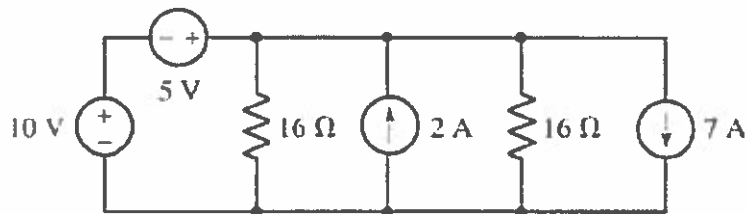


Figure 3.73

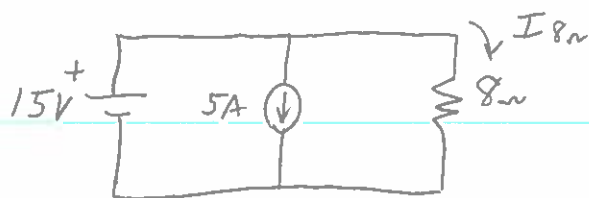

18. See Figure 3.73. What is the total power absorbed by the 16-ohm resistors?

REDRAW



$$I_{8\Omega} = \frac{15V}{8\Omega} = 1.875A$$


$$P_{8\Omega} = (I_{8\Omega})^2 \cdot (8\Omega)$$

$$= \boxed{28.13W}$$

OR, EACH RESISTOR ABSORBS

$$\boxed{14.06W}$$

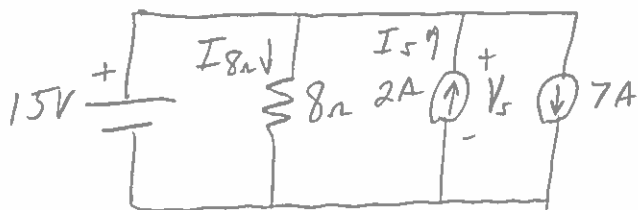$P_{\text{supplied by } 2A \text{ source?}}$




$$P_{2A \text{ supplied}} = (V_s) \cdot (I_s)$$

$$= (15V)(2A)$$

$$= \boxed{30W}$$

**Figure 3.82**

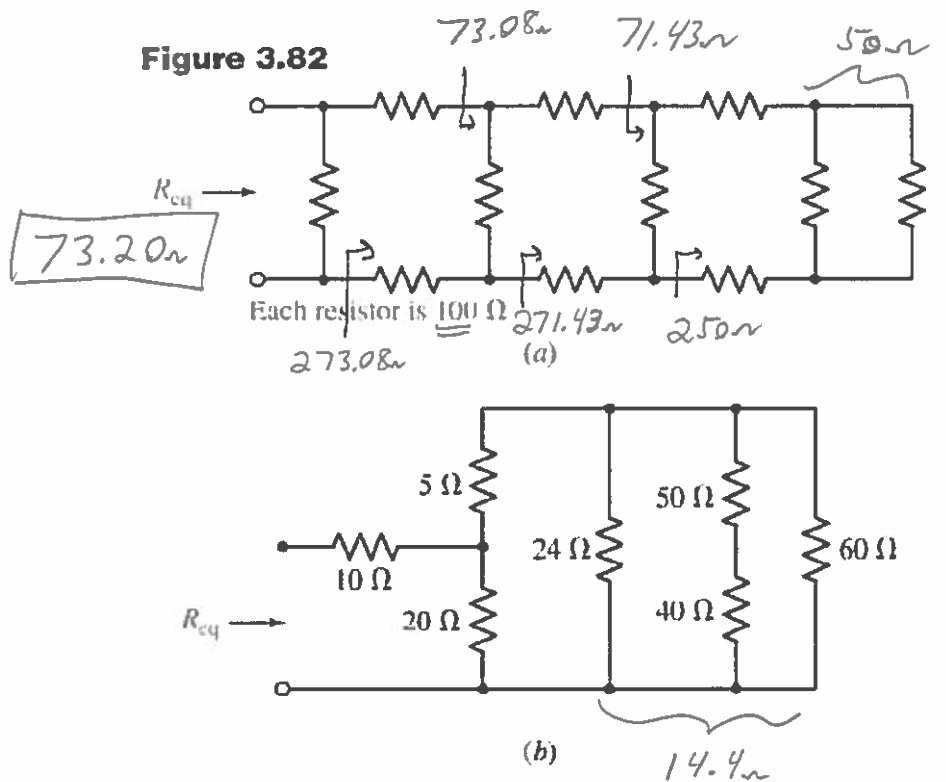

19. See Figure 3.82(a). Find  $R_{eq}$

20. See Figure 3.82(b). Find  $R_{eq}$


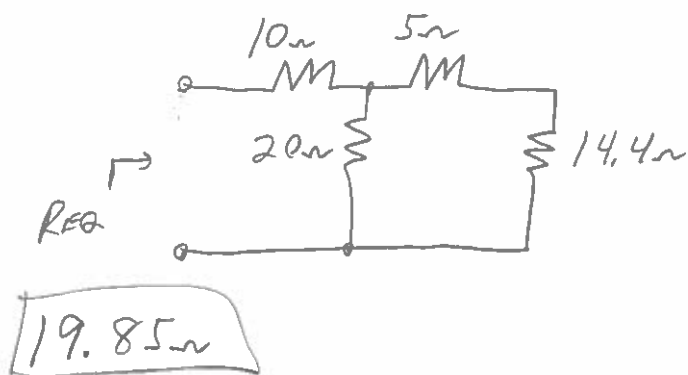



Figure 3.84

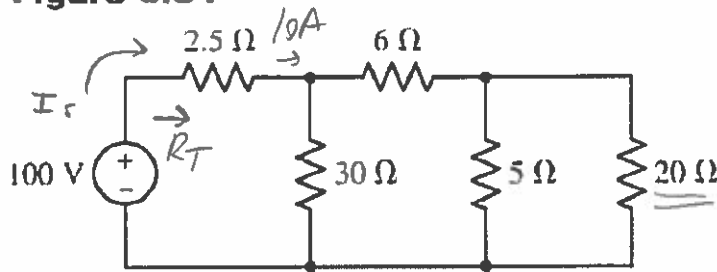

$$R_T = 10\Omega$$


$$I_S = \frac{100V}{10\Omega} = 10A$$

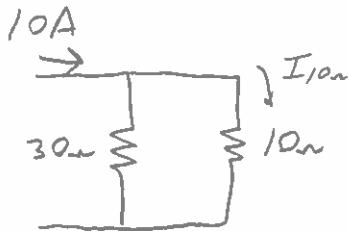21. See Figure 3.84. Find the power absorbed by the 20-ohm resistor



$$I_{10\Omega} = I_T \left( \frac{R_T}{R_x} \right)$$
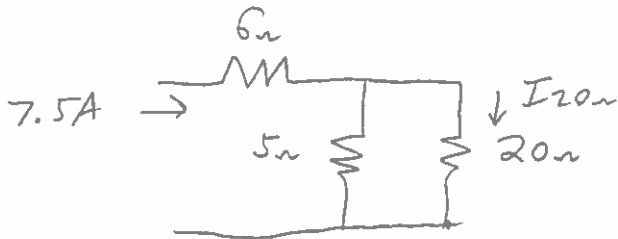
$$= 10A \left( \frac{30\Omega // 10\Omega}{10\Omega} \right) = \underline{7.5A}$$



$$I_{20\Omega} = I_T \left( \frac{R_T}{R_x} \right)$$

$$= 7.5A \left( \frac{4\Omega}{20\Omega} \right)$$

$$I_{20\Omega} = \underline{1.5A}$$


$$\therefore P_{20\Omega} = I^2 \cdot R$$

$$= (1.5A)^2 \cdot (20\Omega)$$

$$P_{20\Omega} = \boxed{45W}$$

# ALTERNATE w/ VOLTAGE DIVIDER

Figure 3.84

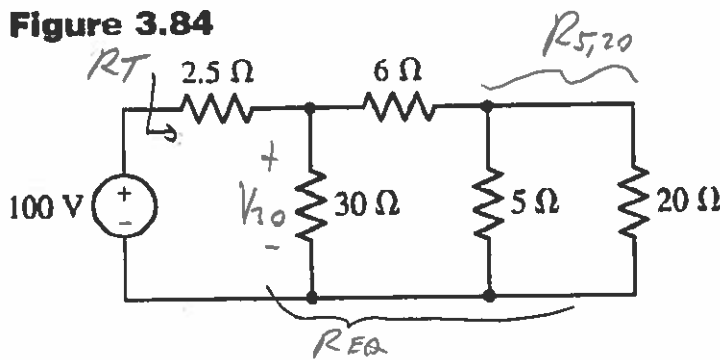


$$R_{EQ} = 7.5\Omega$$

$$\therefore R_T = 10\Omega$$


21. See Figure 3.84. Find the power absorbed by the 20-ohm resistor

USING VOLTAGE DIVIDER:

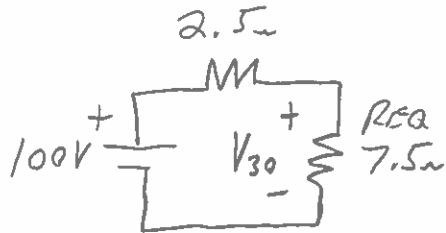

$$V_{30} = 100V \left( \frac{R_{EQ}}{R_T} \right)$$
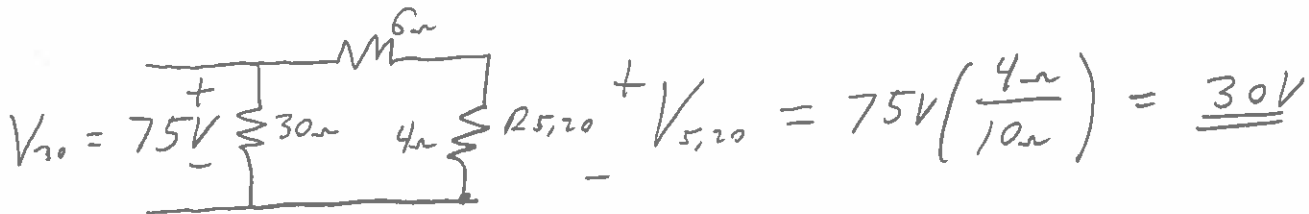
$$= 100V \left( \frac{7.5\Omega}{10\Omega} \right) = \underline{\underline{75V}}$$




$$V_{4} = 75V \left( \frac{4\Omega}{10\Omega} \right) = \underline{\underline{30V}}$$



$$P_{20\Omega} = \frac{(V_{20\Omega})^2}{20\Omega}$$

$$= \frac{(30V)^2}{20\Omega} = \boxed{45W}$$


Figure 3.92

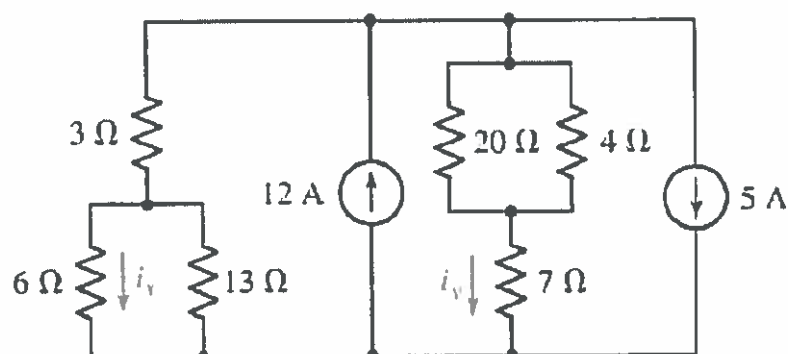

22. See Figure 3.92. Find  $i_x$

*Real*

REORAW

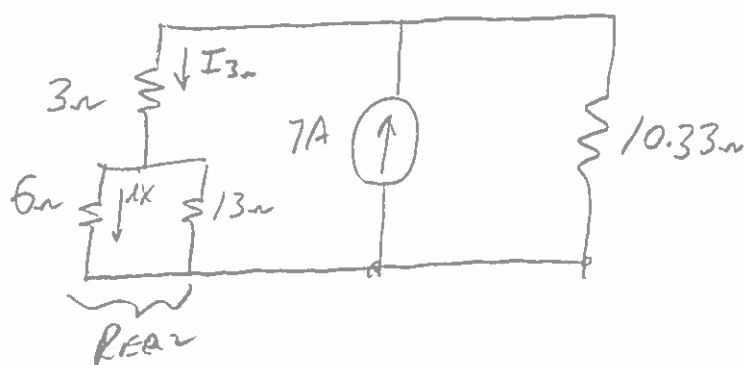

$$I_{3n} = I_T \left( \frac{R_T}{R_X} \right) \quad R_{E01} // R_{E02}$$

$$= 7A \left( \frac{4.21n}{7.105n} \right) \quad R_{E02}$$

$$I_{3n} = \underline{4.148A}$$


$$i_x = I_T \left( \frac{R_T}{R_X} \right)$$

$$= I_{3n} \left( \frac{6n // 13n}{6n} \right)$$

$$= \boxed{2.84A}$$

NODAL

ALTERNATE

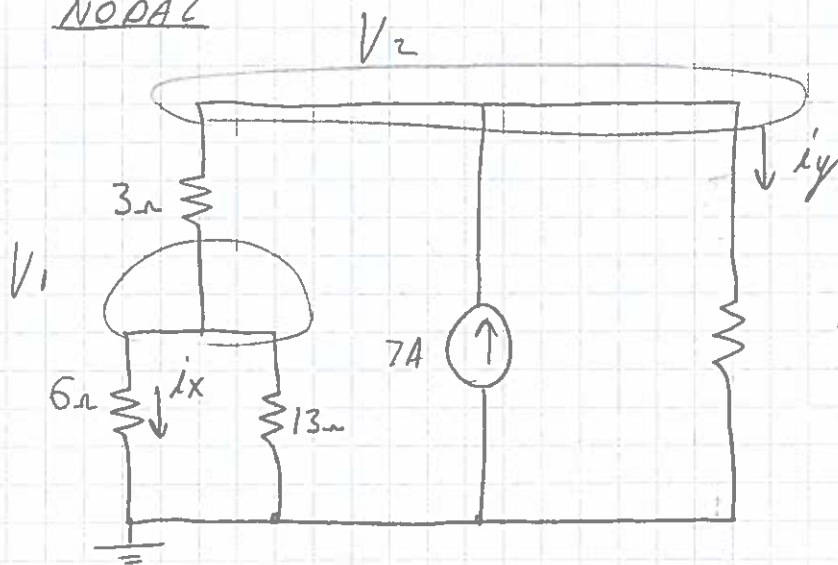

$$20 // 4 + 7 = 10.33\Omega$$

NODE ①

$$\frac{V_1 - V_2}{3} + \frac{V_1}{6} + \frac{V_1}{13} = 0$$

$$V_1 \left( \frac{1}{3} + \frac{1}{6} + \frac{1}{13} \right) - V_2 \left( \frac{1}{3} \right) = 0$$

$$0.577 V_1 - 0.333 V_2 = 0$$

(1)

NODE ②

$$\frac{V_2 - V_1}{3} + \frac{V_2}{10.33} = 7$$

$$-\frac{1}{3} V_1 + \left( \frac{1}{3} + \frac{1}{10.33} \right) V_2 = 7$$

$$-0.333 V_1 + 0.430 V_2 = 7$$

(2)

SOLVE (1) + (2)

$$V_1 = 17.03V$$


$$V_2 = 29.48V$$

$$i_x = \frac{V_1}{6\Omega} = \frac{17.03V}{6\Omega} = \boxed{2.84A}$$


$$i_y = \frac{V_2}{10.33\Omega} = \frac{29.48V}{10.33\Omega} = \boxed{2.85A}$$

$$P_{13\Omega} = \frac{V_1^2}{13\Omega} = \frac{(17.03V)^2}{13\Omega} = \boxed{22.3W}$$

THEVENIN - To FIND  $i_x$

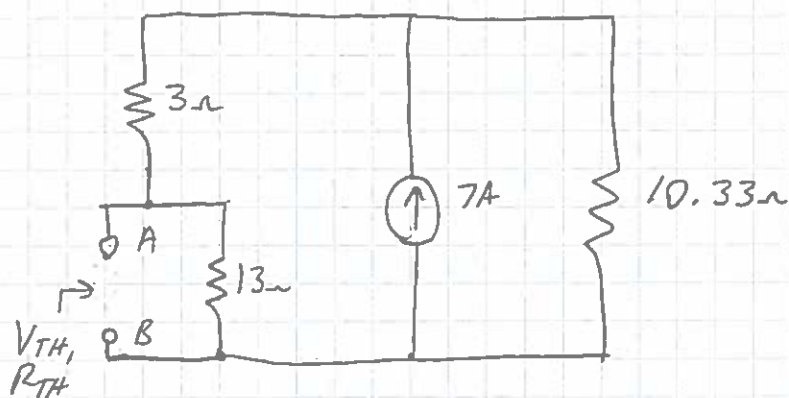


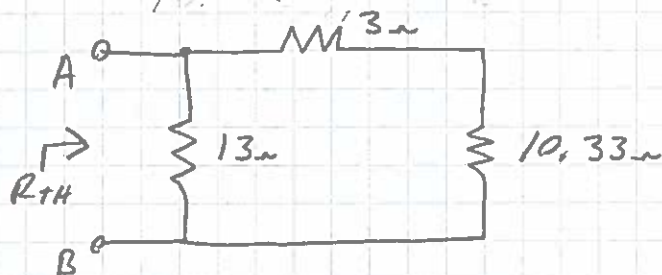R<sub>TH</sub> - o/c THE 7A SOURCE  
- FIND R<sub>AB</sub>



$$R_{TH} = 3\Omega // 10.33\Omega = \underline{\underline{6.58\Omega}}$$

V<sub>TH</sub> - FIND V<sub>AB</sub> o-c

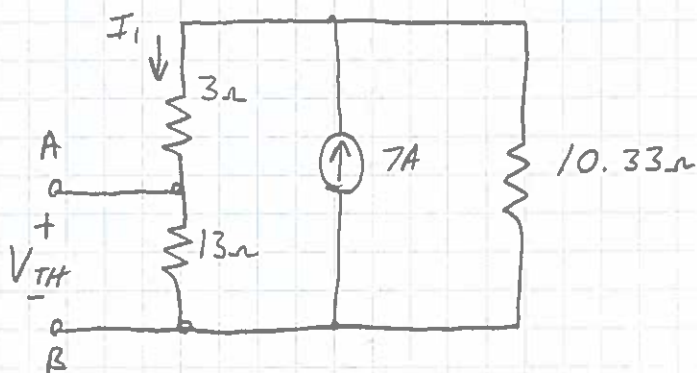

$$I_1 = I_T \frac{R_T}{R_x}$$


$$I_T = 7A$$

$$R_T = 16\Omega // 10.33\Omega = 6.28\Omega$$

$$R_x = 16\Omega$$

$$I_1 = 7A \left( \frac{6.28\Omega}{16\Omega} \right) = \underline{\underline{2.75A}}$$

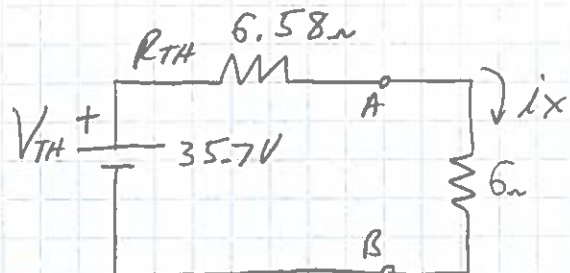
EQUICK ∴  $V_{TH} = (13\Omega)(2.75A) = \underline{\underline{35.7V}}$




$$i_x = \frac{V_{TH}}{R_T} = \frac{35.7V}{12.58\Omega}$$

$$\boxed{i_x = 2.84A}$$


NORTON - TO FIND  $i_y$

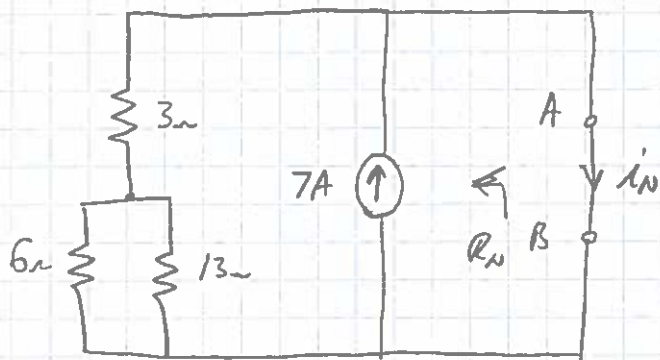


$R_N$  - o/c THE 7A SOURCE

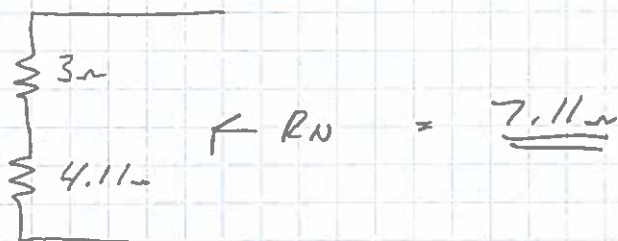

$I_N$  - FIND  $I_{AB}$  s-c

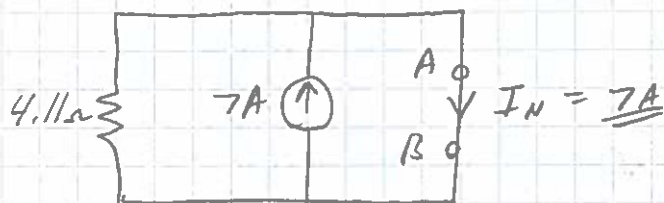

EQ. CKT

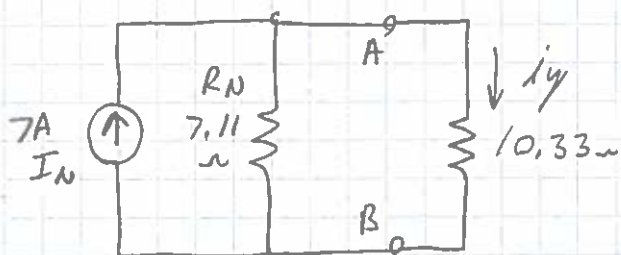

$$i_y = I_N \left( \frac{R_T}{R_x} \right)$$

$$R_T = 7.11\Omega // 10.33\Omega$$

$$R_T = 4.21\Omega$$


$$R_x = 10.33\Omega$$

$$\therefore i_y = 7A \left( \frac{4.21\Omega}{10.33\Omega} \right)$$
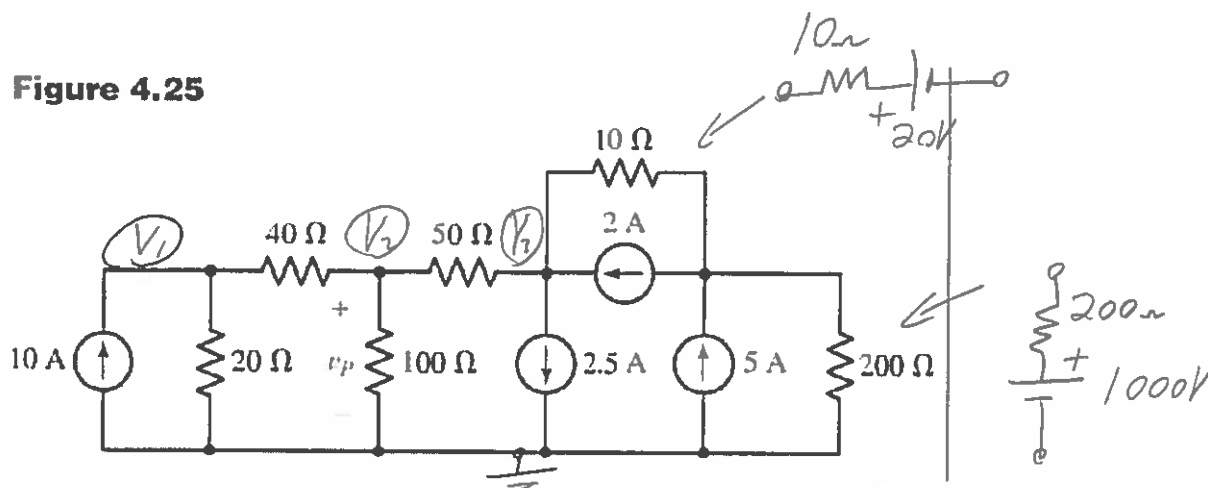
$$i_y = 2.85A$$

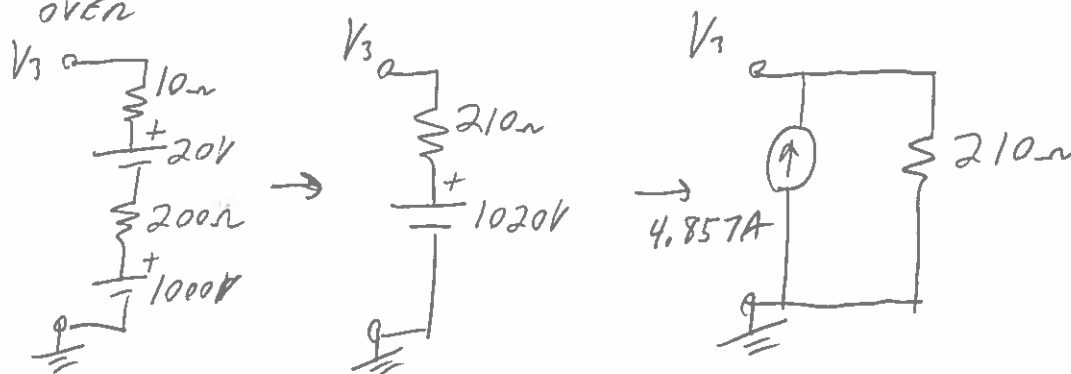


Figure 4.25



25. See Figure 4.25. Find  $v_p$  +  $I_{50\Omega}$

4-NODE PROBLEM, REDRAW AS 3-NODE PROBLEM FROM  $V_3$  OVER



$$V_1: 10 = \frac{V_1}{20} + \frac{V_1 - V_2}{40} \rightarrow 0.075V_1 - 0.025V_2 + 0V_3 = 10 \quad (1)$$

$$V_2: 0 = \frac{V_2 - V_1}{40} + \frac{V_2}{100} + \frac{V_2 - V_3}{50} \rightarrow -0.025V_1 + 0.055V_2 - 0.020V_3 = 0 \quad (2)$$

$$V_3: 4.857 = 2.5 + \frac{V_3 - V_2}{50} + \frac{V_3}{210} \rightarrow 0V_1 - 0.020V_2 + 0.02476V_3 = 2.357 \quad (3)$$

SOLVING YIELDS:

$$\begin{aligned} V_1 &= 190.6V \\ V_2 &= 171.7V \\ V_3 &= 233.8V \end{aligned}$$

$$V_p = V_2 = \boxed{171.7V}$$

$$I_{50\Omega} = \frac{V_3 - V_2}{50\Omega} = \boxed{1.24A, \leftarrow}$$

dc

## Introduction

**Conversions** 1 meter = 100 cm = 39.37 in., 1 in. = 2.54 cm,  
1 yd = 0.914 m = 3 ft, 1 mile = 5280 ft, °F = 9/5°C + 32, °C =  
5/9(°F - 32), K = 273.15 + °C      **Scientific notation**  $10^{12}$  =  
tera = T,  $10^9$  = giga = G,  $10^6$  = mega = M,  $10^3$  = kilo = k,  $10^{-3}$  =  
milli = m,  $10^{-6}$  = micro =  $\mu$ ,  $10^{-9}$  = nano = n,  $10^{-12}$  = pico = p  
**Powers of ten**  $1/10^n = 10^{-n}$ ,  $1/10^{-n} = 10^n$ ,  $(10^n)(10^m) = 10^{n+m}$ ,  
 $10^n/10^m = 10^{n-m}$ ,  $(10^n)^m = 10^{nm}$

## Voltage and Current

**Coulomb's law**  $F = kQ_1Q_2/r^2$ ,  $k = 9 \times 10^9 \text{ N} \cdot \text{m}^2/\text{C}^2$ ,  
 $Q$  = coulombs (C),  $r$  = meters (m)      **Current**  $I = Q/t$  (amperes),  
 $t$  = seconds (s),  $Q_e = 1.6 \times 10^{-19} \text{ C}$       **Voltage**  $V = W/Q$  (volts),  
 $W$  = joules (J)

## Resistance

**Circular wire**  $R = \rho l/A$  (ohms),  $\rho$  = resistivity,  $l$  = feet,  
 $A_{\text{CM}} = (d_{\text{mils}})^2$ ,  $\rho(\text{Cu}) = 10.37$       **Metric units**  $l$  = cm,  $A$  =  $\text{cm}^2$ ,  
 $\rho(\text{Cu}) = 1.724 \times 10^{-6}$  ohm-cm      **Temperature**  $(|T_i| + T_1)/R_1 =$   
 $(|T_i| + T_2)/R_2$ ,  $R_1 = R_{20}[1 + \alpha_{20}(T_1 - 20^\circ\text{C})]$ ,  $\alpha_{20}(\text{Cu}) = 0.00393$   
**Color code** Bands 1-3: 0 = black, 1 = brown, 2 = red, 3 = orange,  
4 = yellow, 5 = green, 6 = blue, 7 = violet, 8 = gray, 9 = white,  
Band 3: 0.1 = gold, 0.01 = silver, Band 4: 5% = gold, 10% = silver,  
20% = no band, Band 5: 1% = brown, 0.1% = red, 0.01% = orange,  
0.001% = yellow      **Conductance**  $G = 1/R$  siemens (S)

## Ohm's Law, Power, and Energy

**Ohm's law**  $I = E/R$ ,  $E = IR$ ,  $R = E/I$       **Power**  $P = W/t =$   
 $VI = I^2R = V^2/R$  (watts), 1 hp = 746 W  
**Efficiency**  $\eta\% = (P_o/P_i) \times 100\%$ ,  $\eta_T = \eta_1 \cdot \eta_2 \cdot \eta_3 \cdots \eta_n$   
**Energy**  $W = Pt$ ,  $W(\text{kWh}) = [P(\text{W}) \cdot t(\text{h})]/1000$

## Series Circuits

$R_T = R_1 + R_2 + R_3 + \cdots + R_N$ ,  $R_T = NR$ ,  $I = E/R_T$ ,  $V = IR$   
**Kirchhoff's voltage law**  $\sum_{\text{c}} V = 0$ ,  $\sum_{\text{c}} V_{\text{rises}} = \sum_{\text{c}} V_{\text{drops}}$   
**Voltage divider rule**  $V_x = R_x E/R_T$

## Parallel dc Circuits

$R_T = 1/(1/R_1 + 1/R_2 + 1/R_3 + \cdots + 1/R_N)$ ,  $R_T = R/N$ ,  
 $R_T = R_1 R_2 / (R_1 + R_2)$ ,  $I = EG_T = E/R_T$   
**Kirchhoff's current law**  $\sum I_{\text{entering}} = \sum I_{\text{leaving}}$   
**Current divider rule**  $I_x = (R_T/R_x)I$ , (Two parallel elements):  
 $I_1 = R_2 I / (R_1 + R_2)$ ,  $I_2 = R_1 I / (R_1 + R_2)$

## Series-Parallel Circuits

**Potentiometer loading**  $R_L \gg R_T$   
**Ammeter**  $R_{\text{shunt}} = R_m I_{\text{CS}} / (I_{\text{max}} - I_{\text{CS}})$   
**Voltmeter**  $R_{\text{series}} = (V_{\text{max}} - V_{\text{VS}}) / I_{\text{CS}}$   
**Ohmmeter**  $R_s = (E/I_{\text{CS}}) - R_m - \text{zero-adjust}/2$

## Methods of Analysis and Selected Topics (dc)

**Source conversions**  $E = IR_p$ ,  $R_s = R_p$ ,  $I = E/R_s$

**Determinants**  $D = \begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix} = a_1 b_2 - a_2 b_1$

**Bridge networks**  $R_1/R_3 = R_2/R_4$        **$\Delta$ -Y conversions**  $R' =$   
 $R_A + R_B + R_C$ ,  $R_3 = R_A R_B / R'$ ,  $R_2 = R_A R_C / R'$ ,  $R_1 = R_B R_C / R'$ ,  $R_Y = R_{\Delta}/3$   
**Y- $\Delta$  conversions**  $R' = R_1 R_2 + R_1 R_3 + R_2 R_3$ ,  $R_C = R' / R_3$ ,  $R_B = R' / R_2$ ,  
 $R_A = R' / R_1$ ,  $R_{\Delta} = 3R_Y$

## Network Theorems

**Superposition** Voltage sources (short-circuit equivalent), current  
sources (open-circuit equivalent)  
**Thévenin's Theorem**  $R_{Th}$ : (all sources to zero),  $E_{Th}$ : (open-circuit  
terminal voltage)  
**Maximum power transfer theorem**  $R_L = R_{Th} = R_N$ ,  $P_{\text{max}} =$   
 $E_{Th}^2 / 4R_{Th} = I_{N}^2 R_N / 4$

## Capacitors

**Capacitance**  $C = Q/V = \epsilon A/d = 8.85 \times 10^{-12} \epsilon_r A/d$  farads (F),  
 $C = \epsilon_r C_o$       **Electric field strength**  $\mathcal{E} = V/d = Q/\epsilon A$  (volts/meter)  
**Transients** (charging)  $i_C = (E/R)e^{-t/\tau}$ ,  $\tau = RC$ ,  $v_C = E(1 - e^{-t/\tau})$ ,  
(discharge)  $v_C = Ee^{-t/\tau}$ ,  $i_C = (E/R)e^{-t/\tau}$        $i_C$   $i_{C_{\text{av}}} = C(\Delta v_C / \Delta t)$   
**Series**  $Q_T = Q_1 = Q_2 = Q_3$ ,  $1/C_T = (1/C_1) + (1/C_2) + (1/C_3) + \cdots +$   
 $(1/C_N)$ ,  $C_T = C_1 C_2 / (C_1 + C_2)$       **Parallel**  $Q_T = Q_1 + Q_2 + Q_3$ ,  
 $C_T = C_1 + C_2 + C_3$       **Energy**  $W_C = (1/2)CV^2$

## Inductors

**Self-inductance**  $L = N^2 \mu A / l$  (henries),  $L = \mu_r L_o$   
**Induced voltage**  $e_{L_{\text{av}}} = L(\Delta i / \Delta t)$       **Transients** (storage)  $i_L =$   
 $I_m(1 - e^{-t/\tau})$ ,  $I_m = E/R$ ,  $\tau = L/R$ ,  $v_L = Ee^{-t/\tau}$  (decay),  $v_L =$   
 $[1 + (R_2/R_1)]Ee^{-t/\tau'}$ ,  $\tau' = L/(R_1 + R_2)$ ,  $i_L = I_m e^{-t/\tau}$ ,  $I_m = E/R_1$   
**Series**  $L_T = L_1 + L_2 + L_3 + \cdots + L_N$       **Parallel**  $1/L_T = (1/L_1) +$   
 $(1/L_2) + (1/L_3) + \cdots + (1/L_N)$ ,  $L_T = L_1 L_2 / (L_1 + L_2)$   
**Energy**  $W_L = 1/2(LI^2)$

## Magnetic Circuits

**Flux density**  $B = \Phi/A$  (webers/m<sup>2</sup>)      **Permeability**  $\mu = \mu_r \mu_o$  (Wb/A · m)  
**Reluctance**  $\mathcal{R} = l/\mu A$  (rels)      **Ohm's law**  $\Phi = \mathcal{F}/\mathcal{R}$  (webers)  
**Magnetomotive force**  $\mathcal{F} = NI$  (ampere-turns)      **Magnetizing**  
**force**  $H = \mathcal{F}/l = NI/l$       **Ampère's circuital law**  $\sum_{\text{c}} \mathcal{F} = 0$   
**Flux**  $\sum \Phi_{\text{entering}} = \sum \Phi_{\text{leaving}}$       **Air gap**  $H_g = 7.96 \times 10^5 B_g$

## Greek Alphabet

Letter	Capital	Lowercase	Letter	Capital	Lowercase
Alpha	A	$\alpha$	Nu	N	$\nu$
Beta	B	$\beta$	Xi	$\Xi$	$\xi$
Gamma	$\Gamma$	$\gamma$	Omicron	O	$o$
Delta	$\Delta$	$\delta$	Pi	$\Pi$	$\pi$
Epsilon	E	$\epsilon$	Rho	P	$\rho$
Zeta	Z	$\zeta$	Sigma	$\Sigma$	$\sigma$
Eta	H	$\eta$	Tau	T	$\tau$
Theta	$\Theta$	$\theta$	Upsilon	$\Upsilon$	$\upsilon$
Iota	I	$\iota$	Phi	$\Phi$	$\phi$
Kappa	K	$\kappa$	Chi	X	$\chi$
Lambda	$\Lambda$	$\lambda$	Psi	$\Psi$	$\psi$
Mu	M	$\mu$	Omega	$\Omega$	$\omega$

## Prefixes

Multiplication Factors	SI Prefix	SI Symbol
1 000 000 000 000 000 000 = $10^{18}$	exa	E
1 000 000 000 000 000 = $10^{15}$	peta	P
1 000 000 000 000 = $10^{12}$	tera	T
1 000 000 000 = $10^9$	giga	G
1 000 000 = $10^6$	mega	M
1 000 = $10^3$	kilo	k
0.001 = $10^{-3}$	milli	m
0.000 001 = $10^{-6}$	micro	$\mu$
0.000 000 001 = $10^{-9}$	nano	n
0.000 000 000 001 = $10^{-12}$	pico	p
0.000 000 000 000 001 = $10^{-15}$	femto	f
0.000 000 000 000 000 001 = $10^{-18}$	atto	a