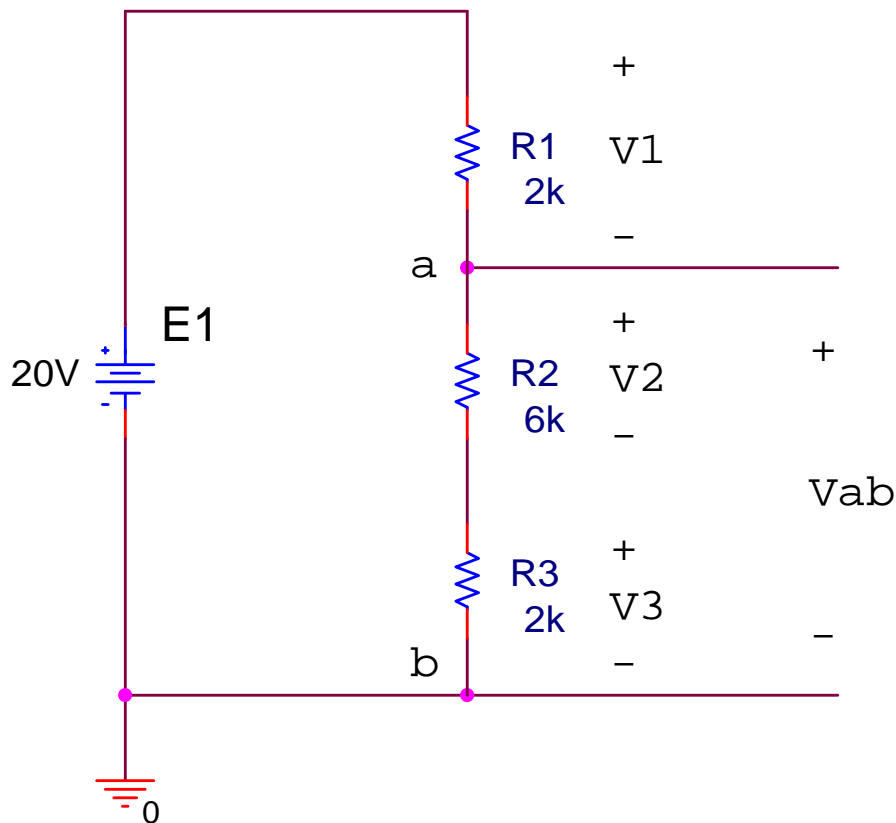


Voltage Divider Rule

- The voltage across resistive elements in a series circuit will divide as the magnitude of resistance levels
 - Series: Same “I”
 - More “R” => More “V”

Voltage Divider Rule

■ Example – Find V_1 , V_2 , V_3 , V_{ab}



$$I_1 = \frac{20V}{R_T} = \frac{20V}{10k\Omega} = 2\text{mA}$$

Leaving E1


$$V_1 = V_3 = 2\text{mA} \cdot 2k\Omega = 4V$$

$$V_2 = 2\text{mA} \cdot 6k\Omega = 12V$$

$$V_{ab} = V_2 + V_3 = 16V$$

Voltage Divider Rule

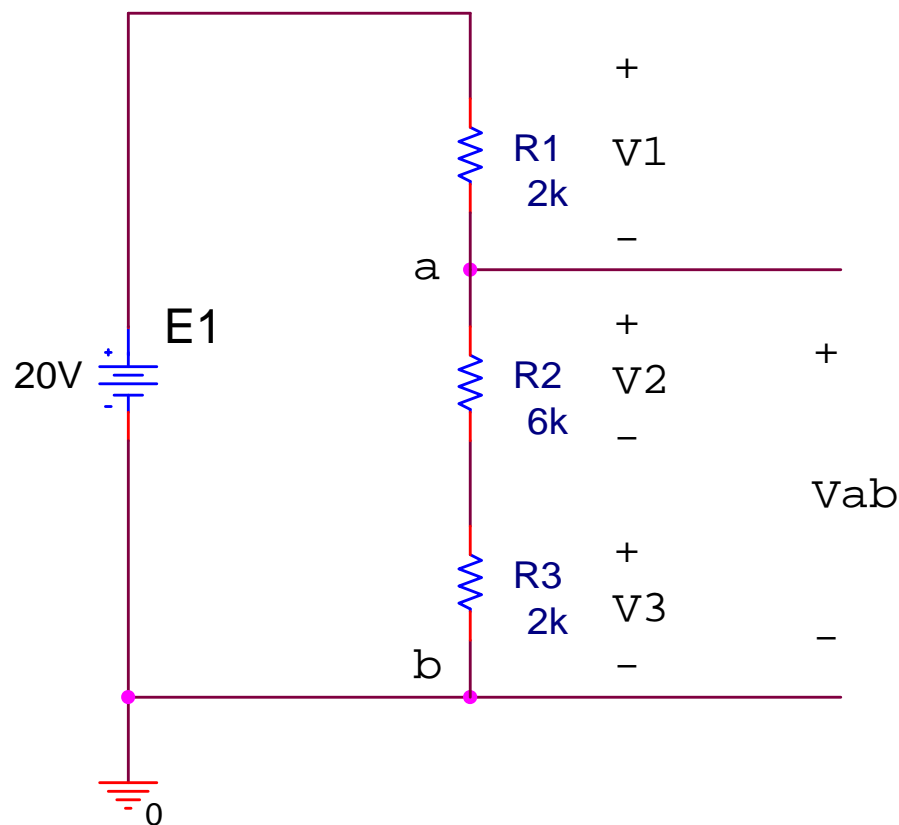■ Example – Find V_1 , V_2 , V_3 , V_{ab}




$$V_1 = \frac{R_1}{R_T} \cdot E_1 = \frac{2\text{k}\Omega}{10\text{k}\Omega} \cdot 20\text{V} = 4\text{V}$$

$$V_2 = \frac{R_2}{R_T} \cdot E_1 = \frac{6\text{k}\Omega}{10\text{k}\Omega} \cdot 20\text{V} = 12\text{V}$$

$$V_{ab} = \frac{R_{ab}}{R_T} \cdot E_1 = \frac{8\text{k}\Omega}{10\text{k}\Omega} \cdot 20\text{V} = 16\text{V}$$

Breakout #1

- Find V_1 , V_2 , and V_3 given:

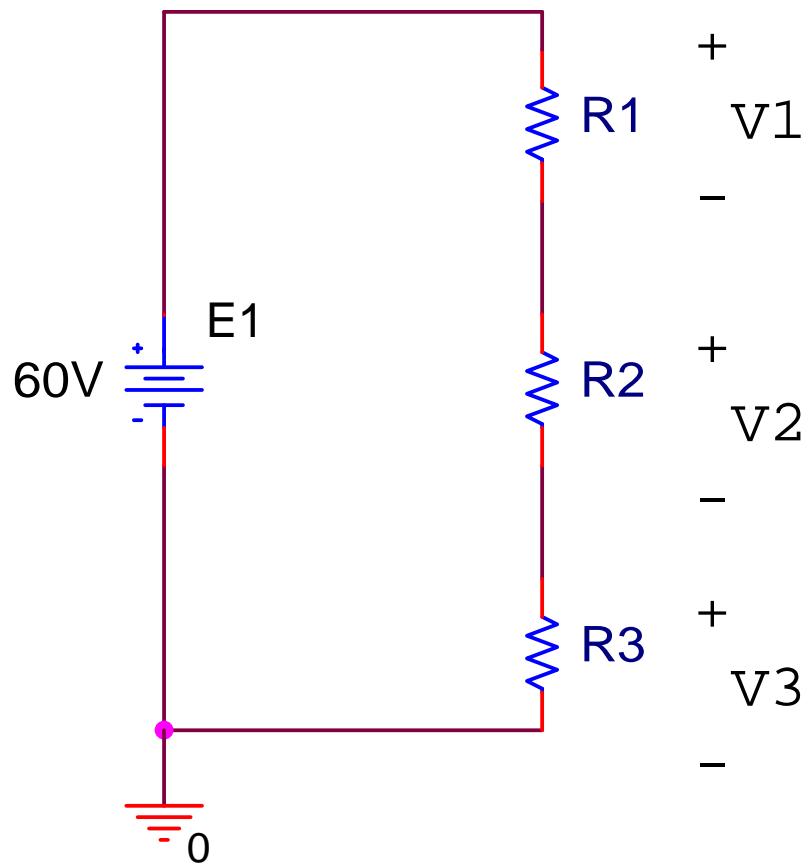


$$R_1 = 2 \cdot R_3$$


$$R_2 = 7 \cdot R_3$$

Breakout #2 - KVL

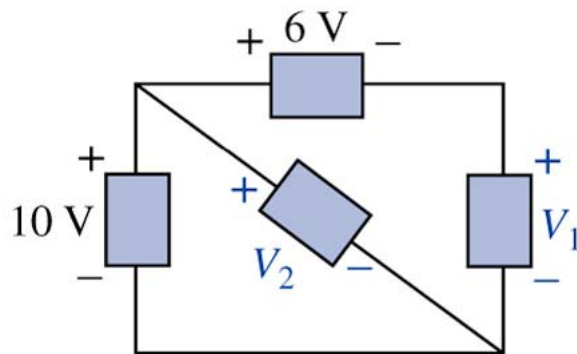- Find V_1 and V_2 in the circuits shown below



(a)


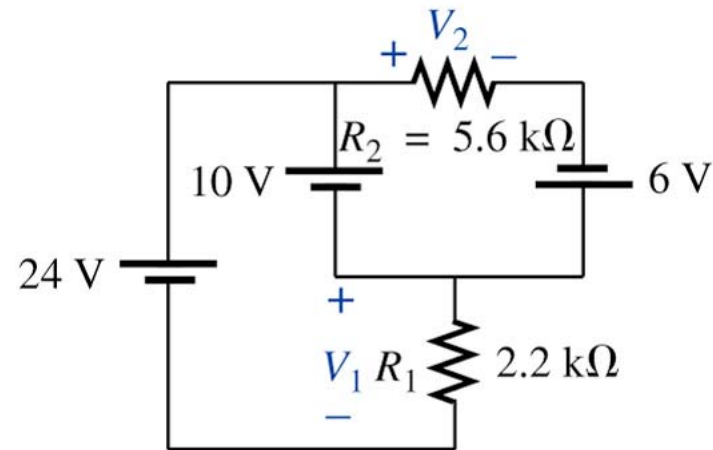


(b)


Practical (non-ideal) Voltage Sources

- The ideal voltage source has no internal resistance and thus delivers an output voltage of “E” volts with no load or under full load.
- Every practical voltage source (generator, battery, or laboratory supply) has some *internal equivalent* resistance.
- The voltage drop across the internal equivalent resistance lowers the source output voltage when a load is connected.

Practical (non-ideal) Voltage Sources

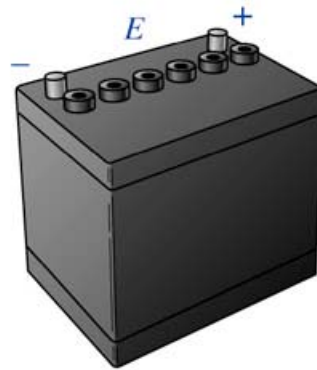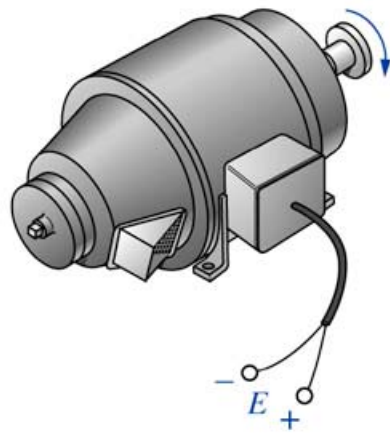


(a)

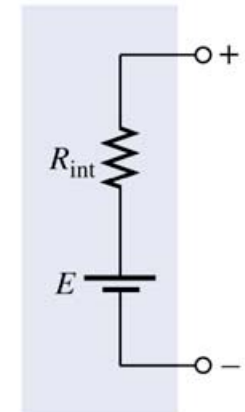

(b)

Practical (non-ideal) Voltage Sources


IDEAL Source

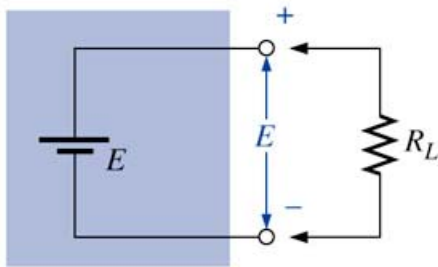

(a)

$$V_L = E$$


Practical Source

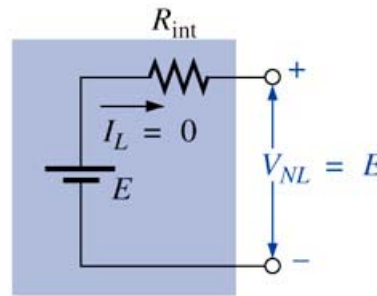

(b)

$$V_{NL} = E$$

Practical Source
w/Load

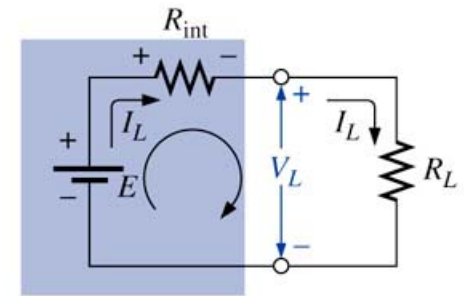


(c)

$$V_L = E \cdot \frac{R_L}{R_L + R_{int}}$$

$$E - V_{R_{int}} - V_L = 0$$

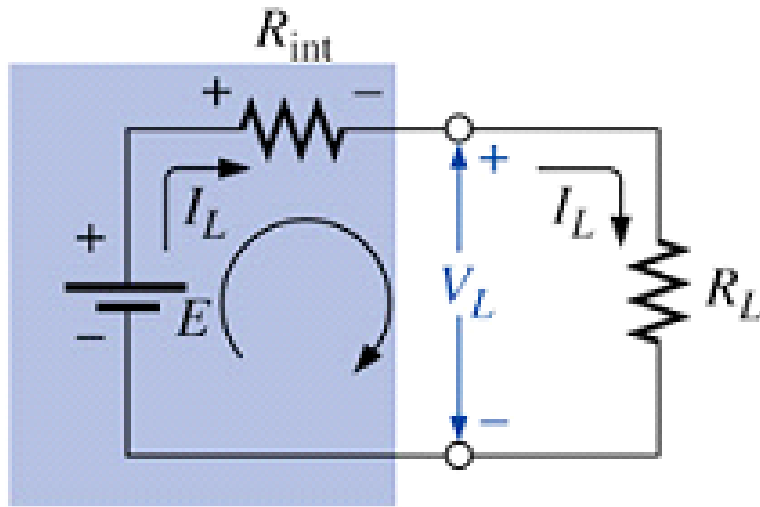Practical Voltage Sources – Finding R_{int}



$$R_{int} = \frac{E - V_L}{I_L}$$

But

$$E = V_{NL} \text{ and } \frac{V_L}{I_L} = R_L$$

$$\therefore R_{int} = \frac{V_{NL}}{I_L} - R_L$$


Practical Voltage Sources – Regulation

$$E - V_{R_{int}} - V_L = 0$$

Rearranging :

$$V_L = -R_{int} \cdot I_L + V_{NL}$$

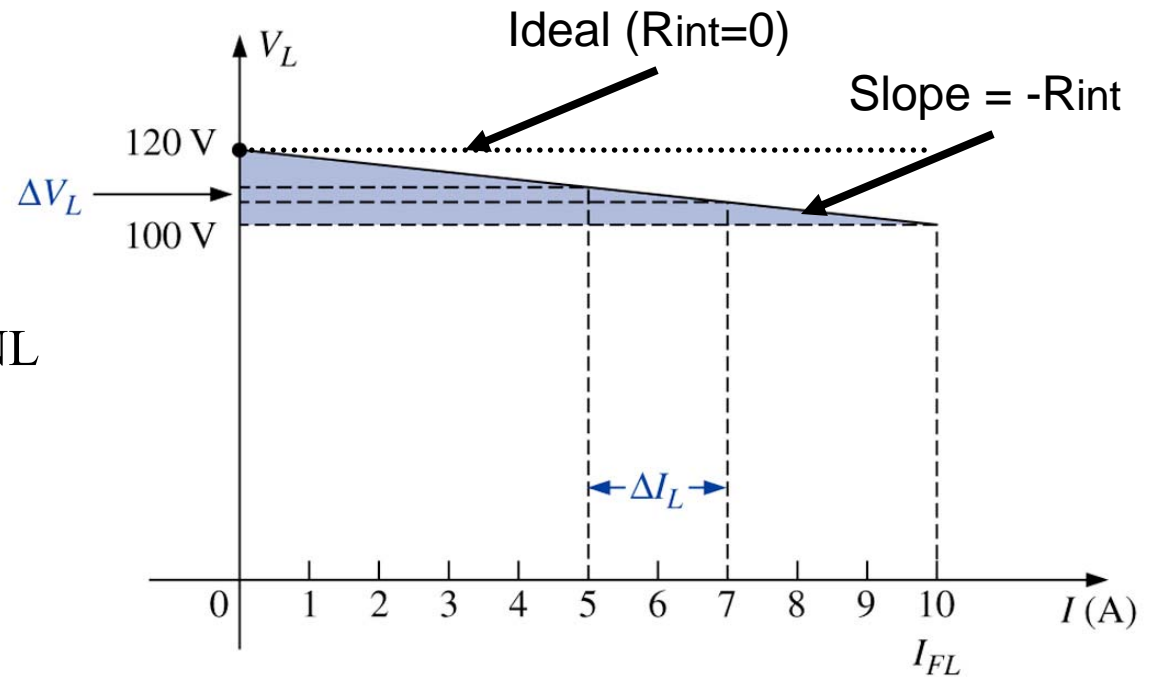$\begin{matrix} \uparrow & \uparrow & \uparrow & \uparrow \\ Y & m & X & b \end{matrix}$



$$\therefore R_{int} = \left| \frac{\Delta V_L}{\Delta I_L} \right|$$

Breakout #3 – R_{int}

- Find the internal resistance of the source, R_{int}

