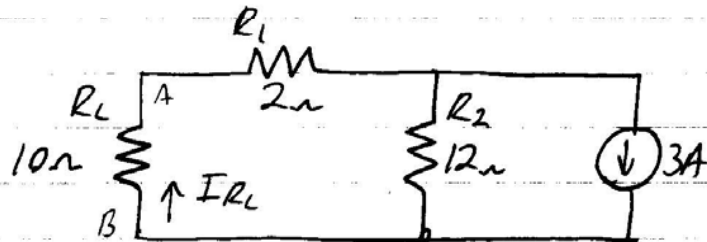


FIND P_{R_L} FOR $R_L = 10\Omega$:

ORIGINAL CIRCUIT




$$I_{R_L} = 3A \left(\frac{R_2}{R_2 + R_1 + R_L} \right) = 3A \left(\frac{12}{12 + 2 + 10} \right) = \underline{1.5A}$$

$$\therefore P_{R_L} = (I_{R_L})^2 R_L = (1.5A)^2 (10\Omega) = \boxed{22.5W}$$

EQUIVALENT
2

THEVENIN EQUIVALENT

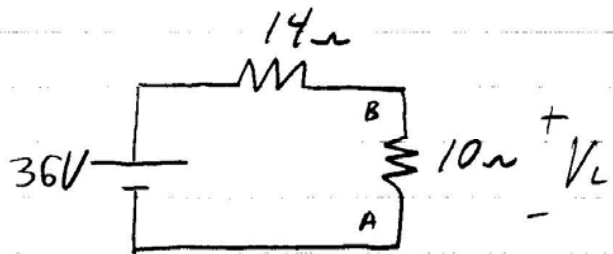


$$V_L = 36V \left(\frac{10}{10 + 14} \right) = \underline{15V}$$

$$\therefore P_{R_L} = \frac{V_L^2}{R_L} = \frac{(15V)^2}{10\Omega} = \boxed{22.5W}$$


FOR MORE COMPLICATED CIRCUITS, IT WOULD BE EASIER TO ANALYZE THE THEVENIN EQUIVALENT CIRCUIT (REPEATEDLY) INSTEAD OF THE ORIGINAL.

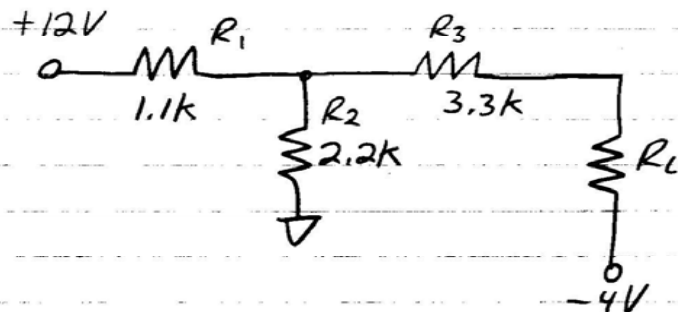(EXAMPLE)


DETERMINE THE THEVENIN EQUIVALENT
CIRCUIT AS SEEN BY R_L .



REDRAW, REMOVE R_L , LABEL A-B:

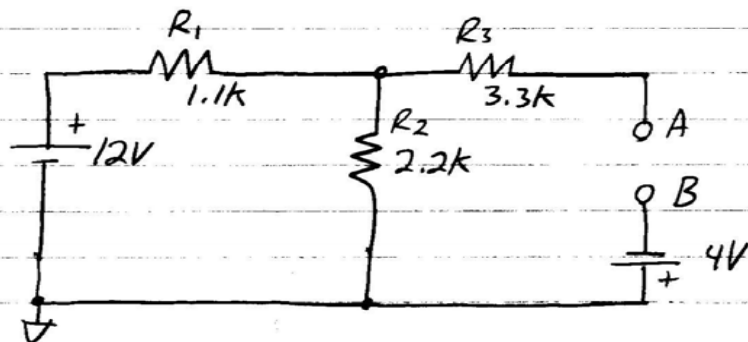


R_{TH} :

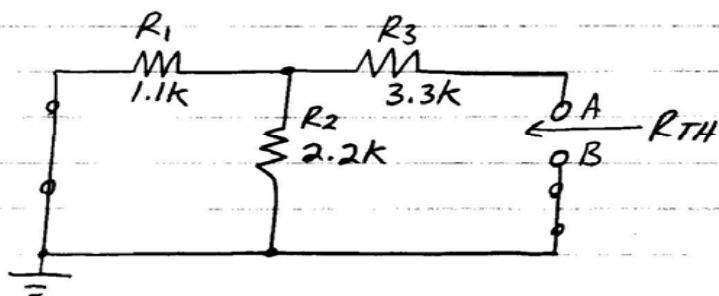

$$R_{TH} = [R_1 // R_2] + R_3$$

$$R_{TH} = (1.1k // 2.2k) + 3.3k$$
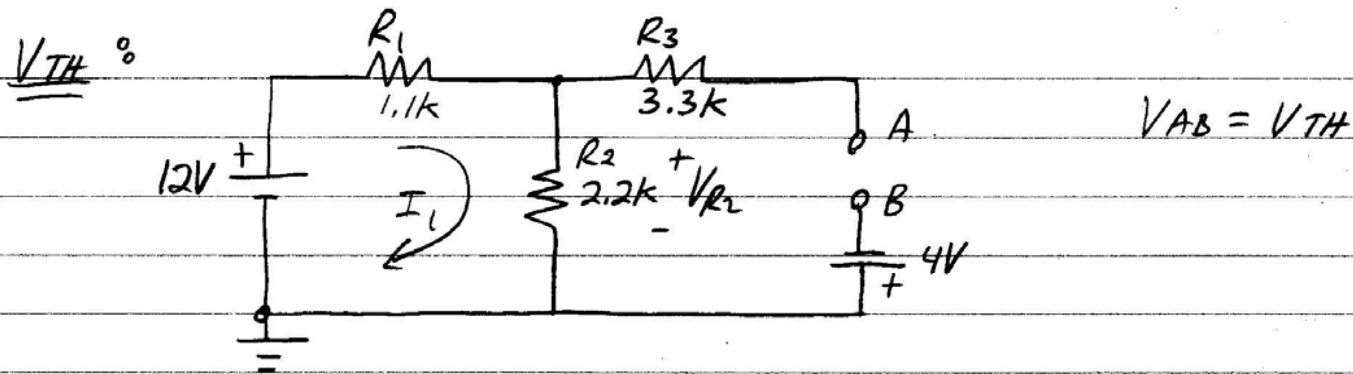
$$\therefore R_{TH} = 733.33\Omega + 3.3k\Omega = \boxed{4.03k\Omega}$$



$$I_1 = \frac{12V}{R_1 + R_2} = \frac{12V}{3.3k\Omega} = 3.636mA$$

$$\therefore V_{R2} = I_1 R_2 = (3.636mA)(2.2k\Omega)$$

$$V_{R2} = 8V$$

$$KVL: +V_{R2} - V_{AB} + 4 = 0, \text{ No current through } R_3$$

$$\therefore V_{AB} = V_{R2} + 4 = \boxed{12V \Rightarrow V_{TH}}$$

THEVENIN EQUIV. CKT

