

(a) WRITE EXPRESSIONS FOR V_C , V_{R_1} , i_C AFTER THE SWITCH IS PUT INTO POSITION 1. $\leftarrow t=0$


$$i_{C \max} \Big|_{t=0+} = \frac{50V}{R_1 + R_2} = 10 \text{ mA}$$

$$\tau = (R_1 + R_2)C = 10 \text{ ms}$$

$$\therefore i_C(t) = 10 \text{ mA } e^{-t/10 \text{ ms}} \quad (1)$$

$$V_{R_1} = i_C(t) \cdot R_1 = 30V e^{-t/10 \text{ ms}} \quad (2)$$
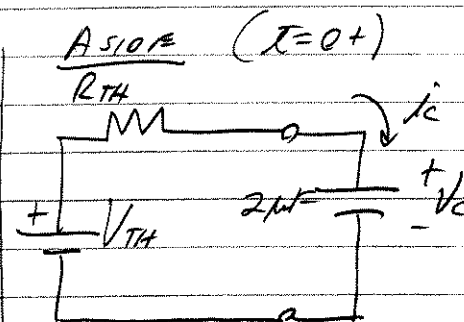
$$V_C(t) = 50V (1 - e^{-t/10 \text{ ms}}) \quad (3)$$



$$V_{TH} = 50V$$

$$R_{TH} = 5k\Omega$$

(b) At $t = 100 \text{ ms}$, POS1 \rightarrow POS2. FIND $V_C(t)$, $V_{R_1}(t)$ & $i_C(t)$

AT 100 ms (JUST BEFORE THE SWITCH CHANGES POSITION)

$$i_C(100 \text{ ms}) = 454 \text{ nA}$$


$$V_{R_1}(100 \text{ ms}) = 1.36 \text{ mV}$$

$$V_C(100 \text{ ms}) = 49.998 \sim 50V$$

FROM (1) - (3)
ABOVE

Holds CHARGE

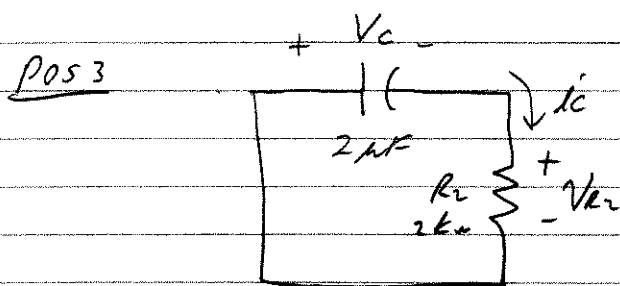- (c) WRITE EXPRESSIONS FOR $V_C(t)$, $V_{R_2}(t)$ & $i_C(t)$
IF THE SWITCH IS MOVED TO POS 3 AT 200 ms
DISCHARGE STARTS



JUST AFTER THE SWITCH IS MOVED TO POS 3:

$$V_C(200\text{ms}) = 50\text{V}$$

$$\therefore V_C(t) = 50\text{V} e^{-t/\tau'}, \quad \tau' = (2\mu\text{F})(2\text{k}\Omega) = 4\text{ms}$$

$$V_C(t) = 50\text{V} e^{-(t-200\text{ms})/4\text{ms}} \quad (4)$$

$$V_{R_2} = -V_C = -50\text{V} e^{-(t-200\text{ms})/4\text{ms}} \quad (5)$$

$$i_C(t) = \frac{V_{R_2}(t)}{R_2} = -25\text{mA} e^{-(t-200\text{ms})/4\text{ms}} \quad (6)$$

GOOD FOR
 $t > 200\text{ms}$

- (d) PLOT V_C , V_{R_2} & i_C FOR $0 < t < 300\text{ms}$

$0 \rightarrow 100\text{ms}$: CHARGE, USE (1) - (3)

$100\text{ms} \rightarrow 200\text{ms}$: $V_C = 50\text{V}$, $i_C \sim 0\text{A}$ (HOLDING CHARGE)


$200\text{ms} \rightarrow 300\text{ms}$: USE (4) - (6)

PLOT = EXCEL OR EQUIVALENT


→

Time msec	Vc(t) V	VR2(t) V	Ic(t) mA
0	00.0E+0	20.0E+0	10.0E+0
10	31.6E+0	7.4E+0	3.7E+0
20	43.2E+0	2.7E+0	1.4E+0
30	47.5E+0	99.6E-2	49.8E-2
40	49.1E+0	36.6E-2	18.3E-2
50	49.7E+0	13.5E-2	6.7E-2
60	49.9E+0	5.0E-2	2.5E-2
70	50.0E+0	1.8E-2	9.1E-4
80	50.0E+0	6.7E-4	3.5E-4
90	50.0E+0	24.7E-4	12.3E-4
100	50.0E+0	00.0E+0	4.5E-4
110	50.0E+0	00.0E+0	00.0E+0
120	50.0E+0	00.0E+0	00.0E+0
130	50.0E+0	00.0E+0	00.0E+0
140	50.0E+0	00.0E+0	00.0E+0
150	50.0E+0	00.0E+0	00.0E+0
160	50.0E+0	00.0E+0	00.0E+0
170	50.0E+0	00.0E+0	00.0E+0
180	50.0E+0	00.0E+0	00.0E+0
190	50.0E+0	00.0E+0	00.0E+0
192	50.0E+0	00.0E+0	00.0E+0
194	50.0E+0	00.0E+0	00.0E+0
196	50.0E+0	00.0E+0	00.0E+0
198	50.0E+0	00.0E+0	00.0E+0
200	50.0E+0	-50.0E+0	-25.0E+0
205	14.3E+0	-14.3E+0	-7.2E+0
210	4.1E+0	-4.1E+0	-2.1E+0
215	1.2E+0	-1.2E+0	-5.8E-2
220	33.7E-2	-33.7E-2	-16.8E-2
225	9.7E-2	-9.7E-2	-4.6E-2
230	2.8E-2	-2.8E-2	-1.4E-2
235	79.2E-4	-79.2E-4	-39.6E-4
240	22.7E-4	-22.7E-4	-11.3E-4
245	6.5E-4	-6.5E-4	-3.3E-4
250	1.9E-4	-1.9E-4	-9.3E-6
255	53.4E-6	-53.4E-6	-26.7E-6
260	15.3E-6	-15.3E-6	-7.6E-6
265	4.4E-6	-4.4E-6	-2.2E-6
270	1.3E-6	-1.3E-6	-6.2E-8
275	36.0E-8	-36.0E-8	-18.0E-8
280	10.3E-8	-10.3E-8	-5.2E-8
285	3.0E-8	-3.0E-8	-1.5E-8
290	84.6E-10	-84.6E-10	-42.3E-10
295	24.2E-10	-24.2E-10	-12.1E-10
300	6.9E-10	-6.9E-10	-3.5E-10


Vc(t) for Problem 10-28

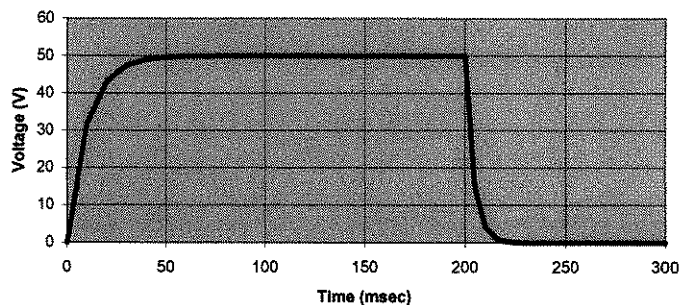

VR2(t) for Problem 10-28

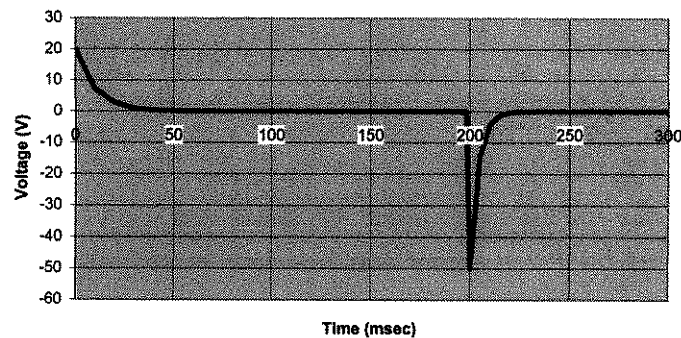



IC(t) for Problem 10-28

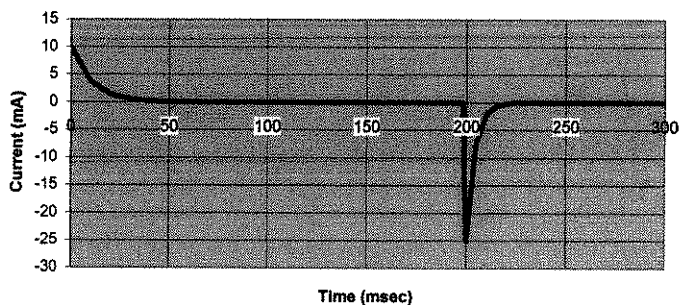

29. a. $v_C = V_f + (V_i - V_f)e^{-t/\tau}$
 $\tau = RC = (4.7 \text{ k}\Omega)(4.7 \text{ }\mu\text{F}) = 22.1 \text{ ms}, \quad V_f = 40 \text{ V}, \quad V_i = 6 \text{ V}$
 $v_C = 40 \text{ V} + (6 \text{ V} - 40 \text{ V})e^{-t/22.1\text{ms}}$
 $v_C = \mathbf{40 \text{ V} - 34 \text{ V}e^{-t/22.1\text{ms}}}$

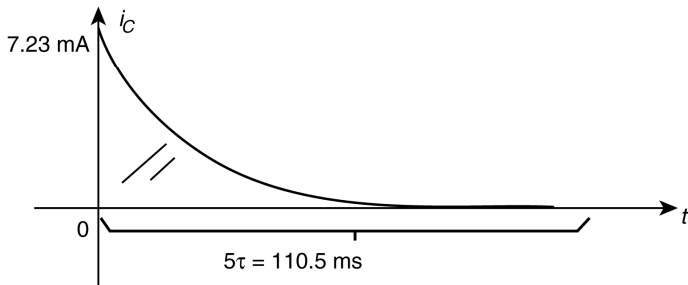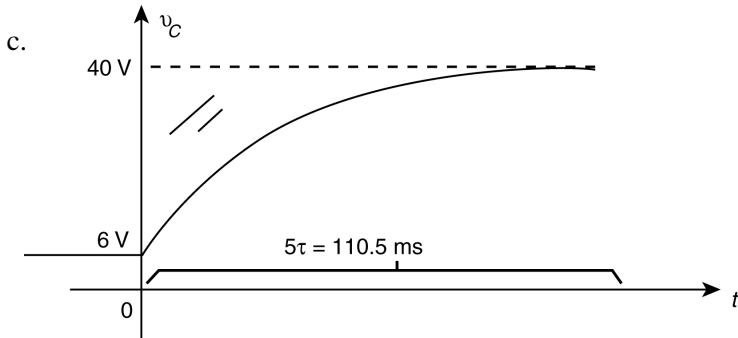b. Initially $V_R = E + v_C = 40 \text{ V} - 6 \text{ V} = 34 \text{ V}$

$$i_C = \frac{V_R}{R} e^{-t/\tau} = \frac{34 \text{ V}}{4.7 \text{ k}\Omega} e^{-t/22.1\text{ms}} = \mathbf{7.23 \text{ mA} e^{-t/22.1\text{ms}}}$$



- a. $v_C = 140 \text{ mV}(1 - e^{-1 \text{ ms}/2 \text{ ms}}) = 140 \text{ mV}(1 - e^{-0.5}) = 140 \text{ mV}(1 - 0.6065)$
 $= 140 \text{ mV}(0.3935) = \mathbf{55.59 \text{ mV}}$
- b. $v_C = 140 \text{ mV}(1 - e^{-10}) = 140 \text{ mV}(1 - 45.4 \times 10^{-6})$
 $\cong \mathbf{139.99 \text{ mV}}$
- c. $100 \text{ mV} = 140 \text{ mV}(1 - e^{-t/2 \text{ ms}})$
 $0.714 = 1 - e^{-t/2 \text{ ms}}$
 $0.286 = e^{-t/2 \text{ ms}}$
 $\log_e 0.286 = \log_e e^{-t/2 \text{ ms}}$
 $1.252 = -t/2 \text{ ms}$
 $t = 1.252 (2 \text{ ms}) = \mathbf{2.5 \text{ ms}}$
- d. $v_C = 138 \text{ mV} = 140 \text{ mV}(1 - e^{t/2 \text{ ms}})$
 $0.986 = 1 - e^{-t/2 \text{ ms}}$
 $-14 \times 10^{-3} = -e^{-t/2 \text{ ms}}$
 $\log_e 14 \times 10^{-3} = -t/2 \text{ ms}$
 $-4.268 = -t/2 \text{ ms}$
 $t = (4.268)(2 \text{ ms}) = \mathbf{8.54 \mu s}$

$$\text{a. } \tau = RC = (12 \text{ k}\Omega + 8.2 \text{ k}\Omega)(6.8 \text{ }\mu\text{F}) = 137.36 \text{ ms}$$

$$v_C = 60 \text{ V}(1 - e^{-t/\tau})$$

$$48 \text{ V} = 60 \text{ V}(1 - e^{-t/\tau})$$

$$0.8 = 1 - e^{-t/\tau}$$

$$0.2 = e^{-t/\tau}$$

$$\log_e 0.2 = \log_e e^{-t/\tau}$$

$$-1.61 = -t/\tau$$

$$t = (1.61)\tau = (1.61)(137.36 \text{ ms}) = \mathbf{221.15 \text{ ms}}$$

$$\text{b. } i_C = \frac{E}{R} e^{-t/\tau} = \frac{60 \text{ V}}{20.2 \text{ k}\Omega} e^{-t/\tau}$$

$$= 2.97 \text{ mA} e^{-t/137.36 \text{ ms}}$$

$$i_C(221.15 \text{ ms}) = 2.97 \text{ mA} e^{-221.15 \text{ ms}/137.36 \text{ ms}}$$

$$= 2.97 \text{ mA} e^{-1.61}$$

$$= 2.97 \text{ mA} (199.89 \times 10^{-3})$$

$$= \mathbf{0.594 \text{ mA}}$$

$$\text{c. } t = 2\tau$$


$$i_C = 2.97 \text{ mA} e^{-2t/\tau} = 2.97 \text{ mA} e^{-2}$$

$$= 0.4 \text{ mA}$$

$$\underbrace{\hspace{1.5cm}}_{0.135}$$


$$P = EI = (60 \text{ V})(0.4 \text{ mA}) = \mathbf{24 \text{ mW}}$$

44)

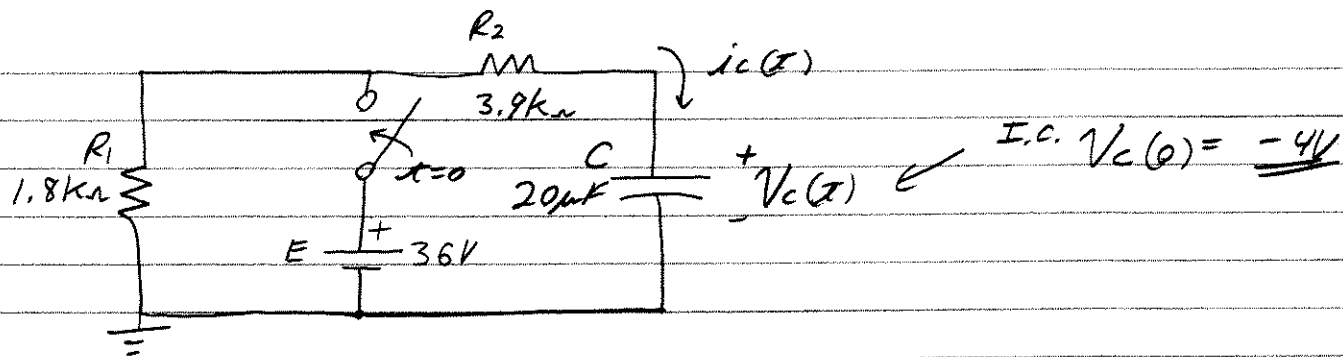

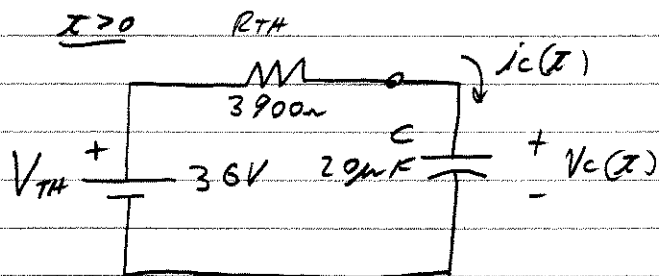(a) FIND $V_c(t)$ & $i_c(t)$ FOR $t > 0$

$t > 0$
 $V_{TH} = E = 36V$
 $R_{TH} = R_2 = 3.9k\Omega$
 $\tau = (R_{TH})(C) = 78mSec$





$i_c(t) = i_{cMAX} e^{-t/\tau}$
 BUT $i_{cMAX} = \frac{36V - (-4V)}{3900\Omega} = 10.26mA$
 $\tau = 78ms$

$\therefore i_c(t) = 10.26mA e^{-t/78ms}$


By KVL: $V_c(t) = V_{TH} - i_c(t) R_{TH}$
 $V_c(t) = 36V - 40V e^{-t/78ms}$

(b) SKETCH $V_c(t)$ & $i_c(t)$

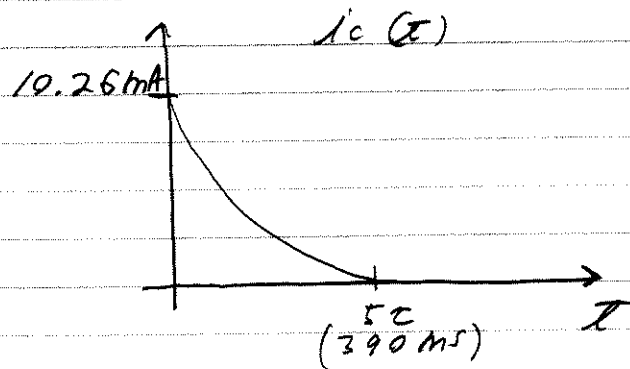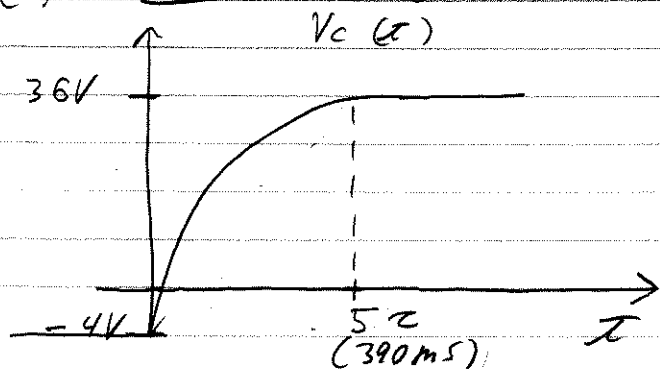


P 52

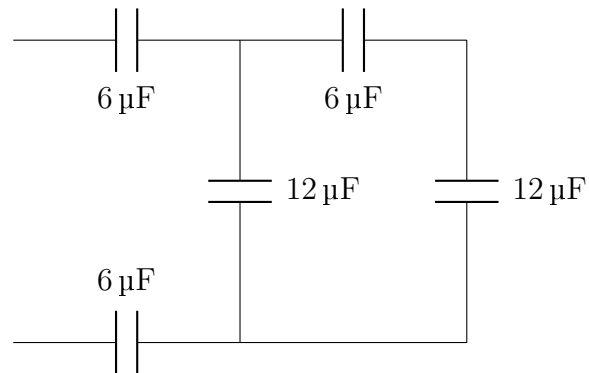Find the total capacitance C_T for the network in Fig. 10.120.



Step 1: Series combination of the $6\ \mu\text{F}$ and $12\ \mu\text{F}$ capacitors

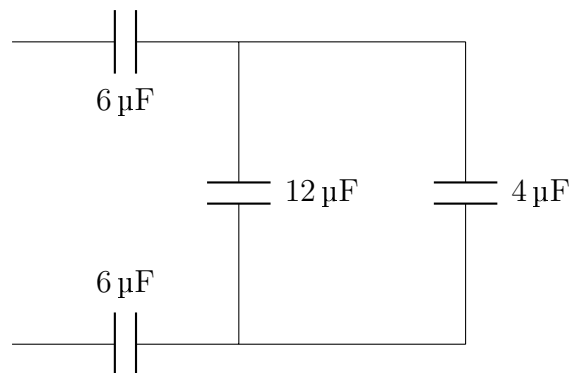
$$C_{EQ_1} = \frac{1}{\frac{1}{6\ \mu\text{F}} + \frac{1}{12\ \mu\text{F}}} = 4\ \mu\text{F}$$



Step 2: Parallel combination of C_{EQ_1} and $12\ \mu\text{F}$


$$C_{EQ_2} = C_{EQ_1} + 12\ \mu\text{F}$$
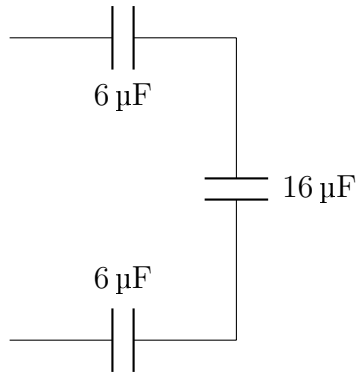
$$C_{EQ_2} = 4\ \mu\text{F} + 12\ \mu\text{F} = 16\ \mu\text{F}$$



Step 3: Parallel combination of $6\ \mu\text{F}$, C_{EQ_2} and $6\ \mu\text{F}$
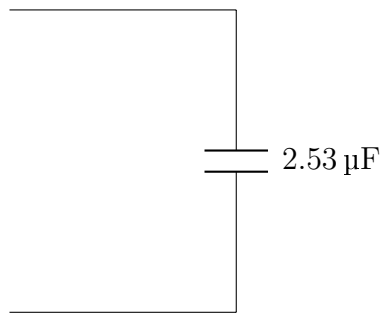
$$C_T = \frac{1}{\frac{1}{6\ \mu\text{F}} + \frac{1}{16\ \mu\text{F}} + \frac{1}{6\ \mu\text{F}}} = 2.53\ \mu\text{F}$$



P 53

Find the steady-state voltage across and the charge on each capacitor for the circuit in Fig. 10.121.

The total capacitance of the circuit is:

Step 1: Series combination of the $10\text{ }\mu\text{F}$ and $100\text{ }\mu\text{F}$

$$C_{EQ_1} = \frac{1}{\frac{1}{10\text{ }\mu\text{F}} + \frac{1}{100\text{ }\mu\text{F}}} = 9.09\text{ }\mu\text{F}$$

Step 2: Parallel combination of C_{EQ_1} and $20\text{ }\mu\text{F}$ capacitor

$$\begin{aligned} C_T &= C_{EQ_1} + 20\text{ }\mu\text{F} = 9.09\text{ }\mu\text{F} + 20\text{ }\mu\text{F} \\ C_T &= 29.09\text{ }\mu\text{F} \end{aligned}$$

Given the 20 V drop across the total capacitance, the total charge across the total capacitor is:

$$Q_T = C_T \cdot V = 29.09\text{ }\mu\text{F} \cdot 20 = 581.82\text{ }\mu\text{C}$$

The charge across the $20\text{ }\mu\text{F}$ capacitor is:

$$Q_{20\text{ }\mu\text{F}} = 20\text{ }\mu\text{F} \cdot 20 = 400\text{ }\mu\text{C}$$

The charge across the C_{EQ_1} is:

$$Q_{EQ_1} = C_{EQ_1} \cdot V = 9.09\text{ }\mu\text{F} \cdot 20 = 181.82\text{ }\mu\text{C}$$

The voltage across the C_{EQ_1} is:

$$Q_{EQ_1} = C_{EQ_1} \cdot V = 9.09\text{ }\mu\text{F} \cdot 20 = 181.82\text{ }\mu\text{C}$$

Given that there is equal amount of charge on the $10\text{ }\mu\text{F}$ and $100\text{ }\mu\text{F}$, the voltage across the capacitors are:

$$\begin{aligned} V_{10\text{ }\mu\text{F}} &= \frac{C_{EQ_1}}{10\text{ }\mu\text{F}} = \frac{181.82\text{ }\mu\text{C}}{10\text{ }\mu\text{F}} = 18.82\text{ V} \\ V_{100\text{ }\mu\text{F}} &= \frac{C_{EQ_1}}{100\text{ }\mu\text{F}} = \frac{181.82\text{ }\mu\text{C}}{100\text{ }\mu\text{F}} = 1.82\text{ V} \end{aligned}$$

P55

steady – state – ignore 10 k Ω resistor

$$330 \mu\text{F} + 120 \mu\text{F} = 450 \mu\text{F}$$

$$C_T = 220 \mu\text{F} \parallel 450 \mu\text{F} = 147.76 \mu\text{F}$$

$$Q_T = Q_1 = C_T E = (147.76 \mu\text{F})(20 \text{ V}) = \mathbf{2.96 \text{ mC}}$$

$$V_1 = \frac{Q_1}{C_1} = \frac{2.96 \text{ mC}}{220 \mu\text{F}} = \mathbf{13.45 \text{ V}}$$


$$V_3 = V_2 = E - V_1 = 20 \text{ V} - 13.45 \text{ V} = \mathbf{6.55 \text{ V}}$$

$$Q_2 = C_2 V_2 = (330 \mu\text{F})(6.55 \text{ V}) = \mathbf{2.16 \text{ mC}}$$


$$Q_3 = C_3 V_3 = (120 \mu\text{F})(6.55 \text{ V}) = \mathbf{0.786 \text{ mC}}$$

See the
next
page for
my
solution
to this
problem

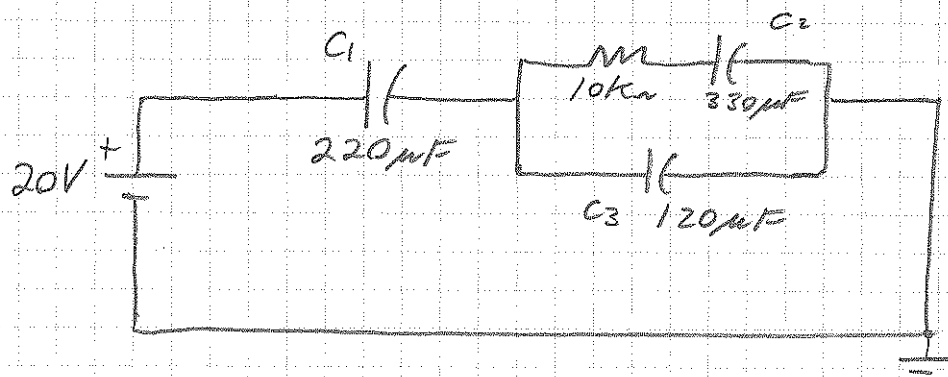FIND THE VOLTAGE ACROSS & CHARGE ON EACH CAPACITOR (STEADY STATE).



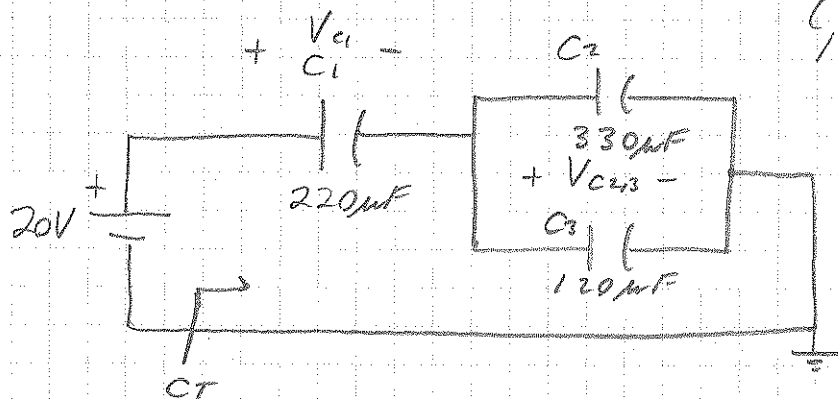STEADY-STATE CONDITIONS, CAPS FULLY CHARGED (NO I FLOW) \therefore IGNORE THE $10k\Omega$ R



$C_T = (C_2 + C_3)$ COMBINED W/ C_1 IN SERIES

$$C_2 + C_3 = 450 \mu F \rightarrow C_{EQ}$$

$$\therefore C_T = \frac{(450 \mu F)(220 \mu F)}{450 \mu F + 220 \mu F} = 147.8 \mu F$$

$$\text{HENCE } Q_T = C_T V = (147.8 \mu F)(20V) = \underline{2.96 mC}$$

SERIES CIRCUIT, HENCE

$$Q_0 = Q_{EQ} = Q_T = \underline{2.96 mC}$$

$$\text{HENCE } V_{C1} = \frac{Q_{C1}}{C_1} = \frac{2.96 mC}{220 \mu F} = \underline{13.43V}$$

$$V_{C2,3} = \frac{Q_{C2,3}}{C_{EQ}} = \frac{2.96 mC}{450 \mu F} = \underline{6.57V}$$

$$Q_2 = (C_2)(V_{C2,3}) = (330 \mu F)(6.57V) = \underline{2.17 mC}$$

$$Q_3 = (C_3)(V_{C2,3}) = (120 \mu F)(6.57V) = \underline{788 \mu C}$$