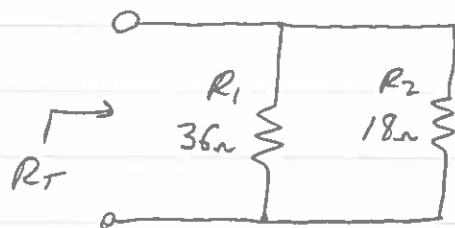


EEET-111 DC LECTURE
HW #5, CHAPTER 5 PROBLEMS

P4) FIND R_T FOR EACH CIRCUIT




(a)

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{1}{36\Omega} + \frac{1}{18\Omega}} = \frac{1}{83.33mS}$$

$$\therefore \boxed{R_T = 12\Omega}$$
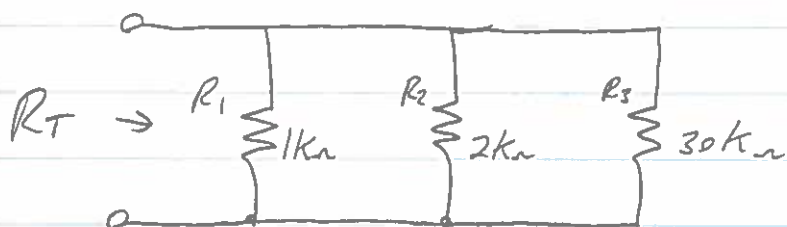
$$\text{OR } R_T = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{(36\Omega)(18\Omega)}{(36 + 18)\Omega} \\ = \frac{684\Omega^2}{54\Omega} = \underline{\underline{12\Omega}}$$




(b)

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \\ = \frac{1}{1.533mS}$$


$$\therefore \boxed{R_T = 652.2\Omega}$$

P4) CONTINUED

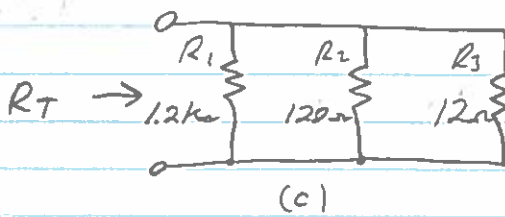


$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \boxed{10.81\Omega}$$

P5) FIND R_T

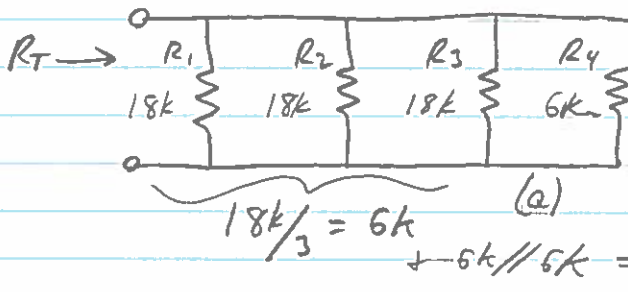

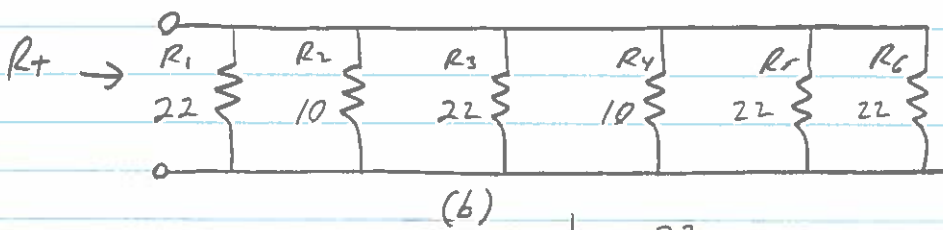
$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \boxed{3K\Omega}$$



$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_6}}$$

$$\boxed{R_T = 2.619\Omega}$$

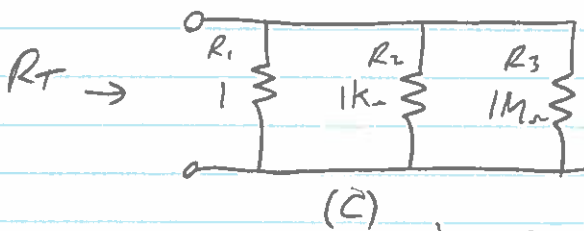
$$\begin{aligned} \frac{22}{4} &= 5.5\Omega \\ \frac{10}{2} &= 5\Omega \end{aligned}$$



$$R_T = \frac{1}{\frac{1}{1} + \frac{1}{1k} + \frac{1}{1 \times 10^6}} = \boxed{0.999\Omega}$$

$$R_T \sim 1\Omega$$

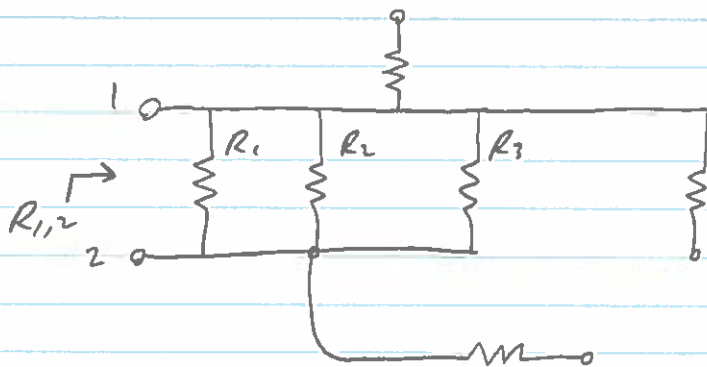P6) FIND $R_{1,2}$ IN EACH CASE
(CIRCUIT VALUES FROM COLOR-CODES)



(a)

$$R_{1,2} = R_1 \parallel R_2 \parallel R_3$$


$$= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 1.2 \text{ k}\Omega$$

$$R_3 = 300 \Omega$$
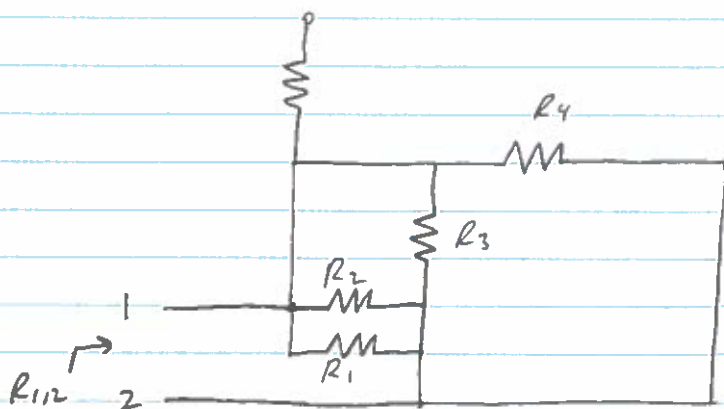
$$\therefore \boxed{R_{1,2} = 193.55 \Omega}$$



(b)

$$R_{1,2} = R_1 \parallel R_2 \parallel R_3 \parallel R_4$$

$$R_1 = 1.2 \text{ k}\Omega$$


$$R_2 = 1 \text{ k}\Omega$$

$$R_3 = 2.2 \text{ k}\Omega$$

$$R_4 = 1 \text{ k}\Omega$$

$$\therefore \boxed{R_{1,2} = 304.15 \Omega}$$

P7) FIND THE UNKNOWN(S)

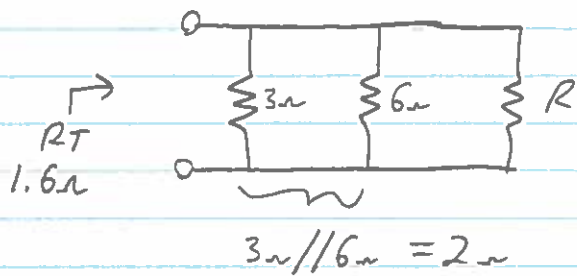

(a)

$$R_T = \frac{2\Omega \cdot R}{2\Omega + R}$$

$$1.6 = \frac{2R}{R+2}$$


$$1.6(R+2) = 2R$$

$$1.6R + 3.2 = 2R$$


$$3.2 = 0.4R$$

$$R = \frac{3.2}{0.4} = 8\Omega$$

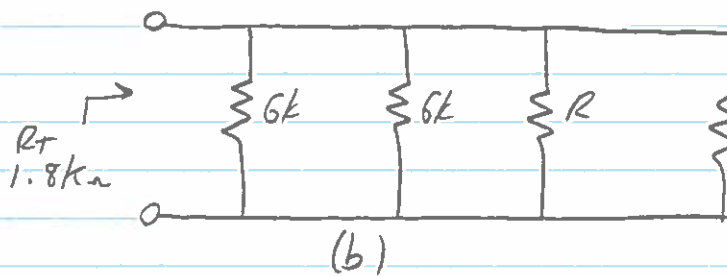
Special Case
of $\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$



$$\frac{6k\Omega}{3} = 2k\Omega$$

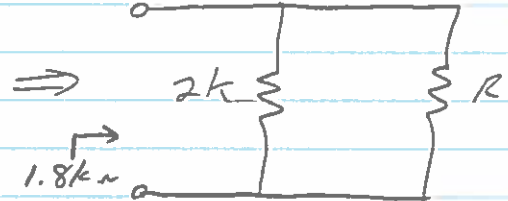
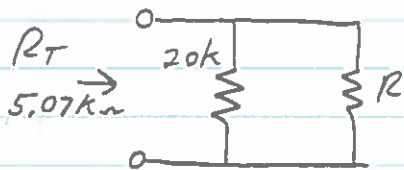
$$1.8k = \frac{(2k)(R)}{R+2k} \therefore R = 18k\Omega$$





$$R_T = \frac{(20k)(R)}{20k + R}$$

$$\text{OR } 5.07k\Omega = \frac{20k\Omega(R)}{20k\Omega + R}$$

$$\therefore R = 6.79k\Omega$$


P8) FIND THE UNKNOWN(S)

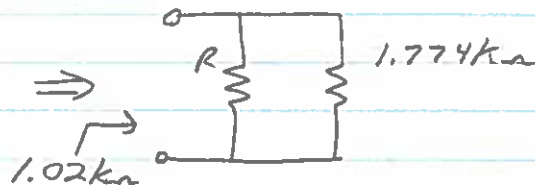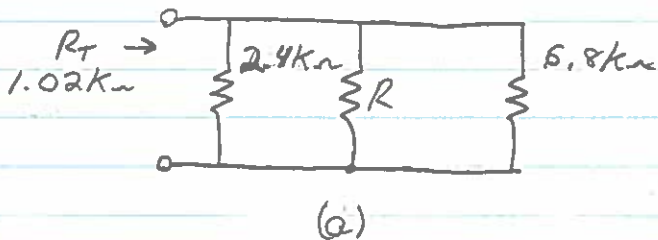

$$1.02k\Omega = \frac{R(1.774k\Omega)}{1.774k\Omega + R}$$

$$R = 2.40k\Omega$$

P8) CONTINUED

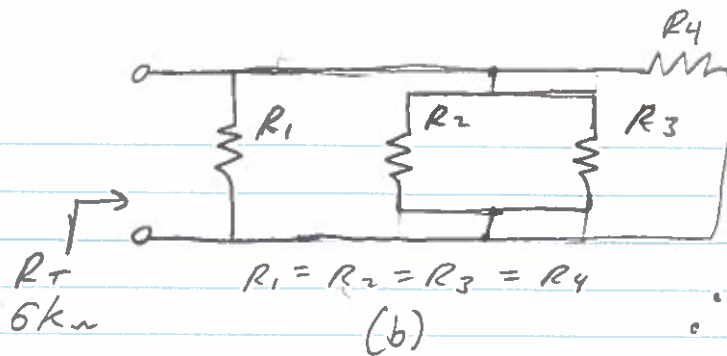


$$R_1 // R_2 // R_3 // R_4$$

$$= R_T = 6k\Omega = \frac{R_1}{4}$$

$$\therefore R_1 = 24k\Omega$$

P9) Ans 2 THROUGH c FOR THIS CIRCUIT

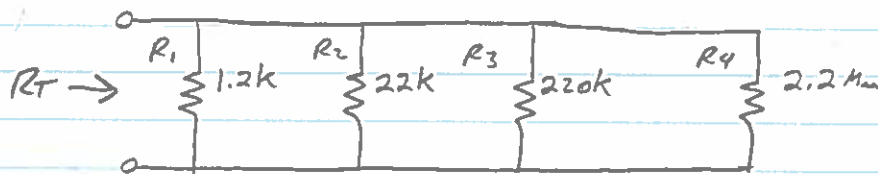

(a) WHICH RESISTOR HAS THE MOST IMPACT ON R_T ?

R_1 , THE LOWEST

(b) Approx R_T (w/o calc):

$$R_T \sim 1.1k\Omega$$

, A LITTLE LESS THAN R_1 ,
SINCE $R_2 // R_3 // R_4 \gg R_1$

(c) FIND R_T

$$R_T = R_1 // R_2 // R_3 // R_4 = 1.132k\Omega$$

CLOSE TO MY
APPROX


(d) APPROX WHICH RESISTORS CAN WE IGNORE
WHEN FINDING R_T ?

$R \gg R_{\text{lowest}}$, HERE THE $220k\Omega + 2.2M\Omega$


(e) IF WE ADD ANOTHER PARALLEL R , WHAT WILL
HAPPEN TO R_T ?

R_T WILL DECREASE


P10) WHAT IS THE OHMMETER READING?

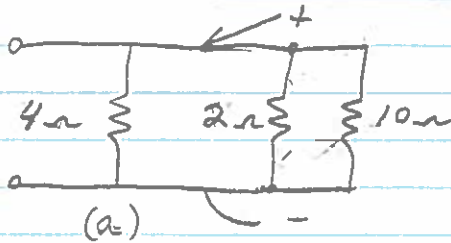
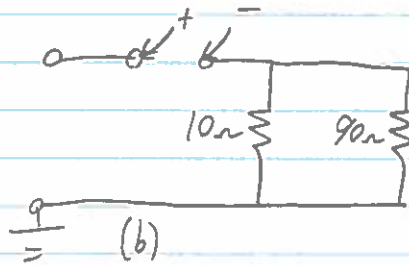
$$R_{OHM} = 4\Omega // 2\Omega // 10\Omega = \boxed{1.18\Omega}$$




$$R_{OHM} = \infty\Omega \quad (o/c)$$

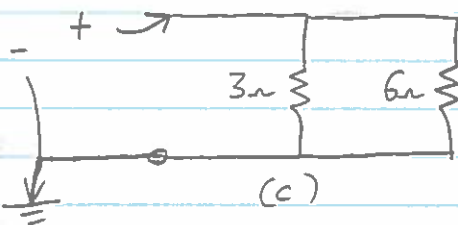

$$R_{OHM} = 2\Omega$$

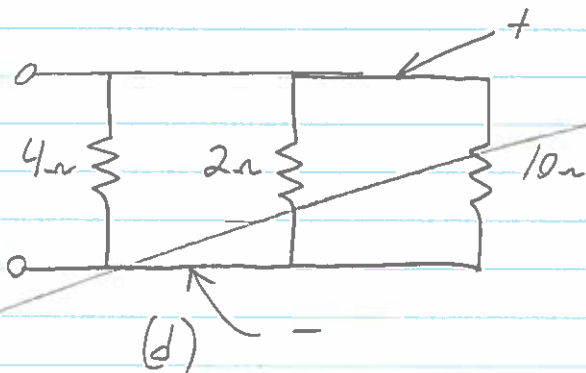
$$3\Omega // 6\Omega = \underline{\underline{2\Omega}}$$



$$R_{OHM} = 4\Omega // 2\Omega // 10\Omega$$

$$R_{OHM} = \boxed{1.177\Omega}$$

P15) FOR THE CIRCUIT BELOW :

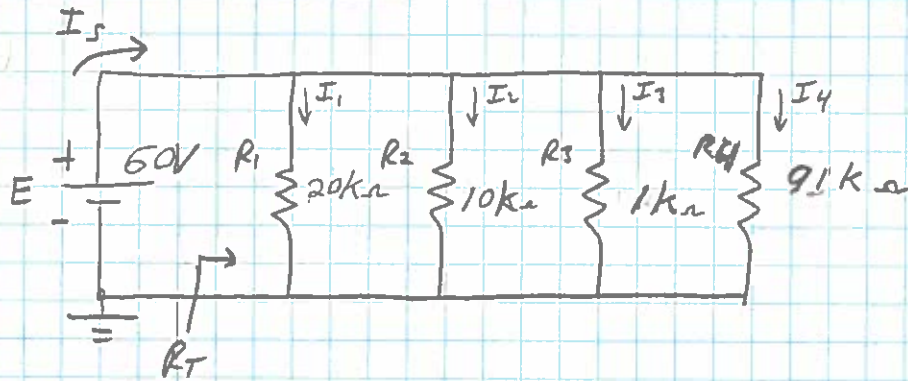

(a) MAKE A GUESS FOR R_T

$$R_T \sim 900 \Omega$$

$$R_3 = 1k\Omega$$

+ R_1, R_2, R_4 ARE ALL $\gg R_3$

R_T MUST BE LESS THAN R_3 + CLOSE IN VALUE

(b) FIND R_T

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = 861.3 \Omega$$

JUST SLIGHTLY LOWER THAN THE "GUESS"

(c) GUESS : WHICH BRANCH CURRENT IS HIGHEST?
" " " " LOWEST?

$$\left. \begin{array}{l} I_3 : \text{HIGHEST} \\ I_4 : \text{LOWEST} \end{array} \right\} I = \frac{E}{R}$$

$$\begin{array}{l} R \uparrow \quad I \downarrow \\ R \downarrow \quad I \uparrow \end{array}$$

(d) CALCULATE $I_1 - I_4$ + COMPARE THE ANS W/ (c)

$$I_1 = \frac{E}{R_1} = \frac{60V}{20k\Omega} = 3.00 \text{ mA}$$

$$I_2 = \frac{60V}{10k\Omega} = 6.00 \text{ mA}$$

$$I_3 = \frac{60V}{1k\Omega} = 60.00 \text{ mA} \leftarrow \text{LARGEST}$$

$$I_4 = \frac{60V}{91k\Omega} = 659.3 \mu A \leftarrow \text{LOWEST}$$

CONTINUED

15) (e) FIND I_S + VERIFY $I_S = \sum I_{\text{BRANCH}}$

$$I_S = \frac{E}{R_T} = \frac{60V}{861.3\Omega} = \boxed{69.7 \text{ mA}}$$

$$I_1 + I_2 + I_3 + I_4 = \boxed{69.7 \text{ mA}}$$


EQUAL
(KCL)

(f) COMPARE $|I_S|$ TO $|I_{\text{BRANCH}}|$

$$|I_S| = |\sum I_{\text{BRANCH}}|, \text{ KCL}$$

$$> |I_{\text{BRANCH}}|$$

18) FIND E , R_1 , + I_3

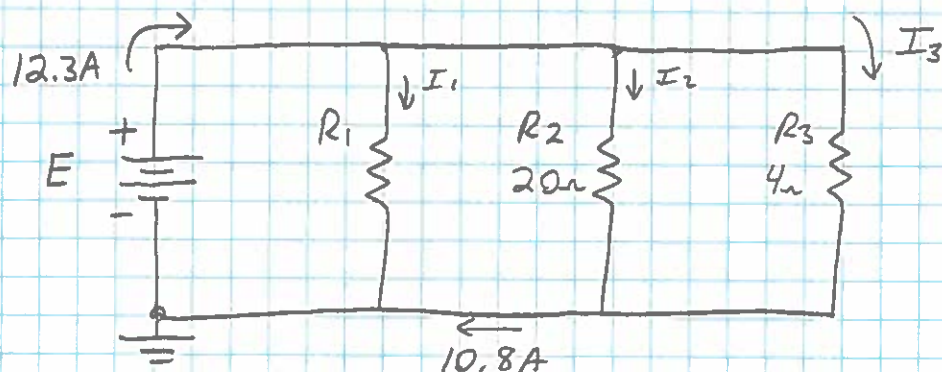

$$I_2 + I_3 = 10.8 \text{ A}, \text{ GIVEN}$$

$$I_3 = 10.8 \text{ A} \frac{R_T}{R_3}, \quad R_T = R_2 // R_3 = 3.33\Omega$$

$$R_3 = 4\Omega$$

$$\boxed{I_3 = 9.00 \text{ A}}$$

$$E = (I_3)(R_3) = (9 \text{ A})(4\Omega) = \boxed{36 \text{ V}}$$


$$R_1 = \frac{E}{I_1}$$

$$I_1 = 12.3 \text{ A} - (I_2 + I_3), \text{ KCL}$$

$$I_1 = 12.3 \text{ A} - 10.8 \text{ A}$$

$$I_1 = 1.50 \text{ A} \quad \therefore R_1 = \frac{36 \text{ V}}{1.5 \text{ A}} = \boxed{24\Omega}$$

P22) FOR THE CIRCUIT SHOWN:

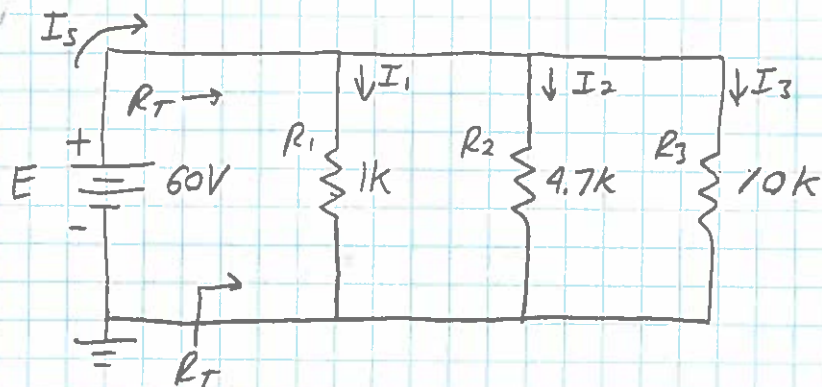

(a) FIND R_T , I_1 , I_2 , I_3

$$R_T = R_1 // R_2 // R_3 = \boxed{761.8 \Omega}$$

$$I_x = I_T \frac{R_T}{R_x}, \quad I_T = \frac{E}{R_T} = \frac{60V}{761.8 \Omega} = \boxed{78.8 \text{ mA}}$$

$$I_1 = 78.8 \text{ mA} \left(\frac{761.8 \Omega}{1k \Omega} \right) = \boxed{60.0 \text{ mA}}$$

$$I_2 = 78.8 \text{ mA} \left(\frac{761.8 \Omega}{4.7k \Omega} \right) = \boxed{12.8 \text{ mA}}$$

$$I_3 = 78.8 \text{ mA} \left(\frac{761.8 \Omega}{10k \Omega} \right) = \boxed{6.00 \text{ mA}}$$

(b) FIND P_{R_1} , P_{R_2} , P_{R_3}

$$P_{R_1} = (I_1)^2 R_1 = (60 \text{ mA})^2 (1k \Omega) = \boxed{3.60 \text{ W}}$$

$$P_{R_2} = \frac{(E)^2}{R_2} = \frac{(60)^2}{4.7k \Omega} = \boxed{766 \text{ mW}}$$

$$P_{R_3} = (E)(I_3) = (60V)(6.00 \text{ mA}) = \boxed{360 \text{ mW}}$$

3 APPROACHES
(TAKE YOUR
PICK)

(c) FIND P_{SOURCE}

$$P_{\text{SOURCE}} = (E)(I_s)$$

$$= (60V)(78.8 \text{ mA}) = \boxed{4.73 \text{ W}}$$

(d) COMPARE P_{SOURCE} TO $\sum_x P_{R_x}$

$$\sum_x P_{R_x} = P_{R_1} + P_{R_2} + P_{R_3} = \boxed{4.73 \text{ W}}$$

↖ THE SAME

(e) R_1 RX THE MOST POWER, LOWEST R W/ E CONSTANT ($I = E/R$)

(e) WHICH RESISTOR RECEIVED THE MOST POWER?
WHY?

R_1


THE LOWEST R IN A PARALLEL
BRANCH

SAME

$$P = \frac{V^2}{R} = \frac{E^2}{R}$$

AS
" $\therefore R \downarrow P \uparrow$ "


P27) FIND I_1 + I_2 :

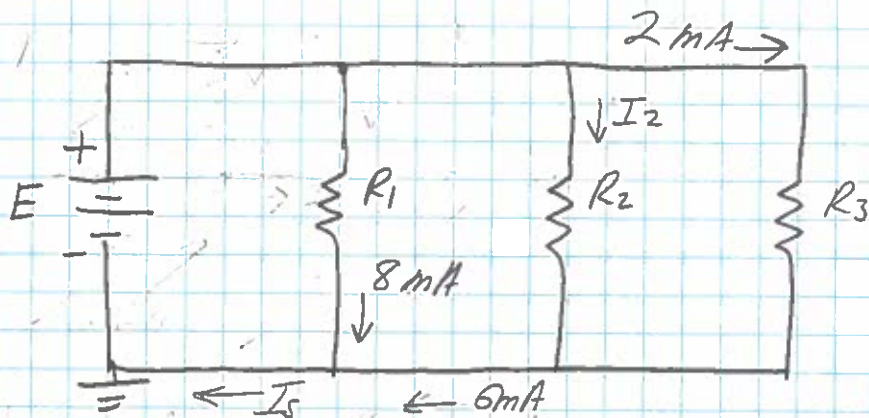

KCL: $8 \text{ mA} + 6 \text{ mA} = I_5 \quad \therefore I_5 = 14 \text{ mA}$

KCL: $I_2 + 2 \text{ mA} = 6 \text{ mA} \quad \therefore I_2 = 4 \text{ mA}$

26)

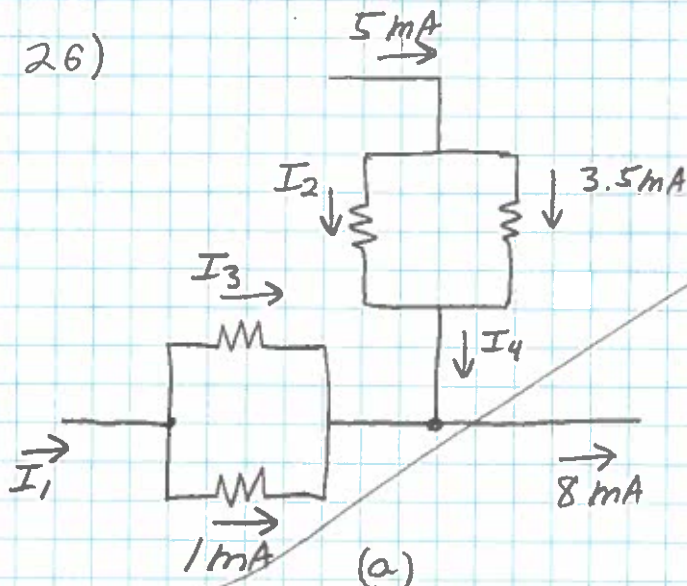

FIND THE UNKNOWN CURRENTS

$I_2 = 5 \text{ mA} - 3.5 \text{ mA} = 1.5 \text{ mA}$


$I_4 = I_2 + 3.5 \text{ mA} = 5 \text{ mA}$

$I_3 = 8 \text{ mA} - I_4 - 1 \text{ mA} = 2 \text{ mA}$

$I_1 = 1 \text{ mA} + I_3 = 3 \text{ mA}$

KCL

FIND THE UNKNOWN CURRENTS

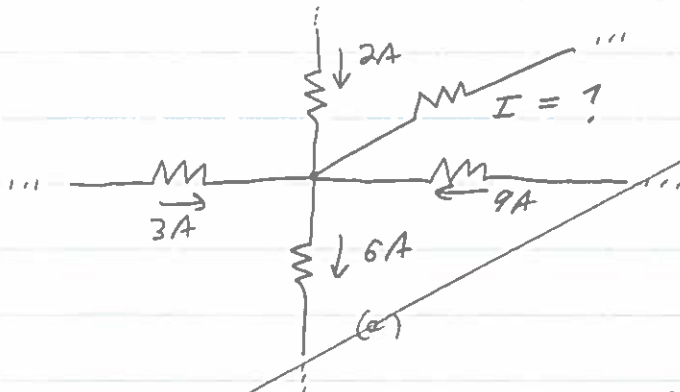


ASSUME I LEAVING (↗ DIRECTION)

$$KCL: 2A + 3A + 9A = I + 6A$$

$$\therefore I = 14 - 6 = \boxed{8A}, \text{ LEAVING, OR } \text{↗ } 8A$$

P286) FIND THE UNKNOWN CURRENTS

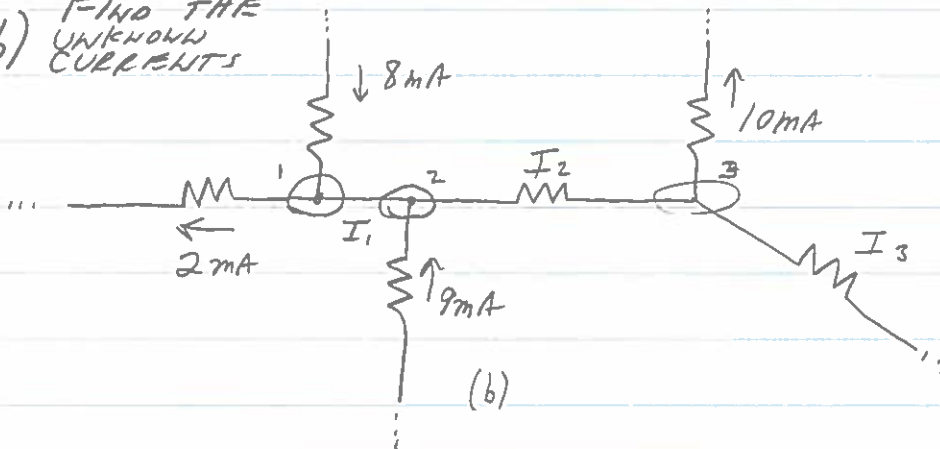

$$KCL @ 1: 8mA = 2mA + I_1 \quad \therefore \boxed{I_1 = 6mA, \text{ TO THE RIGHT}}$$

ASSUME
 $I_1 \rightarrow$ (LEAVING 1)


$$KCL @ 2: 6mA + 9mA = I_2 \quad \therefore \boxed{I_2 = 15mA, \text{ TO THE RIGHT}}$$

ASSUME
 $I_2 \rightarrow$ (LEAVING 2)

$$KCL @ 3: 15mA = 10mA + I_3 \quad \therefore \boxed{I_3 = 5mA, \text{ TO THE RIGHT}}$$

ASSUME
 $I_3 \searrow$ (LEAVING 3)

26)

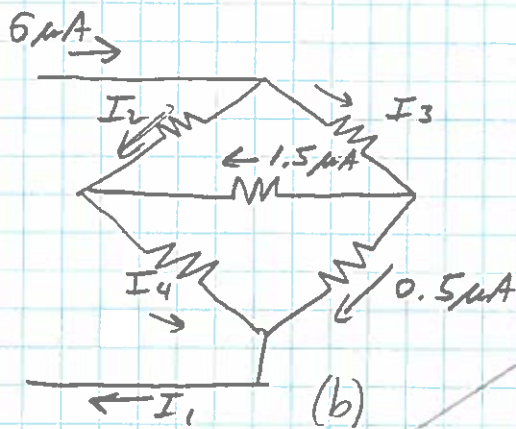

(b)

KCL

$$I_1 = 6 \mu A$$


$$I_4 = 6 \mu A - 0.5 \mu A = 5.5 \mu A$$

$$I_2 + 1.5 \mu A = I_4$$

$$\therefore I_2 = I_4 - 1.5 \mu A = 4 \mu A$$

$$I_3 = 6 \mu A - I_2 = 2 \mu A$$

P33)

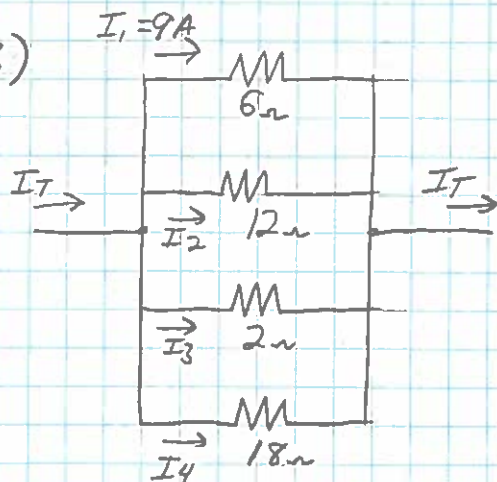

FIND I_2, I_3, I_4 USING
THE RESISTOR VALUES
(NOT OHM'S LAW)

$$I_2 = \left(\frac{1}{2}\right) I_1 = 4.5 A$$

$$I_3 = 3 I_1 = 27 A$$


$$I_4 = \left(\frac{1}{3}\right) I_1 = 3 A$$

THE
CURRENT
DIVIDES IN
INVERSE
PROPORTION
TO
R

$$I_T = I_1 + I_2 + I_3 + I_4, \text{ KCL}$$

$$\therefore I_2 = 43.5 A$$

P41) FIND I_1 & I_2

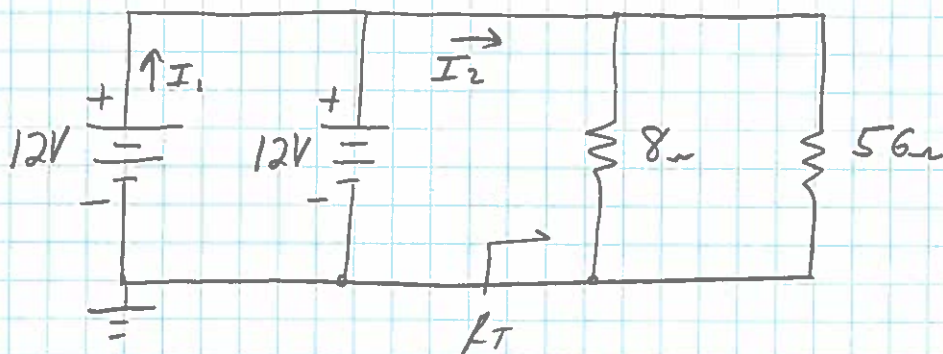


$$R_T = 8\Omega // 56\Omega = 7\Omega$$

$$\therefore I_2 = \frac{12V}{7\Omega} = \boxed{1.714A}$$

$$+ I_1 = \frac{I_2}{2} = \boxed{857.1mA}$$

← IDENTICAL SUPPLIES ASSUMED

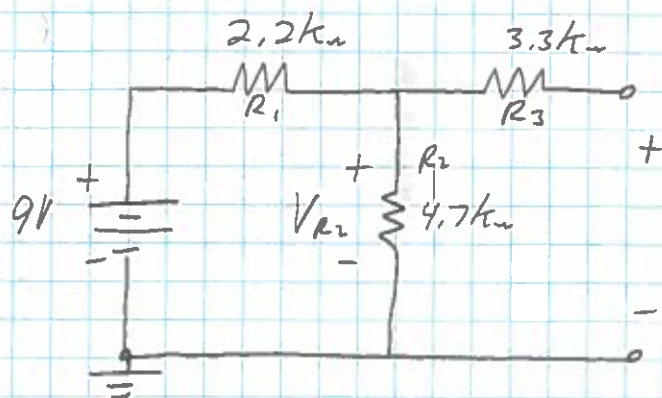

(a) FIND V_L

$$V_L = V_{R2} \quad (R3 \text{ is o/c})$$

$$\therefore V_L = V_{R2} = 9V \left(\frac{4.7k\Omega}{6.9k\Omega} \right) = \boxed{6.13V}$$

(b) IF R_1 is s/c, FIND V_L

$$\boxed{V_L = 9V}$$

SINCE $V_{R2} = 9V$ & $R3$ is o/c


(c) IF R_2 is o/c, FIND V_L

$$\boxed{V_L = 9V}$$

SINCE R_1 & R_3 ARE o/c

39) DESIGN FOR $I_2 = 2I_1$ & $I_3 = 2I_2$

84 mA

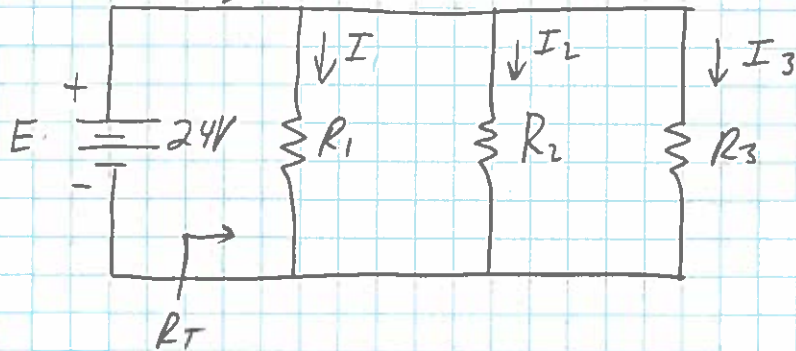

$$R_T = \frac{24\text{V}}{84 \text{ mA}} = 285.7 \Omega$$


$$\text{IF } I_2 = 2I_1, \quad R_2 = \frac{1}{2} R_1$$

$$\text{IF } I_3 = 2I_2, \quad I_3 = 4I_1, \quad \text{HENCE } R_3 = \frac{1}{4} R_1$$

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = 285.7 \Omega$$

$$\text{OR } 285.7 \Omega = \frac{1}{\frac{1}{R_1} + \frac{1}{0.5R_1} + \frac{1}{0.25R_1}}$$
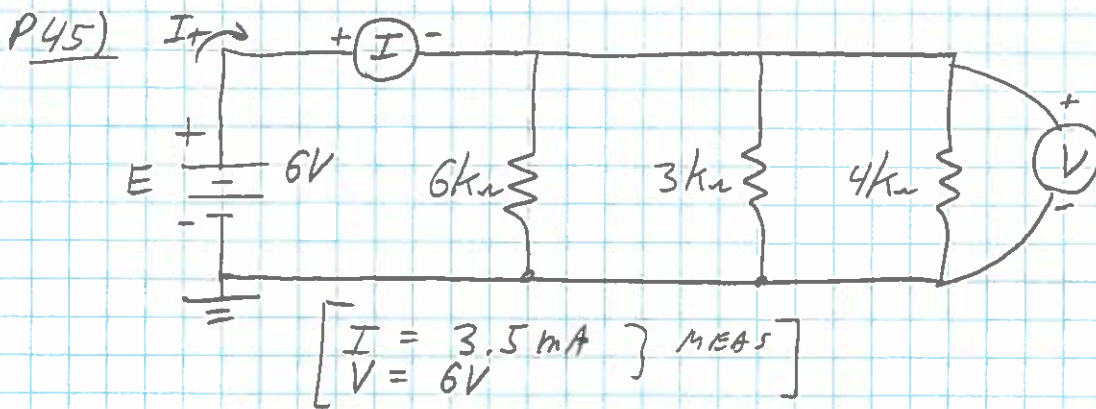
$$\therefore \begin{cases} R_1 = 2 \text{ k}\Omega \\ R_2 = 1 \text{ k}\Omega \\ R_3 = 500 \Omega \end{cases}$$




IS THE CIRCUIT WORKING PROPERLY? EXPLAIN.

$V = 6 \text{ V}$, LOOKS GOOD SINCE $E = 6 \text{ V}$ & IT'S A PARALLEL CIRCUIT

$$I_T = \frac{E}{R_T} = \frac{6 \text{ V}}{1.33 \text{ k}\Omega} = 4.5 \text{ mA CALCULATED} \neq 3.5 \text{ mA MEAS}$$

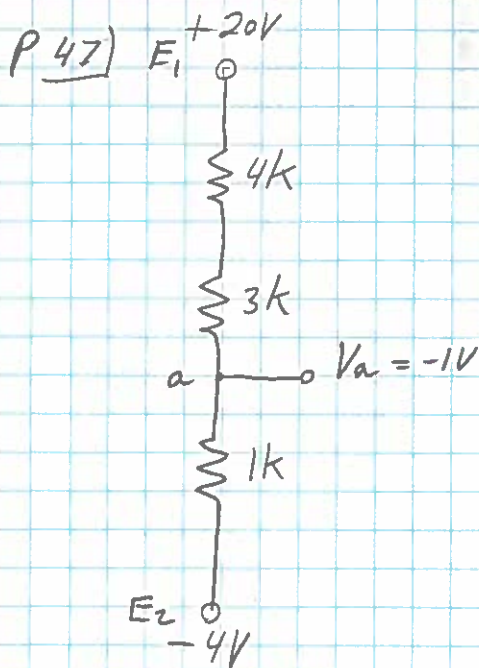IF THE $6 \text{ k}\Omega$ RESISTOR IS O/C, IT WOULD EXPLAIN THE DISCREPANCY



(a) IF V_a JUMPS TO 20 V , WHAT HAPPENED?

THE $1 \text{ k}\Omega$ RESISTOR WENT O/C

(b) IF V_a IS 6 V , WHAT IS WRONG W/ THE NETWORK CONSTRUCTION?

USED A 4 V SOURCE INSTEAD OF -4 V
 OR
 INC RESISTOR VALUE FOR THE $1 \text{ k}\Omega$