


Electrical Engineering Technology

Mesh Analysis Introduction


Fall 2018 (2181)

Breakout #1 (from Friday)

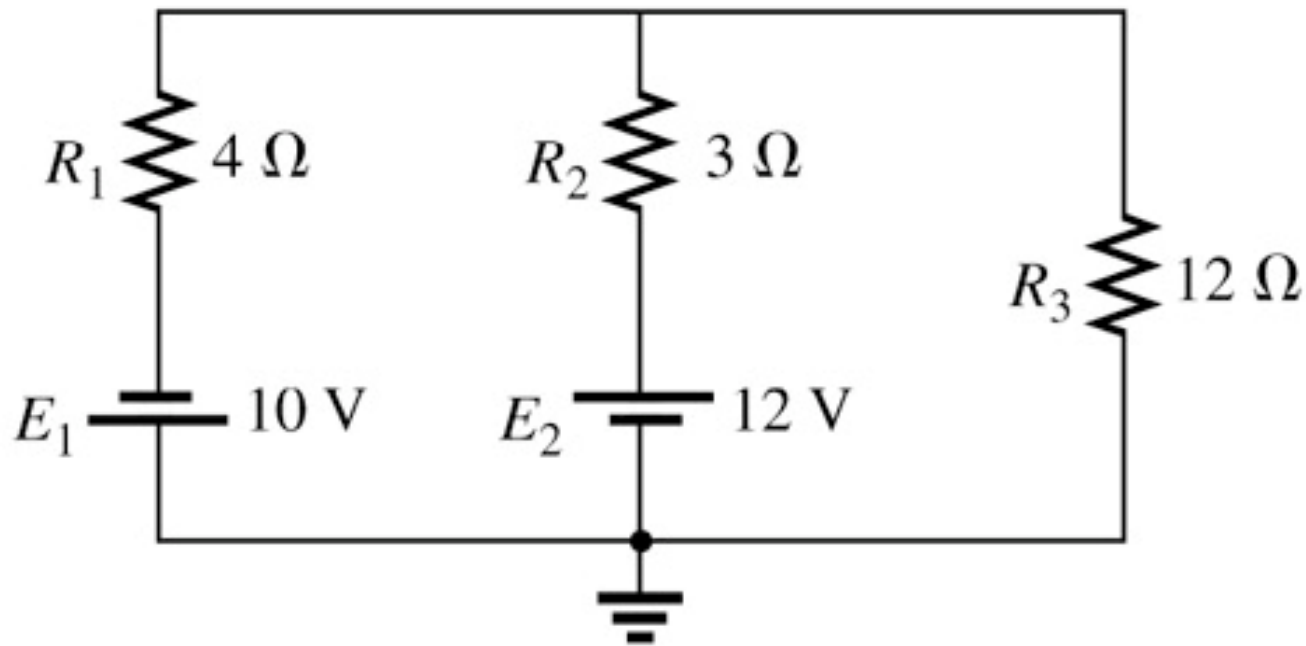- Find P_{E1} , P_{R2} and the current through R_3



Breakout #1

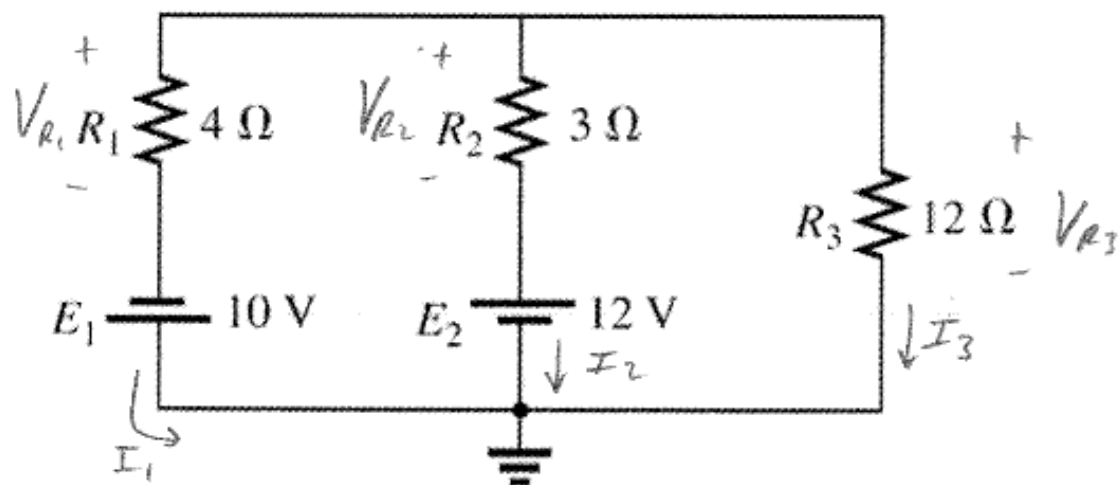

$$\text{KVL } -10 + V_{R1} - V_{R2} - 12 = 0$$

$$4I_1 - 3I_2 = 22 \quad (1)$$

$$\text{KVL } +12 + V_{R2} - V_{R3} = 0$$

$$3I_2 - 12I_3 = -12 \quad (2)$$

$$\text{KCL } -I_1 - I_2 - I_3 = 0$$

$$\text{or } I_1 + I_2 + I_3 = 0 \quad (3)$$

$$\begin{aligned} 4I_1 - 3I_2 + 0I_3 &= 22 \\ 0I_1 + 3I_2 - 12I_3 &= -12 \\ I_1 + I_2 + I_3 &= 0 \end{aligned}$$

SOLVING YIELDS

$$I_1 = 3.063 \text{ A}$$

$$I_2 = -3.25 \text{ A}$$

$$I_3 = 187.5 \text{ mA}$$

$$P_{E1} = (E_1)(I_1) = (10\text{V})(3.063\text{A}) = \boxed{30.63\text{W}}$$

$$P_{R2} = (I_2)^2 R_2 = (-3.25\text{A})^2 (3\Omega) = \boxed{31.69\text{W}}$$

$$I_3 = 187.5 \text{ mA DOWN}$$


8.4 MESH ANALYSIS (GENERAL APPROACH)

- AN ORGANIZED MANNER OF APPLYING BRANCH CURRENT ANALYSIS
- UTILIZES K.V.L. TO SOLVE SIMPLE OR MORE COMPLICATED CIRCUIT ANALYSIS PROBLEMS.

PROCEDURE (ABBREVIATED, SEE PG. 310,311 FOR MORE DETAILS) :

- (1) DRAW THE PLANAR (NO CROSSOVER) NETWORK WITH CLOCKWISE CURRENTS IN EACH "WINDOW."
 - (2) WRITE KVL EQUATIONS FOR EACH LOOP
 - INCREASE VOLTAGE \Rightarrow PLUS
 - VOLTAGE DROP \Rightarrow MINUS
 - TAKE ALL CURRENTS THROUGH EACH COMPONENT INTO ACCOUNT.
 - (3) SIMPLIFY YOUR EQUATIONS & FORMAT.
 - COLLECT TERMS
 - PUT INTO PROPER FORM ($A I_1 + B I_2 + C I_3 + \dots = \#$)
 $\uparrow \quad \uparrow \quad \uparrow$
UNKNOWN
 - (4) SOLVE THE SIMULTANEOUS EQUATIONS
 - SUBSTITUTION (O.K. FOR 2 EQ., DIFFICULT FOR 3 OR MORE)
 - DETERMINANTS METHOD See Appendix B
 - (SHOULD BE REVIEW, SEE APPENDIX D)
- We'll use the Sharp Equation Solver (will handle up to 3x3)
 - You should learn the method of determinants for HW and lab work

(EXAMPLE)

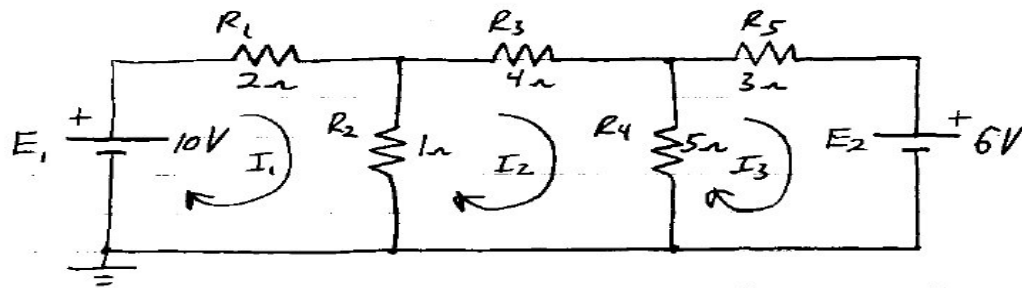

- NOTE LOOP (MESH) CURRENTS I_1 , I_2 & I_3
- RECALL PASSIVE SIGN CONVENTION:



$$\begin{aligned}\text{LOOP 1: } +E_1 - R_1 I_1 - R_2 I_1 + R_2 I_2 &= 0 \\ 10 &= I_1(R_1 + R_2) - R_2 I_2 \\ 10 &= 3I_1 - 1I_2 \rightarrow 3I_1 - I_2 = 10 \quad (1)\end{aligned}$$

$$\begin{aligned}\text{LOOP 2: } -R_2 I_2 + I_1 R_2 - R_3 I_2 - I_2 R_4 + I_3 R_4 &= 0 \\ I_1 R_2 + I_2(-R_2 - R_3 - R_4) + I_3 R_4 &= 0 \\ I_1 - 10I_2 + 5I_3 &= 0 \rightarrow -I_1 + 10I_2 - 5I_3 = 0 \quad (2)\end{aligned}$$

$$\begin{aligned}\text{LOOP 3: } -R_4 I_3 + R_4 I_2 - I_3 R_5 - E_2 &= 0 \\ I_2 R_4 - I_3(R_4 + R_5) &= 6 \\ 5I_2 - 8I_3 &= 6 \rightarrow -5I_2 + 8I_3 = -6 \quad (3)\end{aligned}$$

3 SIMULTANEOUS EQUATIONS:

$$\begin{aligned}3I_1 - I_2 + 0I_3 &= 10 \\ -I_1 + 10I_2 - 5I_3 &= 0 \\ 0I_1 - 5I_2 + 8I_3 &= -6\end{aligned}$$

$$\begin{matrix} \text{UNKNOWN} & & \text{UNKNOWN} \\ \nwarrow & & \nwarrow \\ AI_1 + BI_2 + CI_3 &= & K \text{ FORM} \\ \uparrow & & \uparrow \\ \text{CONSTANT} & & \end{matrix}$$

$$\therefore I_1 = \begin{vmatrix} 10 & -1 & 0 \\ 0 & 10 & -5 \\ -6 & -5 & 8 \end{vmatrix} \begin{matrix} I_1 = 3.312 \text{ A} \\ I_2 = -63.69 \text{ mA} \\ I_3 = -789.8 \text{ mA} \end{matrix}$$


I, COEFFICIENT

$$\begin{vmatrix} 10 & -5 & 8 \end{vmatrix}$$

* DO THIS NOW (CALCULATOR)


NOW, USE THE MESH CURRENTS TO SOLVE FOR THE REQUIRED UNKNOWNNS?

ORIGINAL CIRCUIT :

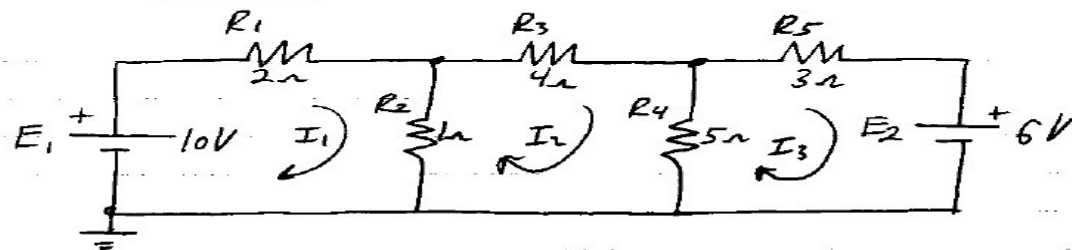


$$\begin{aligned} I_1 &= 3.312 \text{ A} \\ I_2 &= -63.69 \text{ mA} \\ I_3 &= -789.8 \text{ mA} \end{aligned}$$


→ FIND THE CURRENT THROUGH R_1 & R_2 :

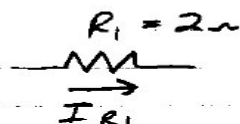
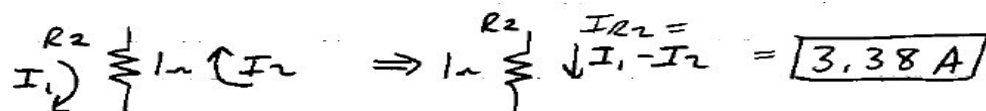
$$\therefore I_{R1} = I_1 = \boxed{3.312 \text{ A}}$$




OR

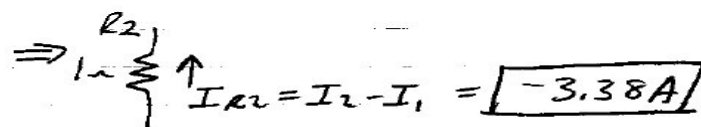


EQUIVALENT

→ FIND V_{R5} & V_{R4} :

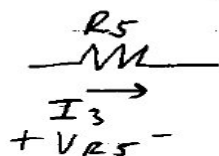

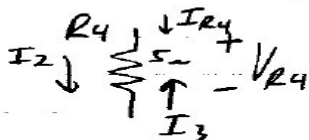
$$V_{R5} = (I_3)(R_5) = (-789.8 \text{ mA})(3\Omega) = \boxed{-2.37 \text{ V}}$$



$$V_{R4} = (I_{R4})(R_4) = (I_2 - I_3)5 = \boxed{3.63 \text{ V}}$$

CHECK : $V_{R4} - V_{R5} - 6 = 0$ $\therefore 3.63 - (-2.37) = 6$ ✓
(KVL)

Breakout Problem 1

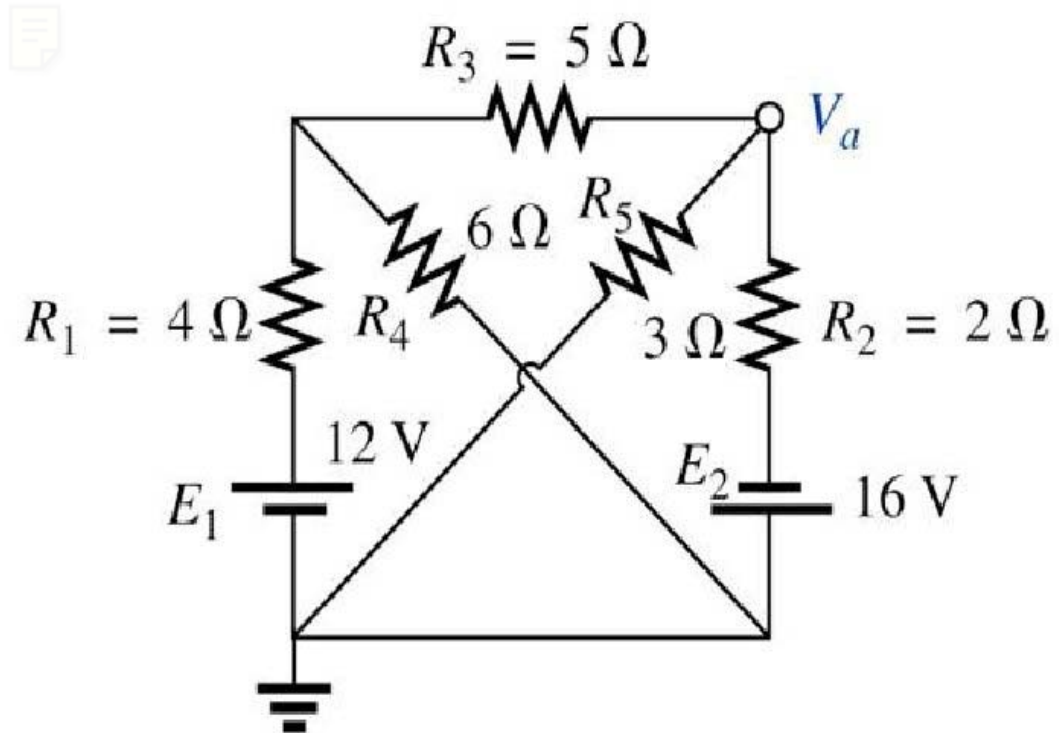


Find:

- 1) The MESH currents I_1, I_2, I_3
- 2) V_a

Use MESH Analysis...

REDRAWN (PLANAR NETWORK)

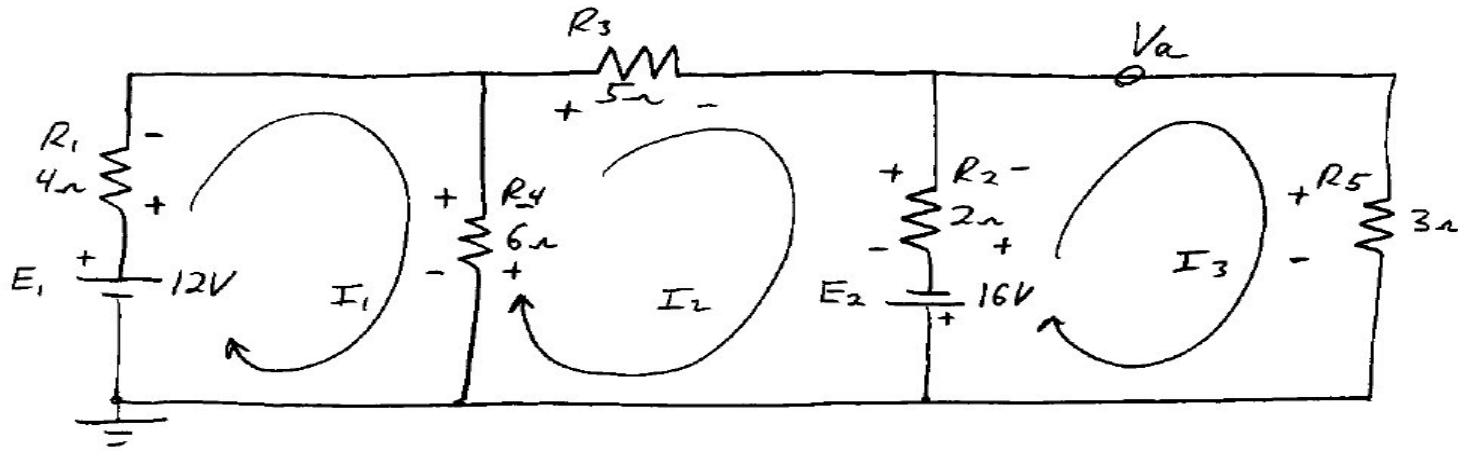

Loop 1 : $E_1 - I_1 R_1 - I_1 R_4 + I_2 R_4 = 0$