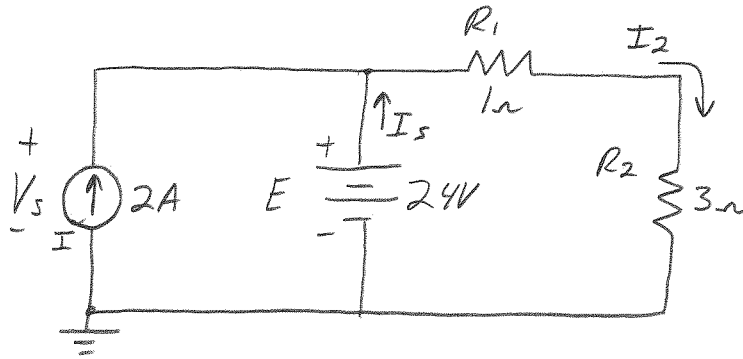


8-4)



a) Find V_s

$$\boxed{V_s = E = 24V}, \quad I \text{ \& } E \text{ ARE IN PARALLEL}$$

b) CALCULATE I_2

$$I_2 = \frac{E}{R_1 + R_2} = \frac{24V}{4\Omega} = \boxed{6A}$$


c) Find I_s

$$\text{KCL: } I + I_s + (-I_2) = 0$$

$$\begin{aligned} I_s &= I_2 - I \\ &= 6A - 2A \end{aligned}$$

$$\boxed{I_s = 4A}$$

(8-5) FIND V_3 + I_2

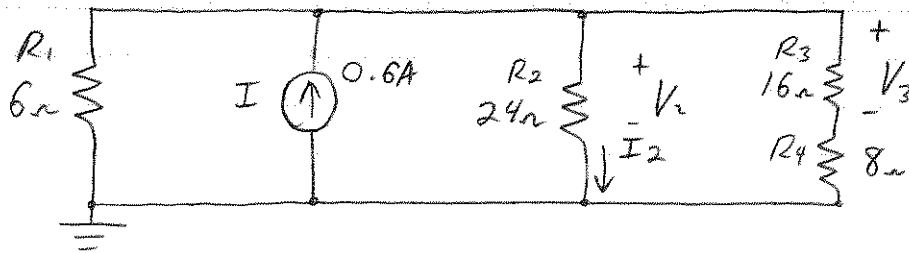

$$I_2 = I_T \left(\frac{R_T}{R_2} \right), \quad I_T = 0.6A$$
$$R_T = R_1 \parallel R_2 \parallel (R_3 + R_4)$$
$$= 4\Omega$$


$$= 0.6A \left(\frac{4\Omega}{24\Omega} \right) = \boxed{100mA}$$

$$V_2 = (I_2)(R_2) = \underline{2.4V}$$

$$V_3 = V_2 \left(\frac{R_3}{R_3 + R_4} \right) = 2.4V \left(\frac{16\Omega}{24\Omega} \right)$$

$$\boxed{V_3 = 1.6V}$$

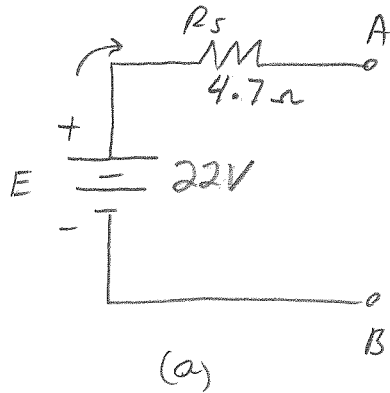
(8-7) CONVERT THE VOLTAGE SOURCES TO CURRENT SOURCES



$$I = \frac{E}{R_s} = \frac{22V}{4.7\Omega} = 4.68A$$


\Rightarrow DIR: UP FROM E

$$R_p = R_s = 4.7\Omega$$

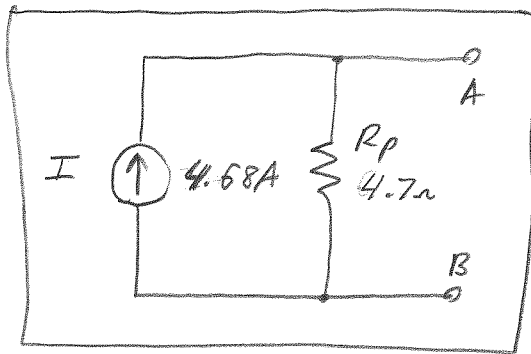

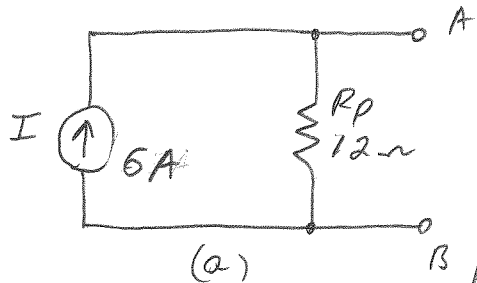(8-8)


CONVERT THE CURRENT SOURCES TO
VOLTAGE SOURCES




$$E = (I)(R_p) = (6A)(12\Omega) = \underline{72V}$$

" + " AT A



$$R_s = R_p = \underline{12\Omega}$$

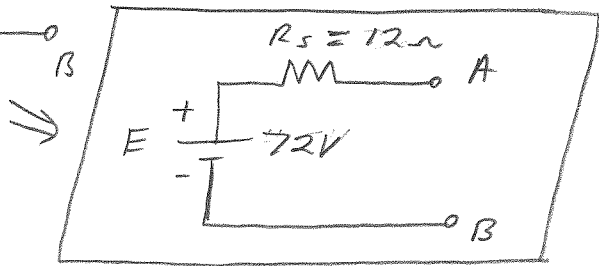

(8-10)

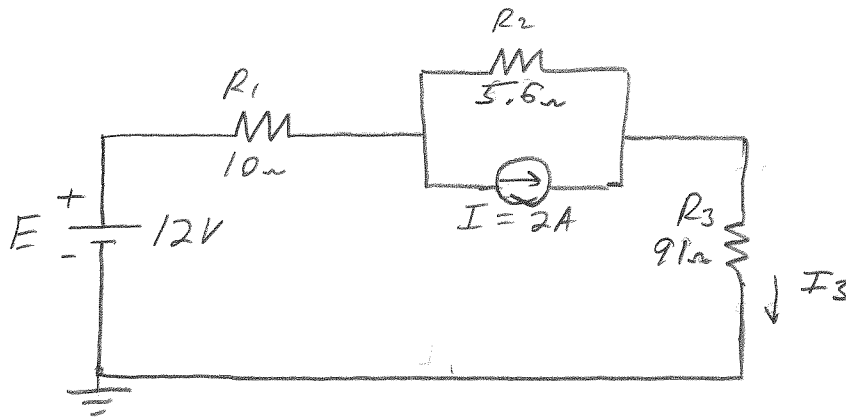


a) CONVERT R_2 & I INTO A VOLTAGE SOURCE

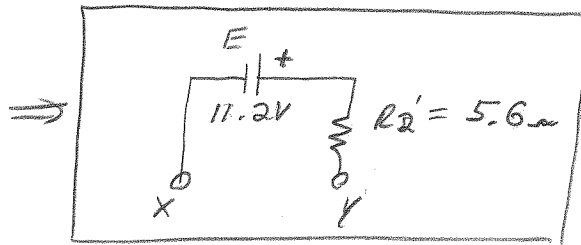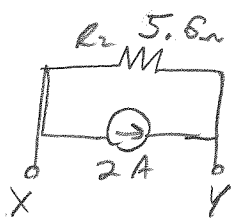

$$E = (2A)(5.6\Omega) \\ = \underline{11.2V}$$


b) COMBINE THE SERIES SOURCES

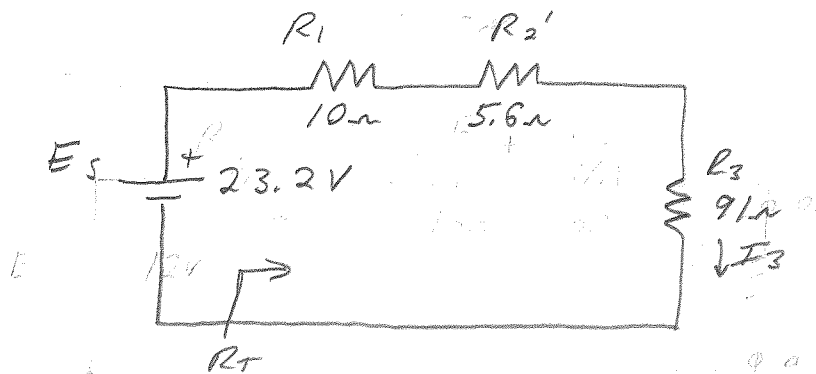

c) FIND I_3


$$I_3 = \frac{E_s}{R_T} = \frac{23.2V}{10\Omega + 5.6\Omega + 91\Omega} = \boxed{217.6 \text{ mA}}$$

(8-11)

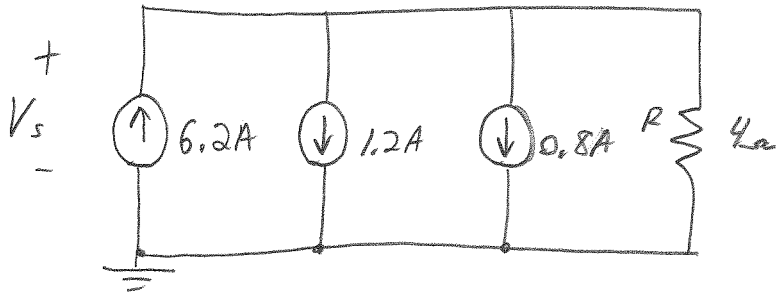

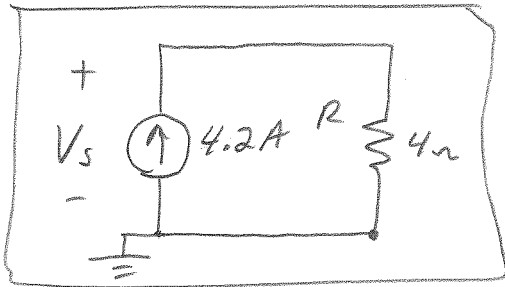a) REPLACE THE CURRENT SOURCES BY A SINGLE EQUIVALENT SOURCE


$$I_{\text{EQUIV}} = 6.2 + (-1.2) + (-0.8) = \boxed{4.2A, \text{up}}$$




b) F/WO V_s

$$V_s = (4.2A)(4\Omega) = \boxed{16.8V}$$

(12) FIND V_s & I_1

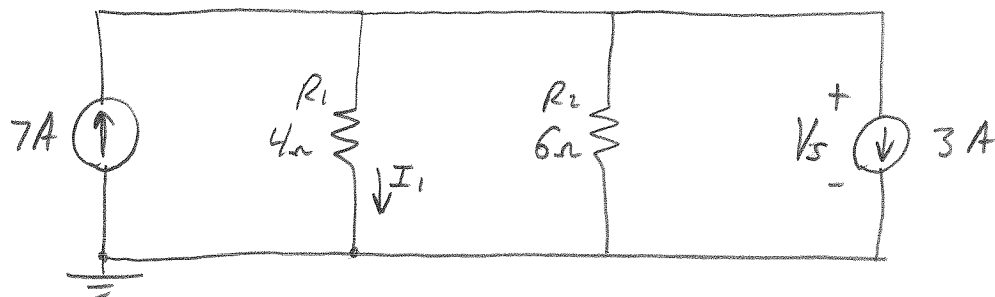

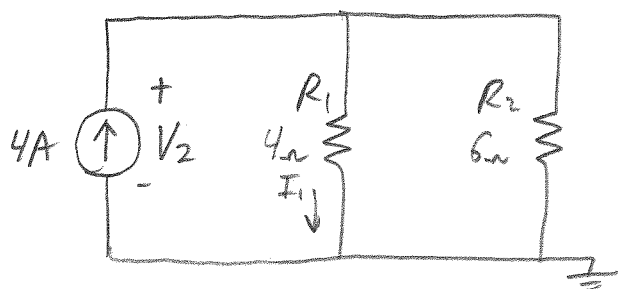- COMBINE THE SOURCES, USE CURRENT DIVIDER




$$I_1 = 4A \left(\frac{4\Omega // 6\Omega}{4\Omega} \right)$$

$$= 4A \left(\frac{2.4\Omega}{4\Omega} \right)$$



$$\boxed{I_1 = 2.4A}$$

$$V_s = (I_1)(R_1) = \boxed{9.6V}$$

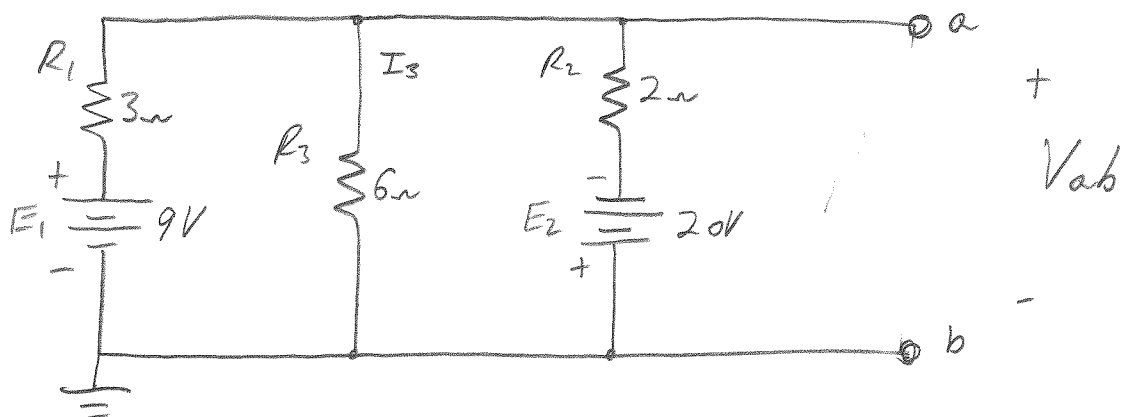
(13) CONVERT THE VOLTAGE SOURCES TO CURRENT SOURCES



(13) CONTINUED

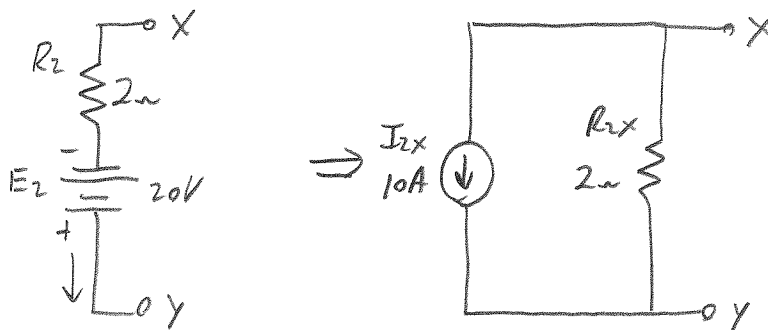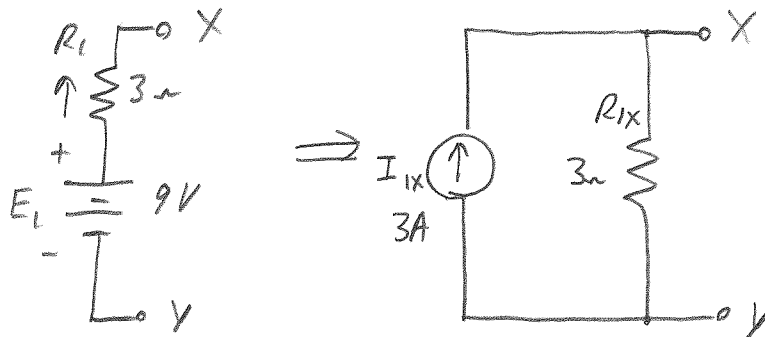


COMBINED, WE HAVE:

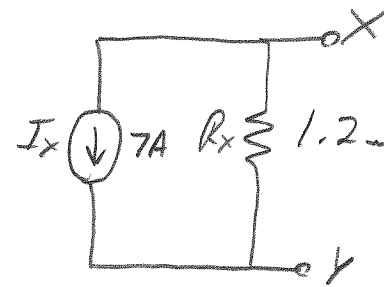

(a)

REDRAWING YIELDS:

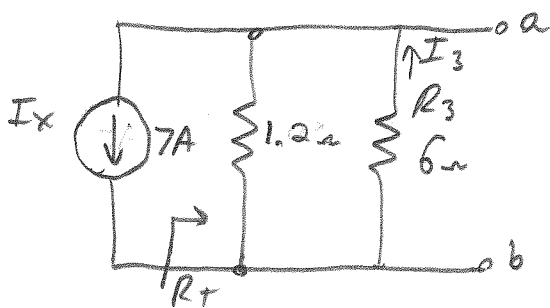

~~a)~~ FIND V_{ab}


$$(b) R_T = 1.2 \Omega // 6 \Omega = 1.0 \Omega$$

$$V_{ab} = (-I_x)(R_T) = \boxed{-7.0 \text{ V}} \therefore V_a < V_b$$

~~b)~~ FIND I_3

$$(c) I_3 = I_x \left(\frac{R_T}{R_3} \right) = 7 \text{ A} \left(\frac{1.0 \Omega}{6 \Omega} \right) = \boxed{1.17 \text{ A, UPWARD}}$$

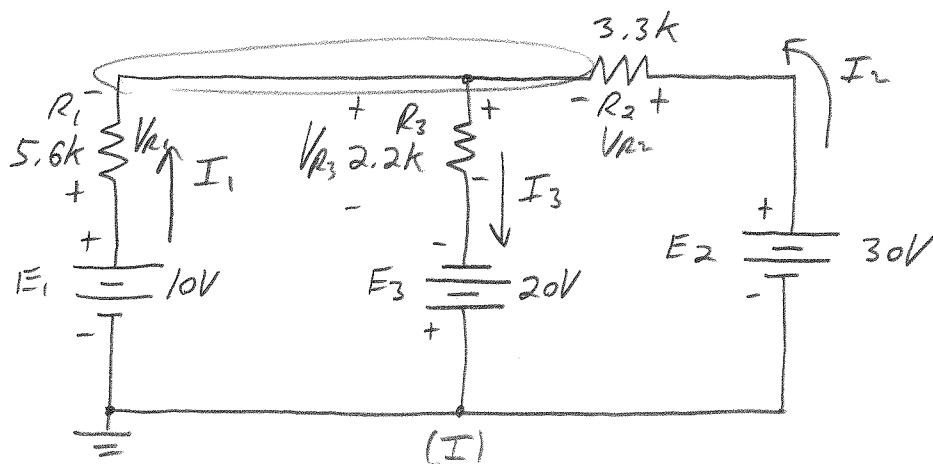(17) USING BRANCH CURRENT ANALYSIS, FIND "I" THROUGH EACH RESISTOR



$$\text{KVL: } E_1 - V_{R1} - V_{R3} + E_3 = 0$$

$$-I_1 R_1 - I_3 R_3 = -E_1 - E_3$$

$$-5.6k I_1 - 2.2k I_3 = -30 \xrightarrow{\text{MULT. BY } (-1)} 5.6k I_1 + 0 I_2 + 2.2k I_3 = 30 \quad (\text{EQ 1})$$

$$\text{KVL: } -E_3 + V_{R3} + V_{R2} - E_2 = 0$$

$$I_3 R_3 + I_2 R_2 = E_2 + E_3$$

$$3.3k I_2 + 2.2k I_3 = 50$$


$$\rightarrow 0 I_1 + 3.3k I_2 + 2.2k I_3 = 50 \quad (\text{EQ 2})$$

$$\text{KCL: } I_1 + I_2 = I_3$$

$$\rightarrow I_1 + I_2 - I_3 = 0 \quad (\text{EQ 3})$$

SOLVING EQ 1 - EQ 3 YIELDS:

$I_1 = 1.45 \text{ mA}$	$\uparrow I_{R1}$
$I_2 = 8.51 \text{ mA}$	$\leftarrow I_{R2}$
$I_3 = 9.96 \text{ mA}$	$\downarrow I_{R3}$

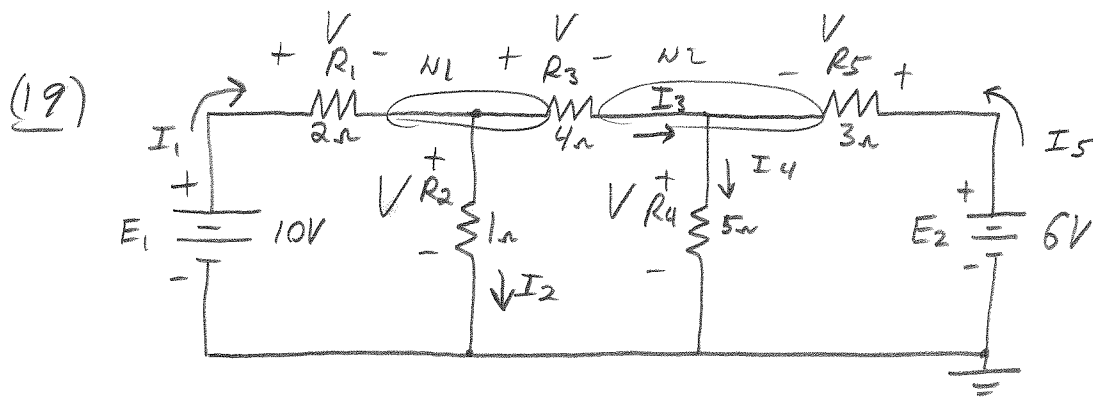

a) WRITE THE EQS TO SOLVE FOR THE BRANCH CURRENTS

KVL: $E_1 - V_{R1} - V_{R2} = 0$

$E - R_1 I_1 - R_2 I_2 = 0 \rightarrow$

$2I_1 + I_2 = 10 \rightarrow 2I_1 + I_2 + 0I_3 + 0I_4 + 0I_5 = 10 \quad (1)$

KVL: $V_{R2} - V_{R3} - V_{R4} = 0$

$R_2 I_2 - R_3 I_3 - R_4 I_4 = 0$

$I_2 - 4I_3 - 5I_4 = 0 \rightarrow 0I_1 + I_2 - 4I_3 - 5I_4 + 0I_5 = 0 \quad (2)$

KVL: $V_{R4} + V_{R5} - E_2 = 0$

$R_4 I_4 + R_5 I_5 = E_2$

$5I_4 + 3I_5 = 6 \rightarrow 0I_1 + 0I_2 + 0I_3 + 5I_4 + 3I_5 = 6 \quad (3)$

KCL @ N1: $I_1 = I_2 + I_3$

$\rightarrow I_1 - I_2 - I_3 + 0I_4 + 0I_5 = 0 \quad (4)$

KCL @ N2: $I_3 + I_5 = I_4$

$\rightarrow 0I_1 + 0I_2 + I_3 - I_4 + I_5 = 0 \quad (5)$

b) REDUCE THE SET TO 3 EQS BY SUBSTITUTION OF KCL

FROM (4): $I_3 = I_1 - I_2$ INTO (1), (2), (3):

(5): $I_5 = I_4 - I_3$

(1): $2I_1 + I_2 + 0I_4 = 10 \rightarrow 2I_1 + I_2 + 0I_4 = 10 \quad (1A)$

(2): $I_2 - 4(I_1 - I_2) - 5I_4 = 0 \rightarrow -4I_1 + 5I_2 - 5I_4 = 0 \quad (2A)$

(3): $5I_4 + 3(I_4 - I_3) = 6$
 $5I_4 + 3I_4 - 3I_3 = 6$
 $5I_4 + 3I_4 - 3(I_1 - I_2) = 6$
 $\rightarrow -3I_1 + 3I_2 + 8I_4 = 6 \quad (3A)$

(18) CONTINUED

c) RE WRITE THE EQS IN A FORMAT TO SOLVE w/
3RD ORDER DETERMINANTS
- SEE PART b

d) SOLVE FOR I_3

SOLVING (1A) - (3A) YIELDS:

$$\begin{aligned} I_1 &= 3.312 \text{ A} \\ I_2 &= 3.376 \text{ A} \\ I_4 &= 726.1 \text{ mA} \end{aligned}$$

FROM (4) $I_3 = I_1 - I_2$

$I_3 = -64 \text{ mA}$, LEFT TO RIGHT

(19) CONTINUED

b) FIND V_B , V_C + V_E

$$V_B = I_{E R_E} + V_{BE} = (4.479 \text{ mA})(510 \Omega) + 0.7 \text{ V}$$
$$\boxed{V_B = 2.98 \text{ V}}$$

$$V_C = I_{E R_E} + V_{CE} = 2.284 \text{ V} + 8 \text{ V}$$
$$\boxed{V_C = 10.28 \text{ V}}$$

$$V_E = I_{E R_E} = \boxed{2.28 \text{ V}}$$

c) FIND $\frac{I_C}{I_B} = \beta_{dc}$

$$\beta_{dc} = \frac{4.416 \text{ mA}}{63.02 \mu\text{A}} = \boxed{70.07}$$