
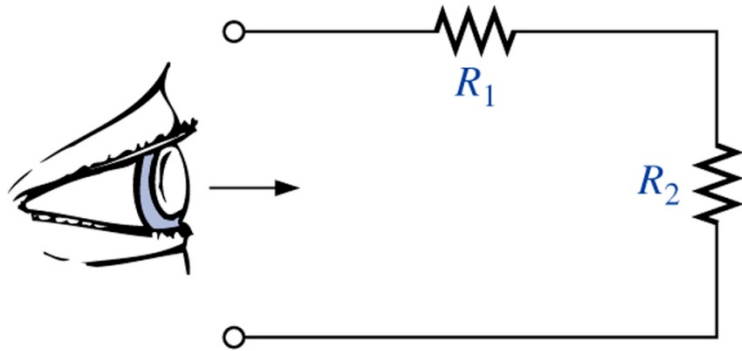


Series Resistance

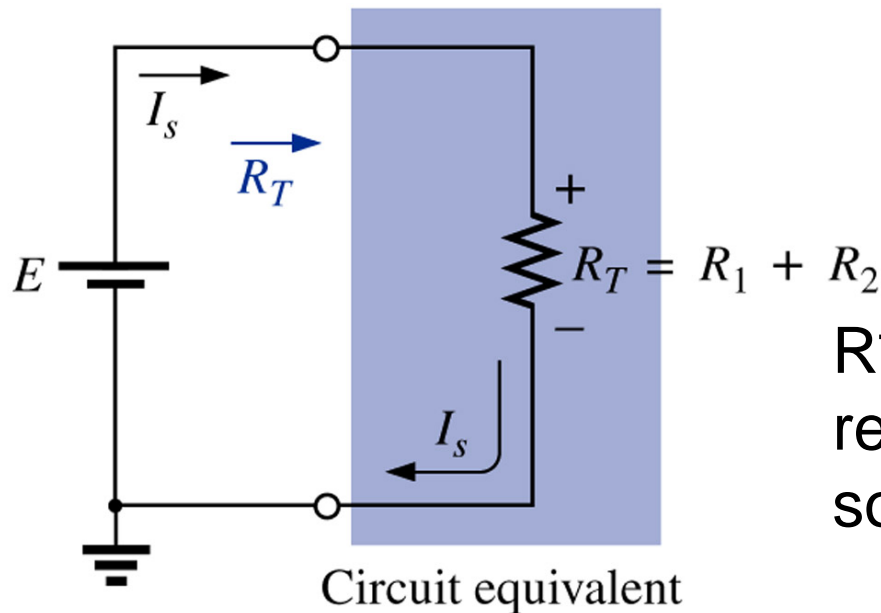

What is the resistance “seen” looking into the series combination of R_1 and R_2 ?



R_T is the equivalent resistance seen by the source “E”

Series Resistance – Breakout #1

- The equivalent resistance of a series circuit with four resistors is 138 k-ohms.

Find R_4 if:

- ☐ $R_1 = 56 \text{ k-ohms}$
- ☐ $R_2 = 22 \text{ k-ohms}$
- ☐ $R_3 = 33 \text{ k-ohms}$

Series Circuit Analysis – Breakout #2

- In the circuit shown below, if $V_{R2} = 878.0 \text{ mV}$, calculate the following:
 - (a) I
 - (b) R_T
 - (c) R_4
 - (d) The power delivered by the source

