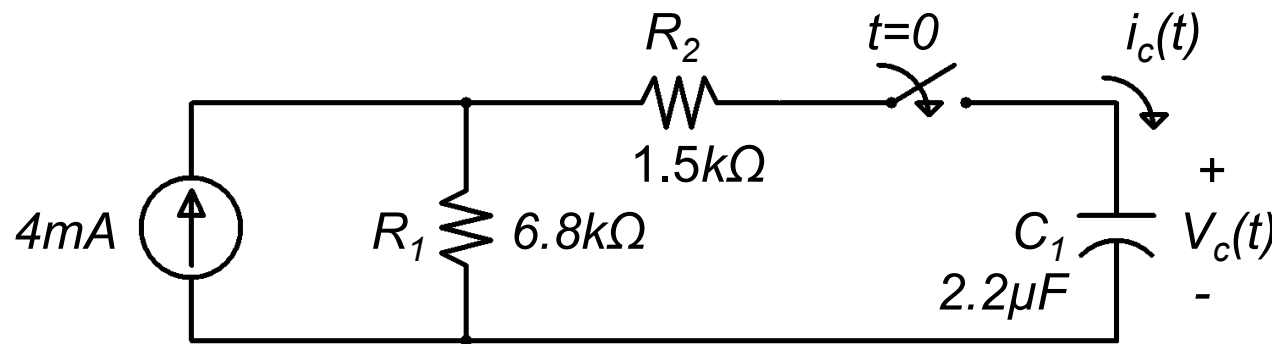


# *Electrical Engineering Technology*

## Capacitor Charging – Initial Values

## Initial Values

- (Example) a) Find  $V_c(t)$  &  $i_c(t)$  for  $t > 0$   
b) Sketch  $V_c(t)$  &  $i_c(t)$




$V_c(t) = 2\text{V}$   
@  $t = 0^-$  (Initial Charge)

What's our first step??

IN CLASS PROBLEM

∴ We have:

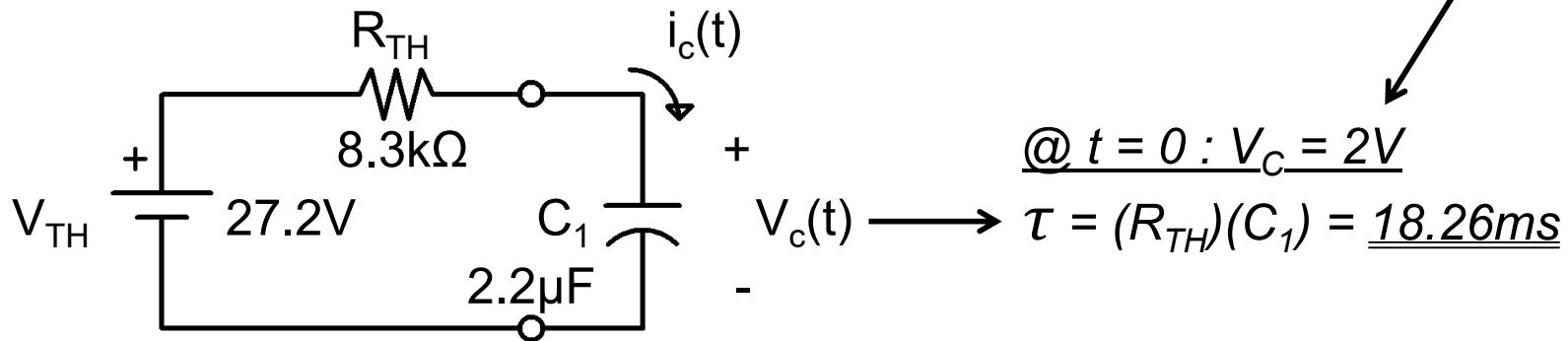

$$@ t = 0^+ : i_c(t) = i_{cmax} = \frac{V_{TH} - 2V}{R_{TH}} = \frac{(27.2 - 2)V}{8.3k\Omega} = \underline{3.036 mA}$$

$$\therefore i_c(t) = 3.036 \times 10^{-3} e^{-t/\tau} \text{ A, } t > 0$$

$$\tau = 18.26ms$$

If there was no initial charge on C1:

$$V_C(t) = V_{TH} \left( 1 - e^{-t/\tau} \right) \quad V, t \geq 0$$

→ From 0V to  $V_{TH}$  over time

$$V_C(t) = \underset{\substack{\uparrow \\ \text{Final} \\ \text{value}}}{V_{TH}} - \underbrace{V_{TH} * e^{-t/\tau}}_{\substack{\text{Transient} \\ \text{period}}}$$

$$t = 0 : \frac{V_C}{0} \quad (\text{Initial})$$

$$t = \infty : V_{TH} \quad (\text{Final})$$

$$V_C(t) = V_F + \underset{\substack{\uparrow \\ \text{Initial } V_C}}{(0 - V_F)} e^{-t/\tau}$$


General charge eq.

With:  $V_C(0) = 2V : V_C(t) = V_F + (V_I - V_F) e^{-t/\tau}$

Arrows in the diagram point from  $V_{TH}$  to  $V_F$  and from  $2V$  to  $V_I$  in the boxed equation above.

Becomes:  $V_C(t) = 27.2 + (2 - 27.2)e^{-t/18.26 \times 10^{-3}} \quad V, t \geq 0$

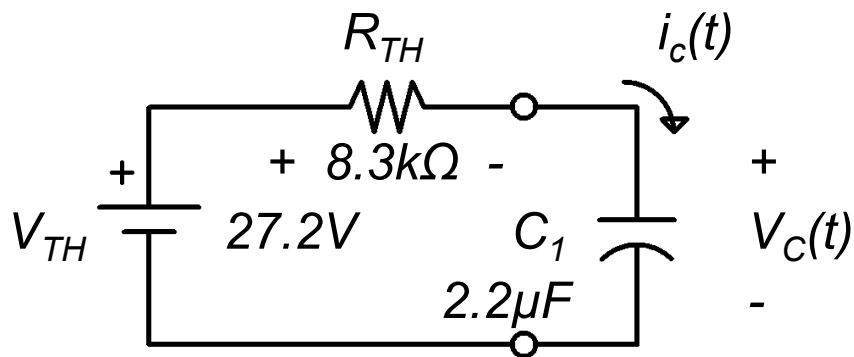\* Alternate determination of  $V_C(t)$  :



$$\left[ \begin{array}{l} i_c(t) = 3.036 \times 10^{-3} e^{-t/\tau} \\ \tau = 18.26 \text{ ms} \\ \& V_c(0) = 2V \end{array} \right]$$

Use  $V_{TH} - i_c(t)R_{TH} - V_c(t) = 0$


**KVL:**  $\therefore V_c(t) = V_{TH} - i_c(t)R_{TH}$

$$\therefore V_C(t) = 27.2 - (3.036 \cdot 10^{-3} \cdot e^{-t/\tau}) (8.3 \cdot 10^3)$$

$$V_C(t) = 27.2 - 25.2 \cdot e^{-t/18.26 \cdot 10^{-3}} V, t \geq 0$$

Same as:  $V_C(t) = 27.2 + (2 - 27.2)e^{-t/18.26 \times 10^{-3}} V, t \geq 0$
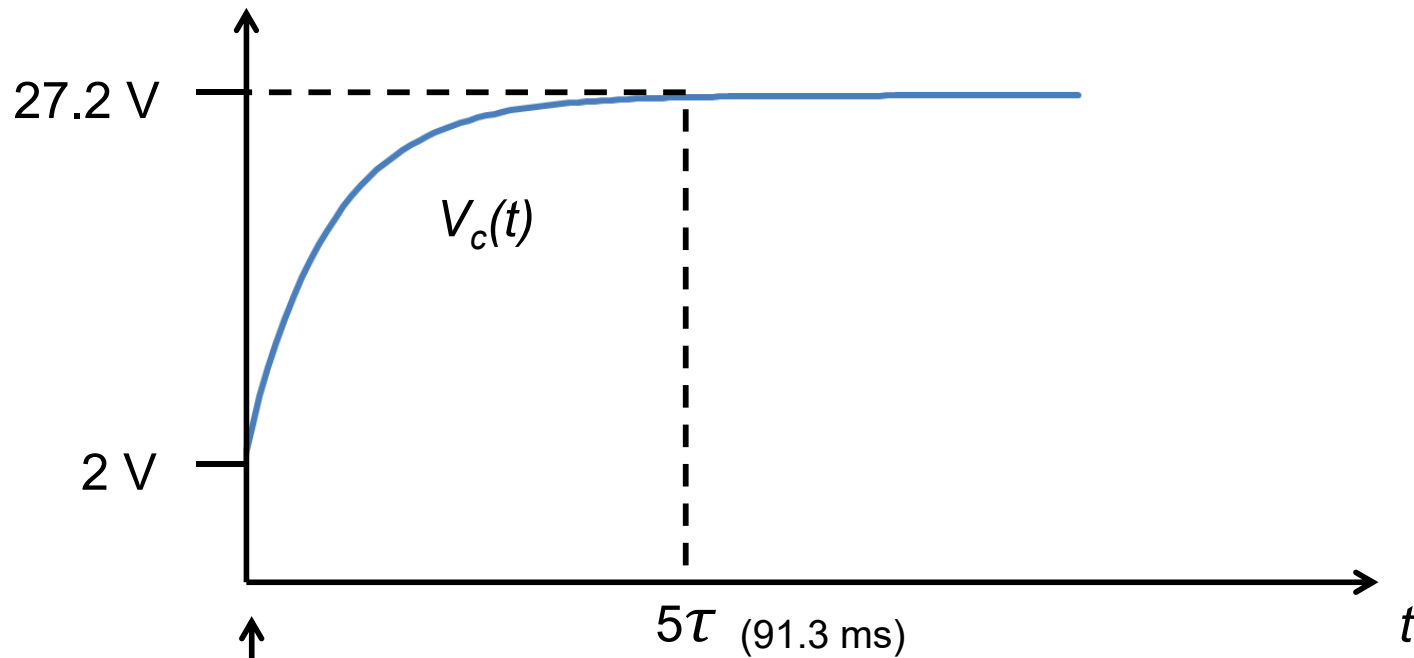
$$V_C(t) = 27.2 - 25.2 \cdot e^{-t/18.26 \cdot 10^{-3}} \text{ V}, t \geq 0$$




3.036 mA

$i_c(t)$

$$i_c(t) = 3.036 \times 10^{-3} e^{-t/\tau} \text{ A}, t > 0$$
$$\tau = 18.26 \text{ ms}$$

$5\tau$

$t$

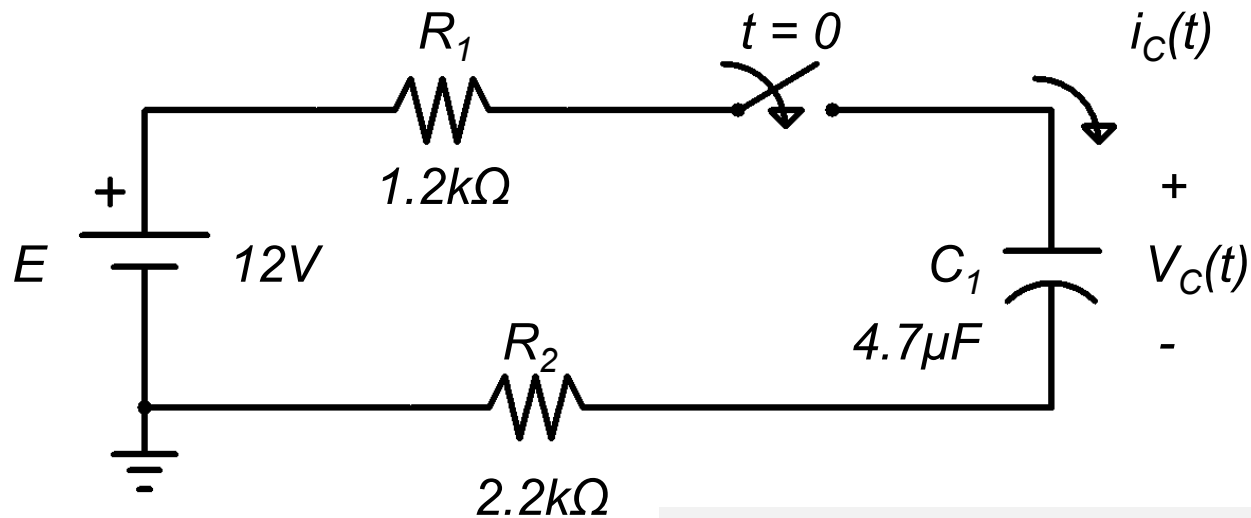

Given:  $V_C(0) = 4V$ , initial charge

(a) Find  $V_C(t)$ ,  $t \geq 0$

(b)  $i_C(t)$ ,  $t > 0$

(c) Sketch  $V_C(t)$  &  $i_C(t)$

(b)

IN CLASS PROBLEM

IN CLASS PROBLEM