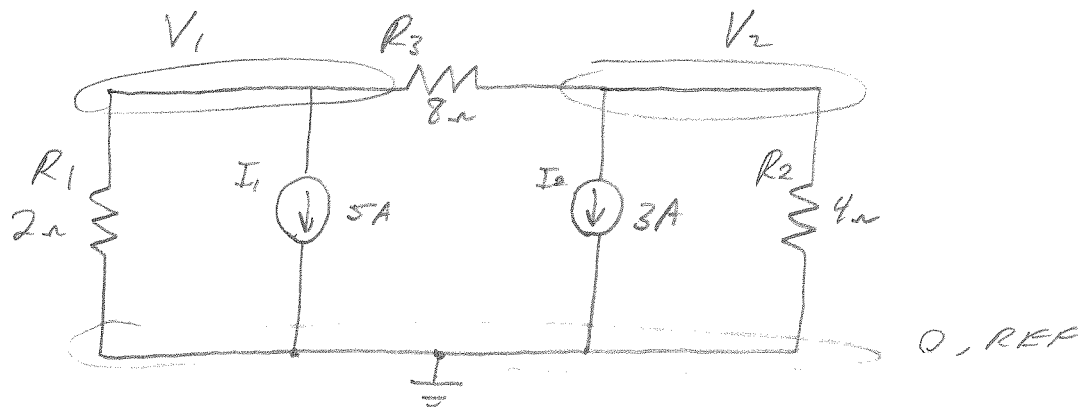


(P40) A - WRITE THE NODAL EQS

P41

B - SOLVE



$$V_1] \sum I_{\text{ENTERING}} = \sum I_{\text{LEAVING}}$$

$$0A = I_1 + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_3}$$

$$-I_1 = V_1 \left(\frac{1}{R_1} + \frac{1}{R_3} \right) - V_2 \left(\frac{1}{R_3} \right)$$

$$\text{OR: } 0.625 V_1 - 0.125 V_2 = -5 \quad (1)$$

$$V_2] 0 = I_2 + \frac{V_2}{R_2} + \frac{V_2 - V_1}{R_3}$$

$$-I_2 = -V_1 \left(\frac{1}{R_3} \right) + V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\text{OR: } -0.125 V_1 + 0.375 V_2 = -3 \quad (2)$$

SOLVING YIELDS :

$$\boxed{V_1 = -10.29V}$$
$$\boxed{V_2 = -11.43V}$$


(C) FIND V_{R3}

$$\textcircled{V_1} \xrightarrow[R_3 \ 8\Omega]{+ \quad -} \textcircled{V_2}$$

$$V_{R3} = V_1 - V_2 = \boxed{1.14V}$$


~~P40~~ **P41** CONTINUED

(d) FIND THE CURRENT THROUGH R_1 + R_2

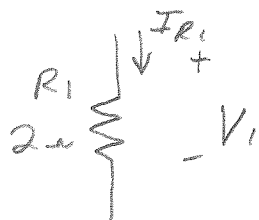

$$I_{R1} = \frac{V_1}{R_1} = \frac{-10.29V}{2\Omega} = -\underline{5.15A}$$
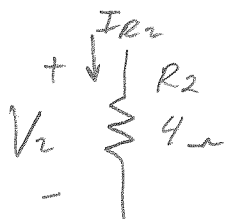
$$\therefore I_{R1} = 5.15A \uparrow (UP)$$




$$I_{R2} = \frac{V_2}{R_2} = \frac{-11.43V}{4\Omega} = -\underline{2.86A}$$

$$\therefore I_{R2} = 2.86A \uparrow (UP)$$

(P41) A+B: WRITE THE NODAL EQS & FIND THE NODE VOLTAGES

P42

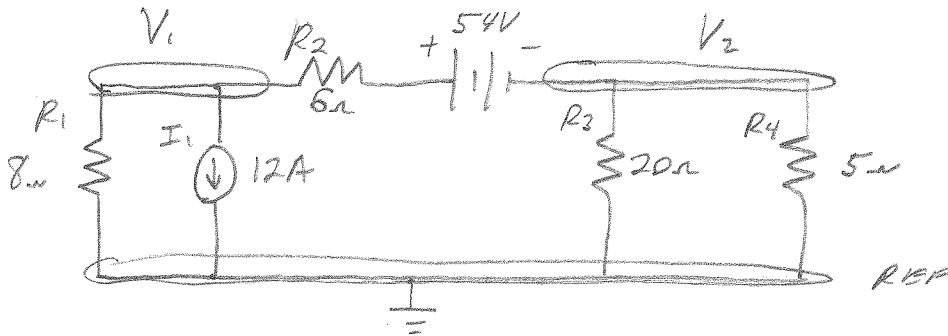


CONVERT $R_2 / 54V$ TO A PRACTICAL CURRENT SOURCE



$$R_2' = R_2 = 6\Omega$$

$$I_s = 54V / 6\Omega = 9A$$

REDRAWN

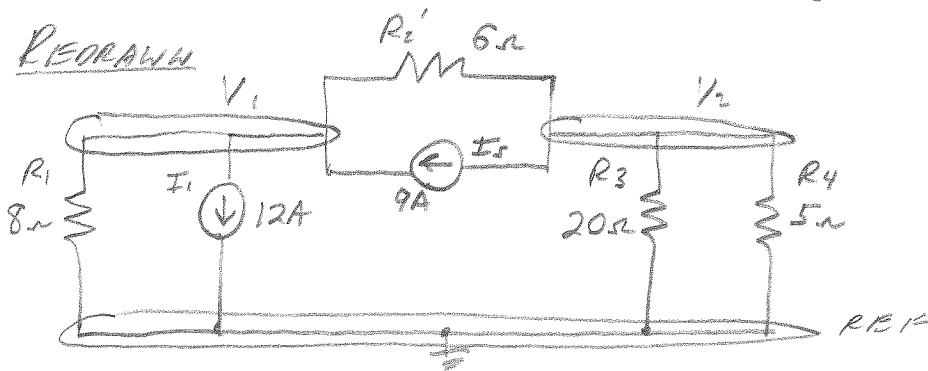

$$V_1] \quad I_s = I_1 + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2'}$$

$$I_s - I_1 = V_1 \left(\frac{1}{R_1} + \frac{1}{R_2'} \right) - V_2 \left(\frac{1}{R_2'} \right)$$

$$\text{OR: } 0.2917 V_1 - 0.1667 V_2 = -3 \quad (1)$$

$$V_2] \quad 0 = I_s + \frac{V_2 - V_1}{R_2'} + \frac{V_2}{R_3} + \frac{V_2}{R_4}$$

$$-I_s = -V_1 \left(\frac{1}{R_2'} \right) + V_2 \left(\frac{1}{R_2'} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$\text{OR: } -0.1667 V_1 + 0.417 V_2 = -9 \quad (2)$$

P42


~~(P41)~~ CONTINUED

Solving (1) + (2) Yields:

$$V_1 = -29.32V$$

$$V_2 = -33.30V$$

(C) FIND THE CURRENT THROUGH R_3

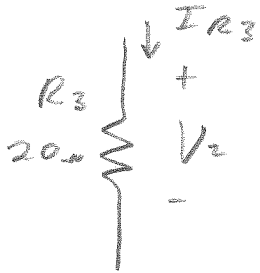


$$I_{R_3} = \frac{V_2}{R_3} = \frac{-33.30V}{20\Omega} = \underline{-1.67A \downarrow}$$

$$\text{OR } I_{R_3} = 1.67A \uparrow (\text{UP})$$

P44

(P43) a+b: WRITE THE NODAL EQS + SOLVE

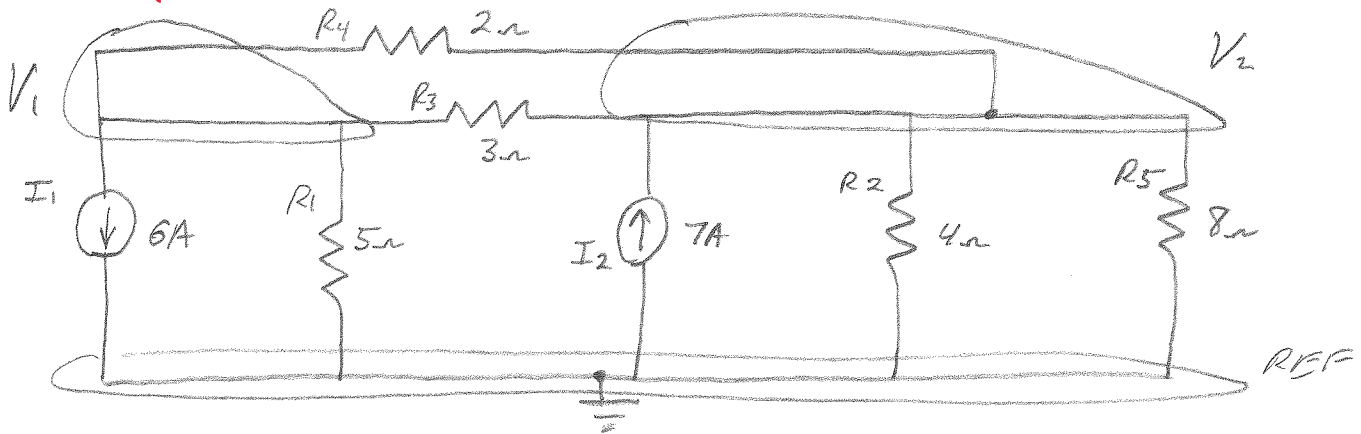


$$\begin{aligned}
 V_1] \quad 0 &= I_1 + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_4} + \frac{V_1 - V_2}{R_3} \\
 -I_1 &= V_1 \left(\frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3} \right) - V_2 \left(\frac{1}{R_4} + \frac{1}{R_3} \right) \\
 \text{OR: } 1.033 V_1 - 0.833 V_2 &= -6 \quad (1)
 \end{aligned}$$

$$\begin{aligned}
 V_2] \quad I_2 &= \frac{V_2 - V_1}{R_4} + \frac{V_2 - V_1}{R_3} + \frac{V_2}{R_2} + \frac{V_2}{R_5} \\
 I_2 &= -V_1 \left(\frac{1}{R_4} + \frac{1}{R_3} \right) + V_2 \left(\frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_5} \right) \\
 \text{OR: } -0.833 V_1 + 1.208 V_2 &= 7 \quad (2)
 \end{aligned}$$

Solving yields:


$$\begin{aligned}
 V_1 &= -2.56V \\
 V_2 &= 4.03V
 \end{aligned}$$

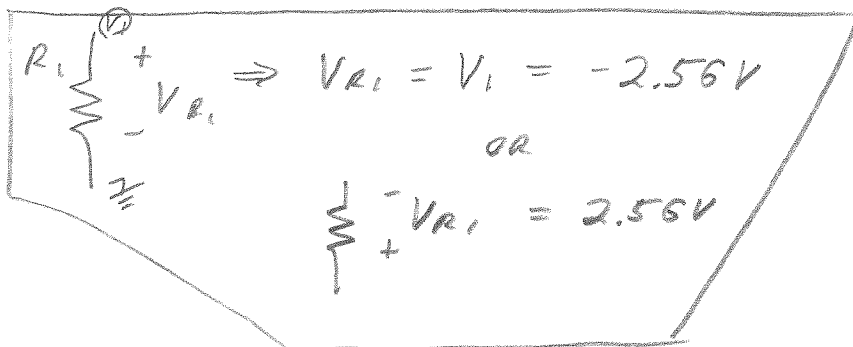(c) FIND THE VOLTAGE ACROSS EACH RESISTOR:



(P43) CONTINUED

$$V_2 = V_{R2} = V_{R5} = V_2 = 4.03V$$

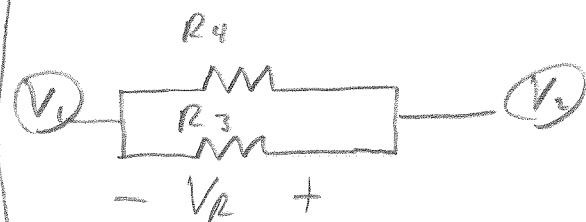


$$V_{R4} = V_{R3} = V_R = V_2 - V_1 = 6.59V$$


(A+B)

EXTRA NODAL SAMPLE PROBLEM #1

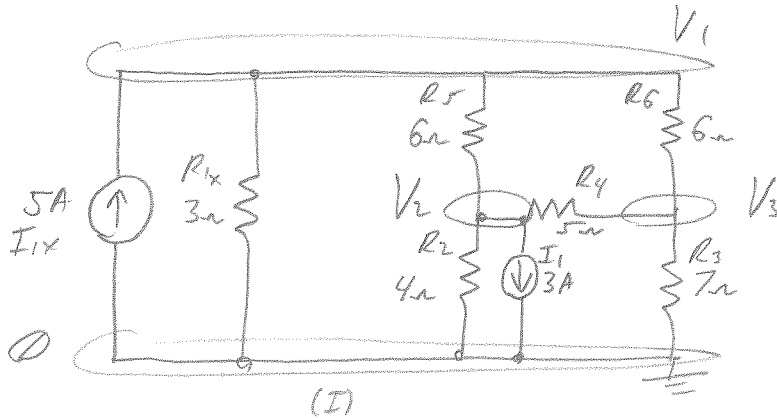(P45) WRITE THE NODAL EQUATIONS & SOLVE FOR THE NODE VOLTAGES



(I) REDRAWN

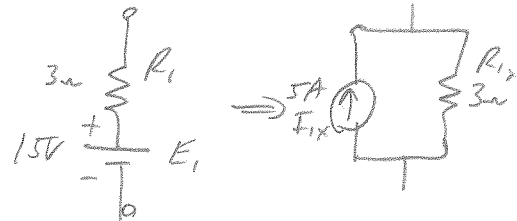

$$\underline{N1} \quad 5 = \frac{V_1}{R_{1X}} + \frac{V_1 - V_2}{R_5} + \frac{V_1 - V_3}{R_6} \rightarrow 0.6667V_1 - 0.1667V_2 - 0.1667V_3 = 5 \quad (1)$$

$$\underline{N2} \quad 0 = \frac{V_2 - V_1}{R_5} + \frac{V_2 - V_3}{R_4} + \frac{V_2}{R_2} + 3 \rightarrow -0.1667V_1 + 0.6167V_2 - 0.200V_3 = -3 \quad (2)$$

$$\underline{N3} \quad 0 = \frac{V_3 - V_1}{R_6} + \frac{V_3 - V_2}{R_4} + \frac{V_3}{R_3} \rightarrow -0.1667V_1 - 0.200V_2 + 0.5095V_3 = 0 \quad (3)$$

SOLVING (1) - (3) YIELDS:

$$\begin{aligned} V_1 &= 7.24V \\ V_2 &= -2.45V \\ V_3 &= 1.41V \end{aligned}$$

(C) FIND V_{R4} 


$$V_{R4} = V_3 - V_2$$

$$\boxed{V_{R4} = 3.86V}$$

A+B - SOLVE FOR V_1, V_2, V_3

(P46)

EXTRA NODAL SAMPLE PROBLEM #2

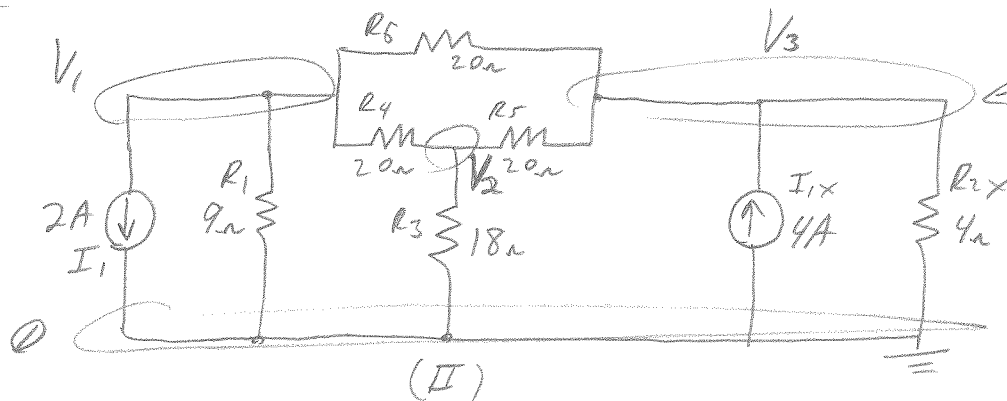

REDRAWN w/ E_1/R_2
CONVERTED TO
 I_{1x} & R_{2x}

$$N1 \quad 0 = 2 + \frac{V_1}{R_1} + \frac{V_1 - V_3}{R_6} + \frac{V_1 - V_2}{R_4} \rightarrow 0.2111V_1 - 0.050V_2 - 0.050V_3 = -2 \quad (1)$$


$$N2 \quad 0 = \frac{V_2 - V_1}{R_4} + \frac{V_2}{R_3} + \frac{V_2 - V_3}{R_5} \rightarrow -0.050V_1 + 0.1556V_2 - 0.050V_3 = 0 \quad (2)$$

$$N3 \quad 4 = \frac{V_3}{R_{2x}} + \frac{V_3 - V_2}{R_5} + \frac{V_3 - V_1}{R_6} \rightarrow -0.050V_1 - 0.050V_2 + 0.350V_3 = 4 \quad (3)$$

SOLVING VOLTAGES:

$$\begin{aligned} V_1 &= -6.64V \\ V_2 &= 1.29V \\ V_3 &= 10.66V \end{aligned}$$

(C) FIND V_{R6}

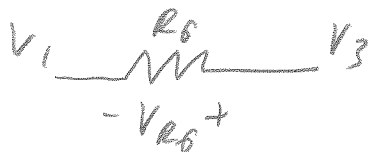


$$V_{R6} = V_3 - V_1 = 17.30V$$

~~(P44)~~ **P50**

DETERMINE THE NODAL VOLTAGES (USE MODIFIED SUPER-NODE)

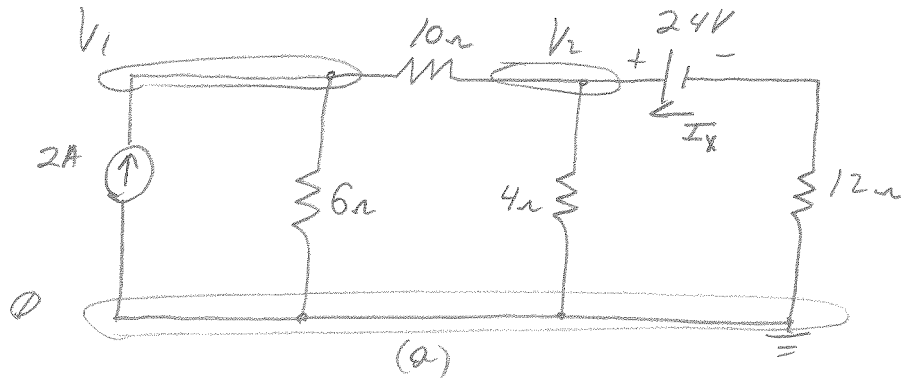- DO NOT PERFORM $V \rightarrow I$ CONVERSION



$$\underline{N1}: 2 = \frac{V_1}{6} + \frac{V_1 - V_2}{10} \rightarrow 0.2667V_1 - 0.10V_2 + 0I_x = 2 \quad (1)$$


$$\underline{N2}: I_x = \frac{V_2 - V_1}{10} + \frac{V_2}{4} \rightarrow -0.10V_1 + 0.350V_2 - I_x = 0 \quad (2)$$

$$\underline{I_x}: I_x = \frac{0 - (V_2 - 24)}{12} \text{ or } 12I_x = -V_2 + 24$$
$$0V_1 - V_2 - 12I_x = -24 \quad (3)$$

SOLVING (1) - (3):

$V_1 = 10.1V$
$V_2 = 6.95V$
$I_x = 1.42A$

Q1) Find the node voltages

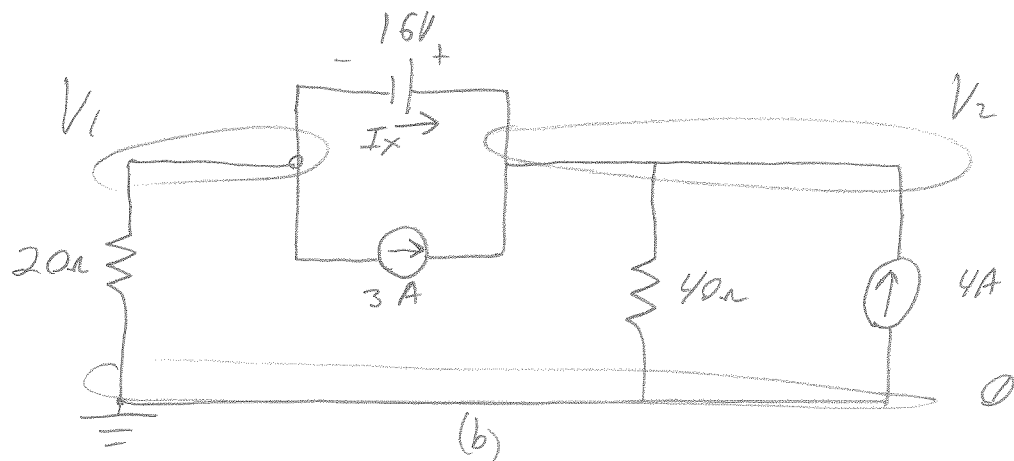

$$N1 \quad 0 = \frac{V_1}{20} + 3 + I_x \rightarrow 0.050 V_1 + 0 V_2 + I_x = -3 \quad (1)$$


$$N2 \quad 3 + 4 + I_x = \frac{V_2}{40} \rightarrow 0 V_1 + 0.025 V_2 - I_x = 7 \quad (2)$$

$$\text{Also know: } V_2 - V_1 = 16 \rightarrow -V_1 + V_2 + 0 I_x = 16 \quad (3)$$

Solving yields:


$V_1 = 48.0V$
$V_2 = 64.0V$
$I_x = -5.4A$

P9.2

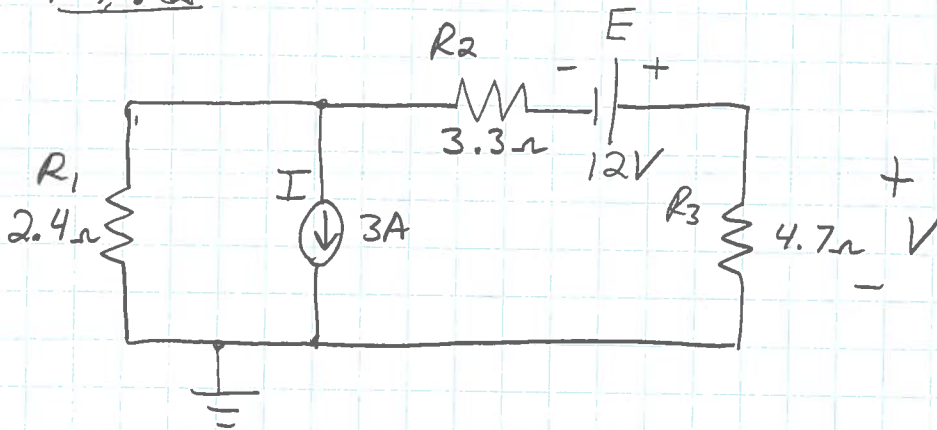

a) FIND V USING SUPERPOSITION

(SOURCE I ACTIVE ONLY)

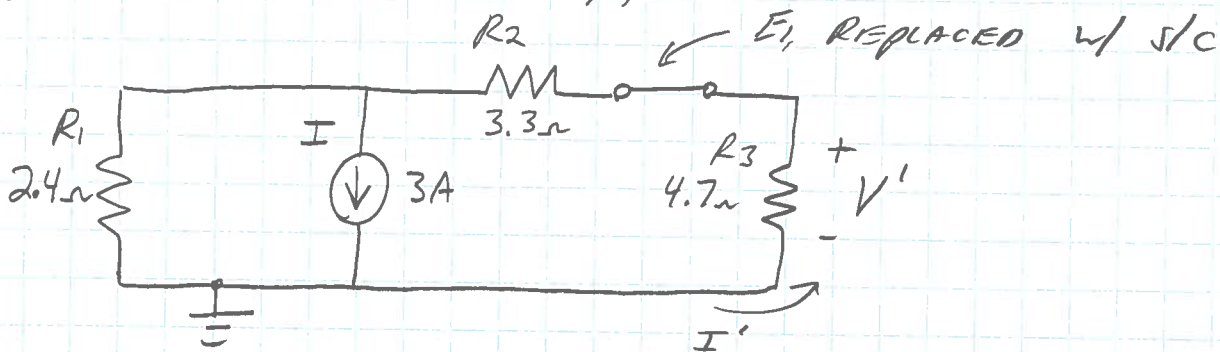


$$I' = I \left(\frac{[R_2 + R_3] // R_1}{[R_2 + R_3]} \right) = 3A \left(\frac{8\Omega // 2.4\Omega}{8\Omega} \right)$$

$$I' = 3A \left(\frac{1.85\Omega}{8\Omega} \right) = \underline{692.3 \text{ mA}}$$

$$\therefore V' = (-I')(R_3) = (-692.3 \text{ mA})(4.7\Omega) \\ = \underline{\underline{-3.25V}}$$

(SOURCE E ACTIVE ONLY)

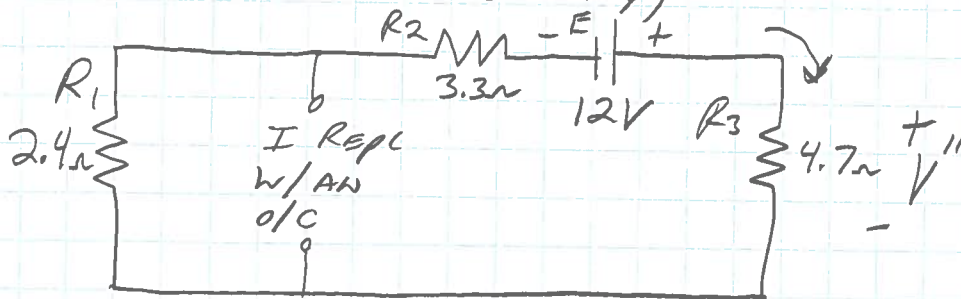

$$V'' = E \left(\frac{R_3}{R_1 + R_2 + R_3} \right) \\ = 12V \left(\frac{4.7\Omega}{10.4\Omega} \right)$$

$$\underline{\underline{V'' = 5.42V}}$$

$$V = V' + V'' = -3.25V + 5.42V = \boxed{2.17V}$$

(P9.2 CONTINUED)

(b) FIND P_{R3} DUE ^{ONLY} TO SOURCE I

$$P_{R3}' = \frac{(V')^2}{R_3} = \frac{(-3.25V)^2}{4.7\Omega} = \boxed{2.25W}$$

(c) FIND P_{R3} DUE ONLY TO SOURCE E

$$P_{R3}'' = \frac{(V'')^2}{R_3} = \frac{(5.42V)^2}{4.7\Omega} = \boxed{6.25W}$$

(d) FIND P_{R3} USING THE RESULT FROM PART (c)

$$P_{R3} = \frac{V^2}{R_3} = \frac{(2.17V)^2}{4.7\Omega} = \boxed{1.00W}$$

(e) COMPARE THE RESULTS OF PART (d) WITH THE SUM OF PARTS (b) + (c). CAN SUPERPOSITION BE USED W/ POWER LEVELS?

$$P_{R3} (\text{ACTUAL}) = P_{R3, \text{PART(d)}} = \underline{\underline{1.00W}}$$

$$\begin{aligned} P_{R3} (\text{SUPERPOSITION DIRECT}) &= P_{R3, (b)} + P_{R3, (c)} \\ &= 2.25W + 6.25W \\ &= \underline{\underline{8.5W}} \end{aligned}$$

$$\therefore \boxed{P_{R3} (\text{ACTUAL}) \neq P_{R3} (\text{SUPERPOSITION DIRECT})}$$

SUPERPOSITION CAN NOT BE DIRECTLY APPLIED TO POWER LEVELS, ONLY TO VOLTAGE & CURRENT LEVELS.