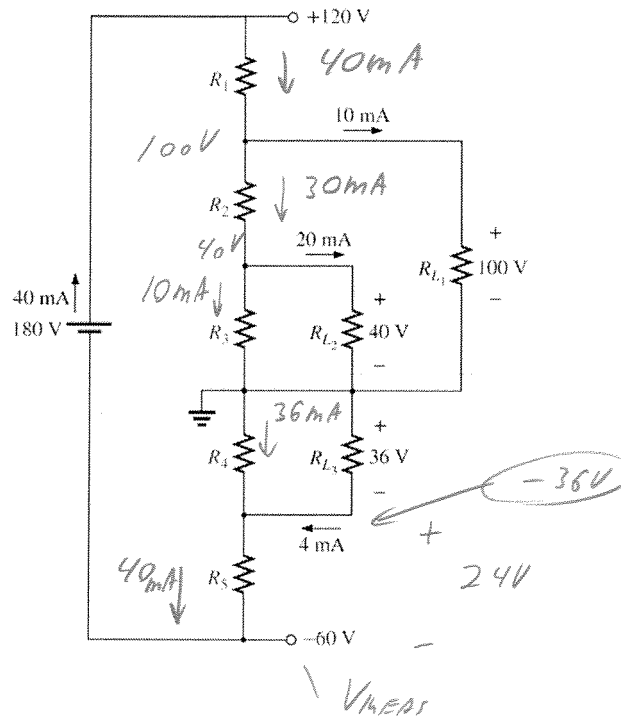


# Breakout #1 (review)

## Find R1 through R5



$$R_1 = \frac{100V}{40mA} = 2.5k\Omega$$

$$R_2 = \frac{40V}{30mA} = 1.33k\Omega$$

$$R_3 = \frac{40V}{10mA} = 4k\Omega$$

$$R_4 = \frac{36V}{36mA} = 1k\Omega$$

$$R_5 = \frac{24V}{40mA} = 600\Omega$$