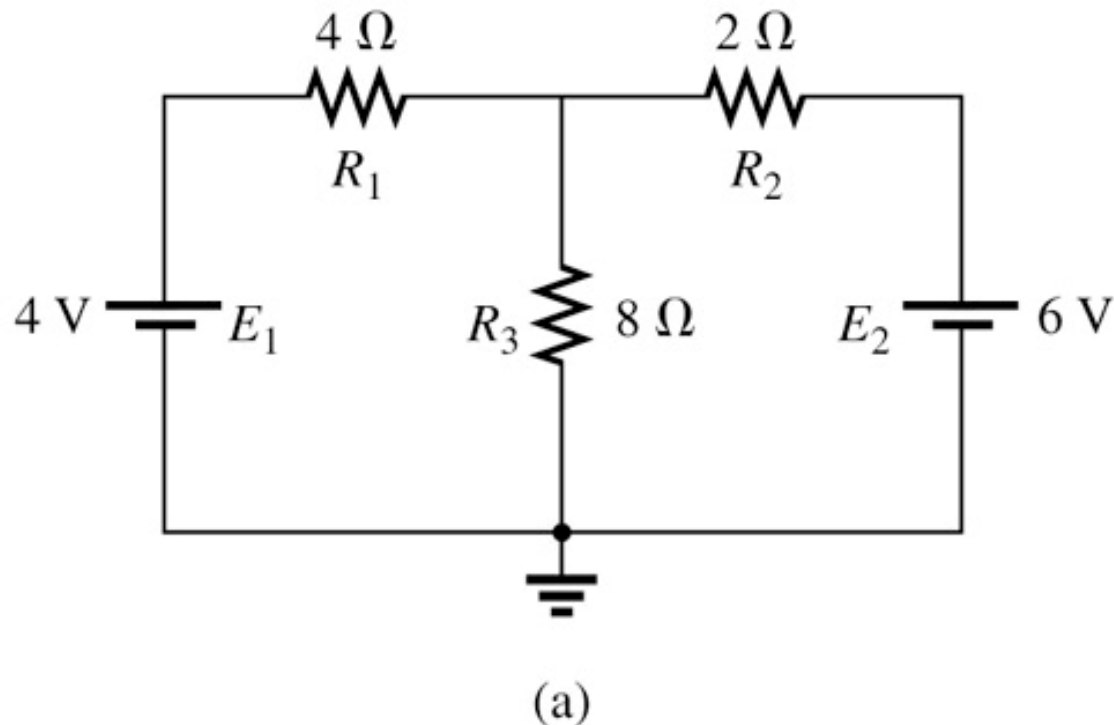


Today's Material

- Branch Current Analysis (with example)
- Breakout #1
 - Branch current analysis problem

Branch Current Analysis (by example)


- Find V_{R3} and the power delivered by E_2
 - Any thoughts?
 - Can we combine circuit elements in series or parallel?



Branch Current Analysis (by example)

■ Method

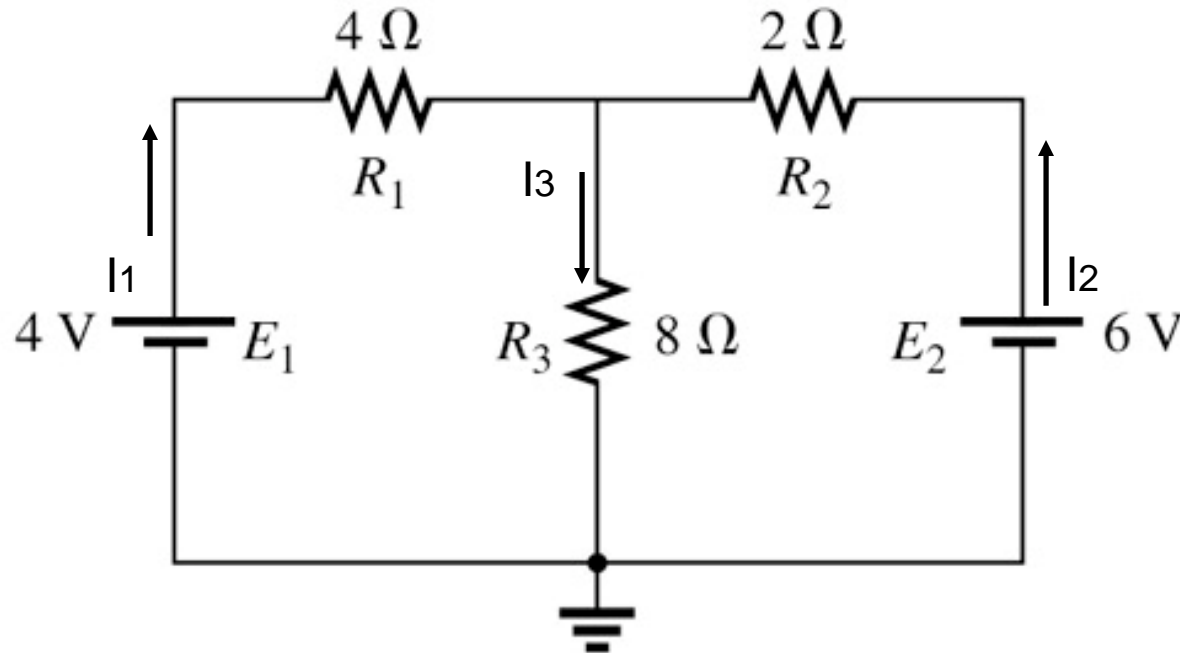1. Assign an arbitrary current to each branch of the network




(a)

Branch Current Analysis (by example)

■ Method

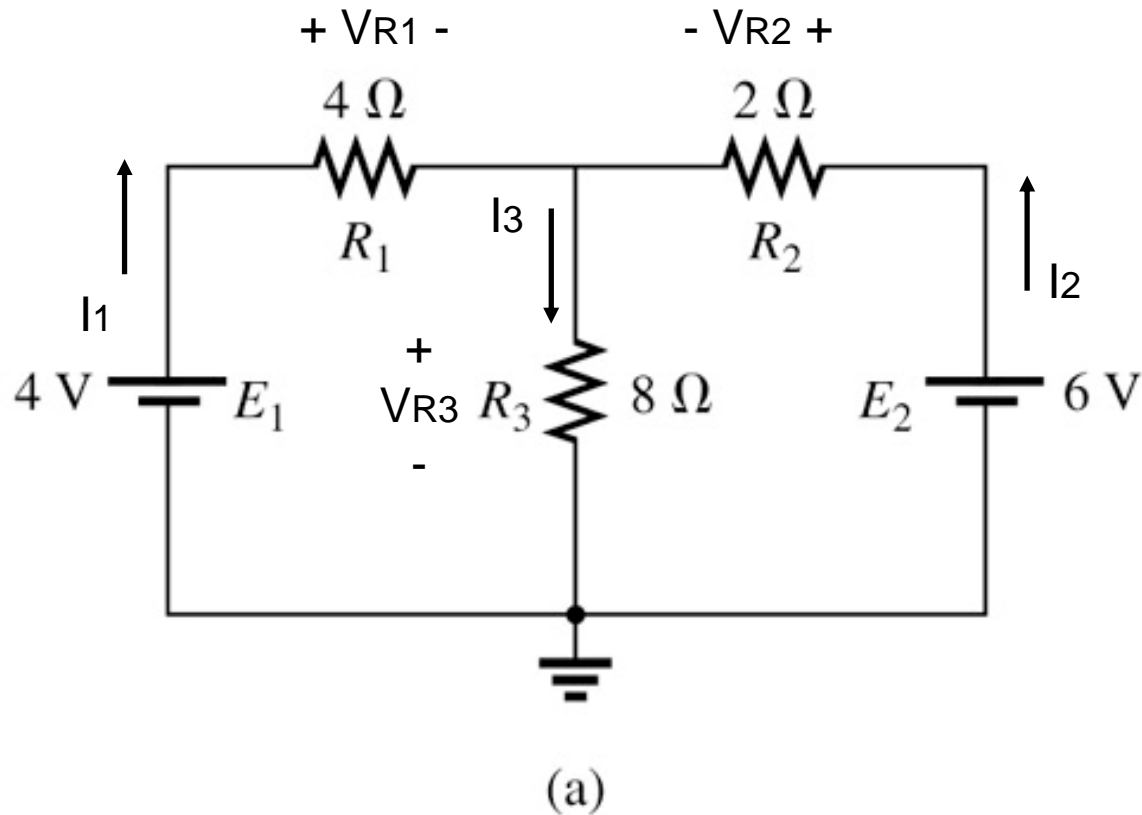
2. Label the voltage drops for each resistor, determined by the appropriate branch current direction



Branch Current Analysis (by example)

■ Method

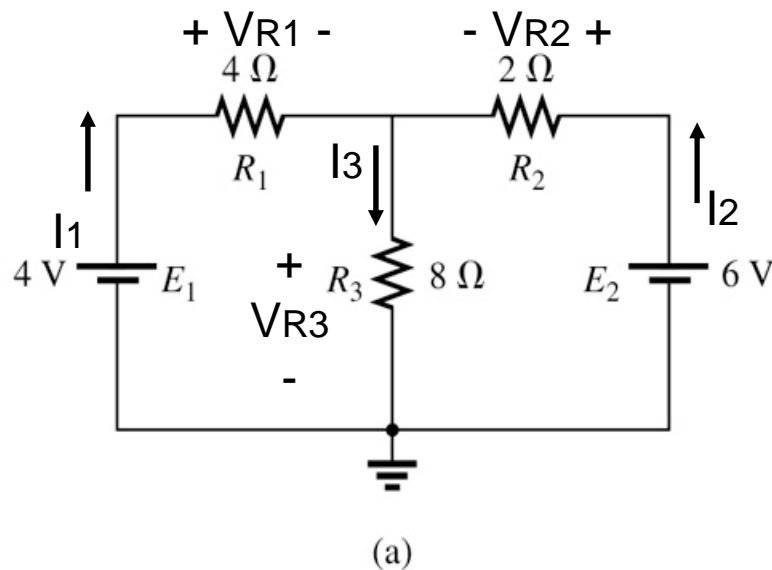3. Apply KVL around each closed, independent loop of the network



$$+ E_1 - V_{R1} - V_{R3} = 0$$

$$+ 4 - 4 \cdot I_1 - 8 \cdot I_3 = 0, \quad (1)$$

$$+ V_{R3} + V_{R2} - E_2 = 0$$


$$+ 8 \cdot I_3 + 2 \cdot I_2 - 6 = 0, \quad (2)$$

Note: We have 2 equations and 3 unknowns at this point

Branch Current Analysis (by example)

■ Method

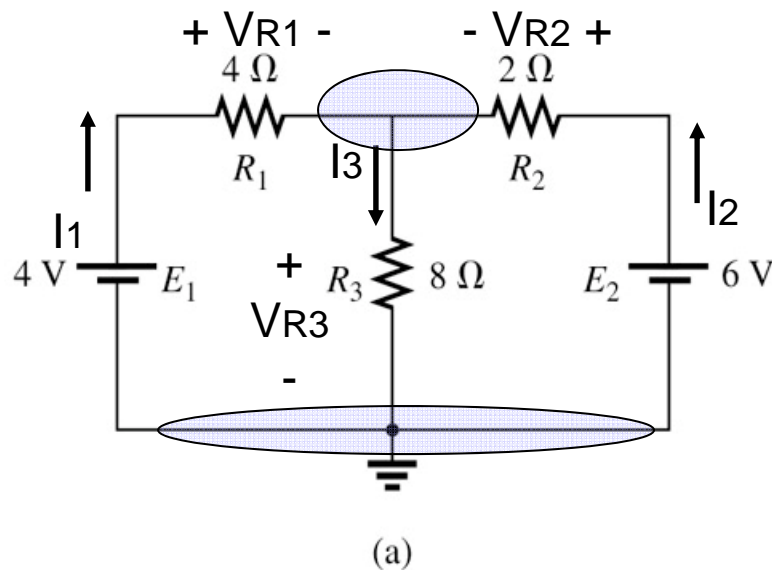4. Apply KCL at the minimum number of nodes that will include all the network's branch currents



Note: Only 2 independent NODES here

Note: Only 1 NODE needed to include all three branch currents

$$I_1 + I_2 - I_3 = 0, \quad (3)$$

Branch Current Analysis (by example)

■ Method

5. Solve the simultaneous linear equations for the branch currents and then relate the solution to the unknown(s)

We have:

$$+4 - 4 \cdot I_1 - 8 \cdot I_3 = 0, \quad (1)$$

$$+8 \cdot I_3 + 2 \cdot I_2 - 6 = 0, \quad (2)$$


$$I_1 + I_2 - I_3 = 0, \quad (3)$$

Rewritten:

$$-4 \cdot I_1 + 0 \cdot I_2 - 8 \cdot I_3 = -4, \quad (1)$$

$$0 \cdot I_1 + 2 \cdot I_2 + 8 \cdot I_3 = 6, \quad (2)$$

$$I_1 + I_2 - I_3 = 0, \quad (3)$$

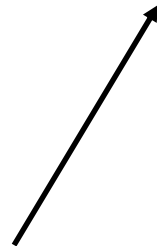

Note: 3 equations and 3 unknowns

Branch Current Analysis (by example)

■ Solving the equations

- Method of determinants (review) - See Appendix B
- Use your calculator for 3x3 or smaller (manual excerpt below and on the next page)

Rewritten:

$$-4 \cdot I_1 + 0 \cdot I_2 - 8 \cdot I_3 = -4, \quad (1)$$

$$0 \cdot I_1 + 2 \cdot I_2 + 8 \cdot I_3 = 6, \quad (2)$$

$$I_1 + I_2 - I_3 = 0, \quad (3)$$

■ For the EL-W516T

- MODE 4 0 (2 eqs)
- MODE 4 1 (3 eqs)

Simultaneous Linear Equations

Simultaneous linear equations with two unknowns (2-VLE) or with three unknowns (3-VLE) may be solved using the following functions.

① 2-VLE: (MODE) (6) (0)

$$\begin{cases} a_1x + b_1y = c_1 \\ a_2x + b_2y = c_2 \end{cases} \quad |D| = \begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}$$

② 3-VLE: (MODE) (6) (1)

$$\begin{cases} a_1x + b_1y + c_1z = d_1 \\ a_2x + b_2y + c_2z = d_2 \\ a_3x + b_3y + c_3z = d_3 \end{cases} \quad |D| = \begin{vmatrix} a_1 & b_1 & c_1 \\ a_2 & b_2 & c_2 \\ a_3 & b_3 & c_3 \end{vmatrix}$$

- If the determinant D = 0, an error occurs.
- If the absolute value of an intermediate result or calculation result is 1×10^{100} or more, an error occurs.

Solving simultaneous linear equations

1. Press (MODE) (6) (0) or (MODE) (6) (1).
2. Enter the value for each coefficient (a_1 , etc.).
 - Coefficients can be entered using ordinary arithmetic operations.
 - To clear the entered coefficient, press (ON/C).
 - Press (▲) or (▼) to move the cursor up or down through the coefficients. Press (2ndF) (▲) or (2ndF) (▼) to jump to the first or last coefficient.
3. When all coefficients have been entered, press (ENTER) to solve the equation.
 - While the solution is displayed, press (ENTER) or (ON/C) to return to the coefficient entry display. To clear all the coefficients, press (2ndF) (CA).

Branch Current Analysis (by example)

- Solving the equations using your calculator:

Work this example first:

	MODE	6	1
$x + y - z = 9$	1	ENTER	1
$6x + 6y - z = 17$	6	ENTER	6
$14x - 7y + 2z = 42$	14	ENTER	(-)
			7
			2
			42
$x = ?$	ENTER		
$y = ?$		X:	3.238095238
$z = ?$		Y:	-1.638095238
$\det(D) = ?$		Z:	-7.4
		D:	105.

- For the EL-W516T

- MODE 4 0 (2 eqs)
- MODE 4 1 (3 eqs)

Now find I_1, I_2, I_3 :

$$-4 \cdot I_1 + 0 \cdot I_2 - 8 \cdot I_3 = -4, \quad (1)$$

$$0 \cdot I_1 + 2 \cdot I_2 + 8 \cdot I_3 = 6, \quad (2)$$

$$I_1 + I_2 - I_3 = 0, \quad (3)$$

$$I_1 = -0.1429 \text{ A}$$


$$I_2 = 0.7143 \text{ A}$$

$$I_3 = 0.5714 \text{ A}$$

Branch Current Analysis (by example)

■ What were we looking for?

□ V_{R3} and P_{E2}

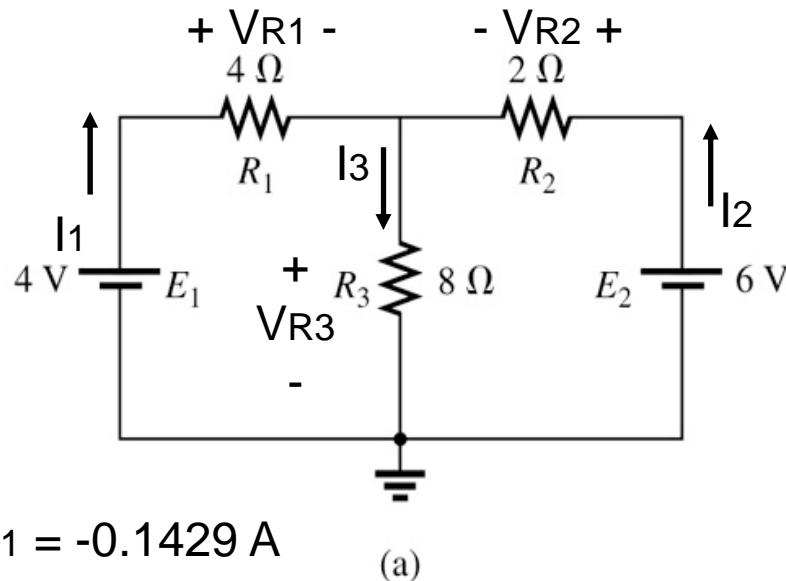

$$I_1 = -0.1429 \text{ A}$$

$$I_2 = 0.7143 \text{ A}$$

$$I_3 = 0.5714 \text{ A}$$

$$\begin{aligned} V_{R3} &= I_3 \cdot R_3 \\ &= 571.4 \text{ mA} \cdot 8 \Omega = 4.57 \text{ V} \end{aligned}$$

$$\begin{aligned} P_{E2} &= E_2 \cdot I_2 \\ &= 6 \text{ V} \cdot 714.3 \text{ mA} = 4.29 \text{ W} \end{aligned}$$

Breakout #1

- Find P_{E1} , P_{R2} and the current through R_3

