
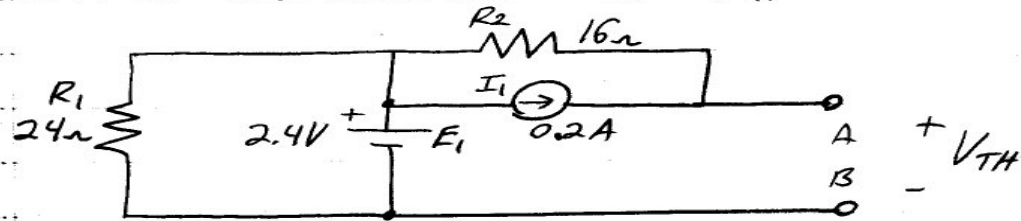


QUICK CALCULATION OF  $V_{TH}$  :

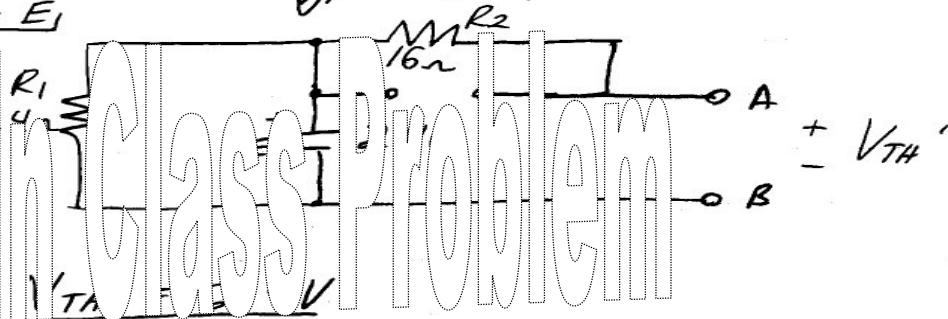


✓✓ SUPERPOSITION

DUE TO  $E_1$




DUE TO  $I_1$

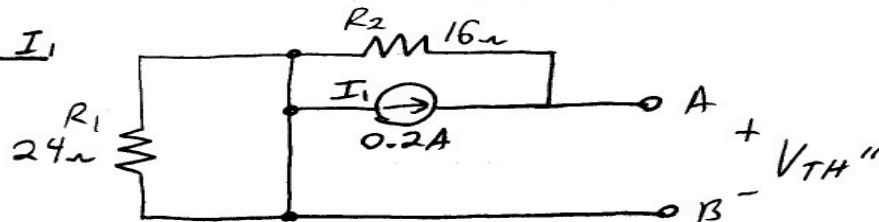


$$V_{TH}'' = (0.2A) \left( \frac{16\Omega}{24\Omega + 16\Omega} \right) = 0.2A \times \frac{16}{40} = 0.2A \times \frac{2}{5} = 0.08V$$

EQUIVALENT CIRCUIT

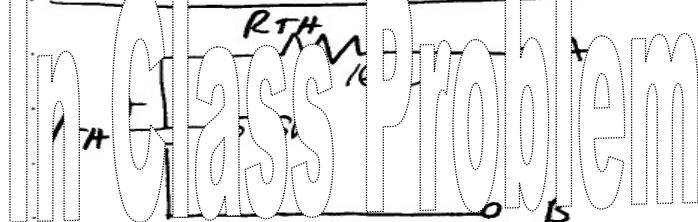

## SUMMARY

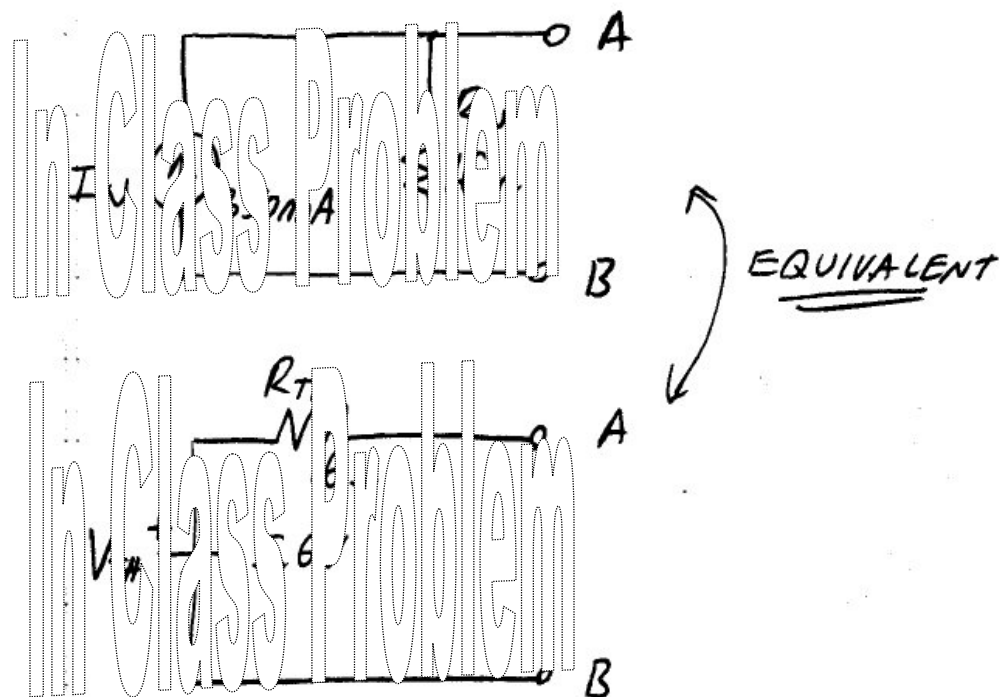


$$V_{TH} = (I_N \cdot R_N) = (0.35 \text{ A} \cdot 16 \Omega) = \underline{\underline{5.6 \text{ V}}} \quad \checkmark$$


$$I_N = \frac{V_{TH}}{R_{TH}} = \frac{5.6 \text{ V}}{16 \Omega} = \underline{\underline{0.35 \text{ A}}} \quad \checkmark$$
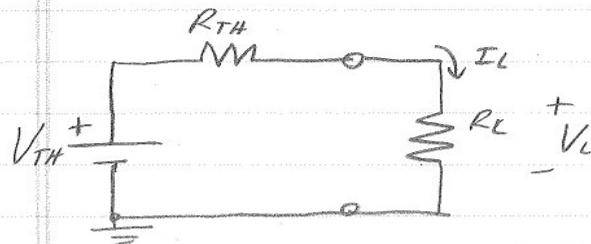
## 9.5 MAXIMUM POWER TRANSFER THEOREM

A LOAD WILL RECEIVE MAXIMUM POWER FROM A LINEAR BILATERAL DC NETWORK WHEN ITS TOTAL RESISTIVE VALUE IS EXACTLY EQUAL TO THE THEVENIN RESISTANCE OF THE NETWORK AS "SEEN" BY THE LOAD.



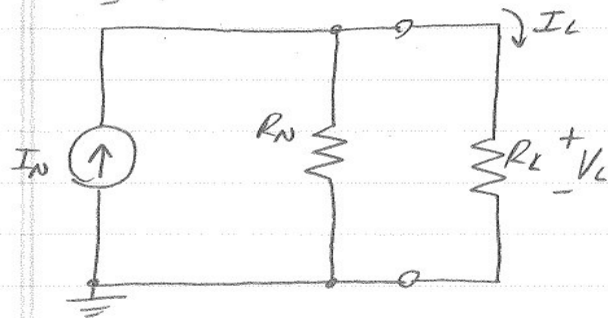$P_{L\text{MAX}} \Rightarrow \text{WHEN } R_L = R_{TH}$



$P_{L\text{MAX}} \Rightarrow \text{WHEN } R_L = R_N$

(EXAMPLE) LET  $V_{TH} = 10V$   
 $R_{TH} = 50\Omega$

$$V_L = V_{TH} \left( \frac{R_L}{R_L + R_{TH}} \right)$$

$$V_L = 10 \left( \frac{R_L}{R_L + 50} \right) \quad (1)$$

$$I_L = \frac{V_L}{R_L} \quad (2)$$

$$P_L = (I_L)^2 R_L \quad (3)$$


Plot for  
 $0\Omega \leq R_L \leq 200\Omega$

Vth	10 V		
Rth	50 ohms		
<b>RL</b>	<b>VL</b>	<b>IL</b>	<b>PL</b>
<b>ohms</b>	<b>Volts</b>	<b>Amps</b>	<b>Watts</b>
0	000.00E+0	000.00E+0	000.00E+0
5	909.09E-3	181.82E-3	165.29E-3
10	1.67E+0	166.67E-3	277.78E-3
15	2.31E+0	153.85E-3	355.03E-3
20	2.86E+0	142.86E-3	408.16E-3
25	3.33E+0	133.33E-3	444.44E-3
30	3.75E+0	125.00E-3	468.75E-3
35	4.12E+0	117.65E-3	484.43E-3
40	4.44E+0	111.11E-3	493.83E-3
45	4.74E+0	105.26E-3	498.61E-3
50	5.00E+0	100.00E-3	500.00E-3
55	5.24E+0	95.24E-3	498.87E-3
60	5.45E+0	90.91E-3	495.87E-3
65	5.65E+0	86.96E-3	491.49E-3
70	5.83E+0	83.33E-3	486.11E-3
75	6.00E+0	80.00E-3	480.00E-3
80	6.15E+0	76.92E-3	473.37E-3
85	6.30E+0	74.07E-3	466.39E-3
90	6.43E+0	71.43E-3	459.18E-3
95	6.55E+0	68.97E-3	451.84E-3
100	6.67E+0	66.67E-3	444.44E-3
105	6.77E+0	64.52E-3	437.04E-3
110	6.88E+0	62.50E-3	429.69E-3
115	6.97E+0	60.61E-3	422.41E-3
120	7.06E+0	58.82E-3	415.22E-3
125	7.14E+0	57.14E-3	408.16E-3
130	7.22E+0	55.56E-3	401.23E-3
135	7.30E+0	54.05E-3	394.45E-3
140	7.37E+0	52.63E-3	387.81E-3
145	7.44E+0	51.28E-3	381.33E-3
150	7.50E+0	50.00E-3	375.00E-3
155	7.56E+0	48.78E-3	368.83E-3
160	7.62E+0	47.62E-3	362.81E-3
165	7.67E+0	46.51E-3	356.95E-3
170	7.73E+0	45.45E-3	351.24E-3
175	7.78E+0	44.44E-3	345.68E-3
180	7.83E+0	43.48E-3	340.26E-3
185	7.87E+0	42.55E-3	334.99E-3
190	7.92E+0	41.67E-3	329.86E-3
195	7.96E+0	40.82E-3	324.86E-3
200	8.00E+0	40.00E-3	320.00E-3


0.2
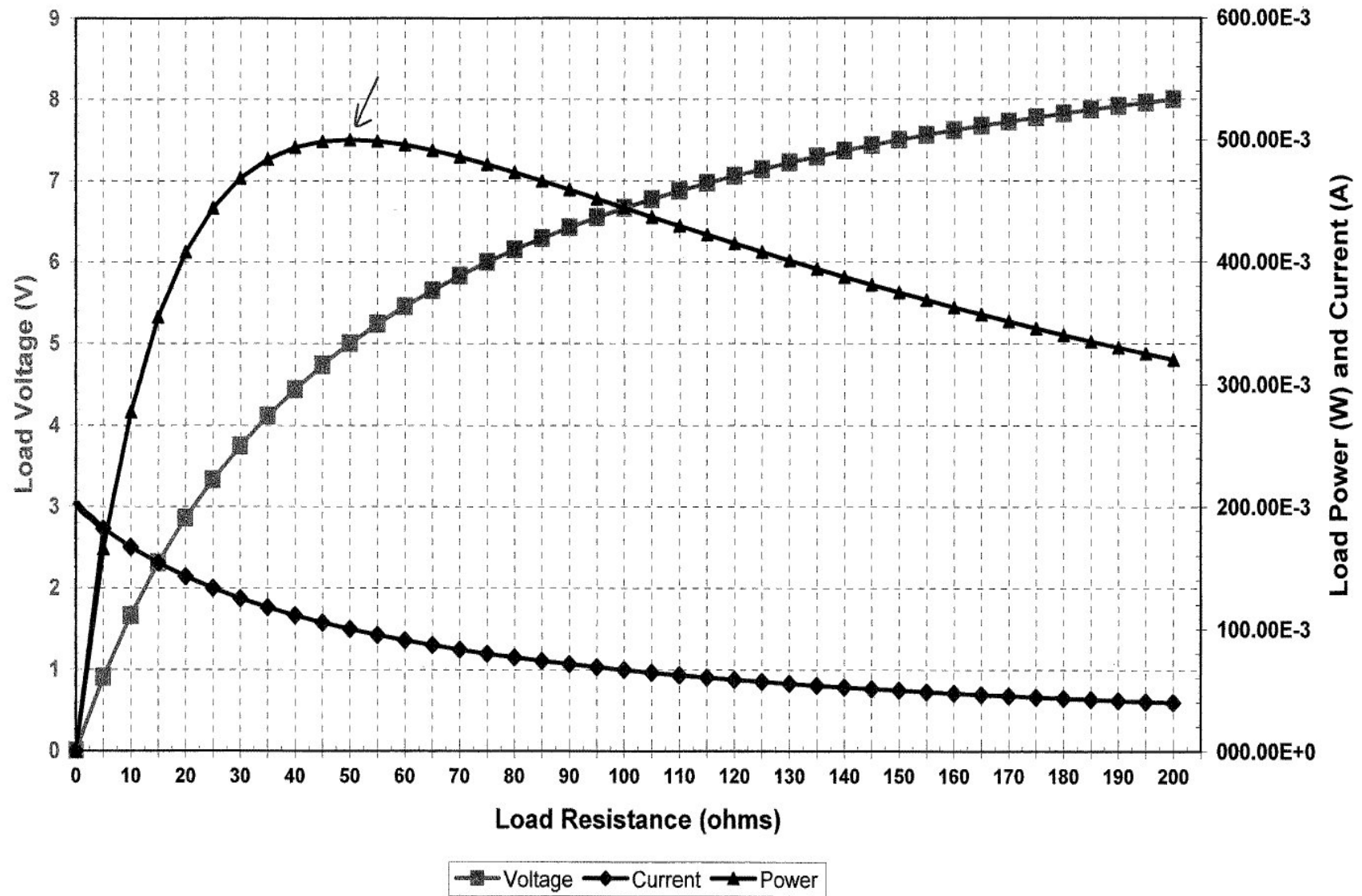
# Load voltage, current and power

$V_{th} = 10V$ ,  $R_{th} = 50\text{ ohms}$



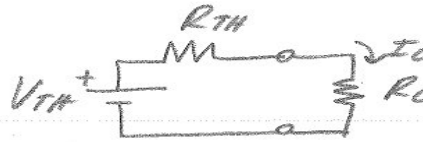$P_{LMAX} \rightarrow$  WHEN  $R_L = R_{TH}$




$$P_L = I_L^2 R_L = \left( \frac{V_{TH}}{R_L + R_{TH}} \right)^2 R_L$$

FOR  $R_L = R_{TH} \therefore P_{LMAX} = \left( \frac{V_{TH}}{R_{TH} + R_{TH}} \right)^2 R_{TH}$

$$P_{LMAX} = \frac{V_{TH}^2}{(2R_{TH})^2} R_{TH}$$

$$P_{LMAX} = \frac{V_{TH}^2}{4 R_{TH}}$$

FOR  
 $R_L = R_{TH}$

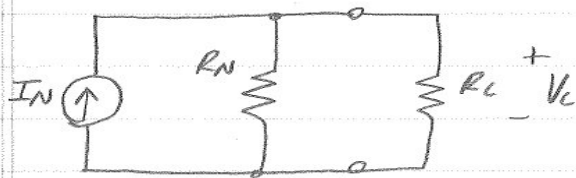

$$P_L = \frac{V_L^2}{R_L}$$

$$V_L = I_N \cdot (R_N // R_L)$$

FOR  $R_L = R_N = R_{TH} \therefore$


$$V_L = I_N \cdot \frac{R_N}{2}$$

$$\therefore P_{LMAX} = \frac{\left( \frac{I_N \cdot R_N}{2} \right)^2}{R_N}$$


$$P_{LMAX} = \frac{I_N^2 R_N}{4}$$

FOR  
 $R_L = R_N$


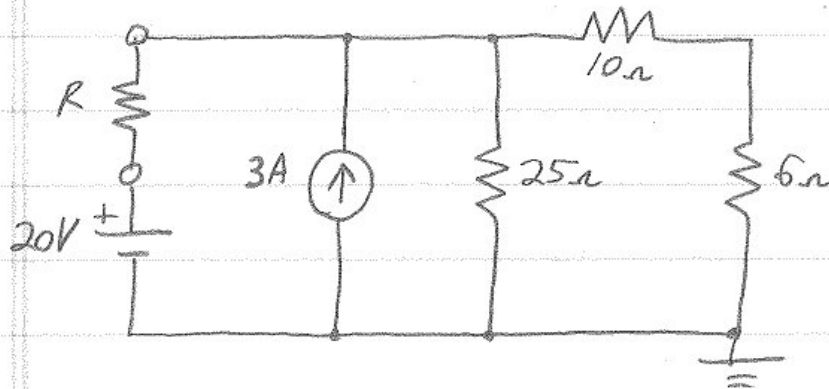
Find the value of  $R$  for maximum power transfer (to  $R$ ) + determine the maximum power to  $R$ .



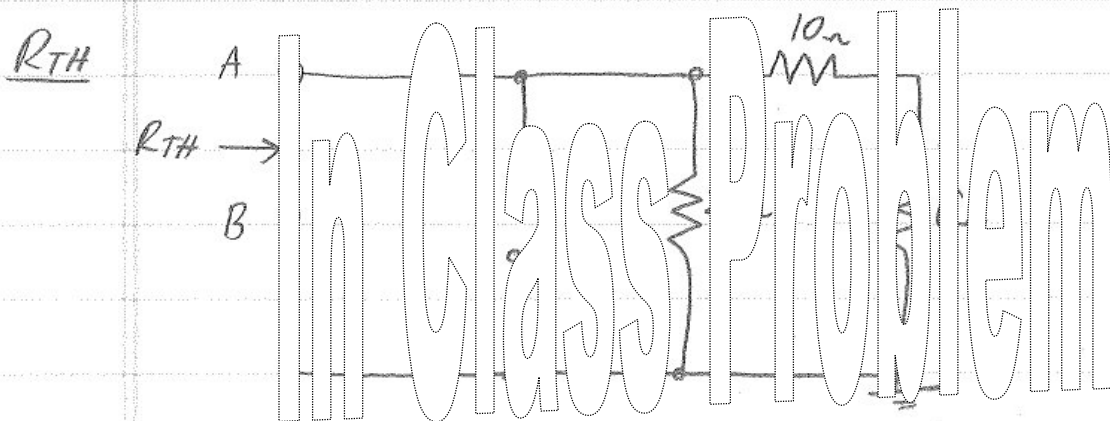- FIND  $V_{TH}, R_{TH}$
- SET  $R = R_{TH}$  + CALCULATE  $P_{LMAX}$





$R_{TH}$

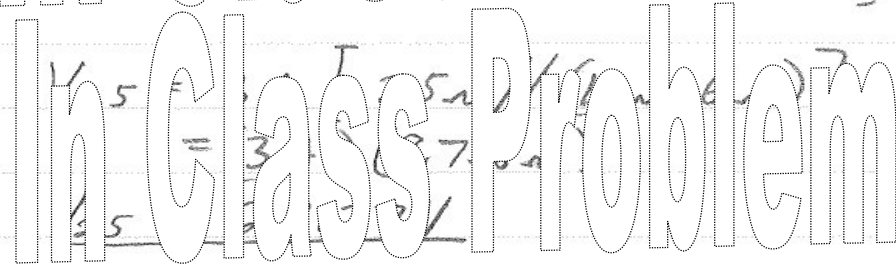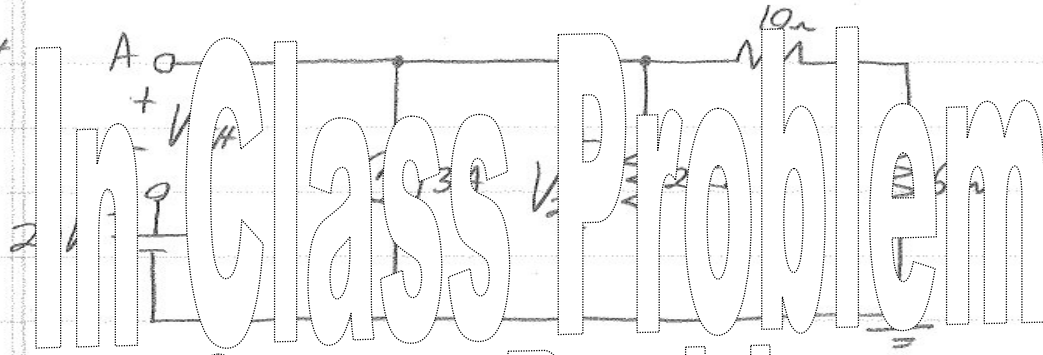V<sub>TH</sub>

$$KVL: +20 + V_D - V_{DS} = 0$$

# In Class Problem

### THEVENIN EQUIV.

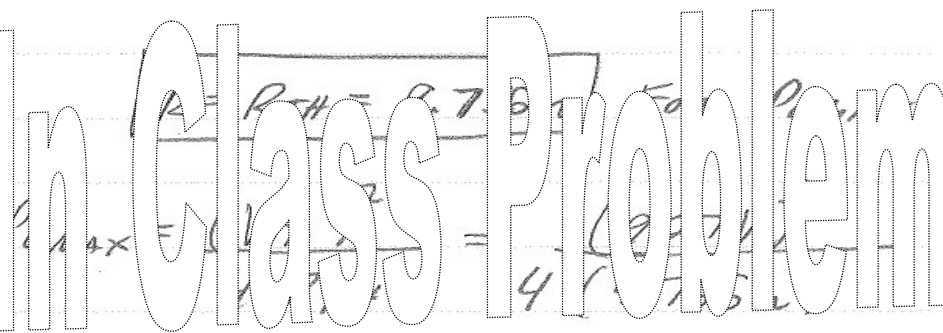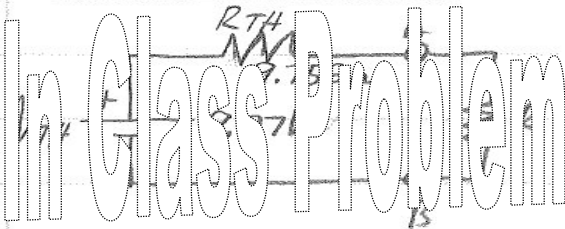

$$P_{LMAX} = 2.2 \text{ W}$$