
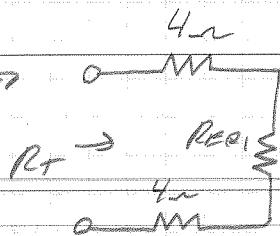


~~(3)~~ DETERMINE  $R_T$

(3)

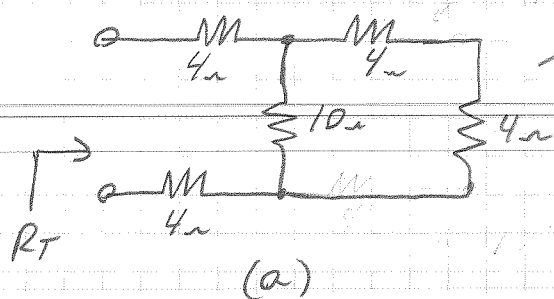


$$R_{EQ1} = 10\Omega // 8\Omega$$

$$= 4.44\Omega$$

$$\therefore R_T = 4\Omega + 4.44\Omega + 4\Omega$$

$$\text{OR}$$

$$R_T = 12.44\Omega$$

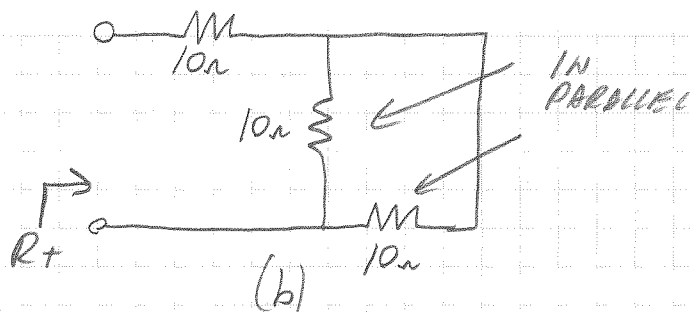


$$R_T = 10\Omega + (10\Omega // 10\Omega)$$

$$= 10\Omega + 5\Omega$$

$$R_T = 15\Omega$$

(4)

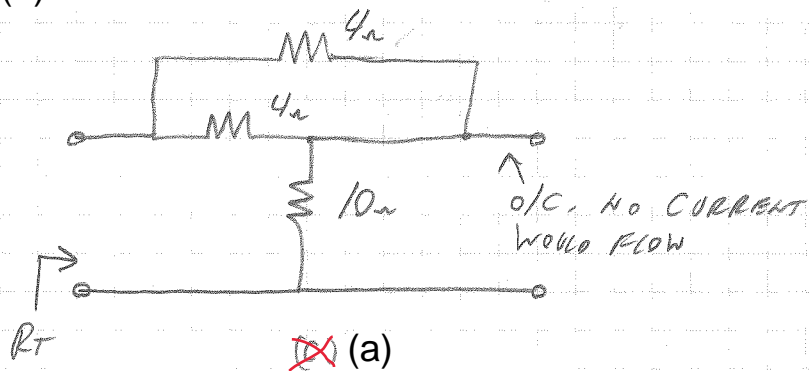


$$R_T = (4\Omega // 4\Omega) + 10\Omega$$

$$= 2\Omega + 10\Omega$$

$$2.5\Omega + 10\Omega$$


$$R_T = 12\Omega$$

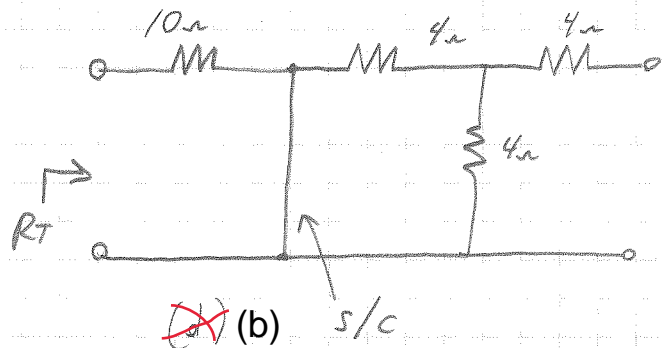

$$R_T = 10\Omega + 0\Omega // (4\Omega + 4\Omega)$$


$$\therefore R_T = 10\Omega$$

(4) FIND:

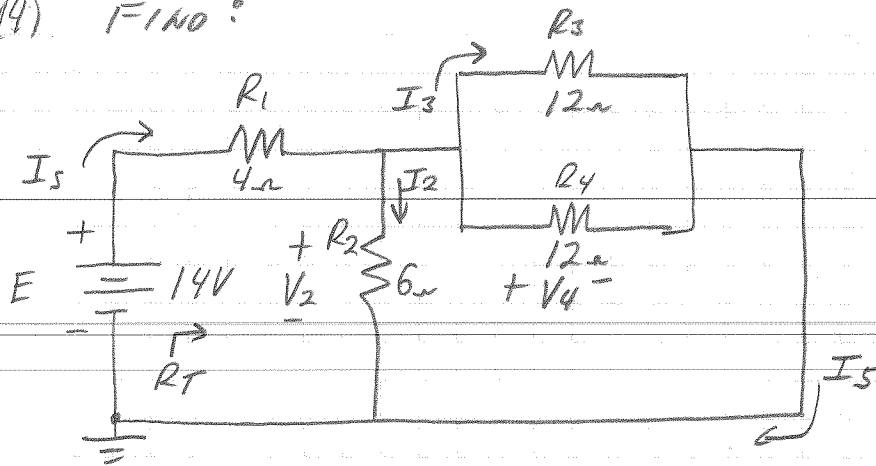

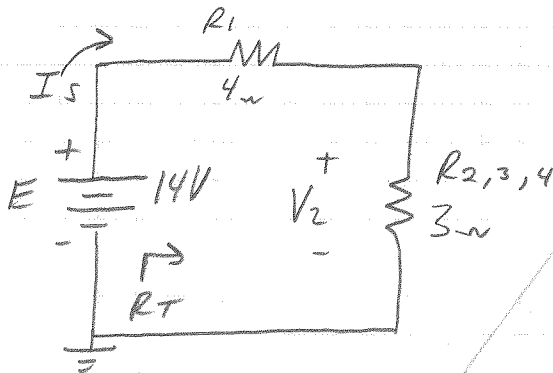(a)  $R_T$

- COMBINE  $R_3$  &  $R_4$  (IN PARALLEL)  
W/  $R_2$  (ALSO IN PARALLEL)  
& REDRAW




$$\begin{aligned} R_{2,3,4} &= (R_3 // R_4) // R_2 \\ &= 12\Omega // 12\Omega // 6\Omega \\ &= \underline{\underline{3\Omega}} \end{aligned}$$

$$R_T = R_1 + R_{2,3,4} = \underline{\underline{7\Omega}}$$

(b)  $I_s, I_2, I_3$

$$I_s = \frac{E}{R_T} = \frac{14V}{7\Omega} = \underline{\underline{2A}}$$

- REDRAW TO CLEARLY SEE  $I_2, I_3$

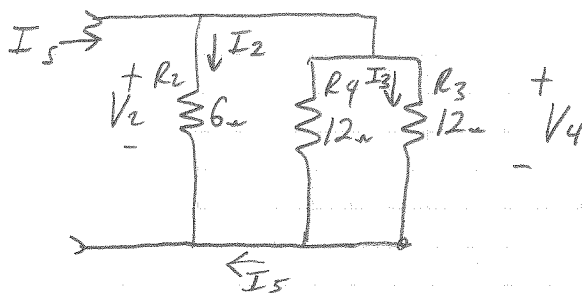


$$I_2 = \frac{V_2}{R_2} \text{ BUT FROM (a)}$$

$$\begin{aligned} V_2 &= E \left( \frac{R_{2,3,4}}{R_T} \right) \\ &= 14V \left( \frac{3\Omega}{7\Omega} \right) = \underline{\underline{6V}} \end{aligned}$$

$$\therefore I_2 = \frac{6V}{6\Omega} = \underline{\underline{1A}}$$

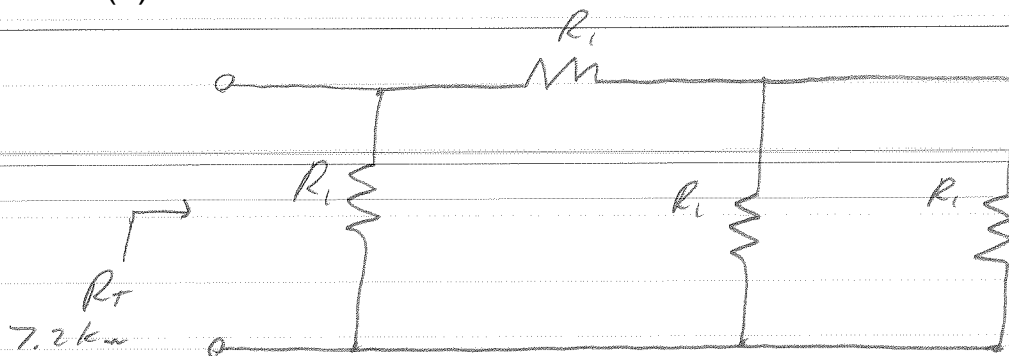(6)

~~(5)~~  $R_T = 7.2 \text{ k}\Omega$ , Find  $R_1$



$$R_T = (R_1 // R_1 + R_1) // R_1$$

$$= \left( \frac{R_1 \cdot R_1}{R_1 + R_1} + R_1 \right) // R_1$$

$$\therefore R_T = \frac{\left( \frac{R_1^2}{2R_1} + R_1 \right) (R_1)}{\left( \frac{R_1^2}{2R_1} + R_1 \right) + R_1} = \frac{\left( \frac{1}{2}R_1 + R_1 \right) (R_1)}{\left( \frac{1}{2}R_1 + R_1 \right) + R_1}$$

$$R_T = \frac{1.5R_1^2}{2.5R_1} = \frac{1.5R_1}{2.5} = 0.6R_1$$

$$\therefore R_T = 7.2 \text{ k}\Omega = 0.6R_1$$

OR

$$R_1 = 12 \text{ k}\Omega$$

(4) (b) CONTINUED

$$I_3 = \frac{V_4}{R_3}, \text{ but } V_4 = V_2 \text{ SINCE } R_4 \text{ \& } R_2 \text{ ARE IN PARALLEL}$$

$$\therefore I_3 = \frac{V_2}{R_3} = \frac{6V}{12\Omega} = \boxed{0.5A}$$

(c) FIND  $I_5$


- SEE THE SCHEMATIC FROM PART (b)

$$I_5 = \frac{V_4}{R_4 \parallel R_3} = \frac{6V}{6\Omega} = \boxed{1A}$$

(d) FIND  $V_2$  &  $V_4$

- DONE IN (b)

$$\boxed{V_2 = V_4 = 6V}$$

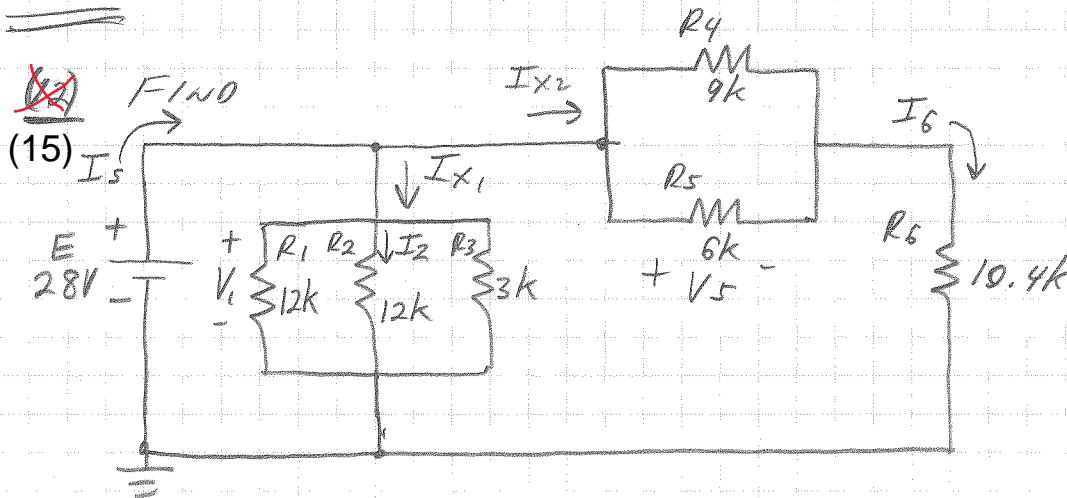

a)  $I_5, I_2, I_6$

- SIMPLIFY THE CIRCUIT & REORAW


$$R_{1,2,3} = R_1 \parallel R_2 \parallel R_3 = 12k \parallel 12k \parallel 3k = 2k\Omega$$

$$R_{4,5} = R_4 \parallel R_5 = 9k \parallel 6k = 3.6k\Omega$$

- FIND  $I_{x1}$  &  $I_{x2}$ , USE THIS TO FIND  $I_2$  &  $I_6$

~~15~~ CONTINUED  
(15)

Q) REORAWN :

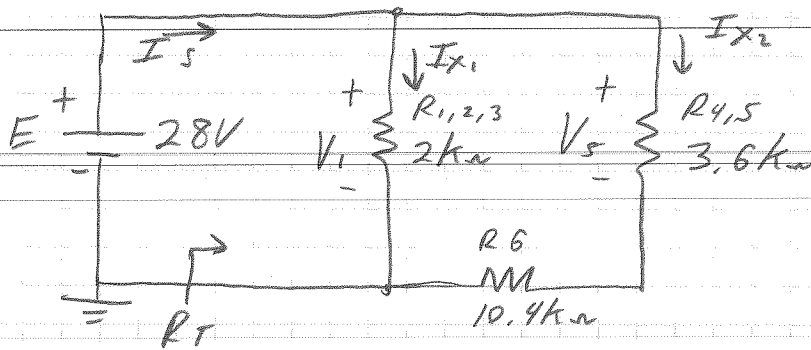

$$I_s] \quad I_s = \frac{E}{R_T}, \quad R_T = R_{1,2,3} \parallel (R_{4,5} + R_6)$$

$$= 2k\Omega \parallel 14k\Omega$$

$$R_T = 1.75k\Omega$$

$$\therefore I_s = \frac{28V}{1.75k\Omega} = \boxed{16mA}$$

$$I_2] \quad I_2 = I_{x1} \left( \frac{R_{1,2,3}}{R_2} \right), \quad \text{CURRENT DIVIDER}$$

REF TO THE ORIGINAL SCHEMATIC

$$I_{x1} = \frac{E}{R_{1,2,3}} = \frac{28V}{2k\Omega} = \underline{14mA}$$

$$\therefore I_2 = 14mA \left( \frac{2k\Omega}{12k\Omega} \right) = \boxed{2.33mA}$$

$$I_6] \quad -I_6 = I_{x2}$$

$$KCL: \quad I_s - I_{x1} - I_{x2} = 0$$

OR

$$I_s = I_{x1} + I_{x2}$$

$$\text{BUT } I_s = 16mA$$

$$I_{x1} = 14mA$$

$$I_{x2} = I_6$$

$$\text{WE HAVE: } I_6 = I_s - I_{x1}$$

$$= 16mA - 14mA$$

$$\boxed{I_6 = 2mA}$$

(15) ~~12~~ CONTINUED

b)  $V_1, V_5$

$$V_1 = E = \boxed{28V}$$

- FOR  $V_5$ , USE VOLTAGE DIVIDER & THE SIMPLIFIED SCHEMATIC

$$V_5 = E \left( \frac{R_{4,5}}{R_{4,5} + R_6} \right) = 28V \left( \frac{3.6k\Omega}{14k\Omega} \right)$$

$$\boxed{V_5 = 7.2V}$$


c)  $P_{R3}$

$$P_{R3} = \frac{(V_{R3})^2}{R_3}$$


$$= \frac{(V_1)^2}{R_3} = \frac{(28V)^2}{3k\Omega} = \boxed{261.3mW}$$

~~16~~ FIND  $I_1$  &  $I_2$

(17)

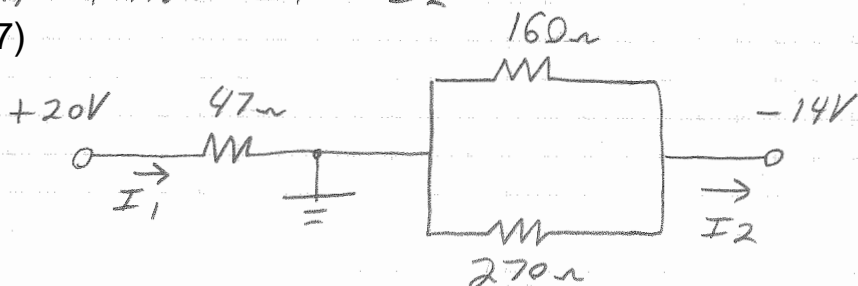

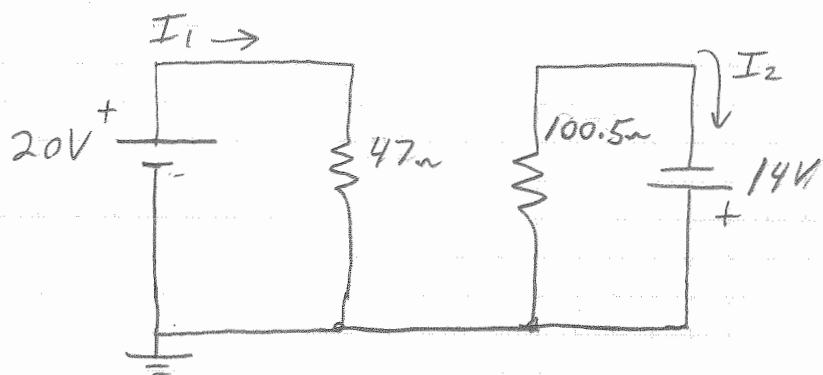- REDRAW THE CIRCUIT SHOWING THE SUPPLIES & COMBINING THE PARALLEL RESISTORS



$$160\Omega \parallel 270\Omega = 100.5\Omega$$

$$I_1 = \frac{20V}{47\Omega} = \boxed{425.5mA}$$

$$I_2 = \frac{14V}{100.5\Omega} = \boxed{139.3mA}$$

### Question 7-19

For the network in Fig. 7.82:

a. Determine the current  $I_1$

$$I_1 = (E_1 - E_2)/R_1$$
$$I_1 = (20V - 15V)/3 = \boxed{1.67A}$$

b. Calculate the currents  $I_2$  and  $I_3$


$$I_2 = (E_2)/R_T$$
$$R_T = R_2 + (R_5 \parallel R_3)$$
$$R_T = 3 + (6 \cdot 6)/(6 + 6) = 6\Omega$$
$$I_2 = 15V/6\Omega = \boxed{2.5A}$$

$$I_3 = \frac{1}{2} \cdot I_2 = \frac{1}{2} \cdot 2.5 = \boxed{1.25A}$$

c. Determine the voltage level  $V_a$

$$V_a = E_2 \cdot \frac{(R_5 \parallel R_3)}{(R_5 \parallel R_3) + R_2}$$
$$V_a = 15 \cdot \frac{3}{3+3} = \boxed{7.5V}$$

1. (16)

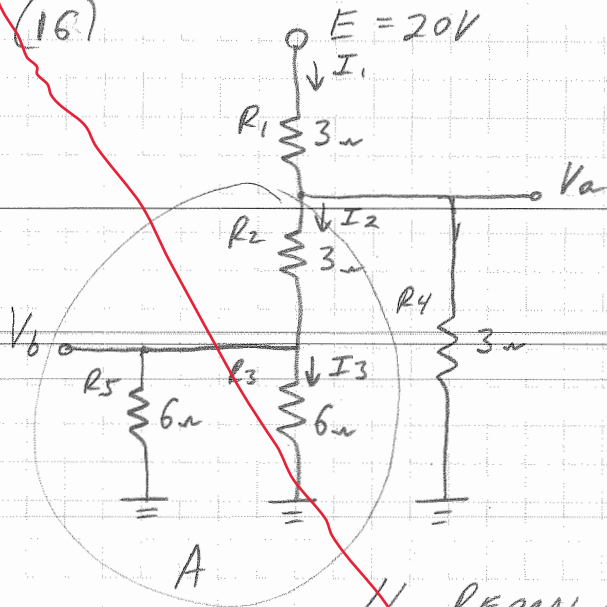


### STRATEGY

- REORAW THE NETWORK,  
COMBINING ELEMENTS  
TO GET TO A SIMPLE  
SERIES - PARALLEL  
CIRCUIT

$$R_A = R_5 // R_3 + R_2$$

$$= 3\Omega + 3\Omega = 6\Omega$$

REDRAWN

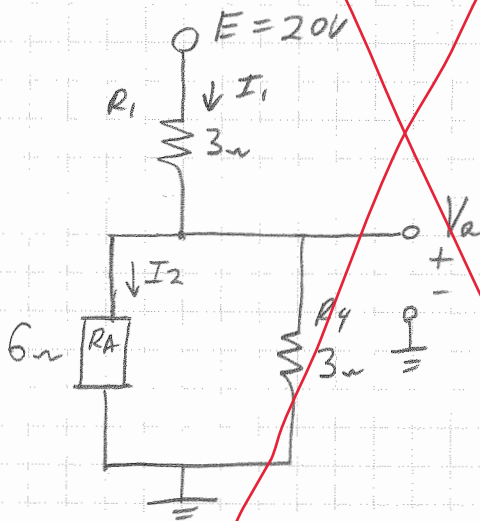

a) FIND  $I_1$

$$I_1 = \frac{E}{R_T}, \quad R_T = R_A // R_4 + R_1$$

$$= 2\Omega + 3\Omega$$

$$R_T = 5\Omega$$

$$I_1 = \frac{20V}{5\Omega} = \boxed{4A}$$

b) FIND  $I_2$  &  $I_3$

$$I_2 = I_1 \left( \frac{R_A // R_4}{R_A} \right) = 4A \left( \frac{2\Omega}{6\Omega} \right) = \boxed{1.33A}$$

CURRENT DIVIDER (SIMPLIFIED CIRCUIT)



~~(18) CONTINUED - b) FIND  $I_3$~~

~~- SEE THE ORIGINAL SCHEMATIC & USE CURRENT DIVIDER~~

~~$$I_3 = I_2 \left( \frac{R_3 // R_5}{R_3} \right)$$~~

~~$$I_3 = 1.33 \text{ A} \left( \frac{3\Omega}{6\Omega} \right) = \boxed{666.7 \text{ mA}}$$~~

c) FIND  $V_a$  &  $V_b$

$$V_a = I_2 \cdot R_A = (1.33 \text{ A})(6\Omega) = \boxed{8 \text{ V}}$$


$$V_b = I_3 \cdot R_3 = (667.7 \text{ mA})(6\Omega) = \boxed{4 \text{ V}}$$

REDUCED  
CIRCUIT

ORIGINAL  
CIRCUIT

~~(21)~~

(23)

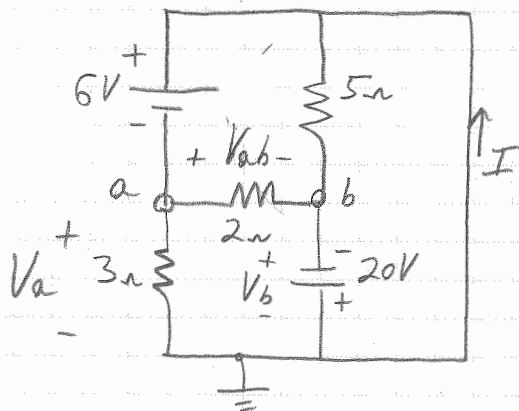

a) FIND  $V_{ab}$

$$\text{KVL: } +V_a + 6\text{V} = 0$$
$$V_a = -6\text{V}$$

$$\text{KVL: } -20\text{V} - V_b = 0$$
$$V_b = -20\text{V}$$

$$\therefore V_{ab} = V_a - V_b = -6\text{V} - (-20\text{V}) = \boxed{14\text{V}}$$


b) CALCULATE  $I$

REDRAW THE CIRCUIT W/ THE KNOWN  
& BRANCH CURRENTS

~~(21)~~ CONTINUED

b) FIND "I"

(23)

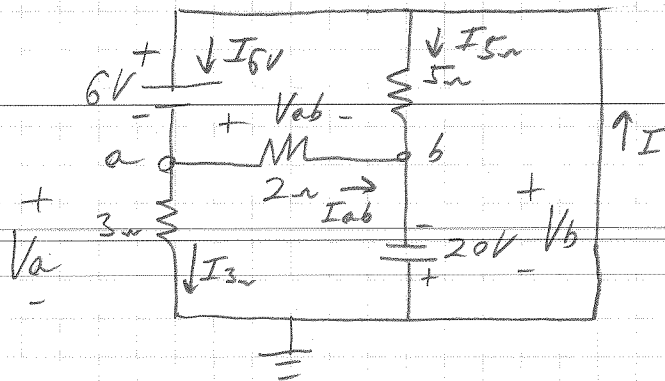

$$V_a = -6V$$

$$V_b = -20V$$

$$V_{ab} = 14V$$

KCL

$$I = I_{6V} + I_{5\Omega}$$

$$I_{6V} = I_{ab} + I_{3\Omega}, \quad I_{ab} = \frac{V_{ab}}{2\Omega} = \frac{14V}{2\Omega} = \underline{7A}$$

$$I_{3\Omega} = \frac{V_a}{3\Omega} = \frac{-6V}{3\Omega} = \underline{-2A}$$

$$\therefore I_{6V} = \underline{5A}$$


$$I_{5\Omega} = \frac{-V_b}{5\Omega} = \frac{-(-20V)}{5\Omega} = \underline{4A}$$

$$\text{HENCE } I = 5A + 4A$$

$$\boxed{I = 9A}$$

~~(23)~~ FINO  $R_3$  IF  $I_{R3} = 2A$

(25)

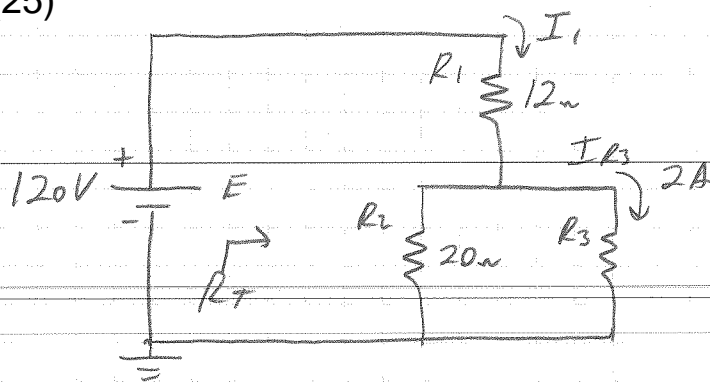

KCL:  $I_{R3} = I_1 \left( \frac{R_2 // R_3}{R_3} \right)$

$\therefore I_1 = I_{R3} \left( \frac{R_3}{R_2 // R_3} \right)$

OR  $I_1 = 2A \left( \frac{R_3}{R_2 // R_3} \right) \quad (1)$

BUT,  $I_1 = \frac{E}{R_T}$

$R_T = R_1 + R_2 // R_3$

OR  $I_1 = \frac{120V}{R_T} = \frac{120V}{12 + R_2 // R_3} \quad (2)$

EQUATING (1) & (2):  $\frac{2 R_3}{R_2 // R_3} = \frac{120}{12 + R_2 // R_3}$ ,  $R_2 // R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{20 R_3}{20 + R_3}$

CROSS MULTIPLY:  $24 R_3 + 2 R_3 (R_2 // R_3) = 120 (R_2 // R_3)$

COMMON  
DENOMINATOR

$24 R_3 + \frac{40 R_3^2}{20 + R_3} - \frac{2400 R_3}{20 + R_3} = 0$

$\frac{24 R_3 (20 + R_3) + 40 R_3^2 - 2400 R_3}{20 + R_3} = 0$

$480 R_3 + 24 R_3^2 + 40 R_3^2 - 2400 R_3 = 0$

COLLECT  
TERMS

$64 R_3^2 - 1920 R_3 + 0 = 0$

$R_3 = 30\Omega$


QUADRATIC  
EQUATION

$\left( \begin{aligned} ax^2 + bx + c &= 0 \\ x &= \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \end{aligned} \right)$

ORIG


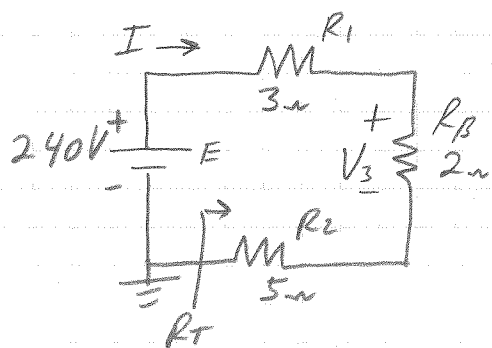
$$R_B = (R_A + R_4) // R_3 = \underline{2\Omega}$$



$$R_T = R_1 + R_2 + R_3$$

$$R_T = 10 \Omega$$

$$I = \frac{E}{R_t} = \frac{240V}{10\omega} = 24A$$

b) FIND  $I_7$  - FIND  $V_3, V_5, V_7$ , USE OHM'S LAW

$$V_3 = E \frac{R_B}{R_T} = 240V \left( \frac{2\Omega}{10\Omega} \right) = \underline{48V} \quad , \text{ CKT II}$$

$$V_5 = V_3 \frac{R_A}{R_A + R_4} = 48V \left( \frac{2\Omega}{4\Omega} \right) = \underline{24V}, \text{ CHTI}$$

$$V_7 = V_5 \frac{R_7}{R_7 + R_6} = 24V \left( \frac{2\Omega}{3\Omega} \right) = 16V, \text{ ORIG}$$

$$I_7 = \frac{V_7}{R_7} = \frac{16V}{2\Omega} = \boxed{8A}$$

~~(26)~~ CONTINUED  
(27)

c) DETERMINE  $V_3$ ,  $V_5$ ,  $V_7$

- SEE b)

$$V_3 = 48V$$

$$V_5 = 24V$$

$$V_7 = 16V$$

d) FIND  $P_{R7}$ ; COMPARE TO  $P_{SOURCE}$


$$P_{R7} = \frac{(V_7)^2}{R_7} = \frac{(16V)^2}{2\Omega} = 128W$$

COMPARE


$$P_{SOURCE} = (E)(I) = (240V)(24A) = 5,760W$$

$$P_{R7} \approx 2.2\% \text{ OF } P_{SOURCE}$$

~~(34)~~  
(33)

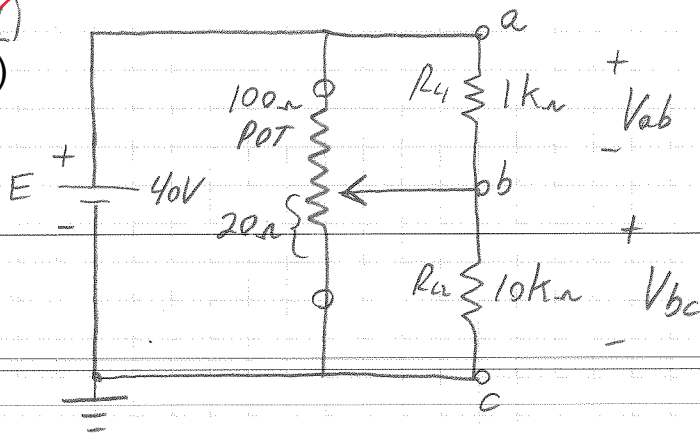

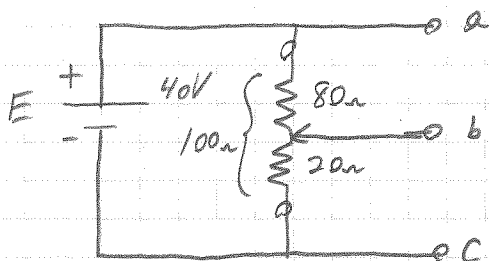Q) FIND  $V_{ab}$  &  $V_{bc}$  w/NO LOAD APPLIED




$$V_{ab} = E \frac{R_{ab}}{R_T} = 40V \left( \frac{80\Omega}{100\Omega} \right)$$

$$V_{ab} = 32V$$

$$V_{bc} = E \frac{R_{bc}}{R_T} = 40V \left( \frac{20\Omega}{100\Omega} \right)$$


$$V_{bc} = 8V$$

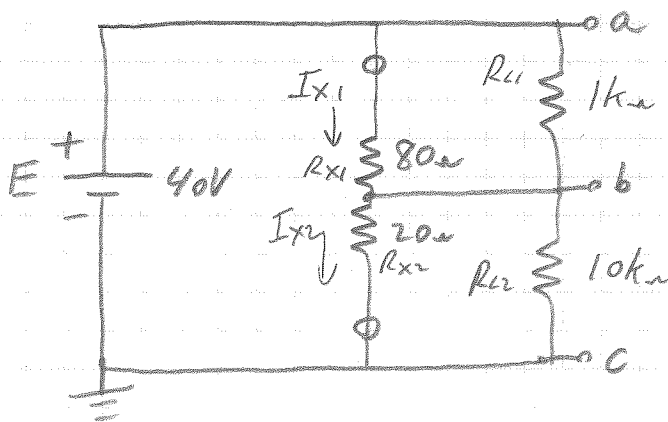b) FIND  $V_{ab}$  &  $V_{bc}$  w/THE INDICATED LOADS APPLIED



$$R_A = 80 // 1000$$

$$R_B = 20 // 10,000$$

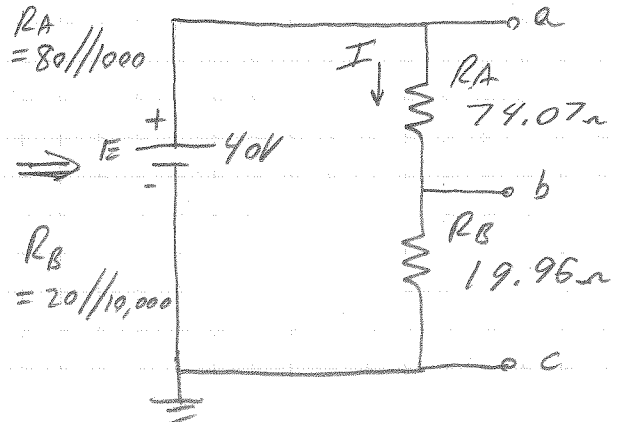

$$V_{ab} = E \left( \frac{R_{ab}}{R_T} \right) = 40V \left( \frac{74.07\Omega}{94.03\Omega} \right) = 31.51V$$

$$KVL: V_{bc} = E - V_{ab} = 40V - 31.51V = 8.49V$$

(~~34~~) CONTINUED

(33)

c) FIND  $P_{\text{POTENTIOMETER}}$  UNDER LOADED CONDITIONS

- SEE THE SCHEMATICS IN b)

$$I = \frac{E}{R_T} = \frac{40V}{94.03 \Omega} = \underline{425.4 \text{ mA}}$$

$$I_{x1} = I \left( \frac{80\Omega // 1k\Omega}{80\Omega} \right) = 425.4 \text{ mA} \left( \frac{74.07\Omega}{80\Omega} \right)$$

$$I_{x1} = 393.9 \text{ mA}$$

$$I_{x2} = 425.4 \text{ mA} \left( \frac{20 \text{ n} // 10 \text{ k}}{20 \text{ n}} \right) = \underline{424.6 \text{ mA}}$$

$$P_{\text{pot}} = (I_{x1})^2 R_{x1} + (I_{x2})^2 R_{x2}$$

$$= 12.41 \text{ W} + 3.61 \text{ W} = \boxed{16.02 \text{ W}}$$



d) FIND  $P_{pot}$  w/No Load

$$P_{\text{por}} = \frac{V^2}{R_{\text{por}}} = \frac{(40\text{V})^2}{100\Omega} = \boxed{16.00\text{W}}$$



~ SAME

~~(42)~~ FIND R FOR EACH CIRCUIT

(45)

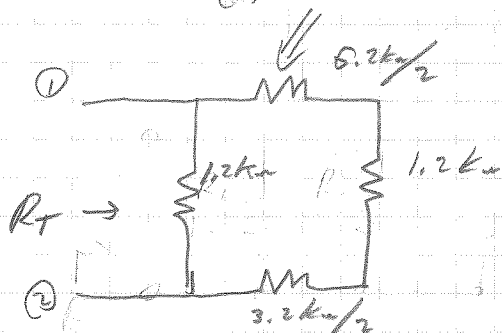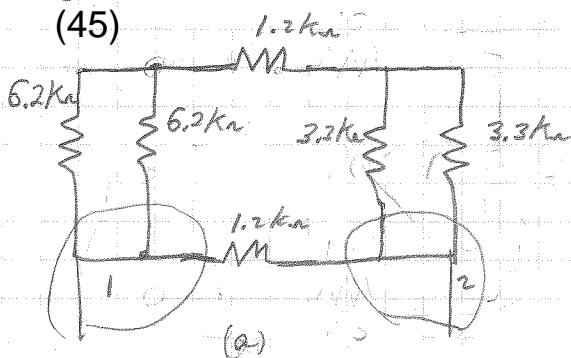
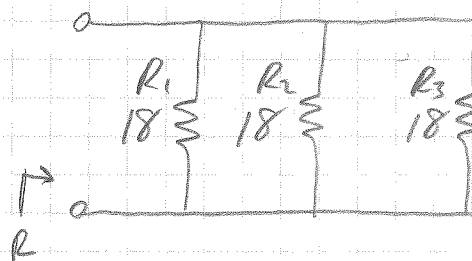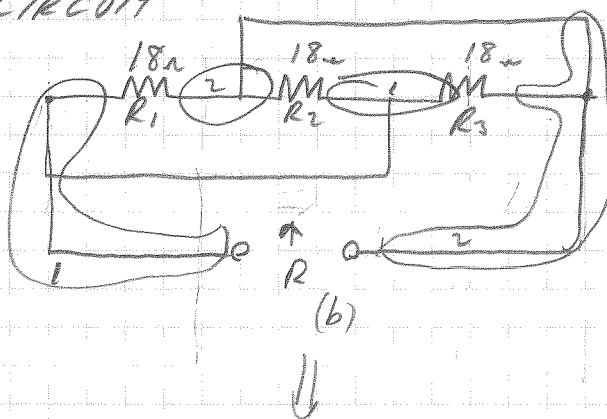
$$R = 1.2 \text{ k}\Omega // 5.9 \text{ k}\Omega = 997.2 \Omega$$



$$l = \frac{18m}{3} = \boxed{6m}$$