
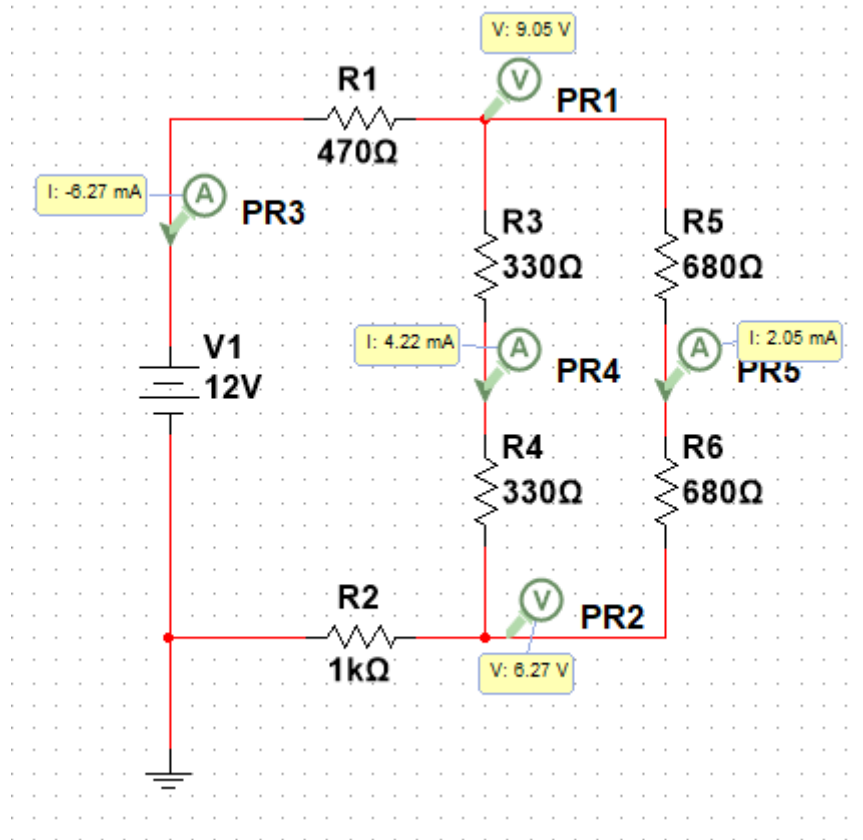


1.

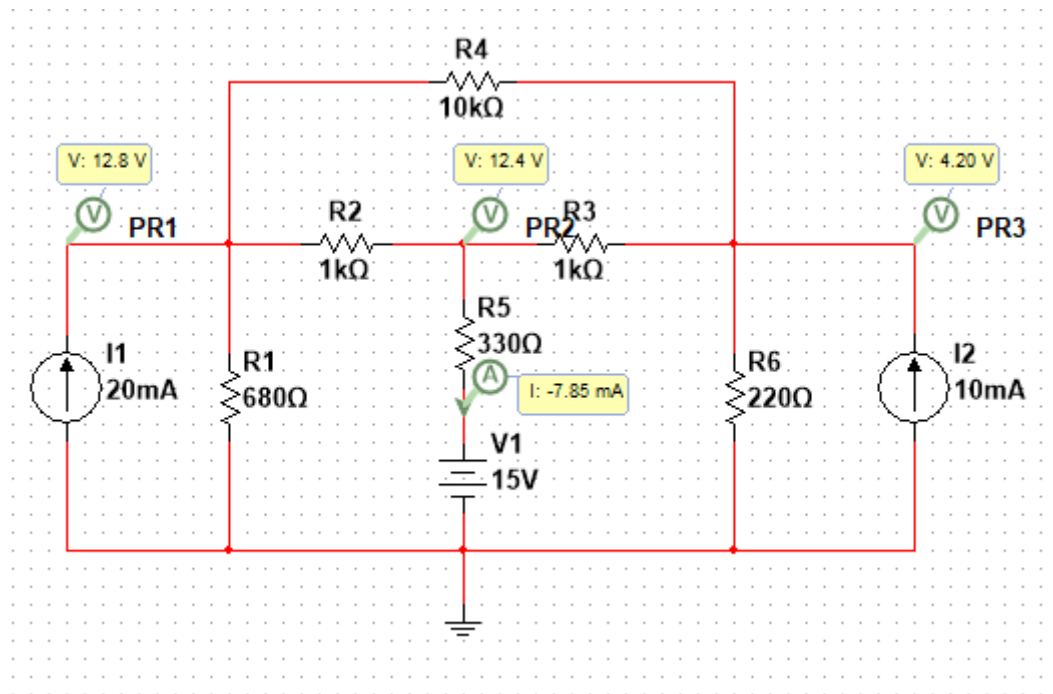


	Value	Units
I_s	6.27	mA
V_{R1}	2.95	V
V_{R2}	6.27	V
V_{R4}	1.39	V
I_{R3}	4.22	mA
I_{R6}	2.05	mA

2.




	Value	Units
V_A	12.8	V
V_B	12.4	V
V_C	4.2	V
P_{V1}	118	mW
I_{R4}	860	uA

3.

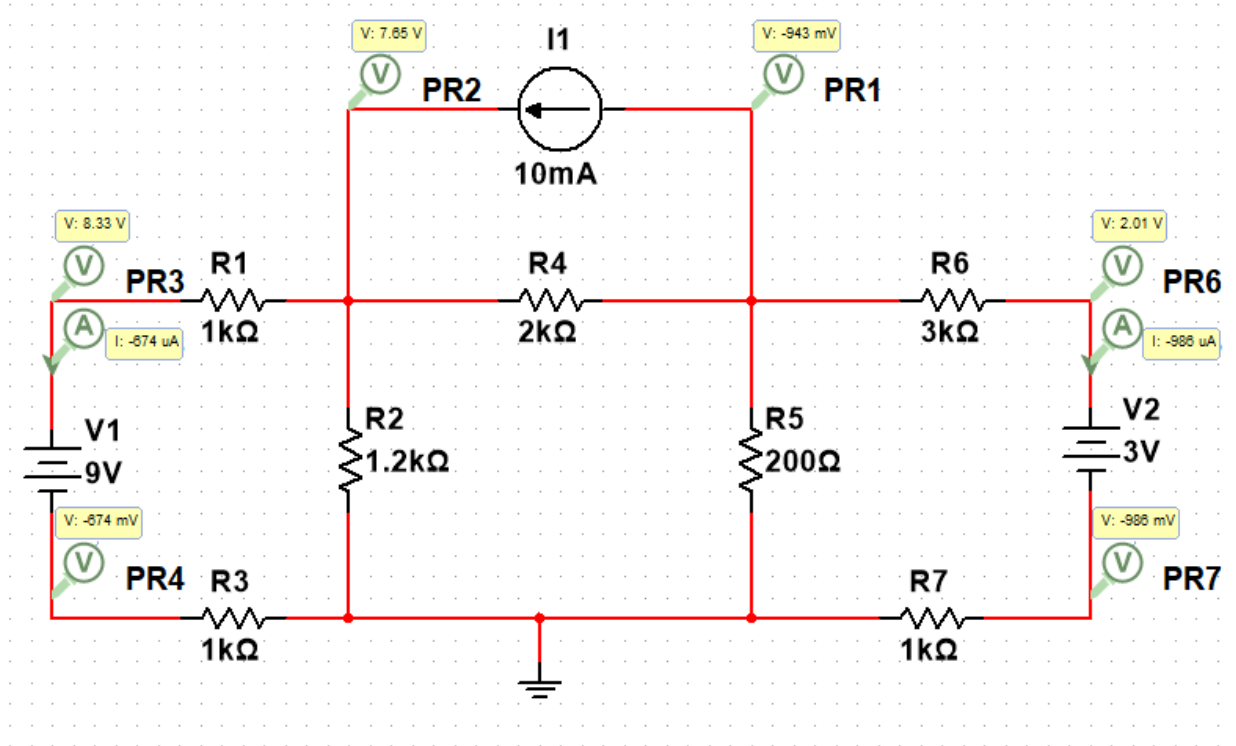


	Value	Units
V_A	8.33	V
V_B	7.65	V
V_C	-943	mV
V_D	2.01	V
P_{I1}	85.93	mW

4.

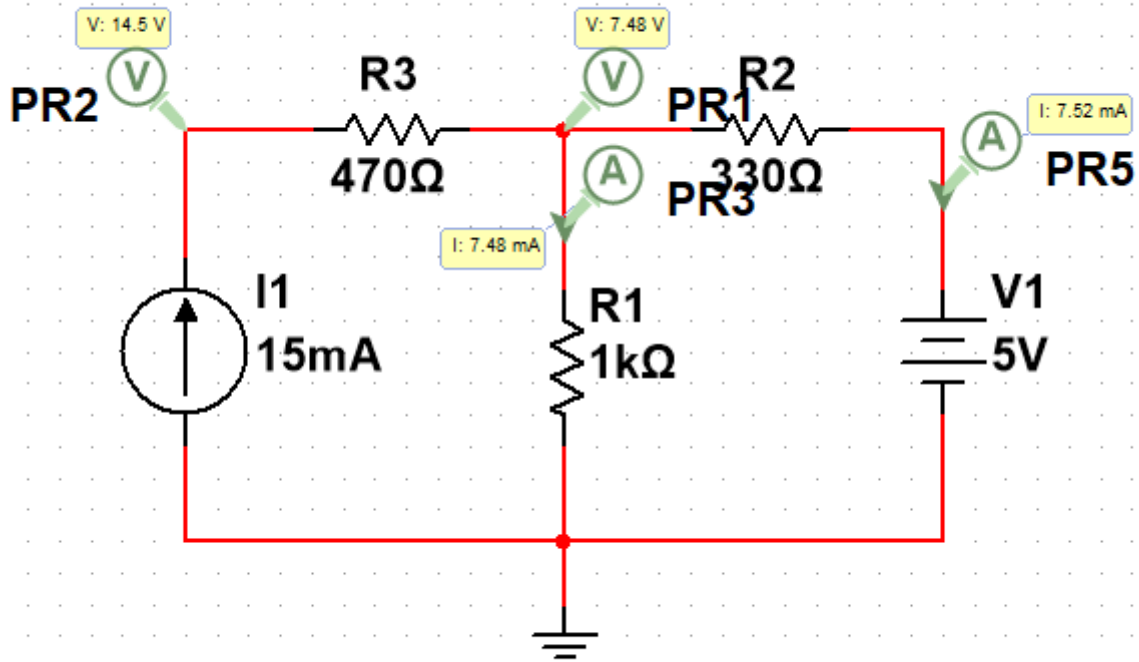

	Value	Units
V_{R1}	7.48	V
P_{I1}	218	mW
P_{V1}	37.6	mW

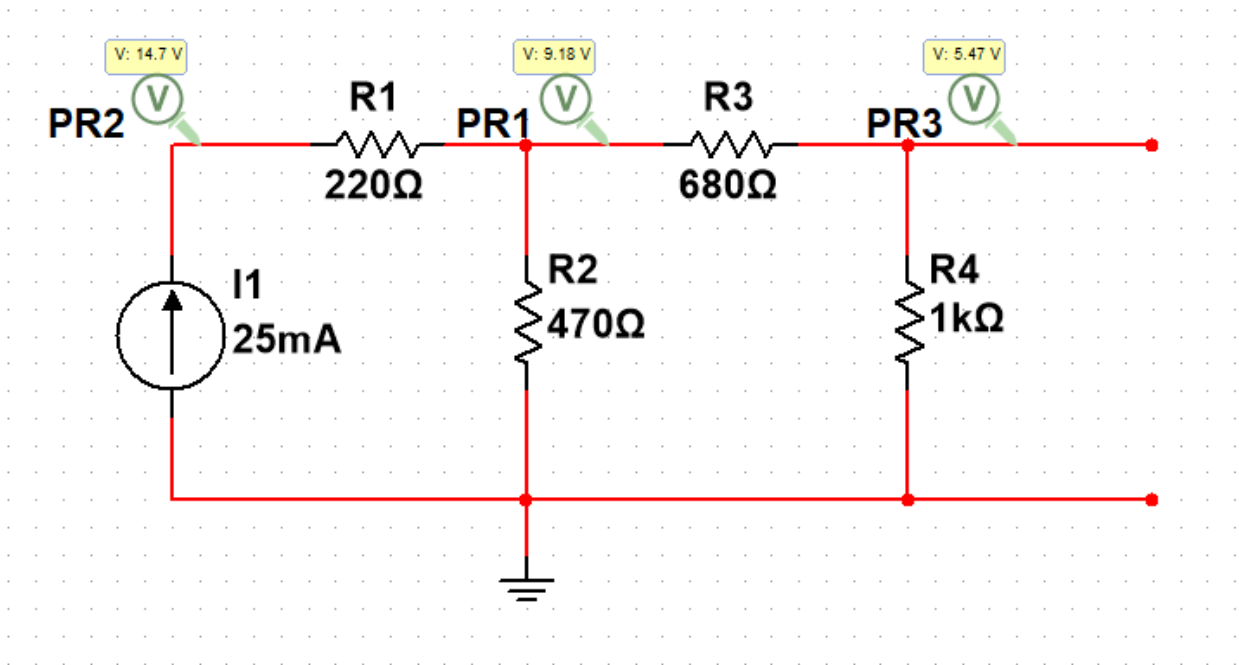

5. Create a Thevenin equivalent circuit for the figure above, with a voltage source and series resistance.

$$V_{TH} = 5.47\text{ V}$$

$$R_{TH} = 535\ \Omega$$


6. A system that is 85% efficient outputs 100 W. What is its input power?

$$100 / .85 = 117.6 \text{ W}$$

7. Three systems are placed in series, having efficiencies of 70%, 60%, and 90%. What is the overall system efficiency?

$$0.7 * 0.6 * 0.9 = 37.8\%$$

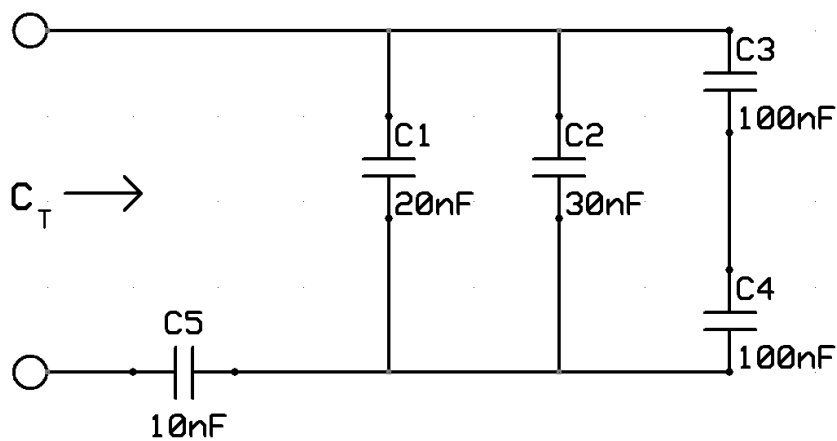8. What is the total capacitance of the network below?




$$9.09 \text{ nF}$$

9. If the capacitor network above had 35nC of charge stored in it, what would be the voltage across it?

$$V = Q / C = 35 \text{ nC} / 9.09 \text{ nF} = 3.85 \text{ V}$$

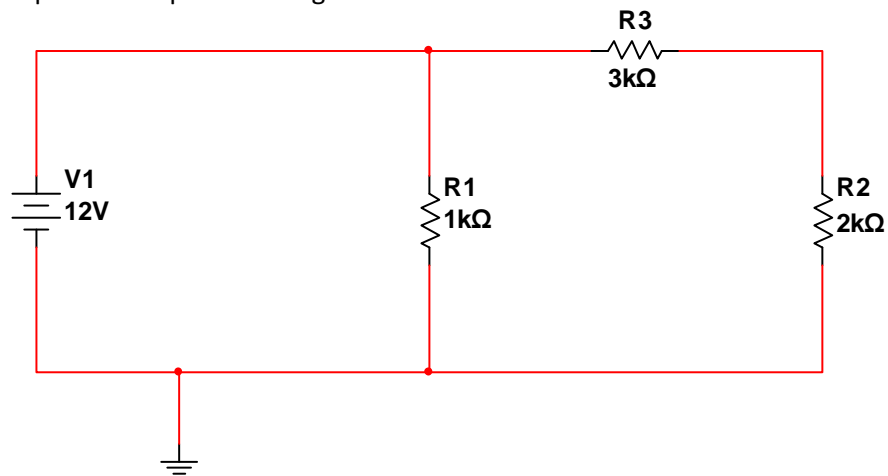10. What is the power dissipated through each resistor?




	Value	Units
P_{R1}	144	mW
P_{R2}	11.52	mW
P_{R3}	17.28	mW

11. What is the power supplied/absorbed by the source? (Select 2)


- a. 24 mW Supplied
- b. -24 mW Absorbed
- c. 173 mW Supplied**
- d. -173 mW Absorbed

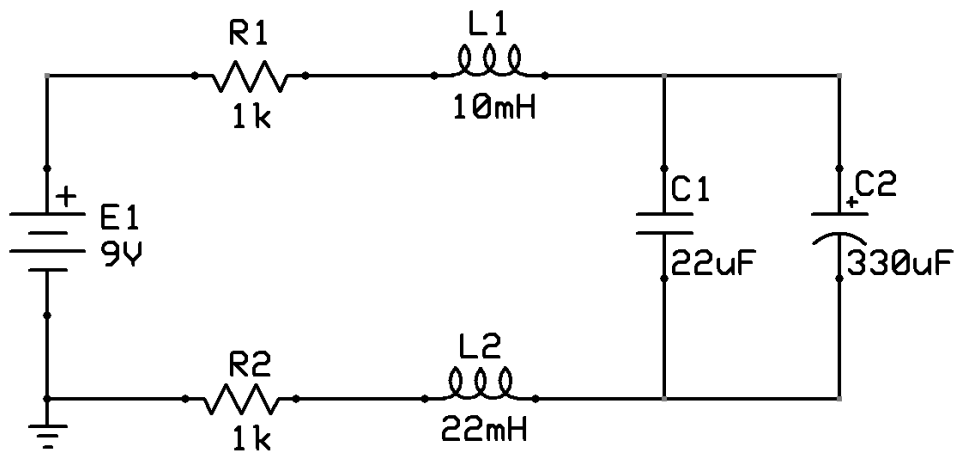12. For the circuit below, fill in the table with **steady-state** values



	Value	Units
V_{C1}	9	V
I_{L1}	0	A
V_{L2}	0	V
I_S	0	A

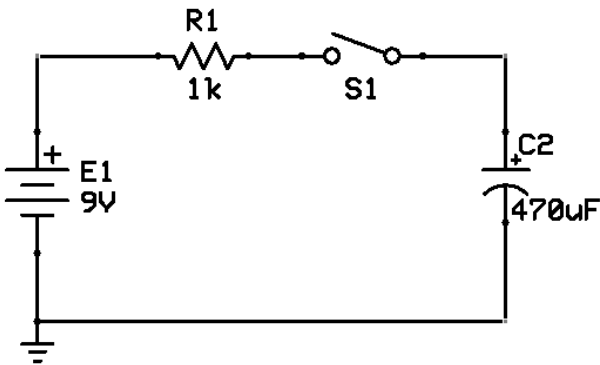13. What is the time constant when charging the capacitor in the circuit below?



$$1k\Omega * 470\mu = 470\text{ ms}$$


14. After 5τ , what will be the voltage across the capacitor?

$$9\text{ V}$$

15. If the switch is opened after 5τ , how long will it take for the capacitor to discharge?

Infinite

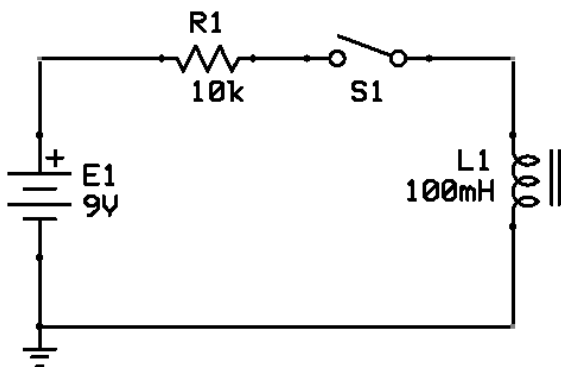16. For the circuit below, what is the time constant for charging the inductor?



$$100\text{ mH} / 10k\Omega = 10\text{ us}$$


17. Write the equation which defines the current through the inductor as a function of time.

$$i_L = 900\text{ uA} (1 - e^{-t/10\text{ us}})$$

18. What will happen if the switch is opened after 5τ ?

Spark

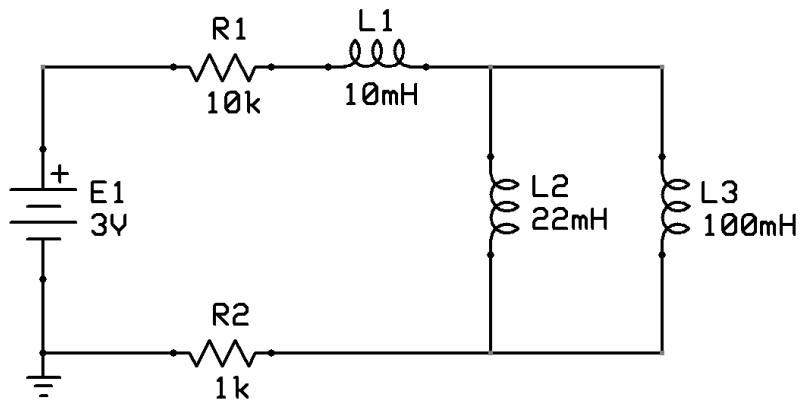19. What is the total inductance of the circuit below?



28 mH

20. Assuming all components are ideal, what is the total resistance of the circuit above?

11 k Ω

21. What wire gauge would be the best choice for conducting 8A of DC current?

- a. 8 AWG
- b. 18 AWG**
- c. 24 AWG
- d. 32 AWG