

## Chapter 10

$$1. \quad (a) \quad \mathcal{E} = k \frac{Q_1}{r^2} = \frac{(9 \times 10^9)(4 \mu\text{C})}{(1 \text{ m})^2} = \mathbf{36 \times 10^3 \text{ N/C}}$$

$$(b) \quad \mathcal{E} = k \frac{Q_1}{r^2} = \frac{(9 \times 10^9)(4 \mu\text{C})}{(1 \text{ mm})^2} = \mathbf{36 \times 10^9 \text{ N/C}}$$

$$\mathcal{E}(1 \text{ mm}): \mathcal{E}(2 \text{ m}) = 36 \times 10^9: 36 \times 10^3 = \mathbf{1 \times 10^6}$$

$$2. \quad \mathcal{E} = \frac{kQ}{r^2} \Rightarrow \sqrt{\frac{kQ}{\mathcal{E}}} = \sqrt{\frac{(9 \times 10^9)(2 \mu\text{C})}{72 \text{ N/C}}} = \mathbf{15.81 \text{ m}}$$

$$3. \quad C = \frac{Q}{V} = \frac{1200 \mu\text{C}}{24 \text{ V}} = \mathbf{50 \mu\text{F}}$$

$$4. \quad Q = CV = (0.15 \mu\text{F})(120 \text{ V}) = \mathbf{18 \mu\text{C}}$$

$$5. \quad a. \quad 1'' \left[ \frac{1 \text{ m}}{39.37''} \right] = 25.4 \text{ mm}$$

$$\mathcal{E} = \frac{V}{d} = \frac{500 \text{ mV}}{25.4 \text{ mm}} = \mathbf{19.69 \text{ V/m}}$$

$$b. \quad \frac{25.4 \text{ mm}}{100} = 0.254 \text{ mm}$$

$$\mathcal{E} = \frac{V}{d} = \frac{500 \text{ mV}}{0.254 \text{ mm}} = \mathbf{1.97 \text{ kV/m}}$$

$$6. \quad V = \frac{Q}{C} = \frac{160 \mu\text{C}}{6.8 \mu\text{F}} = 23.53 \text{ V}$$

$$\mathcal{E} = \frac{V}{d} = \frac{23.53 \text{ V}}{5 \text{ mm}} = \mathbf{4.71 \text{ kV/m}}$$

$$7. \quad 0.1'' \left[ \frac{1 \text{ m}}{39.37''} \right] = 2.54 \text{ mm}$$

$$C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} = 8.85 \times 10^{-12} (1) \frac{(0.1 \text{ m}^2)}{2.54 \text{ mm}} = \mathbf{348.43 \text{ pF}}$$

$$8. \quad C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} = 8.85 \times 10^{-12} (2.5) \frac{(0.1 \text{ m}^2)}{2.54 \text{ mm}} = \mathbf{871.06 \text{ pF}}$$

$$9. \quad C = 8.85 \times 10^{-12} \epsilon_r \frac{A}{d} \Rightarrow d = \frac{8.85 \times 10^{-12} (4) (0.15 \text{ m}^2)}{2 \mu\text{F}} = \mathbf{2.66 \mu\text{m}}$$

$$10. \quad C = \epsilon_r C_o \Rightarrow \epsilon_r = \frac{C}{C_o} = \frac{6.8 \text{ nF}}{1360 \text{ pF}} = \mathbf{5 \text{ (mica)}}$$

$$11. \quad a. \quad C = 8.85 \times 10^{-12} (7) \frac{(0.08 \text{ m}^2)}{0.2 \text{ mm}} = \mathbf{24.78 \text{ nF}}$$

$$b. \quad \mathcal{E} = \frac{V}{d} = \frac{80 \text{ V}}{0.2 \text{ mm}} = \mathbf{400 \text{ kV/m}}$$

$$c. \quad Q = CV = (24.78 \text{ nF})(200 \text{ V}) = \mathbf{4.96 \mu\text{C}}$$

$$12. \quad a. \quad C = \frac{1}{2} (4.7 \mu\text{F}) = \mathbf{2.35 \mu\text{F}}$$

$$b. \quad C = 2(4.7 \mu\text{F}) = \mathbf{9.4 \mu\text{F}}$$

$$c. \quad C = 20(4.7 \mu\text{F}) = \mathbf{94 \mu\text{F}}$$

$$d. \quad C = \frac{(4) \left( \frac{1}{3} \right)}{\left( \frac{1}{4} \right)} (4.7 \mu\text{F}) = \mathbf{25.1 \mu\text{F}}$$

$$13. \quad d = \frac{8.85 \times 10^{-12} \epsilon_r A}{C} = \frac{(8.85 \times 10^{-12})(5)(0.02 \text{ m}^2)}{6800 \text{ pF}} = 130.15 \mu\text{m}$$

$$d = 130.15 \cancel{\mu\text{m}} \left[ \frac{10^{-6} \cancel{\text{m}}}{1 \cancel{\mu\text{m}}} \right] \left[ \frac{39.37 \cancel{\text{in.}}}{1 \cancel{\text{in.}}} \right] \left[ \frac{1000 \text{ mils}}{1 \cancel{\text{in.}}} \right] = 5.12 \text{ mils}$$

$$5.12 \cancel{\text{mils}} \left[ \frac{5000 \text{ V}}{1 \cancel{\text{mil}}} \right] = \mathbf{25.6 \text{ kV}}$$

$$14. \quad \text{mica: } \frac{1200 \text{ V}}{5000 \text{ V}} = 1200 \text{ V} \left[ \frac{\cancel{\text{mil}}}{5000 \text{ V}} \right] = 0.24 \text{ mils}$$

$$0.24 \text{ mils} \left[ \frac{\cancel{\text{mil}}}{1000 \text{ mils}} \right] \left[ \frac{1 \text{ m}}{39.37 \cancel{\text{in.}}} \right] = \mathbf{6.10 \mu\text{m}}$$

$$15. \quad \frac{200}{1 \times 10^6} (22 \mu\text{F})/^{\circ}\text{C} = 4400 \text{ pF}/^{\circ}\text{C}$$

$$\frac{4400 \text{ pF}}{^{\circ}\text{C}} [\Delta T] = \frac{4400 \text{ pF}}{^{\circ}\text{C}} [80^{\circ}\text{C}] = \mathbf{0.35 \mu\text{F}}$$

$$16. \quad J = \pm 5\%, \text{ Size} \Rightarrow 40 \text{ pF} \pm 2 \text{ pF}, \mathbf{38 \text{ pF} \rightarrow 42 \text{ pF}}$$

$$17. \quad F = \pm 1\%, \text{ Size} \Rightarrow 47 \times 10^1 \mu\text{F} = 470 \mu\text{F} \pm 4.7 \mu\text{F}, \mathbf{465.3 \mu\text{F} \rightarrow 474.7 \mu\text{F}}$$

$$18. \quad K = \pm 10\%, \text{ Size} \Rightarrow 18 \times 10^2 \text{ pF} = \mathbf{1800 \text{ pF} \pm 180 \text{ pF}}, \mathbf{1620 \text{ pF} \rightarrow 1980 \text{ pF}}$$


$$19. \quad a. \quad \tau = RC = (10 \times 10^3 \Omega)(10 \mu\text{F}) = \mathbf{100 \text{ ms}}$$

b.  $v_C = E(1 - e^{-t/\tau}) = 20 \text{ V}(1 - e^{-t/100 \text{ ms}})$

c.  $1\tau = 0.632(20 \text{ V}) = 12.64 \text{ V}$ ,  $3\tau = 0.95(20 \text{ V}) = 19 \text{ V}$   
 $5\tau = 0.993(20 \text{ V}) = 19.87 \text{ V}$

d.  $i_C = \frac{20 \text{ V}}{10 \text{ k}\Omega} e^{-t/\tau} = 2 \text{ mA} e^{-t/100 \text{ ms}}$   
 $v_R = E e^{-t/\tau} = 20 \text{ V} e^{-t/100 \text{ ms}}$

e.

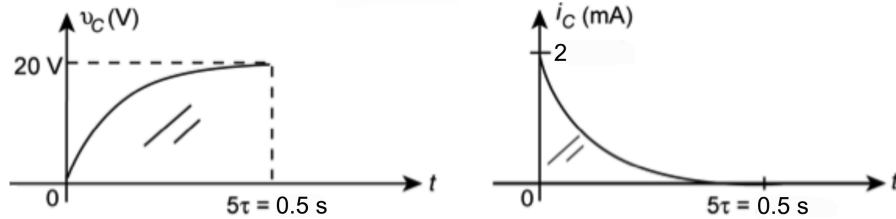

20. a.  $\tau = RC = (100 \text{ k}\Omega)(10 \text{ }\mu\text{F}) = 1 \text{ s}$

b.  $v_C = E(1 - e^{-t/\tau}) = 20 \text{ V}(1 - e^{-t/1 \text{ s}})$

c.  $1\tau = 12.64 \text{ V}$ ,  $3\tau = 19 \text{ V}$ ,  $5\tau = 19.87 \text{ V}$

d.  $i_C = \frac{20 \text{ V}}{100 \text{ k}\Omega} e^{-t/\tau} = 200 \text{ }\mu\text{A} e^{-t/1 \text{ s}}$   
 $v_R = E e^{-t/\tau} = 20 \text{ V} e^{-t/1 \text{ s}}$

e. Same as problem 21 with  $5\tau = 5 \text{ s}$  and  $I_m = 200 \text{ }\mu\text{A}$

21. a.  $\tau = RC = (2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega)1 \text{ }\mu\text{F} = (5.5 \text{ k}\Omega)(1 \text{ }\mu\text{F}) = 5.5 \text{ ms}$

b.  $v_C = E(1 - e^{-t/\tau}) = 100 \text{ V}(1 - e^{-t/5.5 \text{ ms}})$

c.  $1\tau = 63.21 \text{ V}$ ,  $3\tau = 95.02 \text{ V}$ ,  $5\tau = 99.33 \text{ V}$

d.  $i_C = \frac{E}{R_T} e^{-t/\tau} = \frac{100 \text{ V}}{5.5 \text{ k}\Omega} e^{-t/\tau} = 18.18 \text{ mA} e^{-t/5.5 \text{ ms}}$

$$V_{R_2} = \frac{3.3 \text{ k}\Omega (100 \text{ V})}{3.3 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 60 \text{ V}$$

$$v_{R_2} = 60 \text{ V} e^{-t/5.5 \text{ ms}}$$

e.

