



HW: #4

Individual Questions: Chapter 5: 22, 23, 24, 26, 29, 30, 39, 41

Team Questions: Chapter 5: 36 [Use $V_{R1} = (1/5) \cdot V_{R2}$], 45, 48, and 49

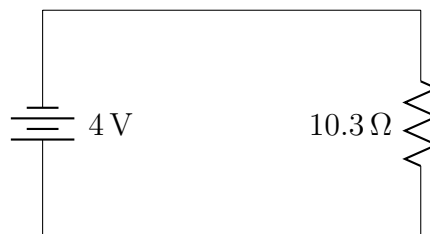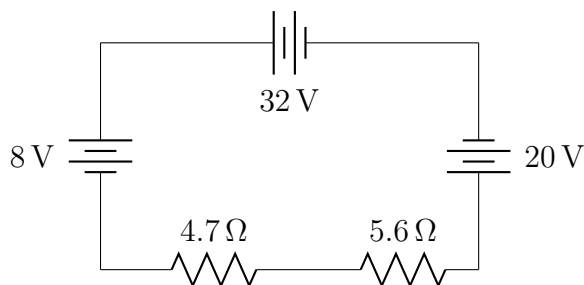Question 5-22

Determine the current I and its direction for each network in Fig.5.109. Before solving for I , redraw each network with a single voltage source.





$$E_T = 20V + 8V - 32V = -4V$$

$$R_T = 4.7\Omega + 5.6\Omega = 10.3\Omega$$

$$I = E_T / R_T = 4V / 10.3\Omega = 388.3mA$$

Current is flowing counter clockwise

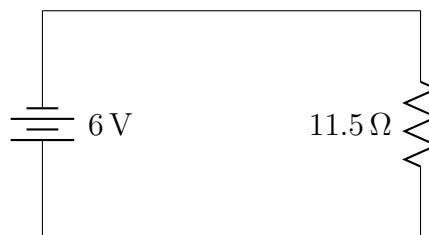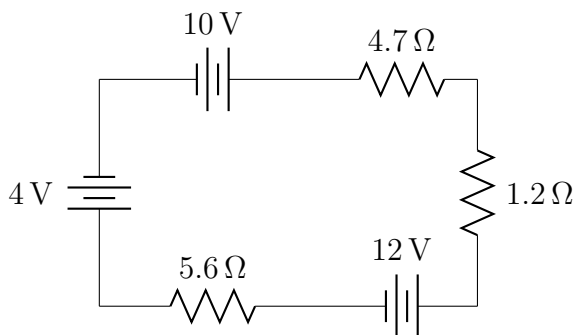

$$E_T = -4V + 10V - 12V = -6V$$


$$R_T = 4.7\Omega + 1.2\Omega + 5.6\Omega = 11.5\Omega$$

$$I = E_T / R_T = 6V / 11.5\Omega = 521.7mA$$

Current is flowing counter clockwise

5-20) FIND "E" + "R" IN EACH NETWORK. FIRST COMBINE THE SERIES SOURCES + INDICATE THE DIRECTION OF CURRENT.

Q5-23

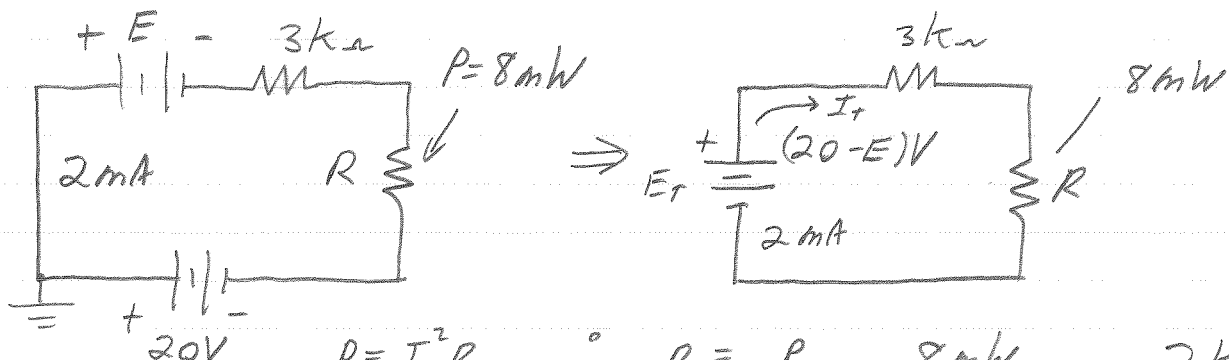

$$P = I^2 R \quad \therefore R = \frac{P}{I^2} = \frac{8\text{mW}}{(2\text{mA})^2} = \underline{2\text{k}\Omega}$$


$$R_T = 5\text{k}\Omega, \quad I_T = 2\text{mA}$$

$$\therefore E_T = (2\text{mA})(5\text{k}\Omega) = \underline{10\text{V}}$$

$$\therefore 10\text{V} = 20 - E, \quad \underline{E = 10\text{V}}$$

$$\begin{aligned} R &= 2\text{k}\Omega \\ E &= 10\text{V} \\ I &\Rightarrow \text{CW} \end{aligned}$$

(6)

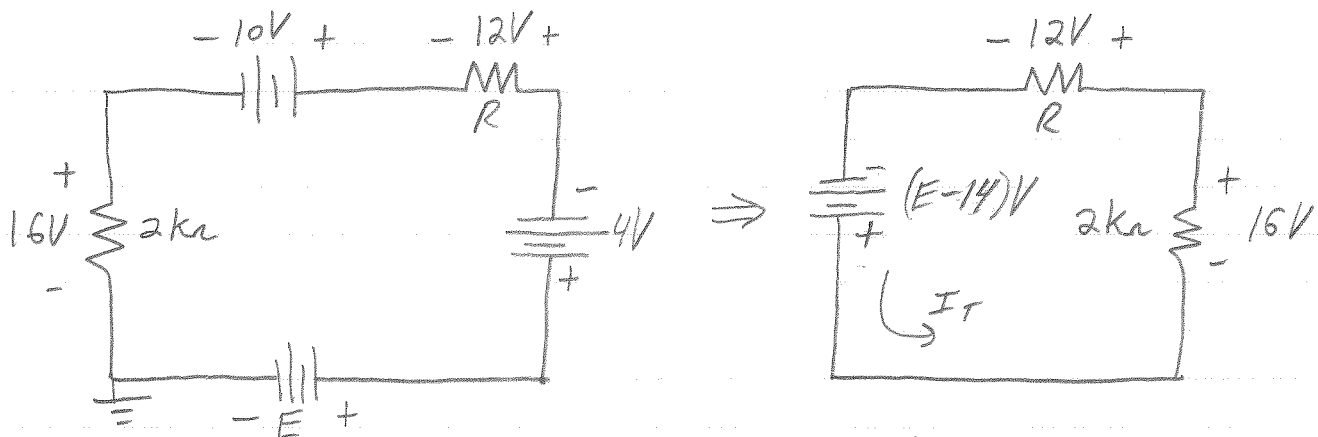

$$|I| = \frac{16\text{V}}{2\text{k}\Omega} = \underline{8\text{mA}}$$

$$\therefore R = \frac{12\text{V}}{8\text{mA}} = \underline{1.5\text{k}\Omega}$$

$$R_T = 3.5\text{k}\Omega, \quad I_T = 8\text{mA}$$

$$\therefore E_T = (8\text{mA})(3500\Omega) = 28\text{V}$$


$$(E-14) = 28$$

$$E = 28 + 14 = 42\text{V}$$


$$\begin{aligned} R &= 1.5\text{k}\Omega & I &= \text{CCW} \\ E &= 42\text{V} \end{aligned}$$

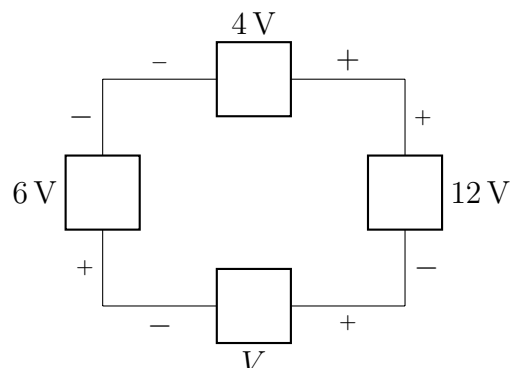Question 5-24


Using Kirchhoff's voltage law, find the unknown voltage for the circuits in Fig. 5.111.


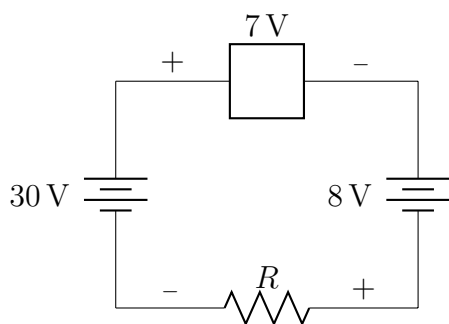
$$\begin{aligned}\text{KVL: } -6 + 4 - 12 - V &= 0 \\ V &= -6 + 4 - 12 \\ V &= \boxed{-14V}\end{aligned}$$



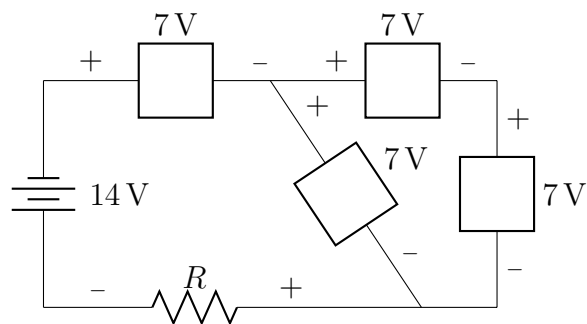
$$\begin{aligned}\text{KVL: } 30 - 7 - 8 - V &= 0 \\ V &= 30 - 7 - 8 \\ V &= \boxed{15V}\end{aligned}$$



$$\begin{aligned}\text{KVL: } -14 - 22 - V_1 + 12 &= 0 \\ V &= -14 - 22 + 12 \\ V &= \boxed{-24V} \\ \text{KVL: } -14 - 22 - V_2 - 12 + 12 &= 0 \\ V_2 &= -14 - 22 - 12 + 12 = 0 \\ V_2 &= \boxed{-36V}\end{aligned}$$

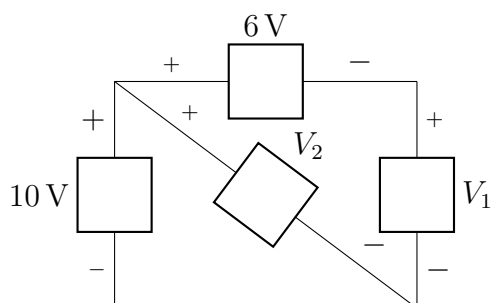Question 5-26

Using Kirchhoff's voltage law, determine the unknown voltages for the series circuits in Fig. 5.113.



$$\text{KVL: } 10 - 6 - V_1 = 0$$


$$V_1 = 10 - 6$$

$$V_1 = \boxed{4V}$$

$$\text{KVL: } 10 - V_2 = 0$$

$$10 - V_2 = 0$$

$$V_2 = \boxed{10V}$$

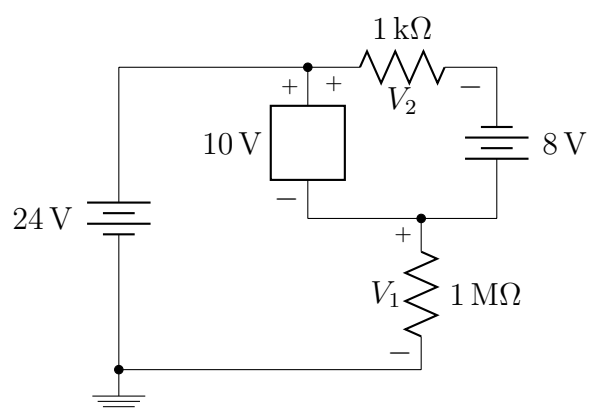

$$\text{KVL: } 24 - 10 - V_1 = 0$$

$$V_1 = 24 - 10$$


$$V_1 = \boxed{14V} \quad \text{KVL: } 10 - V_2 + 8 = 0$$

$$V_2 = 10 - V_2 + 8$$

$$V_2 = \boxed{18V}$$

~~5-26)~~

Q5-29

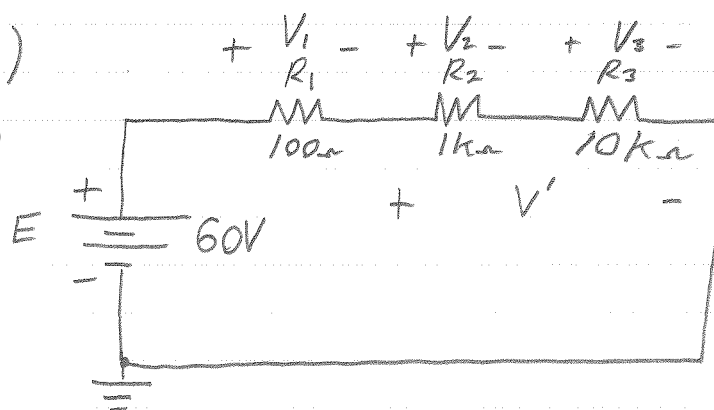

(Q) By INSPECTION, WHICH RESISTOR WILL RECEIVE THE LARGEST SHARE OF APPLIED VOLTAGE? WHY?

R_3 , THE LARGEST RESISTANCE
SINCE $V_x = E \frac{R_x}{R_T}$ — LARGEST $R \Rightarrow$ LARGEST V_x

~~5-26)~~

Q5-29

(b) How MUCH LARGER WILL V_3 BE COMPARED TO $V_2 + V_1$?

$$\begin{aligned} V_3 &= 10 \times V_2 \\ V_3 &= 100 \times V_1 \end{aligned} \quad , \text{ SINCE } \begin{aligned} R_3 &= 10 \times R_2 \\ R_3 &= 100 \times R_1 \end{aligned}$$

(c) FIND THE VOLTAGE ACROSS R_3


$$V_{R_3} = E \left(\frac{R_3}{R_T} \right) = 60V \left(\frac{10k\Omega}{11.1k\Omega} \right) = \boxed{54.1V}$$

(d) FIND V'


$$V' = E \left(\frac{R'}{R_T} \right) = 60V \left(\frac{11k\Omega}{11.1k\Omega} \right) = \boxed{59.5V}$$

~~5-27~~) FIND "V" IN EACH CASE USING VOLTAGE DIVIDER

Q5-30

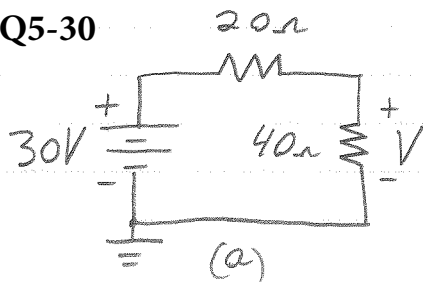

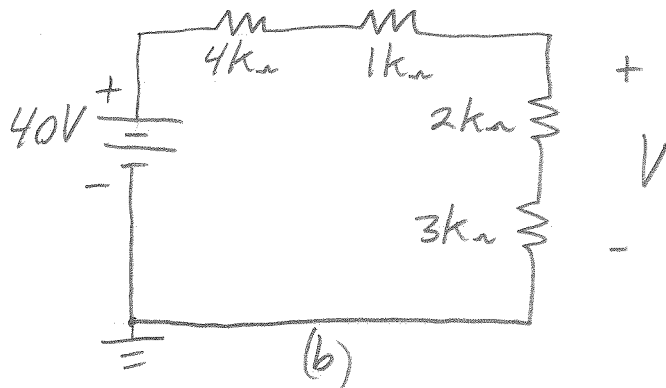
$$V_{40\Omega} = 30V \left(\frac{40\Omega}{60\Omega} \right) = \boxed{20V}$$



$$V = 40V \left(\frac{5k\Omega}{10k\Omega} \right) = \boxed{20V}$$

~~5-27~~)

Q5-30

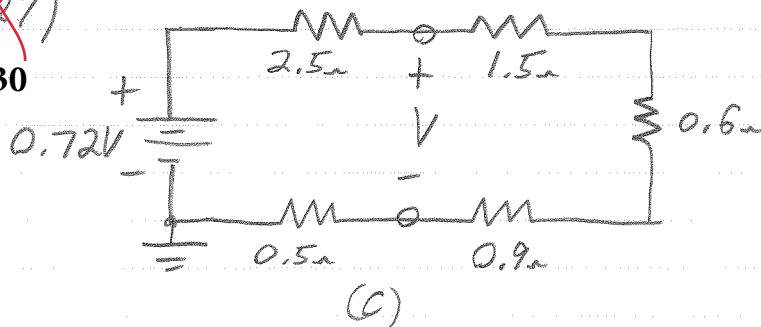


$$V = 0.72V \left(\frac{3\Omega}{6\Omega} \right)$$


$$\boxed{V = 360mV}$$

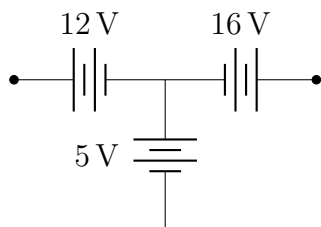Question 5-39


Determine the voltages V_a , V_b , and V_{ab} for the networks in Fig. 5.125


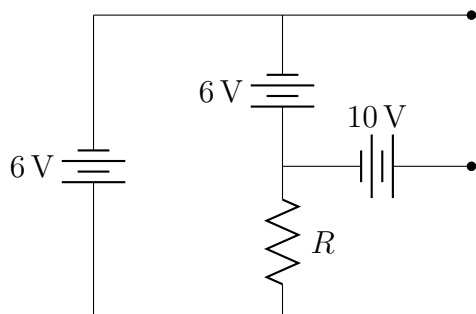
$$\begin{aligned} V_a &= 12V + 5V = 17V \\ V_b &= 16V + 5V = 21V \\ V_{ab} &= 17V - 21V = -4V \end{aligned}$$


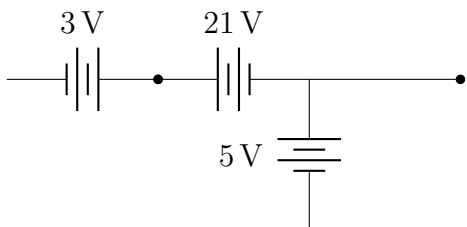
$$\begin{aligned} V_a &= -6V \\ V_b &= -6V + 6V + 10V = 10V \\ V_{ab} &= -6V - 10V = -16V \end{aligned}$$




$$\begin{aligned} -8V + 3V - V_a &= 0 \\ V_a &= -8V + 3V = -5V \\ V_b &= -8V \\ V_{ab} &= V_a - V_b = -5 - (-8) = 3V \end{aligned}$$

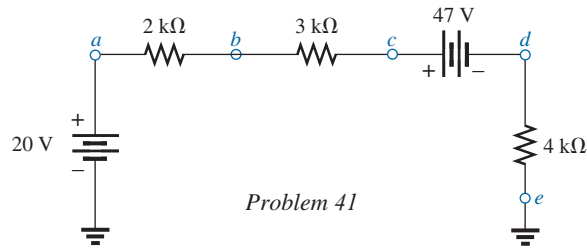Question 5-41

For the network in Fig. 5.127 determine the voltages:

- V_a, V_b, V_c, V_d, V_e
- V_{ab}, V_{dc}, V_{cb}
- V_{ac}, V_{db}




$$I = \frac{47 \text{ V} - 20 \text{ V}}{2 \text{ k}\Omega + 3 \text{ k}\Omega + 4 \text{ k}\Omega} = \frac{27 \text{ V}}{9 \text{ k}\Omega} = 3 \text{ mA (CCW)}$$

$$V_{2\text{k}\Omega} = 6 \text{ V}, V_{3\text{k}\Omega} = 9 \text{ V}, V_{4\text{k}\Omega} = 12 \text{ V}$$

- $V_a = 20 \text{ V}, V_b = 20 \text{ V} + 6 \text{ V} = 26 \text{ V}, V_c = 20 \text{ V} + 6 \text{ V} + 9 \text{ V} = 35 \text{ V}$
 $V_d = -12 \text{ V}, V_e = 0 \text{ V}$
- $V_{ab} = -6 \text{ V}, V_{dc} = -47 \text{ V}, V_{cb} = 9 \text{ V}$
- $V_{ac} = -15 \text{ V}, V_{db} = -47 \text{ V} + 9 \text{ V} = -38 \text{ V}$

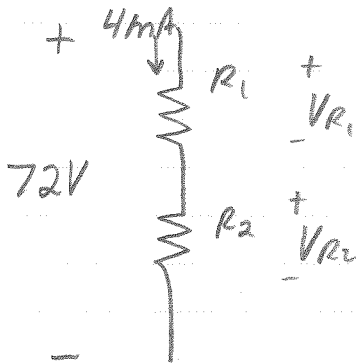~~5-32)~~ DESIGN THE VOLTAGE DIVIDER SUCH THAT
 Q5-36 $V_{R_1} = \frac{1}{5} V_{R_2}$



$$V_{R_1} + V_{R_2} = 72 \text{ V}$$

$$\text{BUT } V_{R_1} = \left(\frac{1}{5}\right) V_{R_2}$$

$$\therefore 0.2 V_{R_2} + V_{R_2} = 72 \text{ V}$$

$$V_{R_2} = 60 \text{ V}$$


$$\text{+ } V_{R_1} = 12 \text{ V}$$

$$R_1 = \frac{12 \text{ V}}{4 \text{ mA}} = \boxed{3 \text{ k}\Omega}$$

$$R_2 = \frac{60 \text{ V}}{4 \text{ mA}} = \boxed{15 \text{ k}\Omega}$$

~~5/41~~) FIND $V_0, V_4, V_7, V_{10}, V_{23}, V_{30}, V_{67}, V_{56} + I$

Q5-45

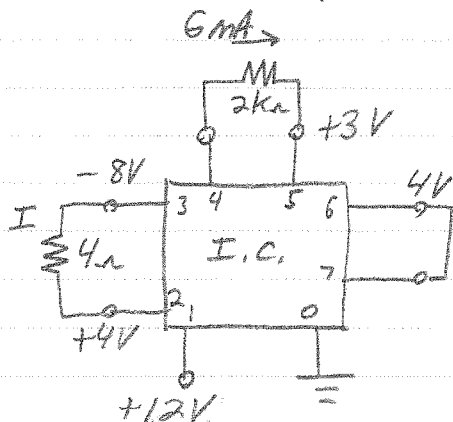

$$V_0 = 0V, \text{ GROUND}$$

$$\text{KVL: } V_4 - (2k\Omega)(6\text{mA}) - (3V) = 0$$

$$V_4 = 12V + 3V = 15V$$

$$V_7 = V_6 = 4V$$

$$V_{10} = V_1 - V_0 = 12V - 0V = 12V$$

$$V_{23} = V_2 - V_3 = 4V - (-8V) = 12V$$

$$V_{30} = V_3 - V_0 = -8V - 0V = -8V$$

$$V_{67} = V_6 - V_7 = 4V - 4V = 0V$$


$$V_{56} = V_5 - V_6 = 3V - 4V = -1V$$

$$I = \frac{-4V - (-8V)}{4\Omega} = \frac{12V}{4\Omega} =$$

3.0A UPWARD
(FROM HIGHER TO LOWER POTENTIAL)

5-44)

Q5-48

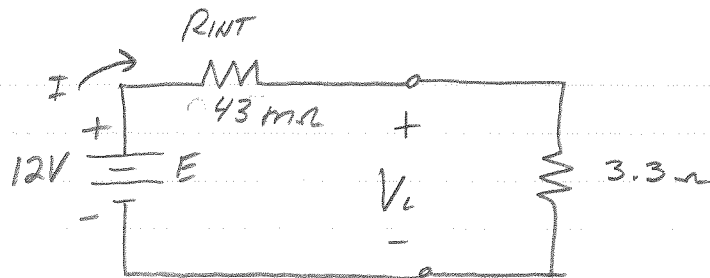

(a) FIND V_L : $V_L = E \left(\frac{R_L}{R_L + R_{INT}} \right) = 12V \left(\frac{3.3 \Omega}{3.343 \Omega} \right)$

$= \boxed{11.85 V}$

(b) FIND THE VOLTAGE REGULATION OF THE SUPPLY

$$V_R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$$= \frac{12V - 11.85 V}{11.85 V} \times 100\% = \boxed{1.27\%}$$

(c) FIND P_{SOURCE} + P_{RINT} UNDER FULL-LOAD

$$P_{SOURCE} = (E)(I)$$


$$\text{BUT } I = \frac{V_L}{R_L} = \frac{11.85V}{3.3 \Omega} = \underline{3.59A}$$

$$\therefore P_{SOURCE} = (12V)(3.59A) = \boxed{43.1 W}$$

$$P_{RINT} = I^2 R_{INT} = (3.59A)^2 (43 m\Omega) = \boxed{554 mW}$$

~~5-15~~

Q5-49

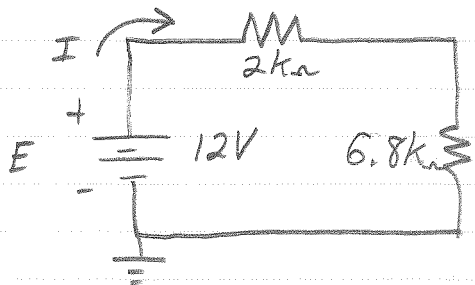

(a) FIND "I"

$$I = \frac{12V}{8.8k\Omega} = \boxed{1.36mA}$$

(b) IF AN AMMETER w/ $R_{INT} = 250\Omega$ IS INSERTED TO MEASURE "I" WHAT IS THE NEW CURRENT LEVEL?

$$I' = \frac{12V}{8.8k\Omega + R_{INT}} = \frac{12V}{9,050\Omega} = \boxed{1.33mA}$$

(c) IS THIS DIFFERENCE A MAJOR CONCERN IN MOST APPLICATIONS?

NO

$$\left(\begin{aligned} \% \text{ DIFF} &= \frac{1.33 - 1.36}{1.36} \times 100\% \\ &\Rightarrow \underline{\underline{-2.2\%}} \end{aligned} \right)$$

